

Department of ARTIFICIAL INTELLIGENCE AND DATA SCIENCE

23EET103-Electric Circuits and Electron Devices
I B.Tech. CSE-IOT/ II SEMESTER



UNIT II : AC CIRCUITS

Topic : Problems with step by step solutions

Power in AC Circuits – Problem 1

- Problem:

Voltage = 240 V

Current = 8 A

Power factor = 0.75

Find the real power.

Solution:

– Formula: $P = V \times I \times \cos\phi$

– $P = 240 \times 8 \times 0.75$

– $P = 1440 \text{ W}$

Power in AC Circuits – Problem 2

- Problem:
Voltage = 230 V
Current = 6 A
Power factor = 0.9
Find the real power.

Solution:

$$\text{Formula: } P = V \times I \times \cos\phi$$

$$P = 230 \times 6 \times 0.9$$

$$P = 1242 \text{ W}$$

Power Factor – Problem 1

Problem:

Real Power = 600 W

Apparent Power = 750 VA

Find the power factor.

Solution:

- Formula: $PF = \text{Real Power} / \text{Apparent Power}$
- $PF = 600 / 750$
- $PF = 0.8$

Power Factor – Problem 2

Problem:

Real Power = 900 W

Apparent Power = 1200 VA

Find the power factor.

Solution:

- Formula: $PF = P / S$
- $PF = 900 / 1200$
- $PF = 0.75$

Three-Phase Power – Problem 1

Problem:

Line Voltage = 415 V

Line Current = 12 A

Power factor = 0.85

Find total power.

Solution:

– Formula: $P = \sqrt{3} \times V_L \times I_L \times \cos\phi$

– $P = 1.732 \times 415 \times 12 \times 0.85$

– $P \approx 7329 \text{ W}$

Three-Phase Power – Problem 2

Problem:

Line Voltage = 400 V

Line Current = 15 A

Power factor = 0.9

Find total power.

Solution:

– Formula: $P = \sqrt{3} \times V_L \times I_L \times \cos\phi$

– $P = 1.732 \times 400 \times 15 \times 0.9$

– $P \approx 9353 \text{ W}$

Three-Phase Power – Problem 2

Problem:

Line Voltage = 400 V

Line Current = 15 A

Power factor = 0.9

Find total power.

Solution:

– Formula: $P = \sqrt{3} \times V_L \times I_L \times \cos\phi$

– $P = 1.732 \times 400 \times 15 \times 0.9$

– $P \approx 9353 \text{ W}$

Thank
you!