

SNS COLLEGE OF

TECHNOLOGY

Kunumbapalayam (Po), Coimbatore – 641 107

An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A'
Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



DEPARTMENT OF COMPUTER SCIENCE AND DESIGN

**COURSE NAME : 23EET103- ELECTRIC CIRCUITS AND
ELECTRON DEVICES**

I YEAR /II SEMESTER

Unit-5 - RECTIFIERS AND POWER SUPPLIES

Topic : **Rectifiers:** Half wave

Story Telling



Topics for discussion

[Half Wave Rectifier Circuit](#)

[Working of Half Wave Rectifier](#)

[Half Wave Rectifier Waveform](#)

[Half Wave Rectifier Capacitor Filter](#)

[Half Wave Rectifier Formula](#)

[Ripple Factor of Half Wave Rectifier](#)

[Efficiency of Halfwave Rectifier](#)

[RMS value of Half Wave Rectifier](#)

[Form factor of a Halfwave Rectifier](#)

[Applications of Half Wave Rectifier](#)

[Disadvantages of Half Wave Rectifier](#)

What is Half-wave rectifiers


Half-wave rectifiers transform AC voltage to DC voltage. A halfwave rectifier circuit uses only one diode for the transformation.

A halfwave rectifier is defined as a type of rectifier that allows only one-half cycle of an AC voltage waveform to pass while blocking the other half cycle. In this session, let us know in detail about the half-wave rectifier.

DT-Empathize

1

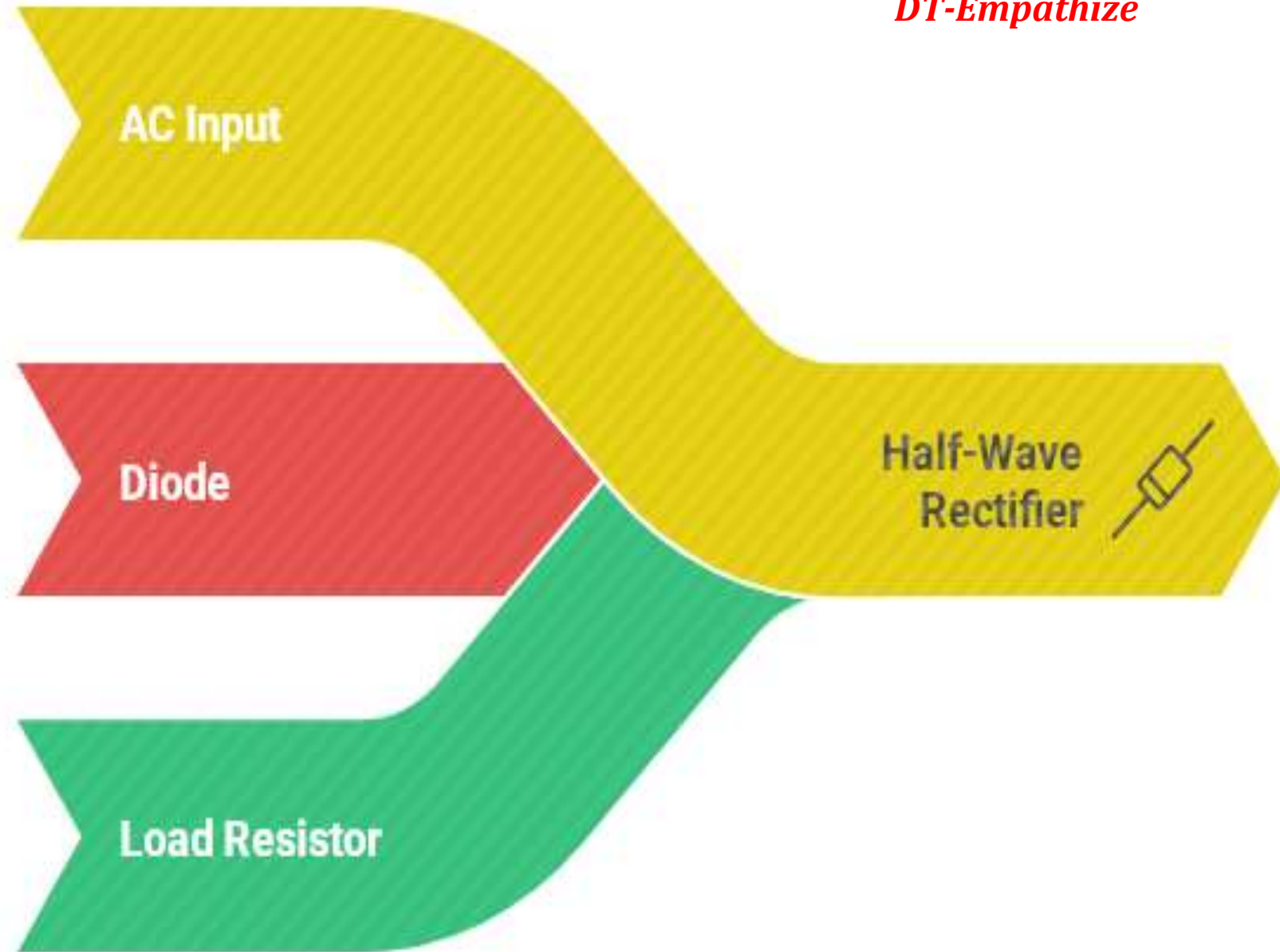Alternating current signal entering the rectifier.



2

Allows current flow in one direction only.

3

Provides resistance for current flow.


Half Wave Rectifier Circuit

A half-wave rectifier is the simplest form of the rectifier and requires only one diode for the construction of a halfwave rectifier circuit.

A halfwave rectifier circuit consists of three main components as follows:

- A diode
- A transformer
- A resistive load

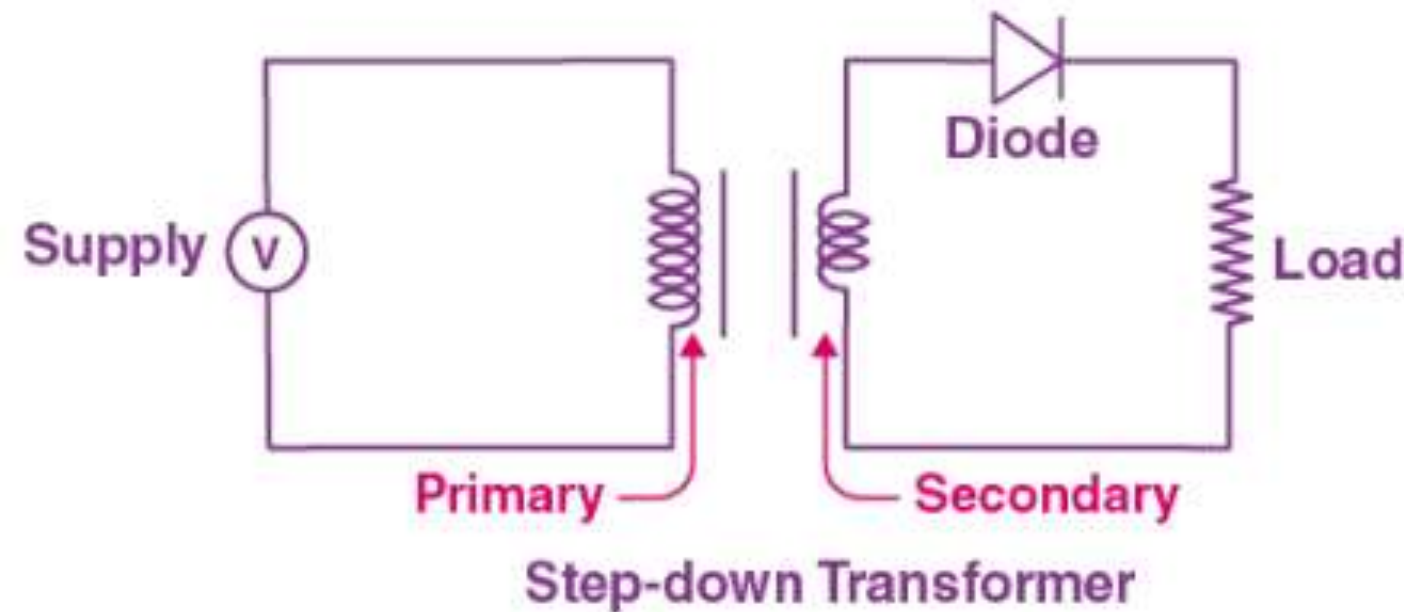Given below is the half-wave rectifier diagram:




Working of Half Wave Rectifier

In this section, let us understand how a half-wave rectifier transforms AC into DC.


A high AC voltage is applied to the primary side of the step-down transformer. The obtained secondary low voltage is applied to the diode.

The diode is forward biased during the positive half cycle of the AC voltage and reverse biased during the negative half cycle.

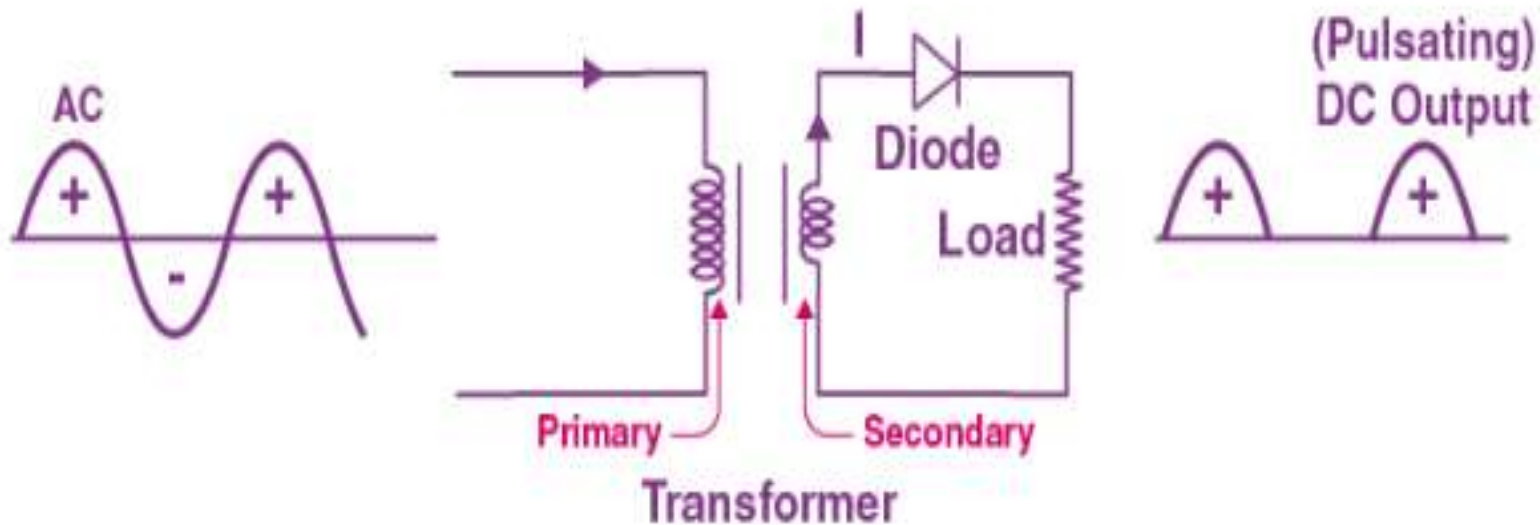
The final output voltage waveform is as shown in the figure below:



DT-DEFINE

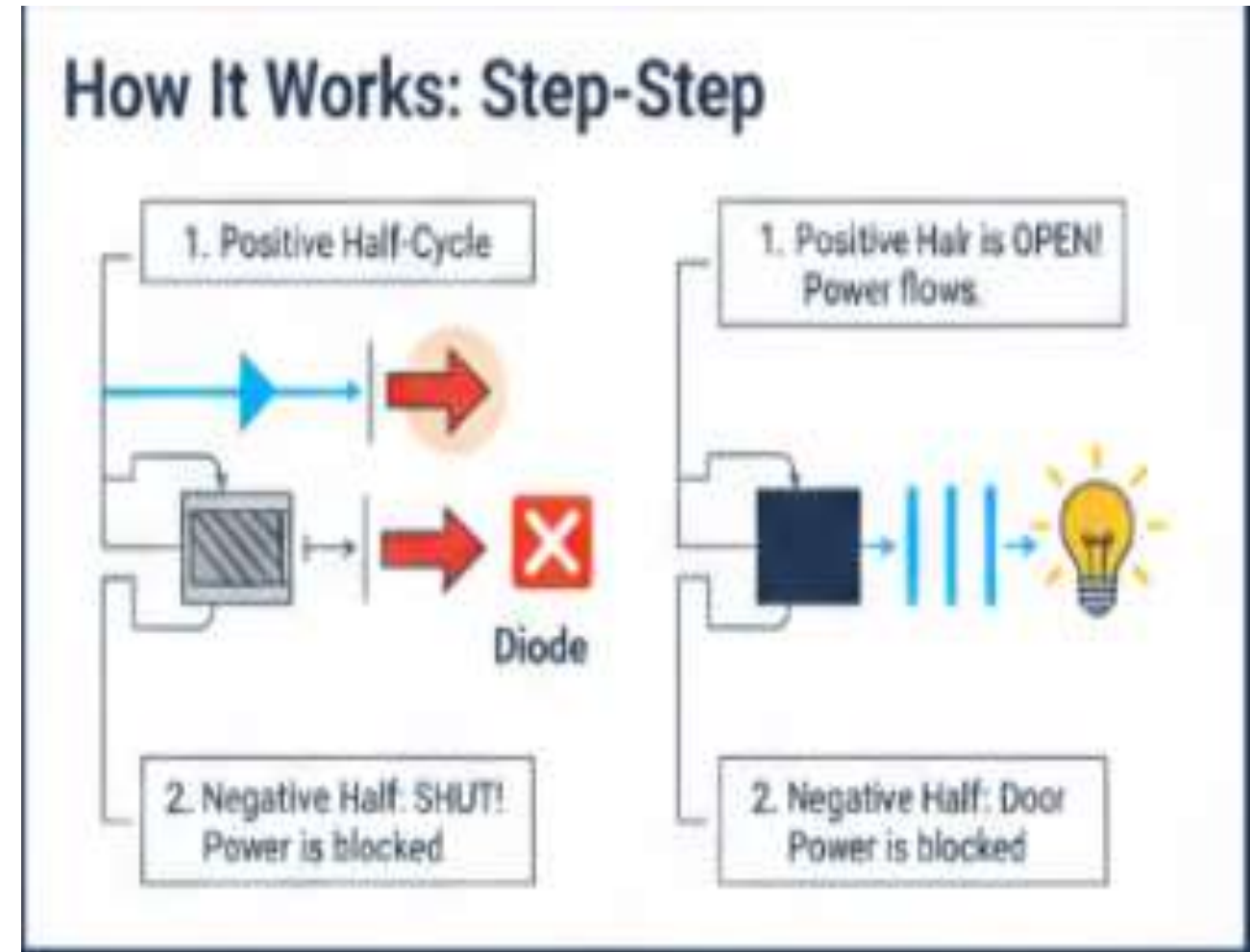

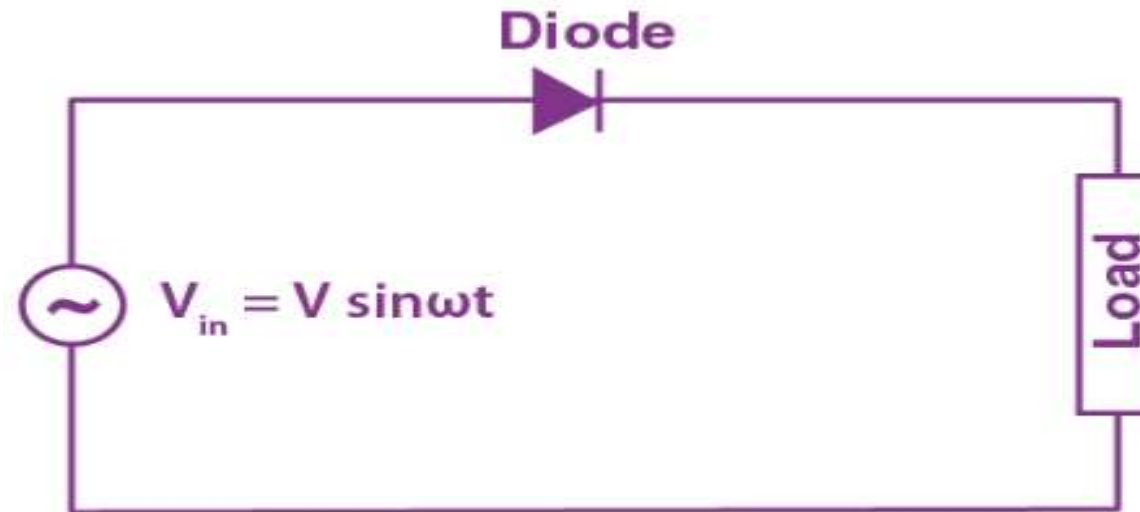For better understanding, let us simplify the half-wave circuit by replacing the secondary transformer coils with a voltage source as shown below:



For the positive half cycle of the AC source voltage, the circuit effectively becomes as shown below in the diagram:




When the diode is forward biased, it acts as a closed switch. But, during the negative half cycle of the AC source voltage, the equivalent circuit becomes as shown in the figure below



When a diode is reverse biased, it acts as an open switch. Since no current can flow to the load, the output voltage is equal to zero.

Half Wave Rectifier Waveform

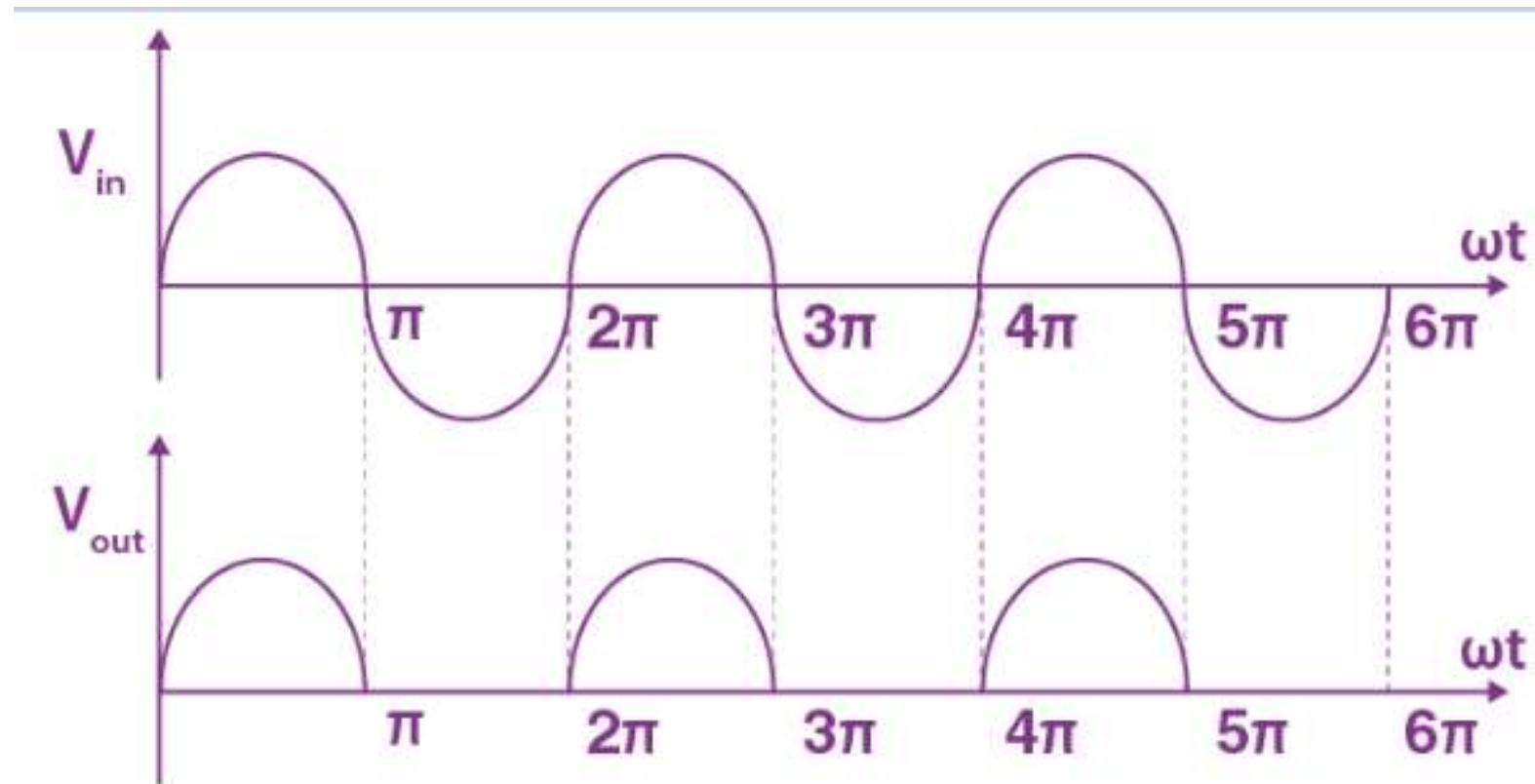The halfwave rectifier waveform before and after rectification is shown below in the figure.




Half Wave Rectifier Capacitor Filter

**DT-
IDEATE**



The output waveform of a halfwave rectifier is a pulsating DC waveform. Filters in halfwave rectifiers are used to transform the pulsating waveform into constant DC waveforms. A capacitor or an inductor can be used as a filter.

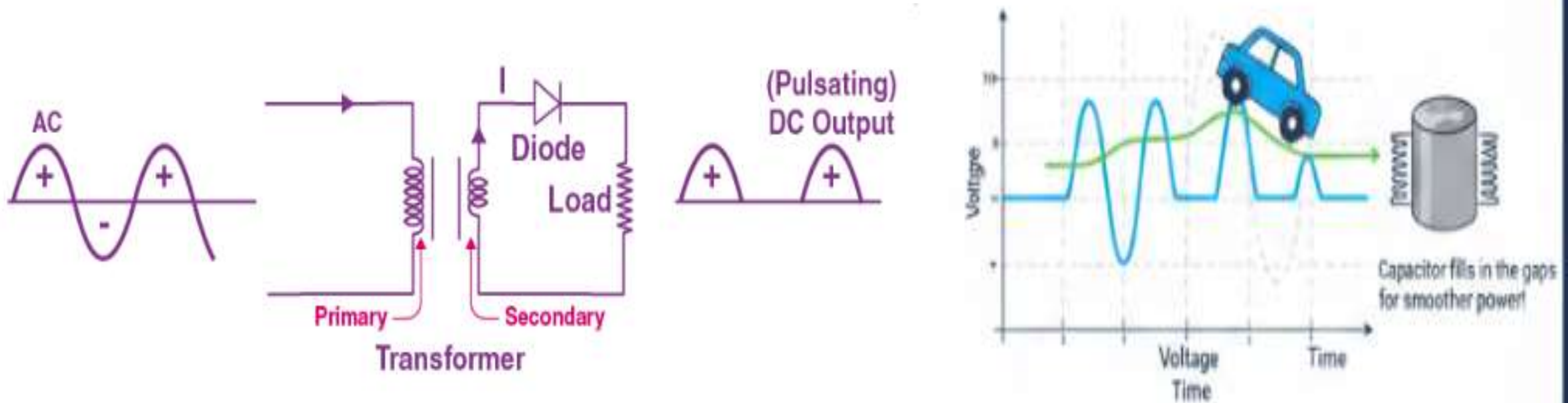The circuit diagram below shows how a capacitive filter is used with halfwave rectifier to smoothen out a pulsating DC waveform into a constant DC waveform.



Applications of Half Wave Rectifier

Here are a few common applications of half wave rectifiers:

They are used for signal demodulation purpose

They are used for rectification applications

They are used for signal peak applications


Disadvantages of Half Wave Rectifier

Power loss

Low output voltage

The output contains a lot of ripples

Real-World Use: Simple Gadgets

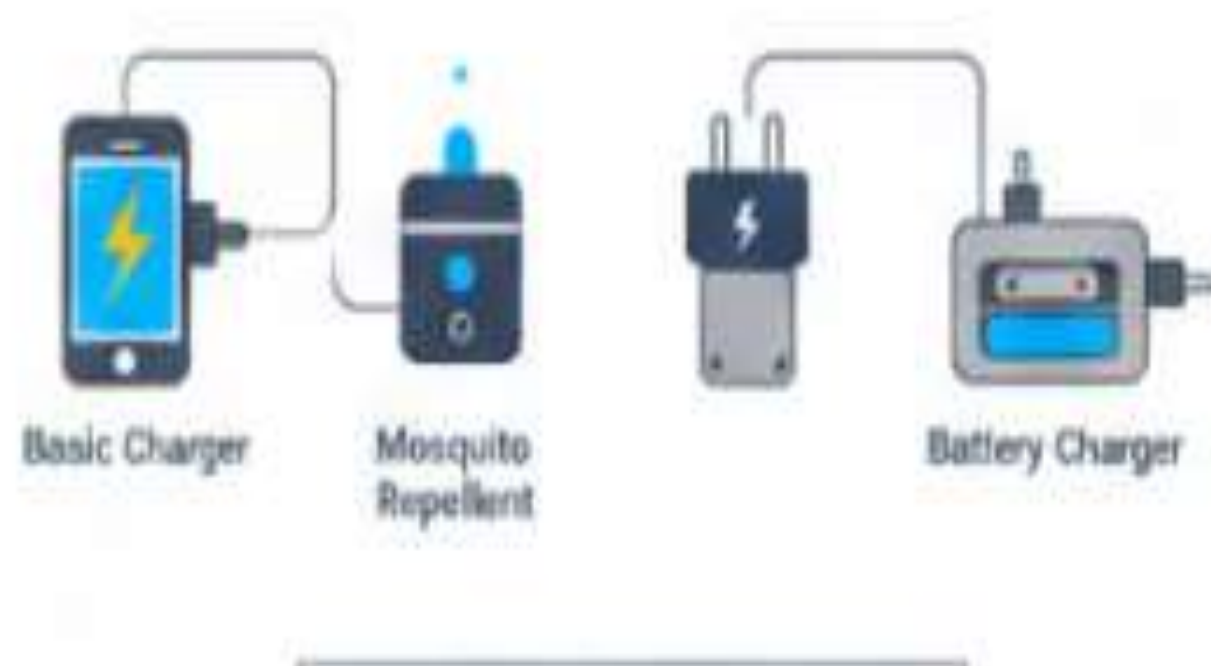

RMS value of Half Wave Rectifier

The RMS value of the load current for a half-wave rectifier is given by the formula:

$$I_{rms} = \frac{I_m}{2}$$

Form factor of a Halfwave Rectifier

The form factor is the ratio between RMS value and average value and is given by the formula:

$$\text{Form Factor} = \frac{\text{RMS Value}}{\text{Average Value}}$$

Half Wave Rectifier Formula

Ripple Factor of Half Wave Rectifier

Ripple factor determines how well a halfwave rectifier can convert AC voltage to DC voltage. Ripple factor can be quantified using the following formula:

$$\gamma = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$$


The ripple factor of a halfwave rectifier

Efficiency of Halfwave Rectifier

The efficiency of a halfwave rectifier is the ratio of output DC power to the input AC power. The efficiency formula for halfwave rectifier is given as follows;

$$\eta = \frac{P_{DC}}{P_{AC}}$$

Summary

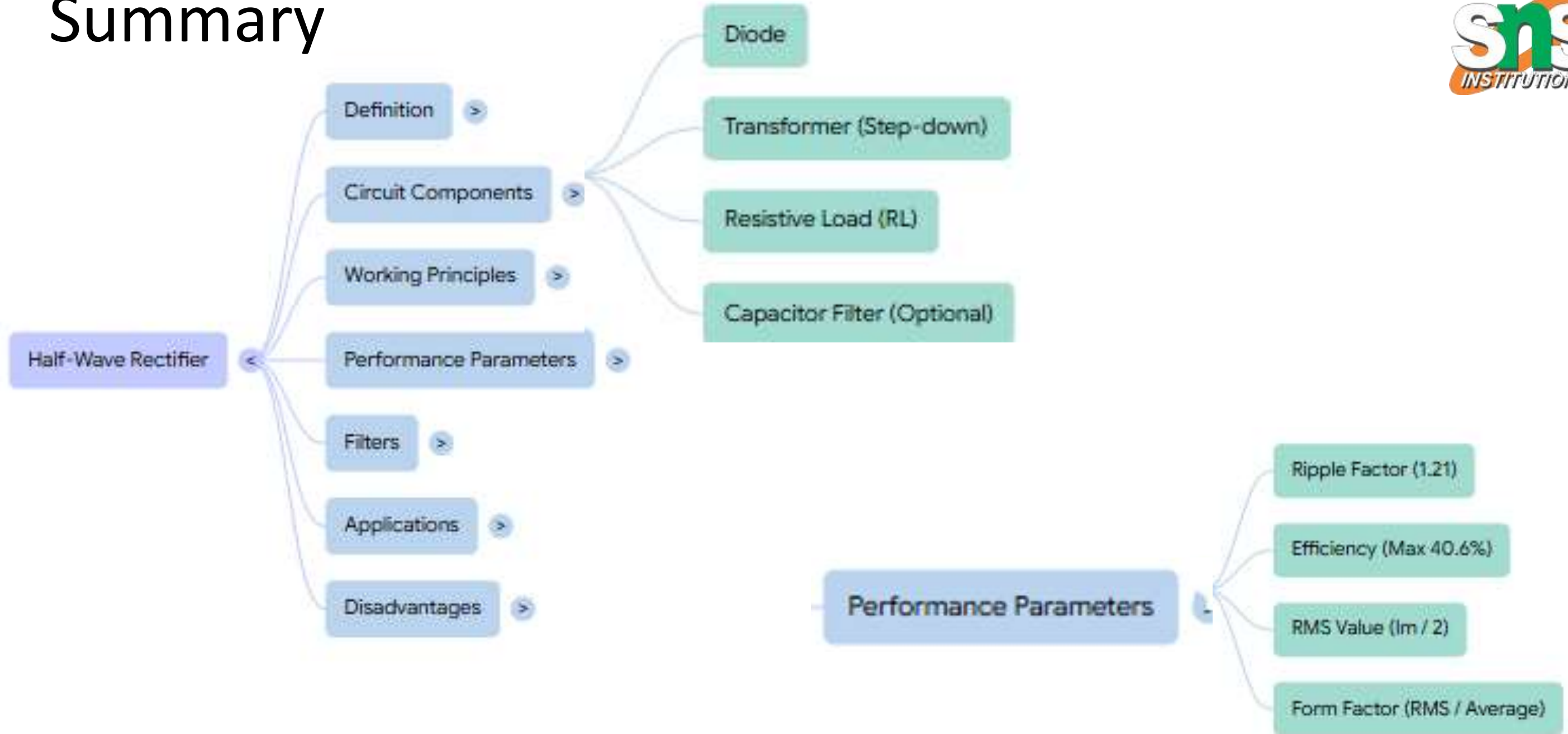

Quiz / Gamified Questions:

1. A diode in a half wave rectifier conducts during:

- A) Positive half cycle
- B) Negative half cycle
- C) Both half cycles
- D) None

(Correct: A)

1. Scenario: You have a small sensor circuit that requires 5V DC but your supply is 9V AC. You want a simple rectification solution. Would a half wave rectifier be ideal? Why or why not?

1. Real-time: If the AC input is 10V RMS and the diode is ideal, calculate the average DC output voltage.

Assessment Q&A

Question

1. Why is ripple factor of half wave rectifier 1.21 and not zero?

Answer

Answer: Only positive half-cycle is passed → output is pulsing, not constant DC
 Ripple factor = $\sqrt{(V_{rms}^2 - V_{dc}^2)}/V_{dc} = 1.21$

2. Can we use half wave rectifier for 100 W laptop charger? Why/Why not?

Answer: NO → Not practical Reasons (with icons):

- Efficiency only 40.6% → 60 W wasted as heat → diode will burn
- High ripple damages laptop battery & components
- Transformer core saturation due to DC component
- Needs at least full-wave + big filter capacitor

3. Curiosity Challenge: Design a circuit to get smooth DC from half wave rectifier (Hint: Add one component)

Answer Revealed: Add one **Electrolytic Capacitor** across load RL
Diagram (before → after):

- Left: Pulsating half-wave output (jagged)
- Right: Smooth DC after adding 1000 μF capacitor (almost flat line)

References



Muthusubramanian R, Salivahanan S, “Basic Electrical and Electronics Engineering”, TataMcGrawHillPublishers,2014.

Kothari DP and I.J Nagrath, “Basic Electrical and Electronics Engineering”, Second Edition, McGraw Hill Education, 2020.

Thank you 