



SNS academy

an International CBSE Finger Print School
Coimbatore



Name :

Date :

Grade :

Worksheet


Submission Date :

Subject : Physics

Parent's sign :

Electric Current and Its Effects

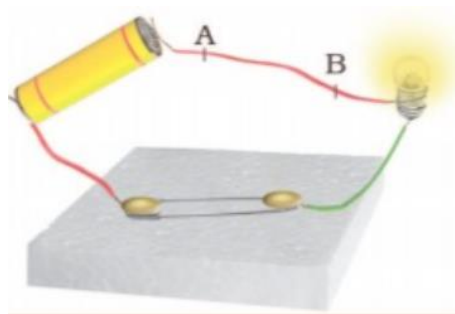1. When an electric current flows through a copper wire AB as shown in Figure 14.1, the wire




- (a) deflects a magnetic needle placed near it
- (b) becomes red hot
- (c) gives electric shock
- (d) behaves like a fuse

2. Choose the statement which is **not correct** in the case of an electric fuse.

- (a) Fuses are inserted in electric circuits of all buildings.
- (b) There is a maximum limit on the current which can safely flow through the electric circuits.
- (c) There is a minimum limit on the current which can safely flow in the electric circuits.
- (d) If a proper fuse is inserted in a circuit it will blow off if current exceeds the safe limit.

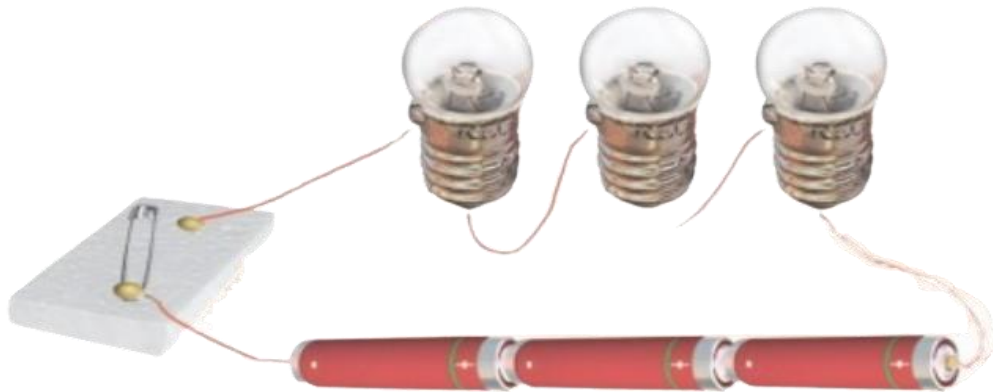3. Three bulbs A, B, C are connected in a circuit as shown in Figure



When the switch is 'ON'

- (a) bulb C will glow first.
- (b) bulb B and C will glow simultaneously and bulb A will glow after some time.
- (c) all the bulbs A, B and C will glow at the same time.
- (d) the bulbs will glow in the order A, B and C.

4. When a switch is in OFF position,


- (i) circuit starting from the positive terminal of the cell stops at the switch.
- (ii) circuit is open.
- (iii) no current flows through it.
- (iv) current flows after some time.

Choose the combination of correct answer from the following.


- (a) all are correct
- (b) (ii) and (iii) are correct
- (c) only (iv) is correct
- (d) only (i) and (ii) are correct

5. In which of the circuits bulb will glow?


(a)

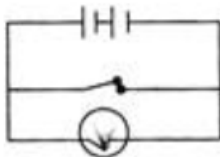


(b)

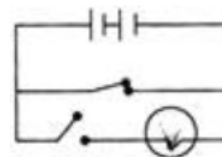

(c)

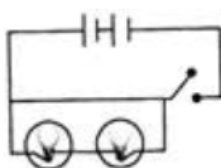


(d)

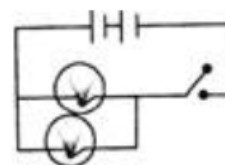

6. Marking on a bulb is 60 W, 220 V. What does it signify?

- (a) The bulb is connected across the 220 volts, 60 joules of energy is consumed for every second.
- (b) The bulb is connected across 220 volts, 60 joules of energy is released.
- (c) 60 unit of current will flow in the bulb.
- (d) 220 unit of current will flow in the bulb.

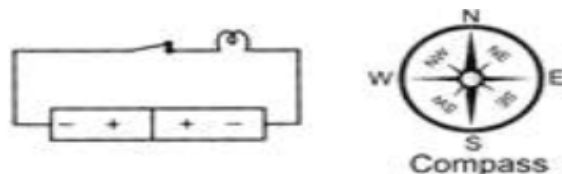7. Which of the following statements is correct for the given circuit?




- (a) The wire has no magnetic effect.
- (b) When compass is kept near to the circuit, it will not show any deflection.
- (c) The given circuit is incomplete because there is no source of electric energy.
- (d) Due to battery in this circuit, electric wire behaves as a magnet.

8. Copper wires are used as connecting wires because

- (a) Copper has very high melting point
- (b) Copper wires are very thick wires
- (c) Copper wire offers a lower resistance
- (d) None of these

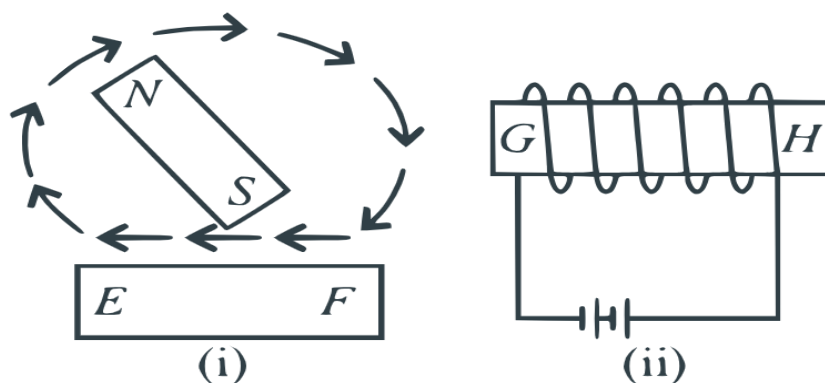
9. Observe the given figures carefully. Figure (i) shows an iron bar stroked by a bar magnet and figure (ii) shows an iron bar which is inserted into a solenoid.



State the polarities of E, F, G and H.

- (a) E – North, F – South, G – South, H – North
- (b) E – South, F – North, G – North, H – South
- (c) E – South, F – North, G – South, H – North
- (d) E – North, F – South, G – North, H – South

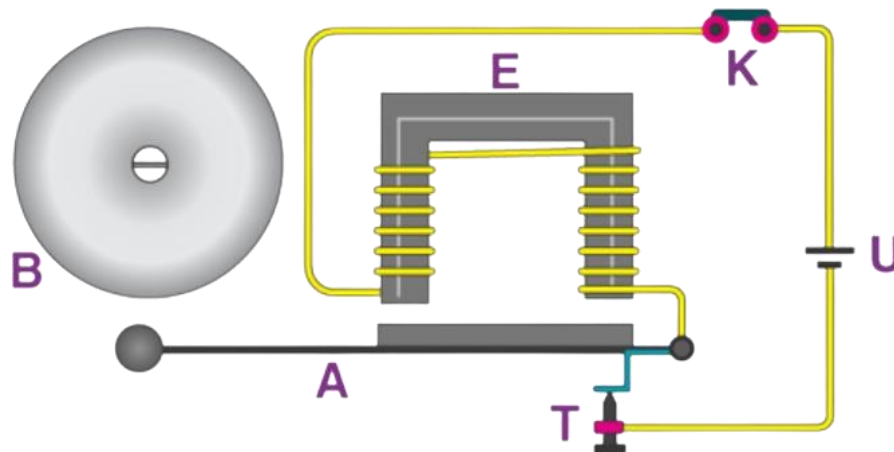10. When the switch of an electric bell is pushed



- (a) flow of the current stops through the electromagnet in the bell
- (b) current starts to flow through the electromagnet
- (c) voltage decreases in the circuit
- (d) none of the above

11. Which of these appliances does not use an electromagnet?

- (a) washing machine
- (b) refrigerator
- (c) room heater
- (d) electric bell

12. If the number of turns in the coil of an electromagnet is more, the strength of the electromagnet will be

- (a) lesser
- (b) greater
- (c) double
- (d) same

13. The coil of wire contained in heater is known as

- (a) circuit
- (b) component
- (c) spring
- (d) element