

## Electricity and circuits

### I Word focus

1. Electricity
2. Circuit
3. Conductor
4. Insulator
5. Battery
6. Switch
7. Current
8. Bulb
9. Cell
10. Resistance

### II KWL

### III Concept map

### IV Q and A

#### 1. Differentiate between a conductor and an insulator. (5 Marks)

Feature	Conductor	Insulator
<b>Definition</b>	A material that allows electric current to pass through it.	A material that does not allow electric current to pass through it.
<b>Flow of Current</b>	Electric current <b>flows easily</b> .	Electric current <b>does not flow</b> .
<b>Examples</b>	Copper, Aluminium, Iron	Plastic, Wood, Rubber
<b>Use in Circuits</b>	Used to <b>carry current</b> (e.g., wires).	Used to <b>prevent electric shocks</b> (e.g., wire coverings).

#### 2. Why does a torch light up only when the switch is turned on? Explain using the concept of an electric circuit.

A torch lights up only when the **switch is turned on** because that action **completes the electric circuit**. When the circuit is complete:

- **Electric current flows** from the **dry cells** (batteries) through the wires.
- The **bulb receives current** and lights up.

- A **dry cell** contains chemicals like **zinc (Zn)** as the **negative terminal** and **carbon (C)** surrounded by **manganese dioxide (MnO<sub>2</sub>)** as the **positive terminal**. A paste of **ammonium chloride (NH<sub>4</sub>Cl)** or **zinc chloride (ZnCl<sub>2</sub>)** is used as the **electrolyte**.
- These chemicals produce electricity through a **chemical reaction**.
- When the **switch is OFF**, the circuit is broken, **no current flows**, and the **bulb does not glow**.

This shows that for any electrical device to work, the **circuit must be complete**, and the **chemical energy in the dry cell is converted into electrical energy** to light the torch.

### 3. What is an electric circuit? Draw a basic electric circuit diagram and prepare a table showing standard symbols used in an electric circuit.

An **electric circuit** is a closed path through which **electric current** flows. It usually includes a **cell, wires, a switch**, and an **electrical component** like a **bulb**. When the circuit is **complete**, the current flows and the device works. If the circuit is **open**, the current does not flow.

Diagram

Table

4. Compare dry cells and secondary cells using a Venn diagram. What are their similarities and differences?

**Electric cells** are devices that convert chemical energy into electrical energy. They are mainly of two types:

- **Primary Cells** (e.g., Dry Cell)
- **Secondary Cells** (e.g., Rechargeable Batteries like Lead-acid cell, Li-ion cell)

#### [ DRY CELLS ]

<ul style="list-style-type: none"> <li>- Used once only</li> <li>- Non-rechargeable</li> <li>- Common in torches, remotes</li> </ul>
--

#### [ SECONDARY CELLS ]

<ul style="list-style-type: none"> <li>- Can be recharged</li> <li>- Reusable</li> <li>- Used in cars, mobiles laptops, etc.</li> </ul>
---

