



SNS COLLEGE OF ALLIED HEALTH SCIENCES- COIMBATORE 35



DEPARTMENT : RADIOGRAPHY AND IMAGNG TECHNOLOGY


**SUBJECT : GENERAL PHYSICS, RADIATION PHYSICS AND PHYSICS OF
DIAGNOSTIC RADIOLOGY**

PAPER : PAPER II (UNIT 5 – PHYSICS OF DIAGNOSTIC RADIOLOGY : X-ray TUBE)

TOPIC : 1. kV and mA circuit – X-ray Tube


Kilovoltage (kV) CONTROL CIRCUIT

- The kilovoltage applied across an X-ray tube determines maximum energy and hence, the penetrating power of the X-rays.
- To have a wide range of penetrating power of X-rays, the applied kilo voltage must be varied in small steps.
- By using a kilovoltage circuit, the kilovoltage can be varied in steps of say 2 kVp.
- A simplified kilovoltage circuit is shown in Figure.
- The circuit has two transformers, namely, an autotransformer and a step-up transformer The autotransformer is actually the kV_p selector and is located in the control panel.
- The voltage across the primary coil of the step-up transformer can be varied by selecting the suitable number of turns in the auto transformer.

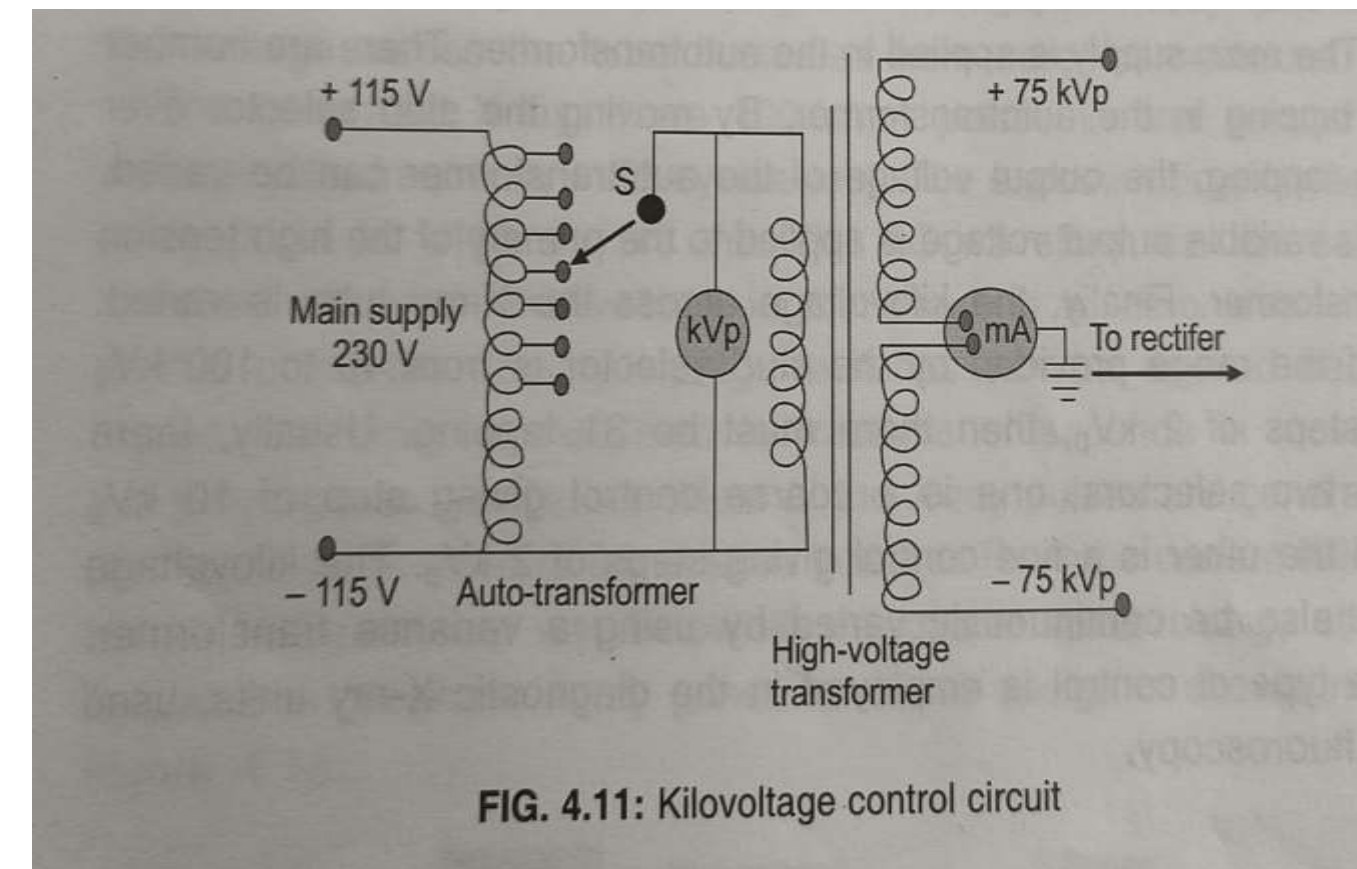


Kilovoltage (kV) CONTROL CIRCUIT

- The secondary coil of the step-up transformer has more turns than primary, and increases the voltage by a factor of 600.
- The potential difference across the secondary coil may be as high as 150,000 V, so the step-up transformer is immersed in oil for maximum insulation.
- There are two meters in the circuit, one to measure kV_p (voltmeter) and the other to measure mA (ammeter).
- The meters are located on the control panel, but their connections are in the high voltage circuit.
- They indicate the potential across the X-ray tube and the actual current flowing through the tube during exposure.

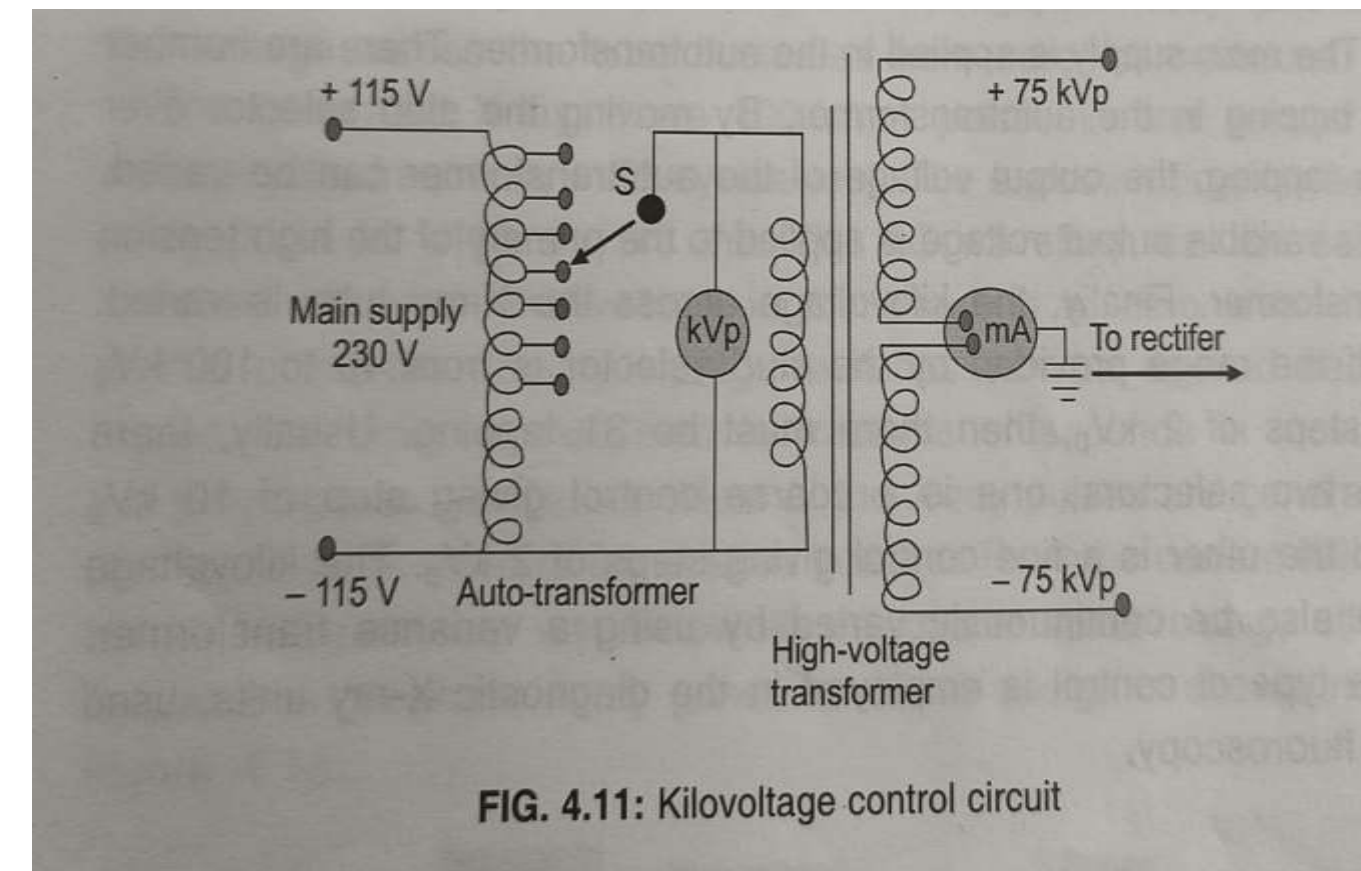


Kilovoltage (kV) CONTROL CIRCUIT

- The potential difference across the X-ray tube can be measured indirectly on the low voltage side of the transformer.
- Therefore, the kV_p meter is placed in the circuit between the autotransformer and step-up transformer. Because the kV_p meter records the selected kV_p before the actual exposure begins it is usually termed as pre-reading kV_p . If the kV_p meter is properly calibrated, it can directly read the applied voltage across the X-ray tube.
- Since the voltage in the primary circuit is relatively small, the meter can be placed on the control panel. This requires minimum insulation without any risk of electrical shock.

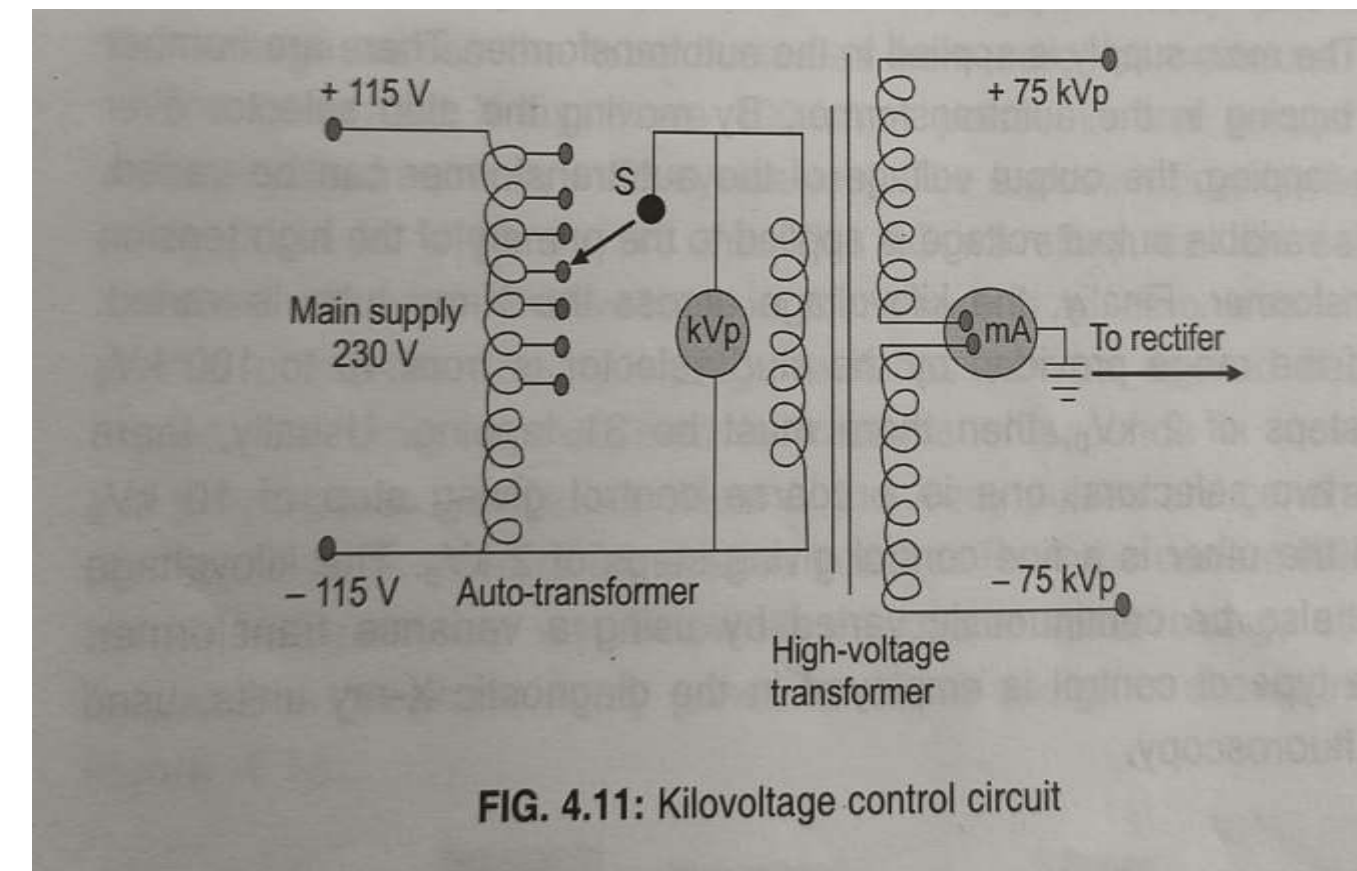


Kilovoltage (kV) CONTROL CIRCUIT

- The connections for the mA meter must be in the secondary winding of the transformer.
- Since the efficiency of the transformer is less than 1, measurement at primary level is not the true representation of the current in the secondary.
- Hence, the mA meter is connected at the center of the secondary coil, at which the transformer is grounded.
- This will minimize the risk of electric shock to the operator, since the center of the coil is at zero potential.
- Though the meter is connected at this point, it may be placed at the control panel.

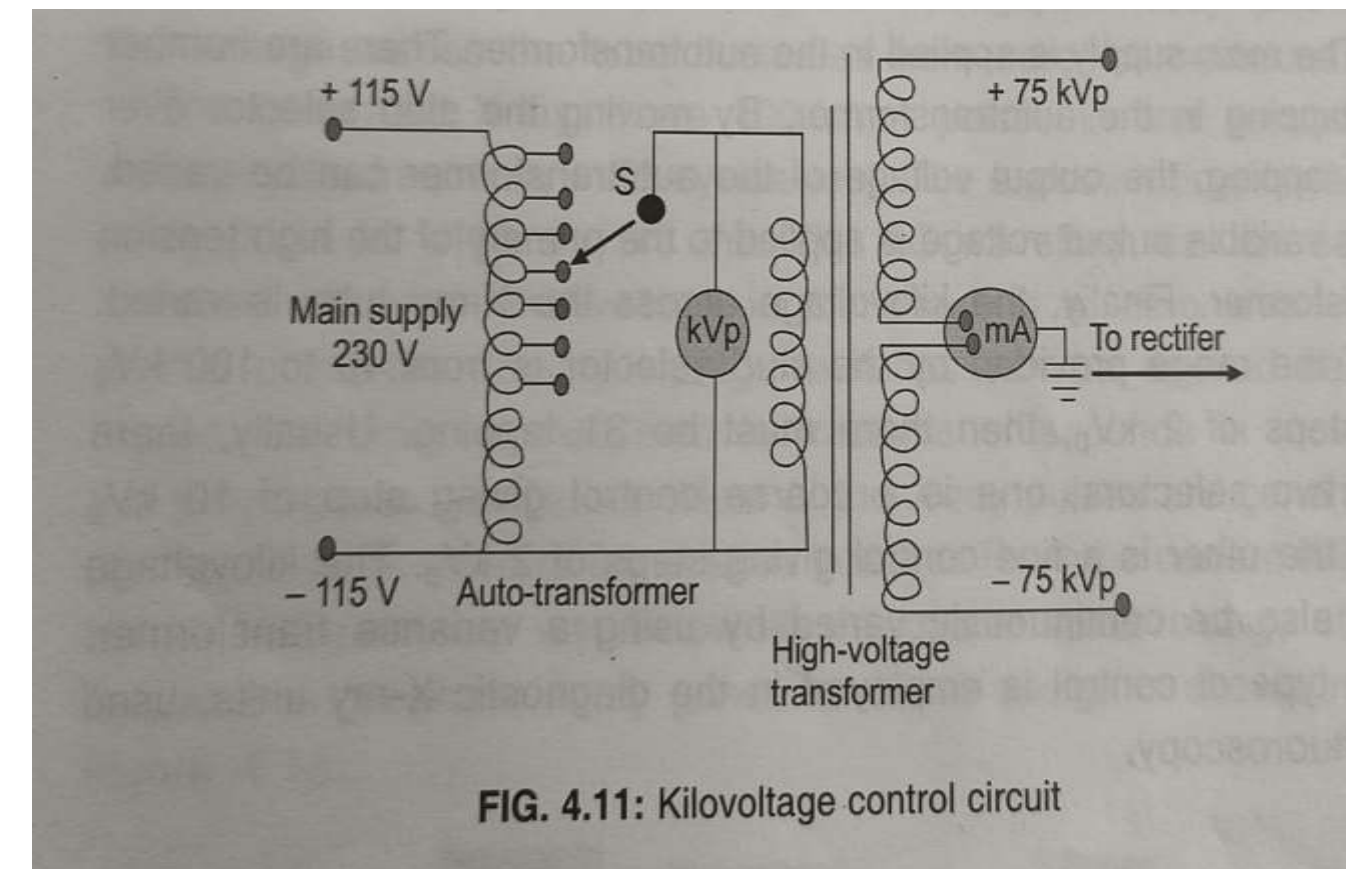

Kilovoltage (kV) CONTROL CIRCUIT

- The main supply is applied to the autotransformer. There are number of tapping in the autotransformer.
- By moving the stud selector over the tapping, the output voltage of the autotransformer can be varied.
- This variable output voltage is applied to the primary of the high tension transformer.
- Finally, the kilovoltage across the X-ray tube is varied. If the range provided by the stud selector is from 40 to 100 kVp in steps of 2 kVp, then there must be 31 tapping.
- Usually, there are two selectors, one is a coarse control giving step of 10 kVp and the other is a fine control giving steps of 2 kVp.
- The kilovoltage can also be continuously varied by using a variance transformer.
- This type of control is employed in the diagnostic X-ray units, used for fluoroscopy.

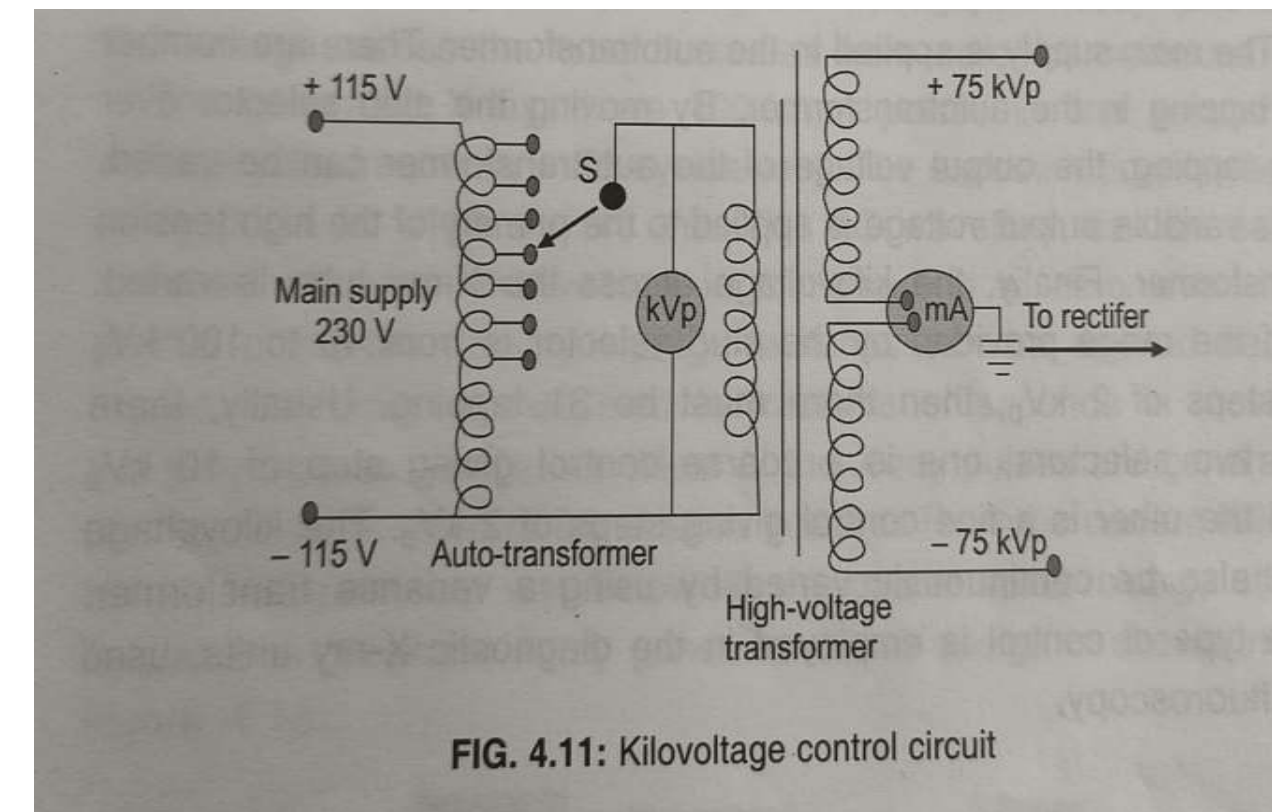

Filament circuit (mA)

- The tube current can be altered by altering the number of electrons emitted by the filament.
- The number of electrons can be altered by changing the temperature of the filament. To achieve this, a filament circuit is used, which will regulate current flow through the filament (Fig).
- The power to heat the filament is provided by a small step-down transformer, called the filament transformer.
- In addition, the circuit consists of a variable resistor network and a focal spot size selector. This transformer has 10-20 times more turns in primary coil, compared to secondary coil. The filament is connected directly to the secondary coil of a step-down transformer.
- The primary coil of the transformer obtains its voltage from the auto transformer. Usually, the primary voltage will be around 100-200 V, whereas the secondary voltage


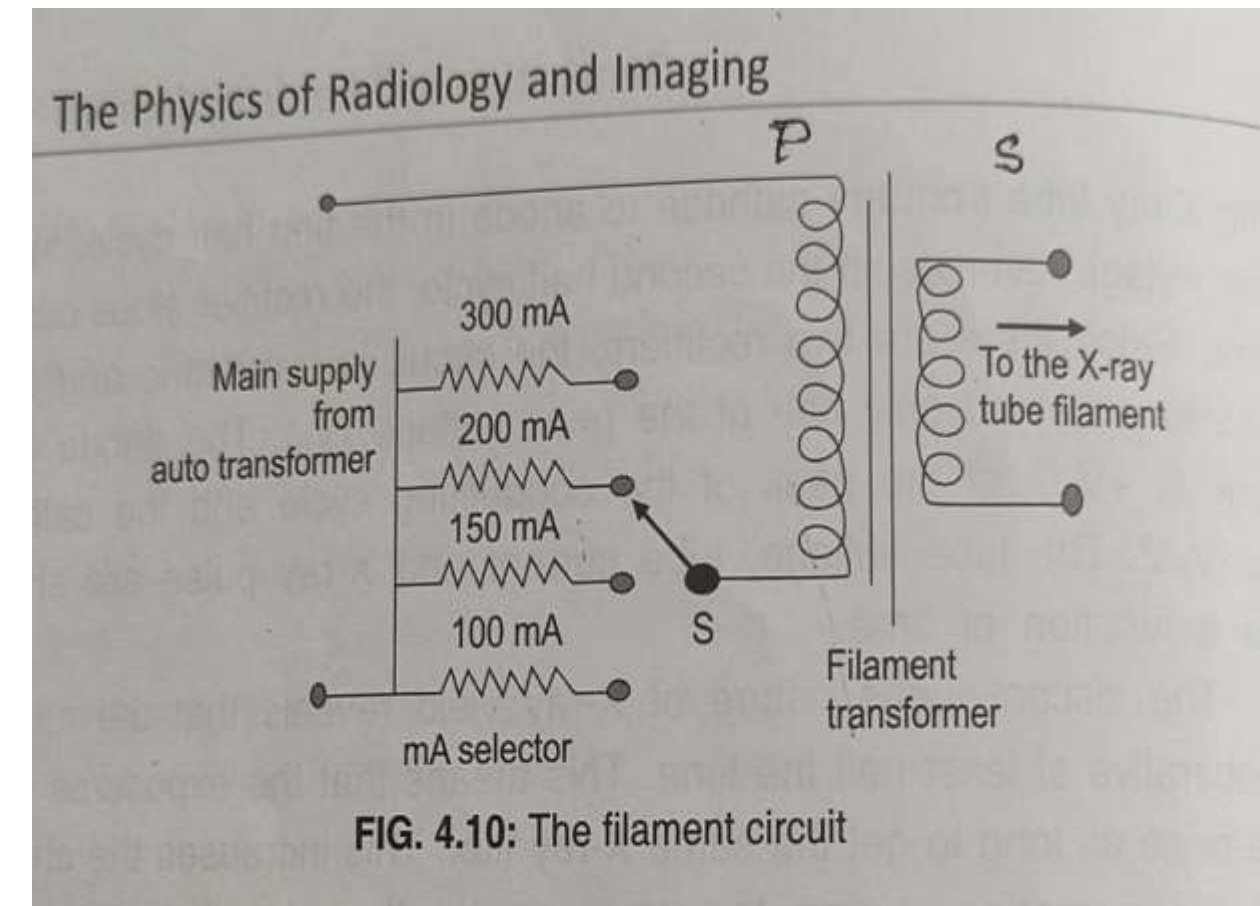


FIG. 4.10: The filament circuit


Filament circuit (mA)

- The power to heat the filament is provided by a small step-down transformer, called the filament transformer.
- In addition, the circuit consists of a variable resistor network and a focal spot size selector.
- This transformer has 10-20 times more turns in primary coil, compared to secondary coil. The filament is connected directly to the secondary coil of a step-down transformer.
- The primary coil of the transformer obtains its voltage from the auto transformer. Usually, the primary voltage will be around 100-200 V, whereas the secondary voltage is around 10 V and current up to 7A.
- This makes it necessary to provide high voltage insulation between primary and secondary coils. Hence, the filament transformer is placed in the same oil-filled grounded metal tank as the high voltage transformer.

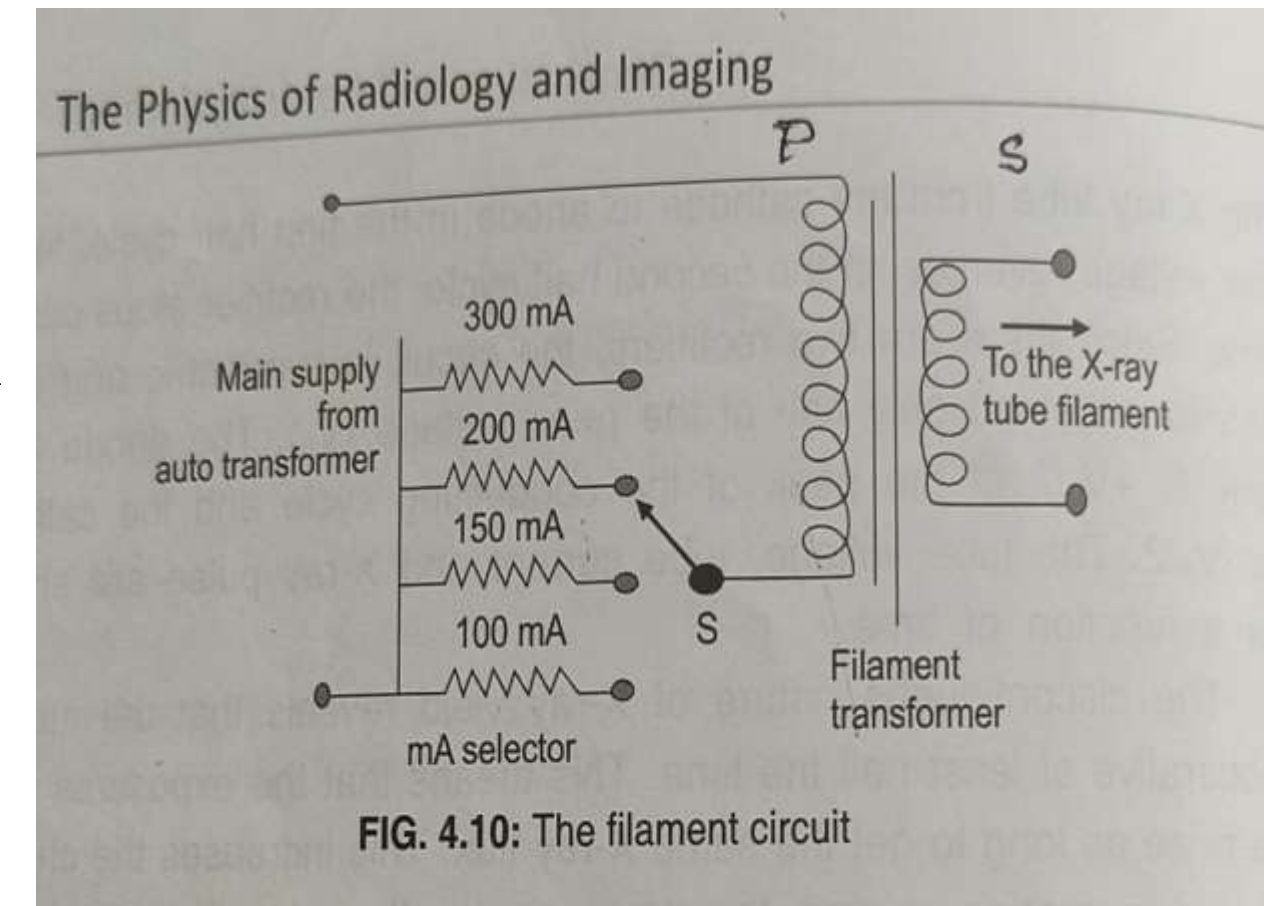

Filament circuit (mA)

- Precise control of filament heating is very essential. A small variation in the filament current results in a large variation in X-ray tube current.
- A 5% change in filament voltage may bring a change of 20-30% in X-ray tube current. The filament current may be controlled, by altering the voltage to the primary of the step-down transformer, by addition of resistors connected in series.
- The resistors may be a number of separate resistors or a single variable resistor. As the resistance increases, the voltage to the filament decreases. For example, a current of 4 A and a resistance of 1.5 ohms will reduce voltage by 6 V.
- When the selector S moves over the resistors, the primary voltage of the transformer is altered. As a result, different values of tube current (mA) are obtained. The selector is either a rotary switch or a push button located on the control panel. The circuit also has other components to stabilize the voltage to the filament transformer that includes a voltage stabilizer and a frequency stabilizer. There is also a circuit that automatically compensates for the space charge effect.

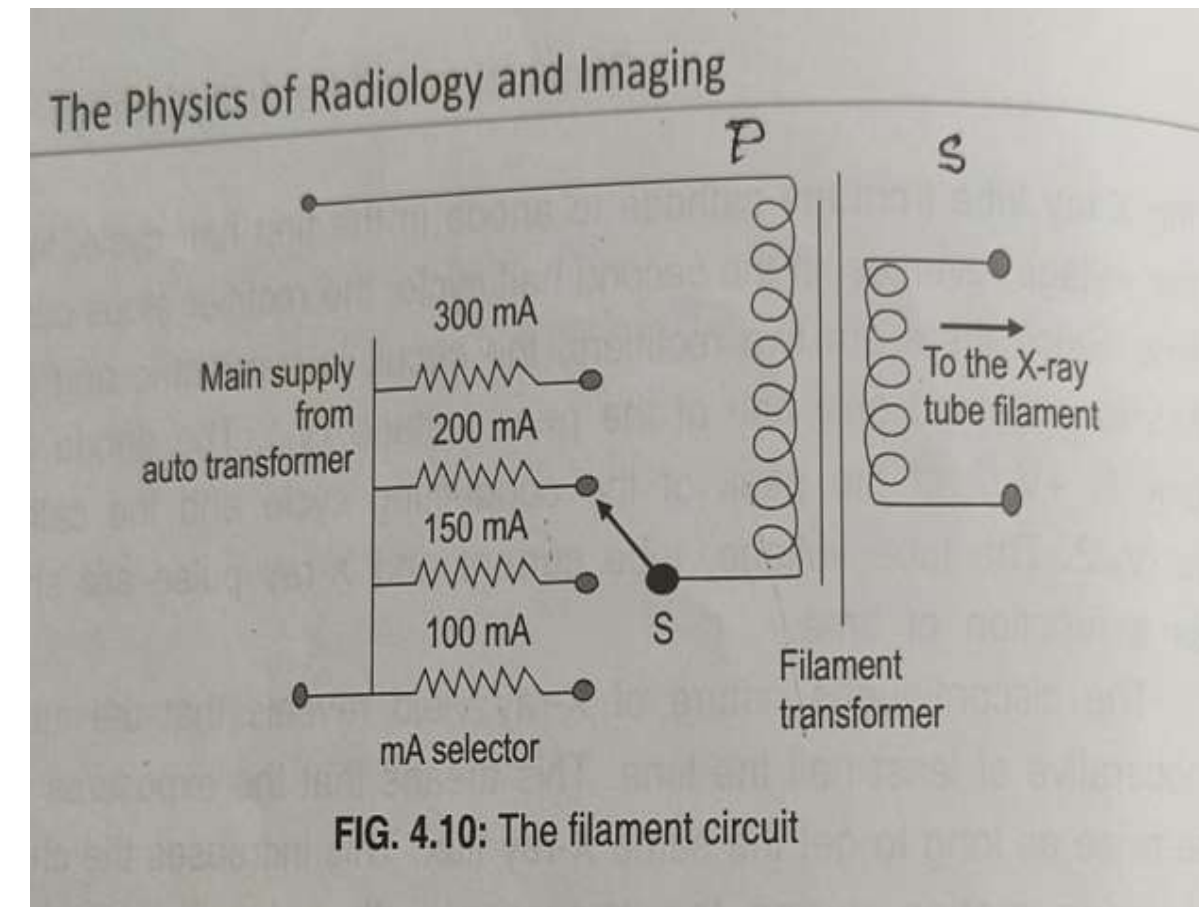



INTERROGATIONS

1. The difference between kV and mA circuit in X-ray tube
2. What dose the kVp and mA control in the X-ray tube ?
3. How dose kV and mAs effect image quality ?



INTERROGATIONS



1. What is Attenuation ?
2. What is Absorption ?
3. What is Scattering ?



REFERENCES

1. Physics for Radiography - Hay and Hughs
2. Ball and mores essential physics radiographers, IV edition, Blackwell publishing.
3. Basic Medical Radiation physics – Stanton.
4. Christensen's Physics of Diagnostic Radiology – Christensen.
5. The physics of Radiology and Imaging – K Thayalan.



THANK YOU