



# SNS COLLEGE OF ENGINEERING

Kurumbapalayam (Po), Coimbatore – 641 107



AN AUTONOMOUS INSTITUTION

Approved by AICTE, New Delhi and Affiliated to Anna University, Chennai



I Semester




B.E-Mechanical Engineering

19EE101 – Basic Electrical and Electronics Engineering

Regulations 2019

## QUESTION BANK FOR IAE 1

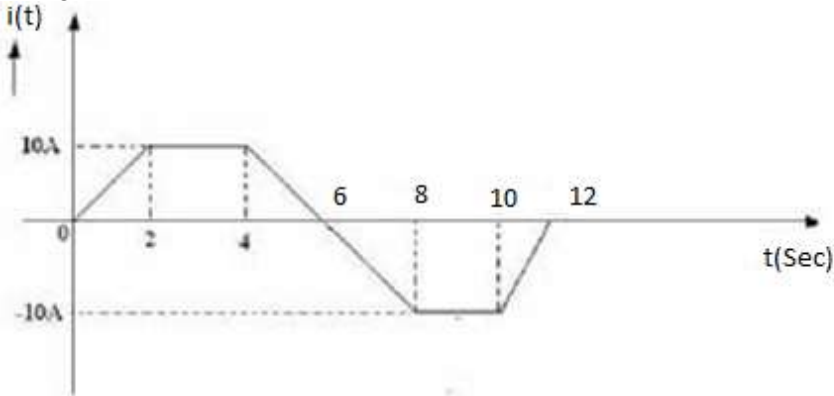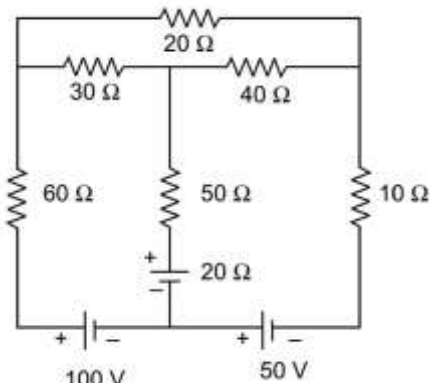PART A	
1	State Kirchoff's Voltage Law.
2	State the limitations of ohms law.
3	List the essential requirements (torque) of an instrument.
4	Define Ohm's Law.
5	State Kirchoff's Current Law.
6	Find the average value of 
7	Write down the EMF equation of a DC generator.
8	List the functions of commutator.
9	Give the application of DC Motor.
10	Differentiate between separately excited DC Generator and self-excited DC generator.
11	Distinguish between series and parallel circuit.
12	Compare Mesh and Loop.
13	Write current division rule.
PART B	
1	Calculate the current in the 50 Ω resistor in the network shown in fig using mesh analysis. Also determine the voltage drop across the 20 Ω resistor. 

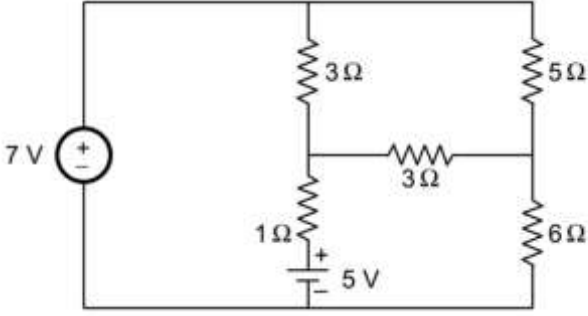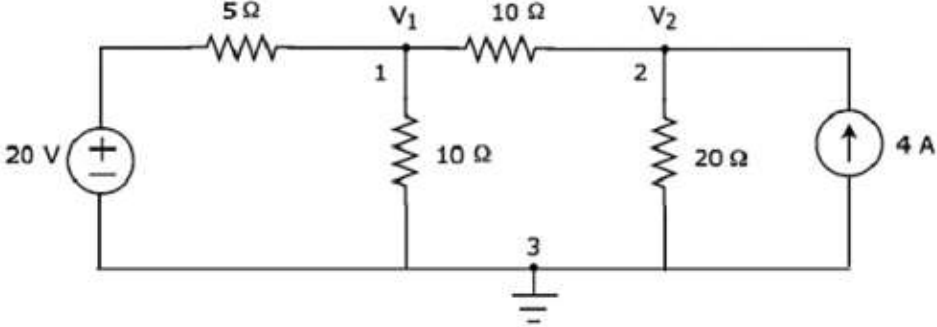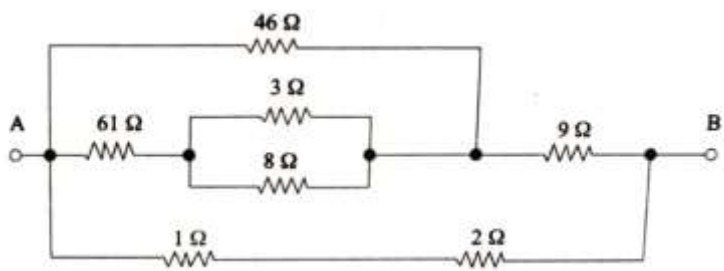2	<p>Illustrate the mesh currents and also the current through <math>1\ \Omega</math> resistance in the circuit shown in fig.</p> 
3	<p>Use Kirchoff's law to determine the node voltage <math>V_1</math> and <math>V_2</math> for shown in fig.</p> 
4	<p>With a neat schematic diagram explain the operation of single phase energy meter.</p>
5	<p>Discuss the principle of operation of permanent magnet moving coil instruments with neat sketches.</p>
6	<p>Determine the amount of total resistance between points A and B of the circuit shown in fig.</p> 
7	<p>Discuss the principle of operation of dynamometer type wattmeter.</p>
8	<p>Elaborate the constructional details and working principle of DC Generator with a neat sketch also list its applications.</p>
9	<p>Elaborate the construction and operation of rotating device, which convert electrical energy to mechanical energy.</p>
10	<p>A wave connected armature winding has 19 slots with 54 conductors per slot. If the flux per pole is <math>0.025\text{wb}</math> and number of poles is 8, find the speed at which the generator should be run to give 513V. Also find the speed if the armature is lap connected.</p>
11	<p>(i) A 50 KW, 250 V Shunt generator operates on full load at 1500 rpm. The armature has 6 poles and is lap wound with 200 turns. Find the induced EMF and the flux per pole at full load. Given that the armature and field resistances are <math>0.01\ \Omega</math> <math>125\ \Omega</math> respectively. Neglect armature reaction.</p> <p>(ii) Obtain the mathematical expression for generated EMF of DC Generator and explain each term.</p>
12	<p>With a suitable sketch explain the principle of operation of attraction type and repulsion type of moving iron instruments.</p>

13

Use circuit reduction technique, to determine the equivalent resistance between A and B for given circuit.

