



SNS COLLEGE OF ENGINEERING

Kurumbapalayam (Po), Coimbatore – 641 107

An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

UNIT – I

Representation of Power System

Z- Bus Building Algorithm



Flow of Presentation



1. Introduction
2. Addition of branch and link
3. Case – 1 Modification
4. Case – 2 Modification
5. Case – 3 Modification
6. Case – 4 Modification



Introduction



1. **Step by Step programmable technique**
2. **Proceeds branch by branch**
3. **Advantageous as complete rebuilding not required**



Four Different Ways





1. **Case 1: Adding a branch of impedance from new bus $-p$ to the reference bus.**
2. **Case 2: Adding a branch of impedance from new bus $-p$ to an existing bus q .**
3. **Case 3: Adding a branch of impedance from an existing bus q to the reference bus.**
4. **Case 4: Adding a branch of impedance between two existing buses h and q**



Four Different Ways




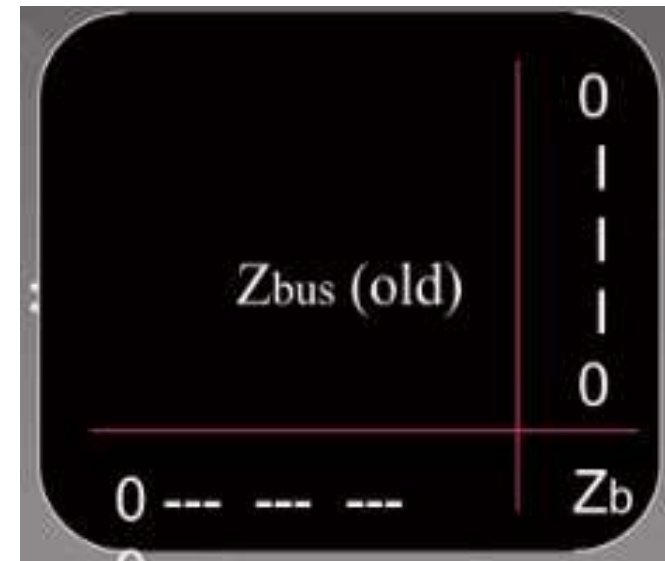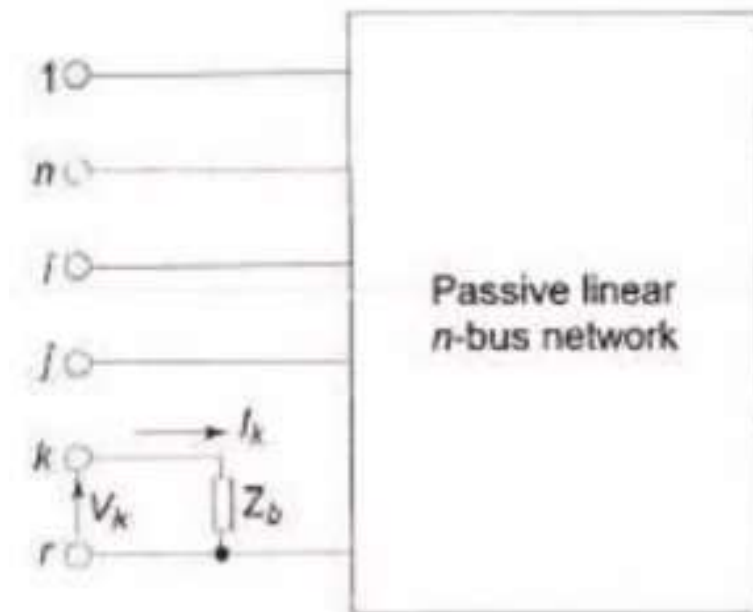1. **Case 1: Adding a branch of impedance from new bus –k to the reference bus.**



Four Different Ways

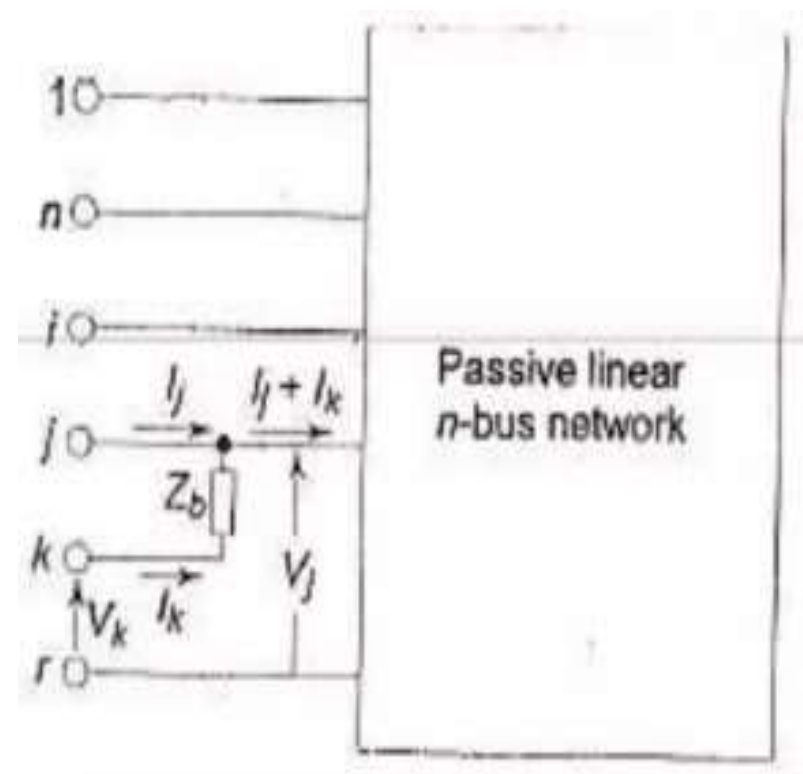
- Case 2: Adding a branch of impedance from new bus –p to an existing bus q.**



$$Z_{\text{BUS}} (\text{new}) = \left[\begin{array}{c|c} Z_{\text{BUS}} (\text{old}) & \begin{array}{c} Z_{1j} \\ Z_{2j} \\ \vdots \\ Z_{nj} \end{array} \\ \hline \begin{array}{c} Z_{j1} \quad Z_{j2} \quad \dots \quad Z_{jn} \end{array} & Z_{jj} + Z_b \end{array} \right]$$

Four Different Ways

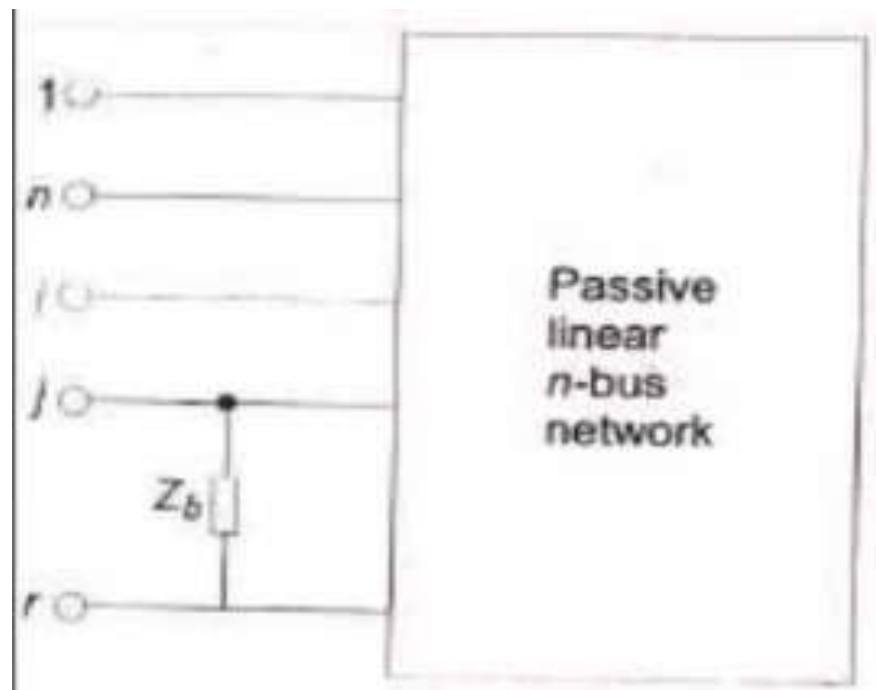1. **Case 3: Adding a branch of impedance from an existing bus q to the reference bus.**




$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_n \\ 0 \end{bmatrix} = \begin{bmatrix} & & & Z_{1j} \\ & & & Z_{2j} \\ & & & \vdots \\ & & & Z_{nj} \\ \hline Z_{j1} & Z_{j2} & \dots & Z_{jn} & Z_{jj} + Z_b \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_n \\ I_k \end{bmatrix}$$

$$Z_{BUS} \text{ (new)} = Z_{BUS} \text{ (old)} - \frac{1}{Z_{jj} + Z_b} \begin{bmatrix} Z_{1j} \\ \vdots \\ Z_{nj} \end{bmatrix} [Z_{j1} \dots Z_{jn}]$$

Four Different Ways

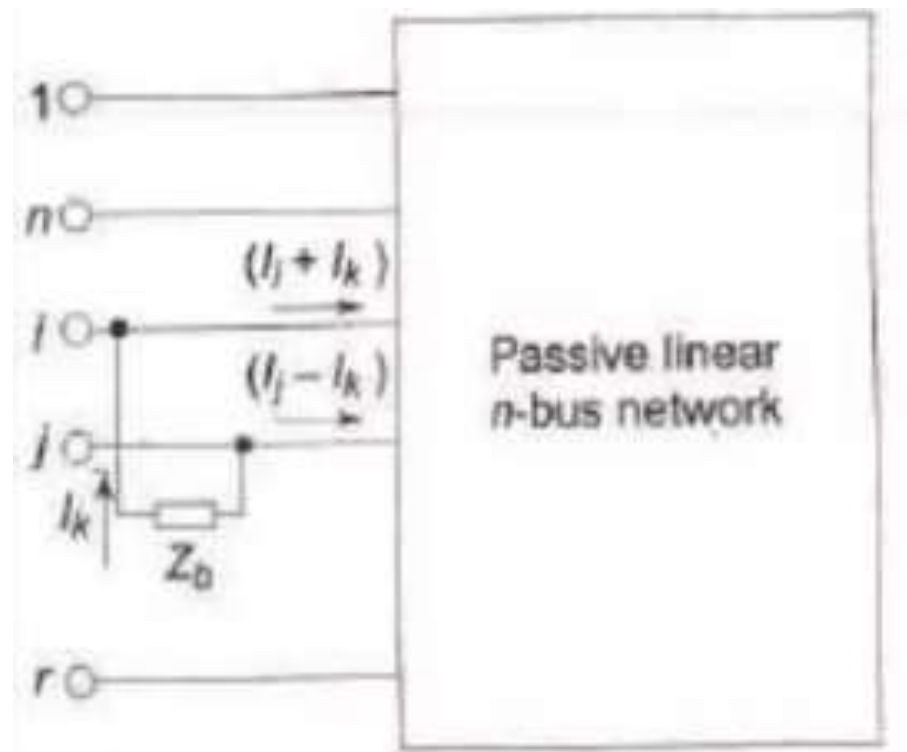- Case 4: Adding a branch of impedance between two existing buses h and q**



$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_n \\ - \\ 0 \end{bmatrix} = \left[\begin{array}{c|c} Z_{BUS} & \begin{matrix} (Z_{ji} - Z_{kj}) \\ \vdots \\ (Z_{ni} - Z_{nj}) \end{matrix} \\ \hline \begin{matrix} (Z_{ji} - Z_{kj}), \dots, (Z_{mi} - Z_{mj}) \end{matrix} & Z_h + Z_{ij} + Z_{ij} - 2Z_{ij} \end{array} \right]$$



ASSESSMENT



1. In determining a Z bus matrix what is the procedure to be followed while we connect both existing busses.

