



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai




19EET101 / BASICS OF ELECTRICAL AND ELECTRONICS ENGINEERING I YEAR / I SEMESTER

UNIT-II: ELECTRICAL MACHINES

PRINCIPLE OF OPERATION OF DC GENERATOR




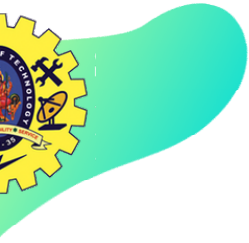

TOPIC OUTLINE




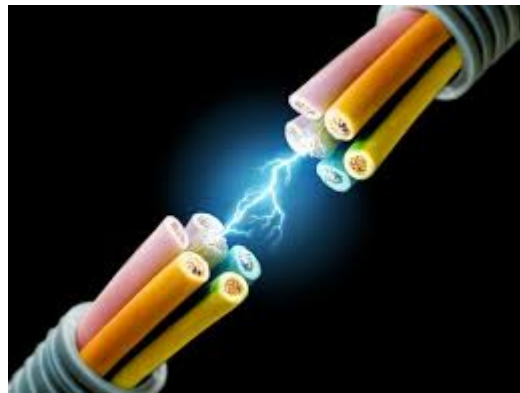- ✓ Faraday's Laws
- ✓ Lenz Law
- ✓ Working Principle
- ✓ EMF Equation
- ✓ Applications






Types of DC generator

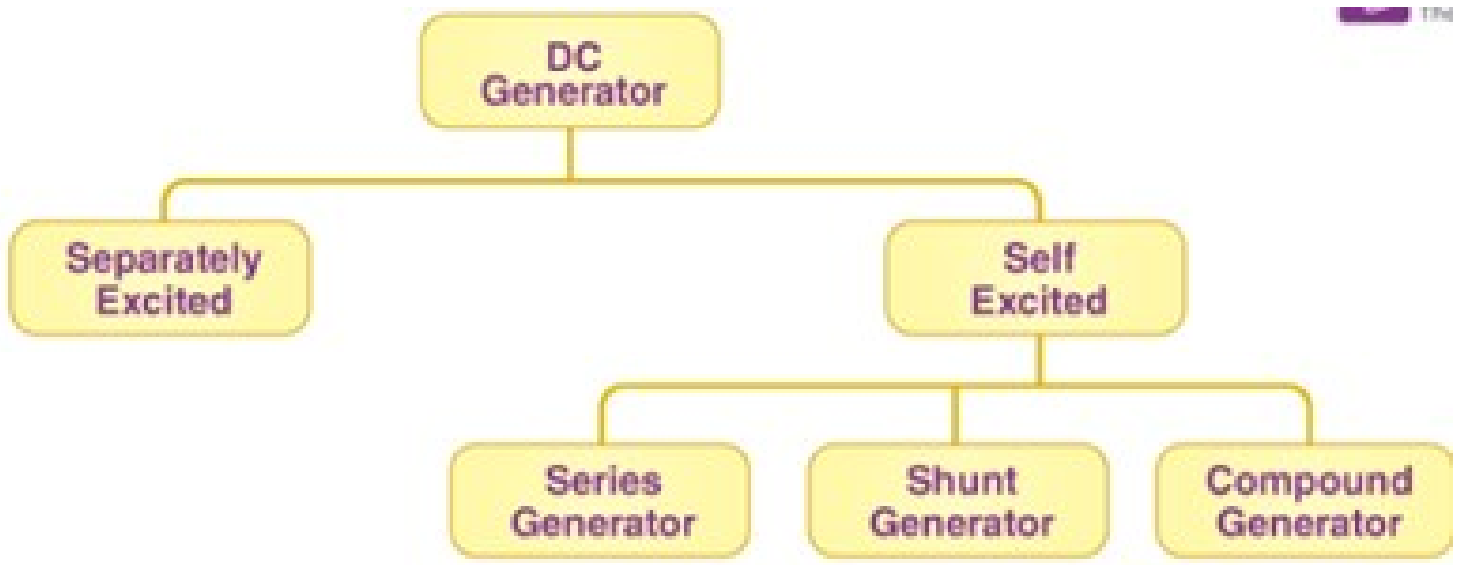



Separately Excited

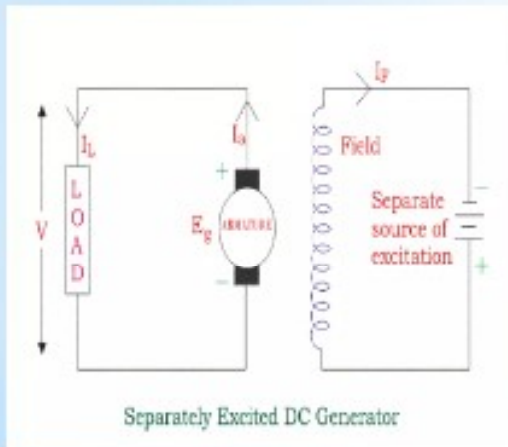These are the generators whose field magnets are energized by some external dc source such as Battery.



Separately Excited DC Generator

I_a = Armature current

I_L = Load current

V = Terminal voltage


E_g = Generated emf

Voltage drop in the armature = $I_a \times R_a$ (R_a is the armature Resistance)

Let, $I_a = I_L = I$ (say)

Then, Voltage across the load, $V = IR_a$

Power generated, $P_g = E_g \times I$

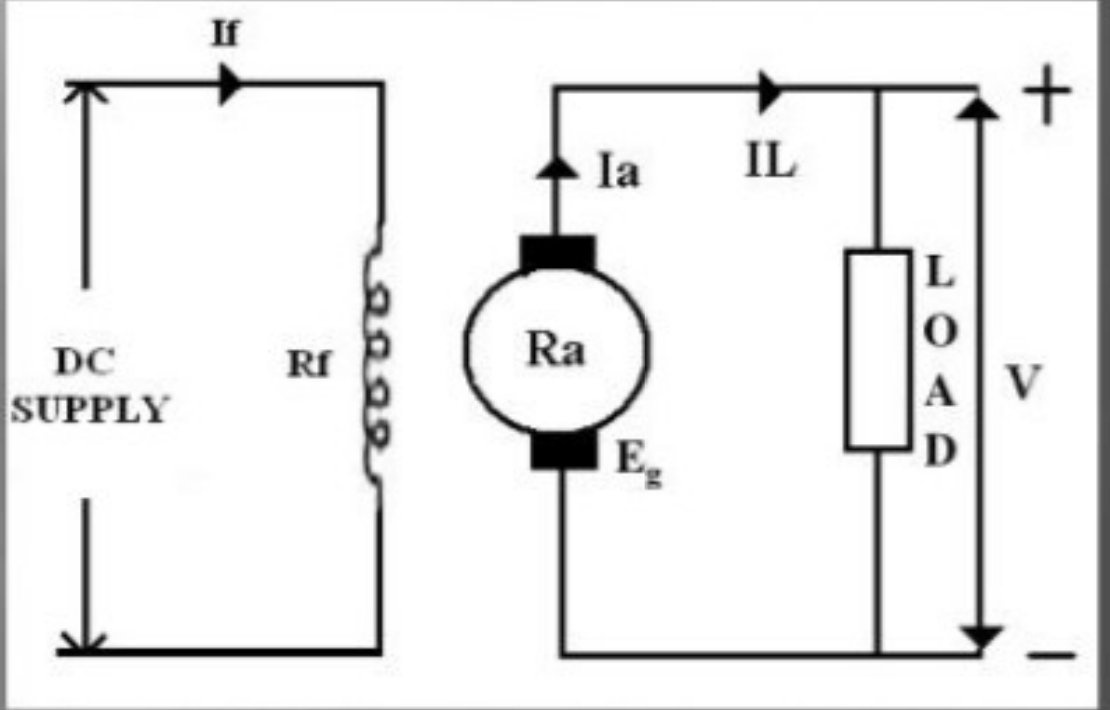


Armature current, $I_a = I_L$
Terminal voltage, $V = E_g - I_a R_a$
Electric power developed = $E_g I_a$
Power delivered to load = $E_g I_a - I_a^2 R_a = I_a (E_g - I_a R_a) = V I_a$





SELF EXCITED SHUNT GENERATOR

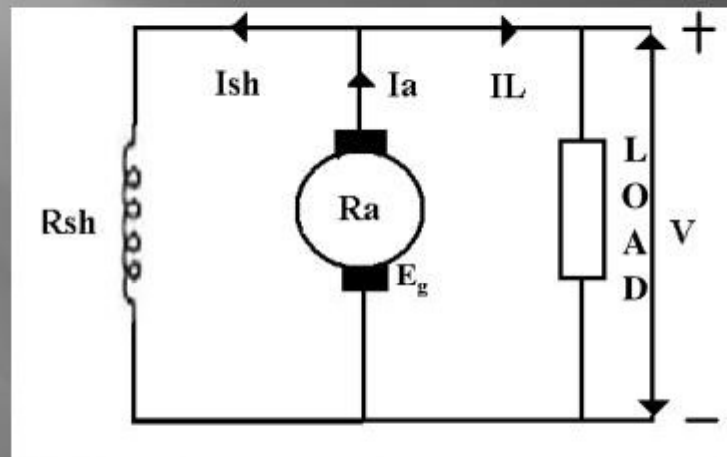


Shunt field current, $I_{sh} = V/R_{sh}$
Armature current, $I_a = I_L + I_{sh}$
Terminal voltage, $V = E_g - I_a R_a$
Power developed in armature = $E_g I_a$
Power delivered to load = $V I_L$

D.N.DEVANI (ELECTRICAL)





SELF EXCITED SERIES GENERATOR

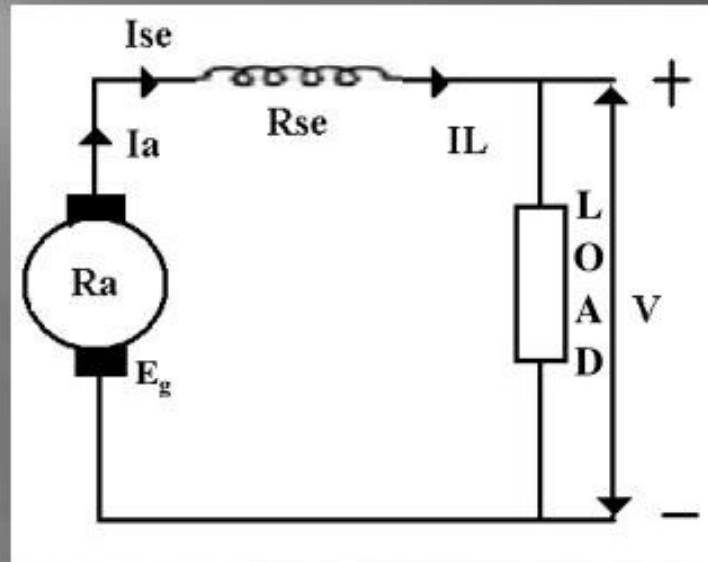

Armature current, $I_a = I_{se} = I_L = I$ (say)

Terminal voltage, $V = E_g - I(R_a + R_{se})$

Power developed in armature = $E_g I_a$


Power delivered to load

$$= E_g I_a - I_a^2 (R_a + R_{se}) = I_a [E_g - I_a (R_a + R_{se})] = VI_a \text{ or } VI_L$$

D.N.DEVANI (ELECTRICAL)



SELF EXCITED COMPOUND GENERA.

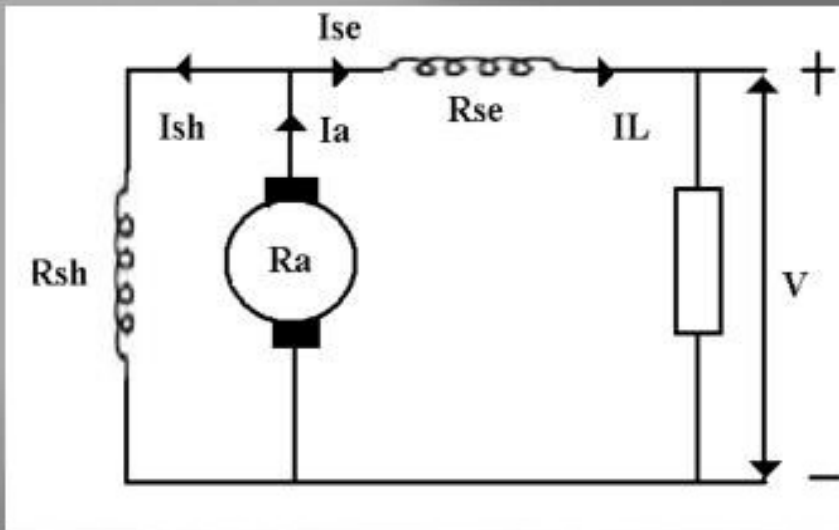

Short shunt


Series field current, $I_{se} = I_L$

Shunt field current, $I_{sh} = \frac{V + I_{se}R_{se}}{R_{sh}}$

Terminal voltage, $V = E_g - I_a R_a - I_{se} R_{se}$

Power developed in armature = $E_g I_a$

Power delivered to load = $V I_L$

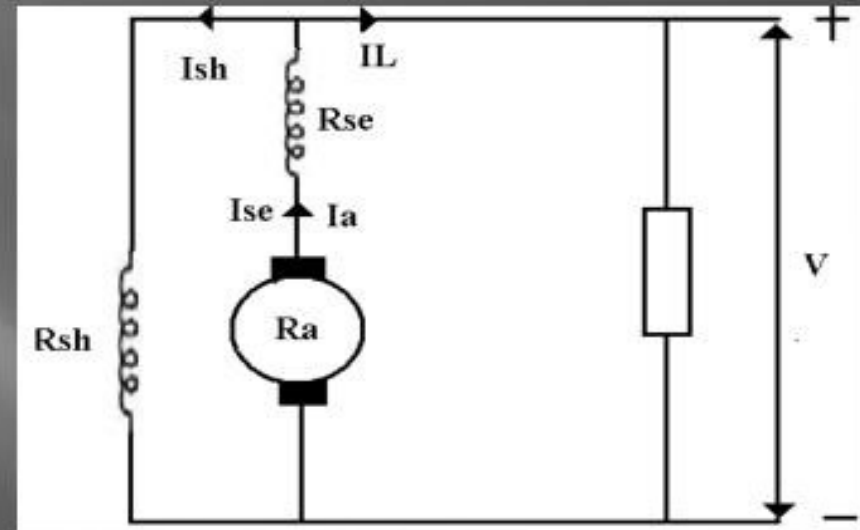

Long shunt

Series field current, $I_{se} = I_a = I_L + I_{sh}$

Shunt field current, $I_{sh} = V/R_{sh}$

Terminal voltage, $V = E_g - I_a(R_a + R_{se})$

Power developed in armature = $E_g I_a$


Power delivered to load = $V I_L$

D.N.DEVANI (ELECTRICAL)



Basic requirements to be satisfied for generation of E.M.F

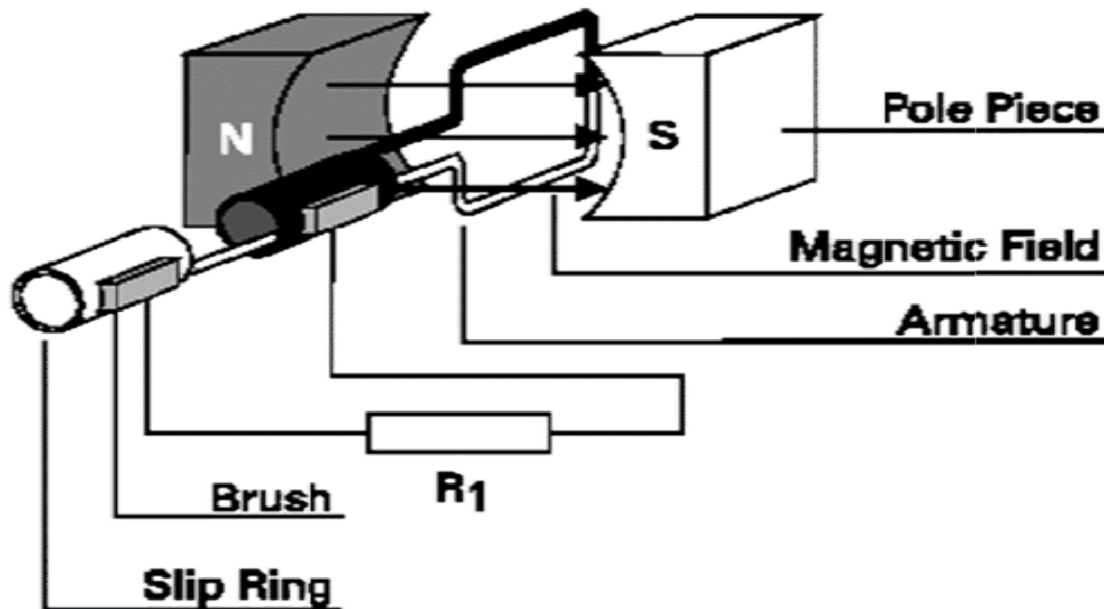
1. A uniform Magnetic field
2. A System of conductors
3. Relative motion between the magnetic field and conductors






PRINCIPLE OF OPERATION

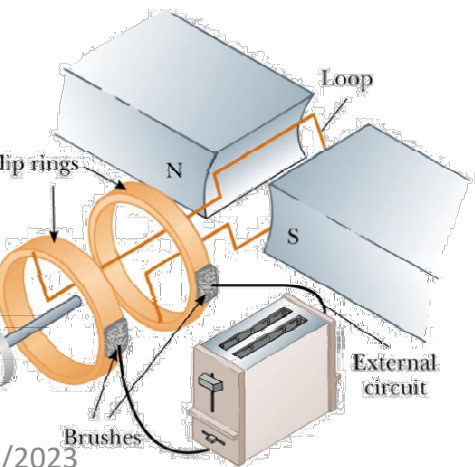
- ✓ DC generator converts mechanical energy into electrical energy.
- ✓ when a conductor move in a magnetic field in such a way conductors cut across a magnetic flux of lines and e.m.f. produces in a generator and it is defined by faradays law of electromagnetic induction e.m.f. causes current to flow if the conductor circuit is closed.




Operation of a Generator

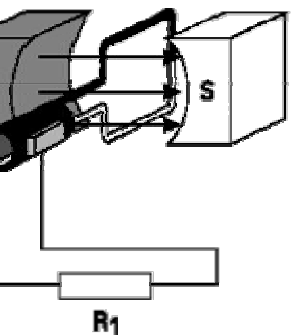


(A)

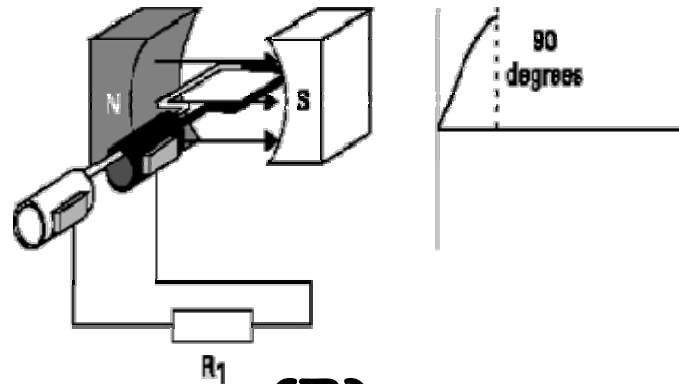


(B)

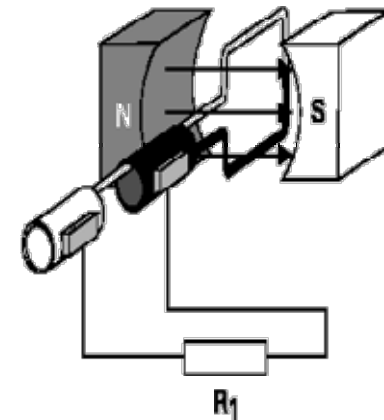

(C)

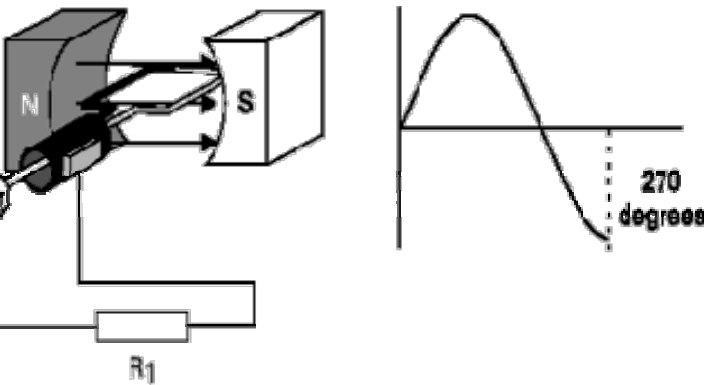


(D)

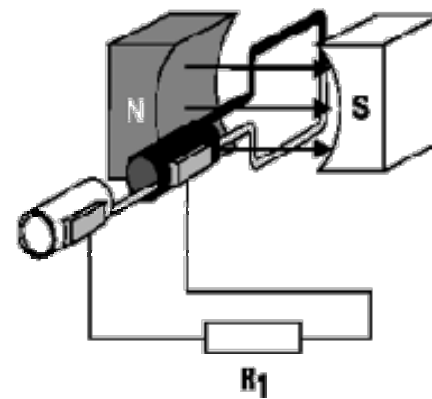


(E)

Operation of DC Generator - Split Rings

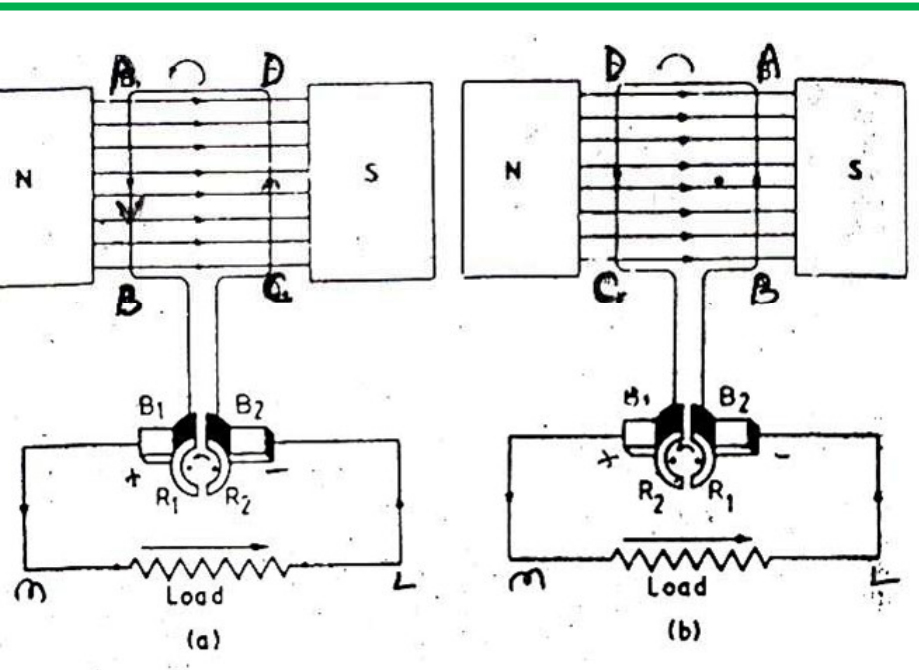

1st half cycle (0° to 180°) Path of current
 $ABR_1B_2MLR_2B_1CD$

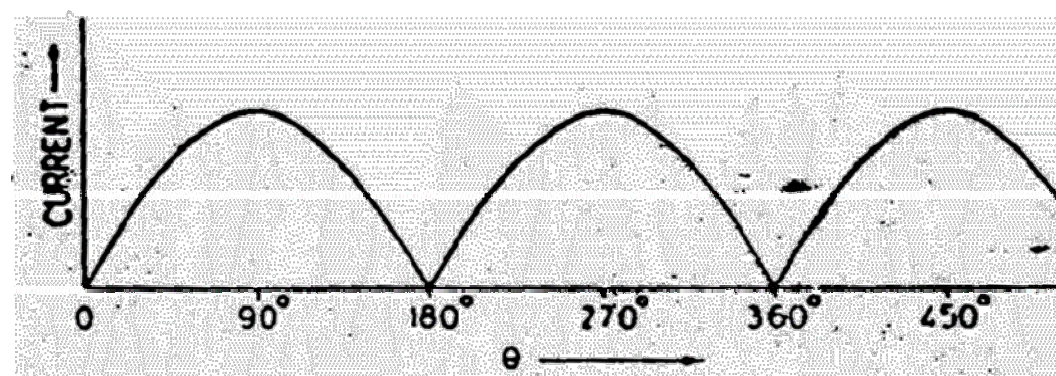2nd half cycle (180° to 360°) Path of current
 $DCR_2B_1MLB_2R_1BA$





EMF Equation of DC Generator



As the armature rotates, a voltage is generated in its coils. In the case of a generator, the emf of rotation is called the Generated emf or Armature emf and is denoted as $E_r = E_g$.

P – number of poles of the machine

ϕ – Flux per pole in Weber.

Z – Total number of armature conductors.

N – Speed of armature in revolution per minute (r.p.m).

A – number of parallel paths in the armature winding.

If the DC Machine is working as a Motor, the induced emf is given by the equation shown below:

$$E_g = \frac{PZ \phi N}{60 A} \quad \text{volts}$$





APPLICATIONS

They are used for **general lighting**.

They are used to **charge battery**.

They are used for giving **the excitation** to the alternators.


They are also used for **small power supply** (such as a portable generator).

They are used for supplying field excitation current in **DC locomotives** for regenerative braking.

This types of generators are used as boosters to compensate the voltage drop in the feeder in various types of distribution systems such as **railway service**.



RECAP...

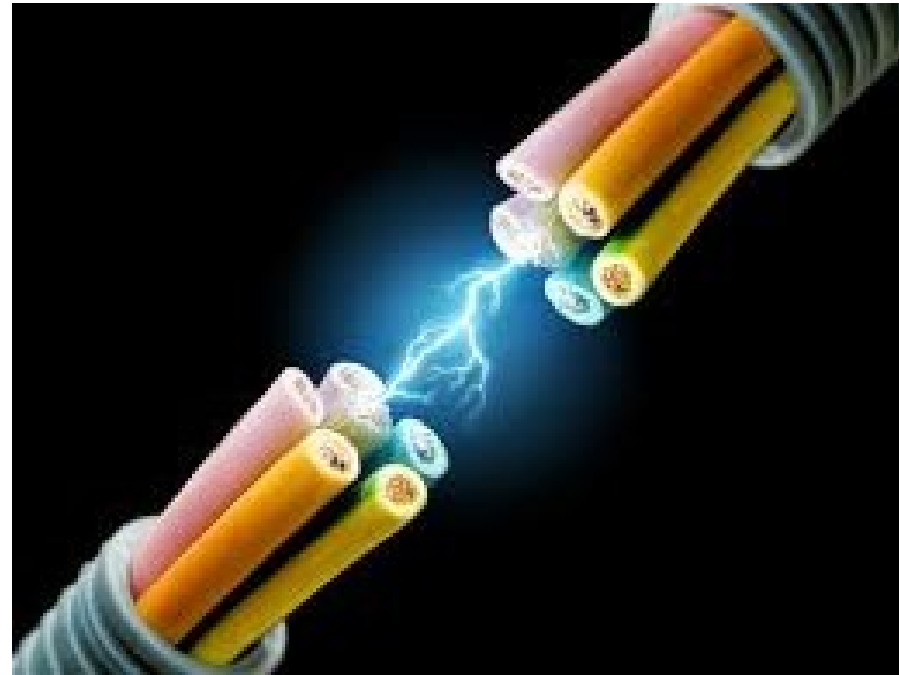

...THANK YOU

