

## **SNS COLLEGE OF TECHNOLOGY**



Coimbatore-35
An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

#### 19ECB311 -OPTICAL AND MICROWAVE ENGINEERING

TOPIC- TEE JUNCTION



#### MICROWAVE PASSIVE COMPONENTS



- Microwave passive devices are used inside microwave measurement instruments, and they are used to combine instruments to create more complex measurement systems.
- ➤In all cases, these devices will split, combine, filter, attenuate, and/or shift the phase of a microwave signal as it propagates through a particular transmission system.
- >Examples:
- Power Divider (TEE JUNCTIONS)
- Directional Coupler
- Magic Tee
- Attenuator
- Resonator



## **TEE JUNCTIONS**



• MICROWAVE T- JUNCTIONS

T junction is an intersection of three waveguides in the form of English alphabet T'. There are several types of Tee junctions.

• In microwave circuits a waveguide or coaxial-line with Three independent ports is commonly referred to as a Tee junction.







## **TEE JUNCTIONS**




- They are used to connect branch (or) section of the waveguides in series or parallel with the main waveguide transmission line
- providing means of splitting and also of combining power in a waveguide system.
- The two basic Types are
  - i) E -plane Tee (Series)
  - (ii) H-plane Tee (Shunt).


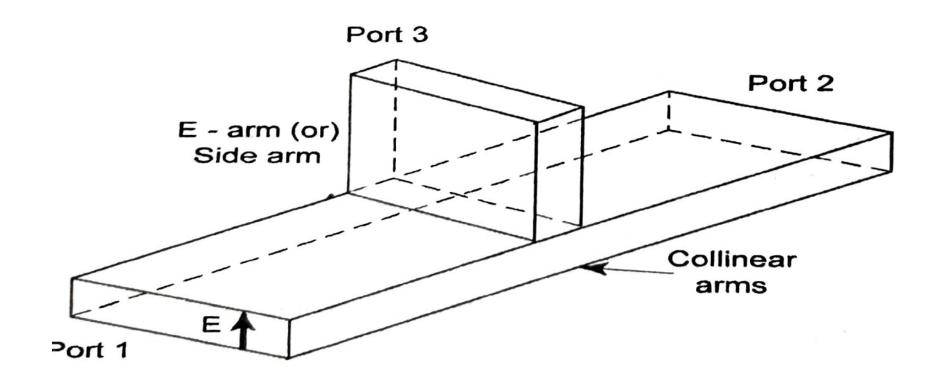
## **E-PLANE TEE (SERIES TEE)**



- An E-plane tee is a waveguide tee in which the axis of its side arm is parallel to the E- field of the main guide.
- Ports I and 2 are the collinear arms and port 3 is the E- arm (side arm).
- A rectangular slot is cut along the broader dimension of a long waveguide and a side arm is attached





## **E-PLANE TEE (SERIES TEE)**



- When the waves are fed into the side arm (port 3)
- The waves appearing at port 1 and port 2 of the collinear arm will be in opposite phase and in the same magnitude.

$$S13 = -S23$$

- In general, the power out port 3 (side or E arm) is proportional to the difference between instantaneous powers entering from ports I and 2.
- Difference Arm

If two input waves are fed into port I and port 2 of the collinear arm, the output wave at port 3 will be opposite in phase and subtractive. Sometimes, this third port is called the difference arm





For E-plane tee, [S] is a3 x3 matrix since there are 3 ports,

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix} \dots (1)$$

The scattering coefficient due to difference arms are,

$$S_{23} = -S_{13}$$
 ... (2)

• The equation represents that the outputs at ports 1 and 2 are out of phase by 180 °with an input at port 3.

1/22/2024





If port 3 is perfectly matched to the junction,

$$S_{33} = 0$$

... (3)

Using symmetric property,  $S_{ij} = S_{ji}$ 

$$S_{12} = S_{21}$$
 $S_{13} = S_{31}$ 
 $S_{23} = S_{32}$ 

... (4)

$$\begin{bmatrix} \mathbf{S} \end{bmatrix} = \begin{bmatrix} \mathbf{S}_{11} & \mathbf{S}_{12} & \mathbf{S}_{13} \\ \mathbf{S}_{12} & \mathbf{S}_{22} & -\mathbf{S}_{13} \\ \mathbf{S}_{13} & -\mathbf{S}_{13} & \mathbf{0} \end{bmatrix}$$

... (5)





Apply unity property of [S] matrix for equation(5), we get

$$[S] \cdot [S]^* = [I]$$

$$\begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{12} & S_{22} & -S_{13} \\ S_{13} & -S_{13} & 0 \end{bmatrix} \begin{bmatrix} S_{11}^* & S_{12}^* & S_{13}^* \\ S_{12}^* & S_{22}^* & -S_{13}^* \\ S_{13}^* & -S_{13}^* & 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$\mathbf{R_1C_1}$$
:  $\left|\mathbf{S_{11}}\right|^2 + \left|\mathbf{S_{12}}\right|^2 + \left|\mathbf{S_{13}}\right|^2 = 1$  ... (6)

**R<sub>2</sub>C<sub>2</sub>:** 
$$|S_{12}|^2 + |S_{22}|^2 + |S_{13}|^2 = 1$$
 ... (7)

**R<sub>3</sub>C<sub>3</sub>:** 
$$|S_{13}|^2 + |S_{13}|^2 = 1$$
 ... (8)





Using zero property of [S] matrix, we get

**R<sub>3</sub>C<sub>1</sub>:** 
$$S_{13}.S_{11}^* - S_{13}S_{12}^* = 0$$
 ... (9)

By equating equations (6) and (7), we get

$$|S_{11}|^{2} + |S_{12}|^{2} + |S_{13}|^{2} = |S_{12}|^{2} + |S_{22}|^{2} + |S_{13}|^{2}$$

$$S_{11} = S_{22}$$
... (10)

From Equation (8), we get the value of  $S_{13}$  as

$$2 |S_{13}|^2 = 1$$

$$|S_{13}|^2 = \frac{1}{2}$$

$$|S_{13}| = \frac{1}{\sqrt{2}}$$
... (11)





From equation (9),

$$S_{13} \left( S_{11}^* - S_{12}^* \right) = 0$$

$$S_{11}^* - S_{12}^* = 0$$

$$S_{11} = S_{12} = S_{22}$$
... (12)

By using equations (10), (11) and (12) in equation (6), we get

$$|S_{11}|^{2} + |S_{11}|^{2} + \frac{1}{2} = 1$$

$$2|S_{11}|^{2} = \frac{1}{2}$$

$$S_{11} = \frac{1}{2}$$
... (13)





• Thus the equation represents the scattering matrix for E-plane tee.

[S] = 
$$\begin{bmatrix} 1/2 & 1/2 & 1/\sqrt{2} \\ 1/2 & 1/2 & -1/\sqrt{2} \\ 1/\sqrt{2} & -1/\sqrt{2} & 0 \end{bmatrix}$$



## H-PLANE TEE (SHUNT TEE)




- H-plane tee junction is formed by cutting a rectangular slot along the width of a main waveguide and attaching another waveguide the side arm called the H-arm.
- The port 1 and port 2 of the main waveguide are called collinear ports and port3 is the H-arm (or) Side arm.
- An H plane tee is a waveguide tee in which the axis of its side arm is "shunting" the E field (or) parallel to the H- field of the main guide.
- Sum Arm:
- In a H-plane tee if two input waves are fed into port1 and port 2 of the collinear arm, the output wave at port 3 will be in phase and additive. Hence, the third port is called the sum arm.



## H-PLANE TEE (SHUNT TEE)



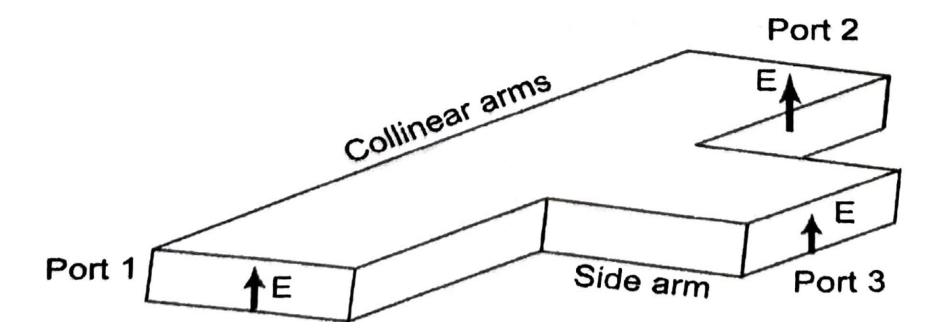

• For H-plane tee, [S] is a 3 x3 matrix since there are 3 ports.

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix}$$

**→** (1)





... (2)

- If the input is fed into the port 3, then the wave will split equally into port I and port 2 in phase and in the same magnitude.
- Here, the scattering coefficients S13 and S23 must be equal.

$$S13 = S23$$

$$S_{13} = S_{23}$$

From the symmetric property,  $S_{ij} = S_{ji}$ 

$$S_{12} = S_{21}$$
 $S_{23} = S_{32} = S_{13}$ 
 $S_{13} = S_{31}$  ... (3)

Since port 3 is perfectly matched to the junction.

$$S_{33} = 0$$
 ... (4)





... (6)

$$\begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{12} & S_{22} & S_{13} \\ S_{13} & S_{13} & 0 \end{bmatrix} \begin{bmatrix} S_{11}^* & S_{12}^* & S_{13}^* \\ S_{12}^* & S_{22}^* & S_{13}^* \\ S_{13}^* & S_{13}^* & 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$R_1C_1$$
:  $S_{11}S_{11}^* + S_{12}S_{12}^* + S_{13}S_{13}^* = 1$ 

$$|S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 = 1$$

Similarly,

**R<sub>2</sub>C<sub>2</sub>:** 
$$|S_{12}|^2 + |S_{22}|^2 + |S_{13}|^2 = 1$$
 ... (7)

**R<sub>3</sub>C<sub>3</sub>:** 
$$|S_{13}|^2 + |S_{13}|^2 = 1$$
 ... (8)





Using zero property of [S] matrix, we get

 $R_3C_1$ :

$$S_{13}.S_{11}^* + S_{13}S_{12}^* = 0$$

From equation (8),

$$2|S_{13}|^2 = 1$$

$$|S_{13}|^2 = \frac{1}{2}$$

$$S_{13} = \frac{1}{\sqrt{2}}$$

... (10)

... (9)





Comparing equations (6) and (7), we get

$$|S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 = |S_{12}|^2 + |S_{22}|^2 + |S_{13}|^2$$

$$|S_{11}|^2 = |S_{22}|^2$$

$$S_{11} = S_{22}$$

... (11)

From equation (9),

$$S_{13}(S_{11}^* + S_{12}^*) = 0$$
, since  $S_{13} \neq 0$ ,





$$S_{11}^* + S_{12}^* = 0$$

$$S_{11}^* = -S_{12}^* \qquad \dots (12)$$

Using above value in equation (6), we get

$$|S_{11}|^{2} + |S_{11}|^{2} + \frac{1}{2} = 1$$

$$2|S_{11}|^{2} = \frac{1}{2}$$

$$S_{11} = \frac{1}{2}$$
... (13)

From equations (11), (12) and (13),

$$S_{12} = -\frac{1}{2}$$
 $S_{22} = \frac{1}{2}$  ... (14)





This equation represents the scattering matrix for H-plane tee.

$$\begin{bmatrix} \mathbf{S} \end{bmatrix} = \begin{bmatrix} 1/2 & -1/2 & 1/\sqrt{2} \\ -1/2 & 1/2 & 1/\sqrt{2} \\ 1/\sqrt{2} & 1/\sqrt{2} & 0 \end{bmatrix}$$

We know that 
$$[b] = [s][a]$$

$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \end{bmatrix} = \begin{bmatrix} \frac{1}{2} & -\frac{1}{2} & \frac{1}{\sqrt{2}} \\ -\frac{1}{2} & \frac{1}{2} & \frac{1}{\sqrt{2}} \\ \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} & 0 \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ a_3 \end{bmatrix}$$



#### **ASSESSMENT**



1. Why E plane Tee junction is called as Series Tee?

#### **Answer:**

As the axis of the side arm is parallel to the electric field, this junction is called E-Plane Tee junction. This is also called as Voltage or Series junction. The ports 1 and 2 are 180° out of phase with each other.

2. The diagonal elements of the s matrix of a resistive T junction are:

**Answer: zero** 

3. Why third port is sum arm in H plane Tee?

**Answer:** The output wave at port 3 will be in phase and additive.





# THANK YOU