



# SNS COLLEGE OF TECHNOLOGY

COIMBATORE-35



## DEPARTMENT OF EEE

### ANALOG ELECTRONICS GATE QUESTIONS

1. A transistor circuit is given below. The Zener diode breakdown voltage is 5.3 V as shown. Take base to emitter voltage drop to be 0.6 V. The value of the current gain  $\beta$  is \_\_\_\_\_.


a) 1.

b) 0.

c) 11.

d) 19.

(answer: d)

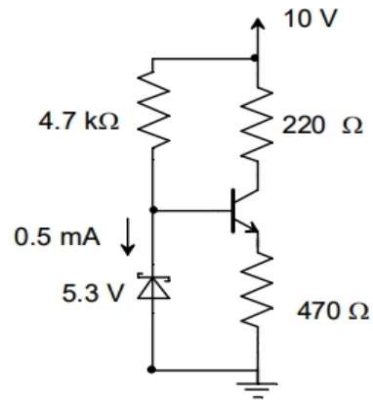

2. When a bipolar junction transistor is operating in the saturation mode, which one of the following statements is TRUE about the state of its collector-base (CB) and the base-emitter (BE) junctions ?

a) The CB junction is forward biased , and the BE junction is reverse biased.

b) The CB junction is reverse biased , and the BE junction is forward biased.

c) Both CB and BE junctions are forward biased.

d) Both CB and BE junctions are reverse biased.

(answer: c)

3. The maximum efficiency of a half-wave rectifier is \_\_\_\_\_.

a) 33.3%.

b) 40.6%.


c) 66.6%.

d) 72.9%.

(answer: b)

4. For the circuit shown below with ideal diodes, the output will be \_\_\_\_\_?

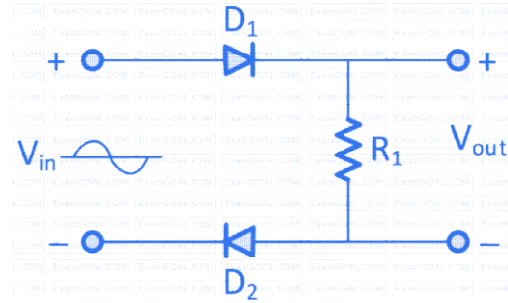
- a)  $V_{out} = V_{in}$  for  $V_{in} > 0$ .
- b)  $V_{out} = V_{in}$  for  $V_{in} < 0$ .
- c)  $V_{out} = -V_{in}$  for  $V_{in} > 0$ .
- d)  $V_{out} = -V_{in}$  for  $V_{in} < 0$ .



(answer: a)

5. The output  $V_0$  of the diode circuit shown in the figure is connected to an averaging DC voltmeter. The reading on the DC voltmeter in Volts, neglecting the voltage drop across the diode, is \_\_\_\_\_.

- a) 3.18
- b) 2.72
- c) 3.89
- d) 2.18

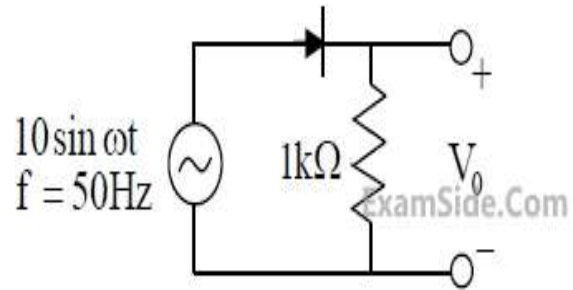

(answer: a)

6. The depletion region (or) space charge region (or) transition region in a semiconductor p-n junction diode has \_\_\_\_\_.


- a) Electrons and holes.
- b) Positive ions and electrons.
- c) Positive and negative ions.
- d) Negative ions and holes.

(answer: c)

7. The diode in the circuit given below has  $V_{ON} = 0.7V$  but is ideal otherwise. The current (in mA) in the  $4k\Omega$  resistor is \_\_\_\_\_.

- a) 0.2
- b) 0.7
- c) 0.1
- d) 0.6


(answer: d)

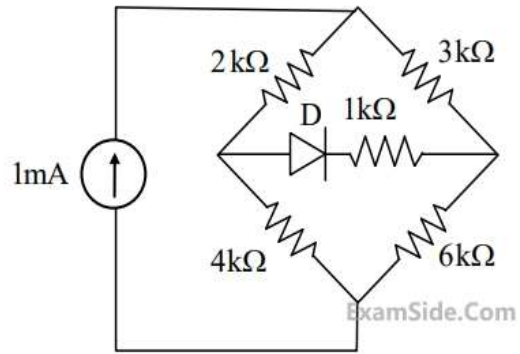

8. Which circuit has been represented in the associated circuit diagram?

- a) Half-wave rectifier.
- b) Full-wave rectifier.
- c) NOT Gate.
- d) AND Gate


(answer: a)

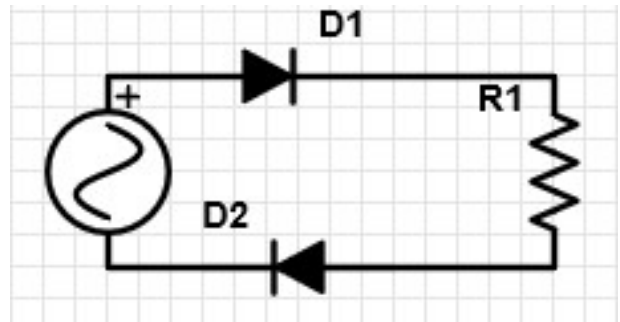

9. In the given circuit, what will be the nature of the output waveform?

- a) Half-wave Rectified.
- b) Full-wave Rectified.
- c) Sinusoidal.
- d) DC.


(answer: b)

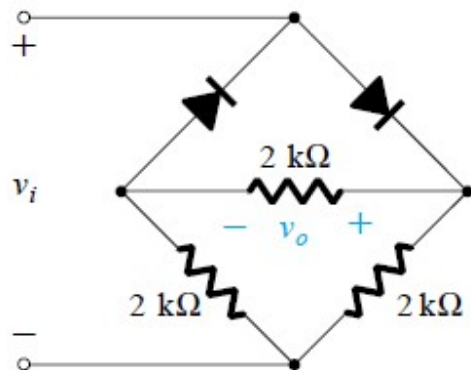

10. The figure shows a half-wave rectifier with a  $475 \mu\text{F}$  filter capacitor. The load draws a constant current  $I_0 = 1 \text{ A}$  from the rectifier. The figure also shows the input voltage  $V_i$ , the output voltage  $V_C$  and the peak-to-peak voltage ripple on  $V_C$ . The input voltage  $V_i$  is a triangle-wave with an amplitude of  $10 \text{ V}$  and a period of  $1 \text{ ms}$ .

- a) 3.5
- b) 2.1
- c) 1.8
- d) 3.2

(answer: b)

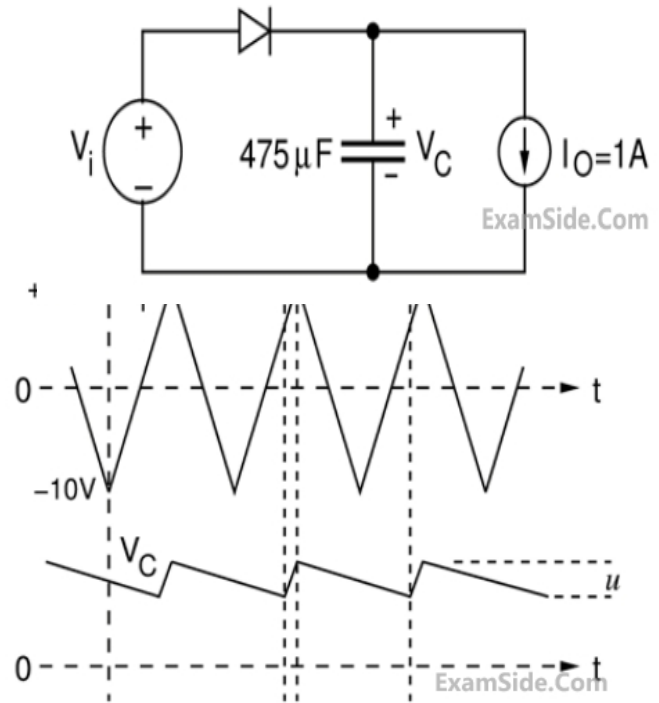

## IGBT

1. What does IGBT stand for?

- a) Insulated Grounded Bipolar Transistor
- b) Integrated Gate Bipolar Transistor
- c) Isolated Gate Bridge Transistor
- d) Inductive Gate Blocking Transistor

Answer: b) Integrated Gate Bipolar Transistor

2. Which of the following is not a key advantage of IGBTs?

- a) High voltage capability
- b) High switching speed
- c) Low conduction losses
- d) Low gate drive power

Answer:

- b) High switching speed

3. IGBTs are commonly used in which type of applications?

- a) Low-power digital circuits
- b) Audio amplifiers
- c) High-power switching applications
- d) RF communication devices

Answer:

- c) High-power switching applications

4. What is the primary function of the gate terminal in an IGBT?

- a) To provide electrical isolation
- b) To control the IGBT's switching action
- c) To carry the main current
- d) To dissipate heat

Answer:

- b) To control the IGBT's switching action

5. Which semiconductor devices are combined to create an IGBT?

- a) Diode and MOSFET
- b) Diode and BJT
- c) MOSFET and BJT
- d) Diode and JFET

Answer:

- c) MOSFET and BJT

6. What is the typical voltage rating of IGBTs used in high-power applications?

- a) 5 volts
- b) 12 volts
- c) 48 volts
- d) Hundreds of volts to several kV

Answer:

- d) Hundreds of volts to several kV

7. Which region of operation does an IGBT primarily operate in during the "ON" state?

- a) Cutoff
- b) Saturation
- c) Linear
- d) Active

Answer: b) Saturation

8. What is the primary reason for using IGBTs over traditional BJTs (Bipolar Junction Transistors) in many applications?

- a) Lower cost
- b) Faster switching speed
- c) Higher current-carrying capacity
- d) Reduced conduction losses

Answer:

- d) Reduced conduction losses

9. In which layer of the IGBT structure does most of the current flow during conduction?

- a) P-type collector
- b) N-type drift region
- c) P-type gate region
- d) N-type emitter

Answer:

- b) N-type drift region

10. What is the most common voltage rating for the gate-source voltage in IGBTs?

- a) 5V
- b) 12V
- c) 15V
- d) 20V

Answer:

- c) 15V