



SNS COLLEGE OF TECHNOLOGY
Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++'(III Cycle) Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

23ECB101 – CIRCUIT ANALYSIS AND DEVICES

I YEAR/ II SEMESTER

UNIT 1 – MESH AND NODE ANALYSIS OF ELECTRIC CIRCUITS

TOPIC - Basic Components of electric Circuits



OVERVIEW



- **Basic Components and Electric Circuits**
 - Units and Scales
 - Charge, Current, Voltage, and Power



Charge



- One of the most fundamental concepts in electric circuit analysis is that of *charge conservation*.
- There are **two types** of charge: positive (corresponding to a proton) and negative (corresponding to an electron).
- There are many devices in which positive charge motion is important to understanding internal operation.
- But external to the device we typically **concentrate on the electrons** which flow through the connecting wires.
- Although we continuously transfer charges between different parts of a circuit, we do nothing to change the total amount of charge.



Charge SI Unit and Representation



- In other words, we neither create nor destroy electrons (or protons) when running electric circuits.
- Charge in motion represents a *current*.
- In the SI system, the fundamental unit of charge is the ***coulomb (C)***.
- A quantity of charge that does not change with time is typically represented by Q .
- *The instantaneous amount of charge* is commonly represented by $q(t)$, or simply q .



Definition of Current using charge



- It is defined in terms of the **ampere by counting the total charge that** passes through an arbitrary cross section of a wire during an interval of one second.

- one coulomb is measured each second for a wire carrying a current of 1 ampere.

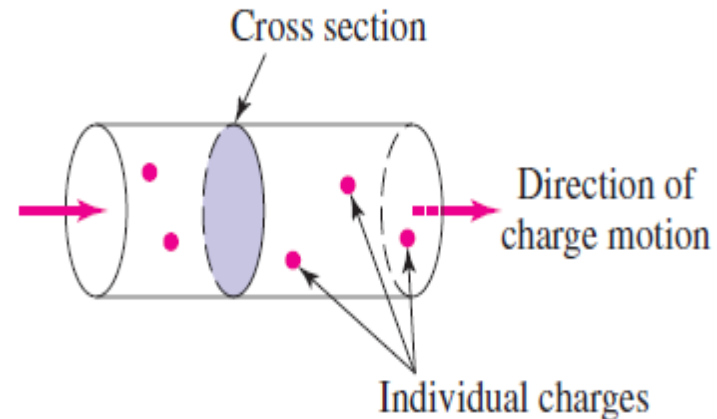


Figure: The definition of current illustrated using current flowing through a wire.

- In this system of units, the charge of **a single electron is $-1.602 \times 10^{-19} \text{ C}$** **a single proton is $+1.602 \times 10^{-19} \text{ C}$.**



Current



- The idea of “**transfer of charge**” or “**charge in motion**” is of vital importance to us in studying electric circuits.
- In moving a charge from place to place, we may also transfer energy from one point to another.
- This process is the basis of communication systems such as radio, television, and telemetry.
- The current present in a discrete path has both a *numerical value and a direction* associated with it
- It is a measure of the rate at which charge is moving past a given reference point in a specified direction.



Current SI Unit and Representation




- A contribution to this total charge will be negative if negative charge is moving in the reference direction, or if positive charge is moving in the opposite direction.
- Current is symbolized by I or i , and so

$$i = \frac{dq}{dt}$$


- The unit of current is **ampere (A)**, named after A. M. Ampere, a French physicist.
- One ampere equals *1 coulomb per second*.




Types of Current

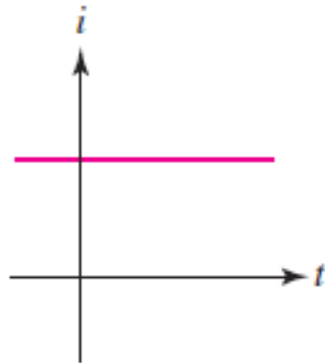


(a)

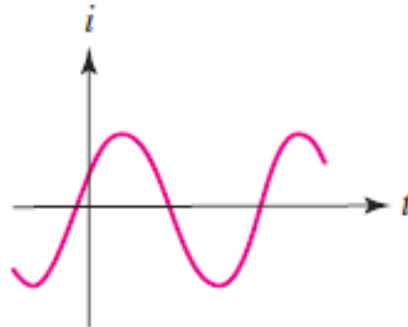

(b)

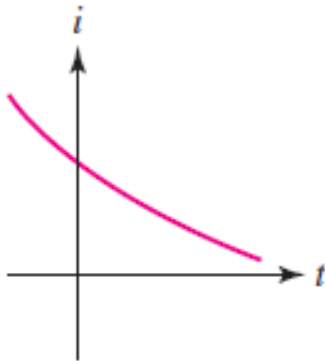

(c)

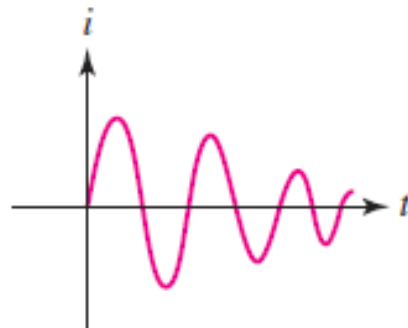


(d)

Types of current:

- (a) Direct current (dc).
- (b) Sinusoidal current (ac).
- (c) Exponential current.
- (d) Damped sinusoidal current.



Graphical Symbol for Current

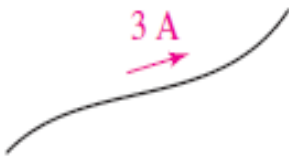

(a)




(b)

Two methods of representation for the exact same current.

(a, b) Incomplete, improper, and incorrect definitions of a current.


(c) The correct definition of $i_1(t)$.

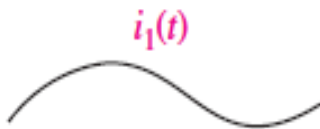

(a)



(b)

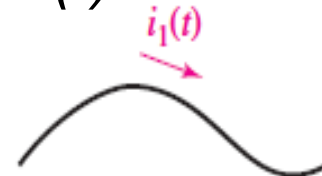

(c)




Voltage




- The voltage across a terminal pair is a measure of the *work required to move charge* through the element.
- The unit of voltage is the **volt**, and 1 volt is the same as 1 J/C. Voltage is represented by **V** or **v**.
- A voltage can exist between a pair of electrical terminals whether a current is flowing or not.
- According to the *principle of conservation of energy*, the energy that is expended in forcing charge through the element must appear somewhere else.
- The sense of the voltage is indicated by a *plus-minus* pair of algebraic signs.



Sign for the Voltage Terminal

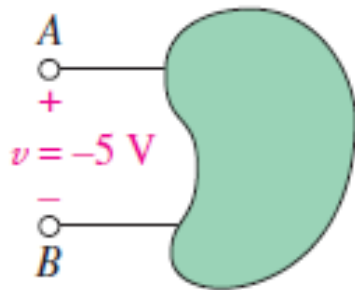


(a)

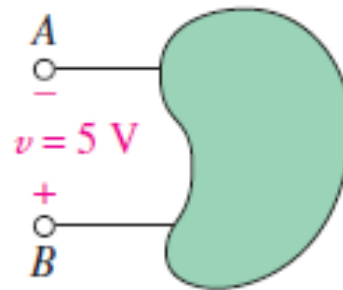


(b)

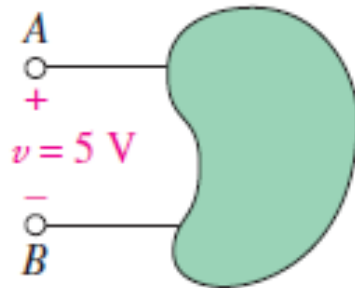(a, b) Terminal B is 5 V positive with respect to terminal A



(c)

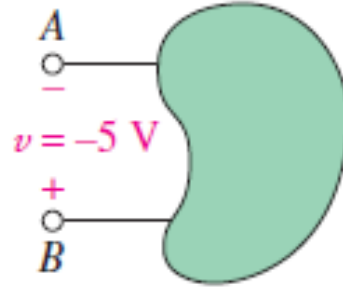


(d)

(c, d) terminal A is 5 V positive with respect to terminal B.




Sign for the Voltage Terminal

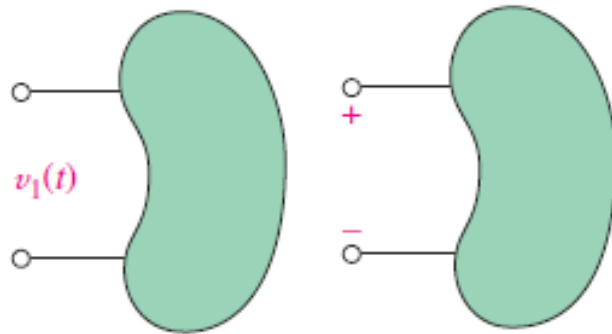

(a)

(b)

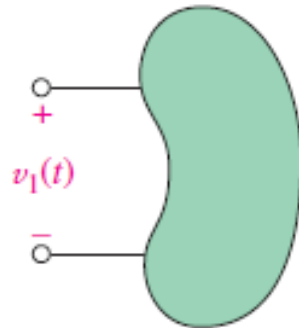(a, b) These are inadequate definitions of a voltage.



(c)

(c) A correct definition includes both a symbol for the variable and a plus-minus symbol pair.



Power



- If *one joule of energy* is expended in transferring one coulomb of charge through the device in one second, then the *rate of energy transfer* is one watt.
- The absorbed power must be proportional both to the number of coulombs transferred per second (current) and to the energy needed to transfer one coulomb through the element (voltage). Thus,

$$p = vi$$


- Voltage was defined in terms of an *energy expenditure*, and power is the rate at which energy is expended.



Sign for the Power Terminal



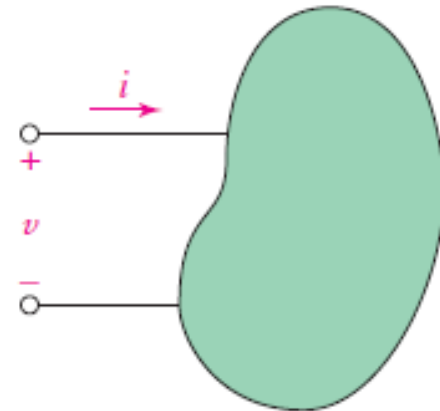- If the current arrow is directed into the “+” marked terminal of an element, then $p=vi$ yields the *absorbed* power.
- If the current arrow is directed out of the “+” terminal of an element, then $p=vi$ yields the *supplied* power.



The power absorbed by the element is given by the product $p=vi$



Voltage and Current Sources



Using the concepts of current and voltage, it is possible to be more specific in defining a circuit element.


- The mathematical model which we will use to analyze its behaviour in a circuit.
- All the simple circuit elements can be classified according to the relationship of the current through the element to the voltage across the element.
- The sources are classified as *independent sources* and *dependent sources*.
- *Dependent sources* are used a great deal in electronics to model both dc and ac behaviour of transistors, especially in amplifier circuits.



Independent Voltage Sources



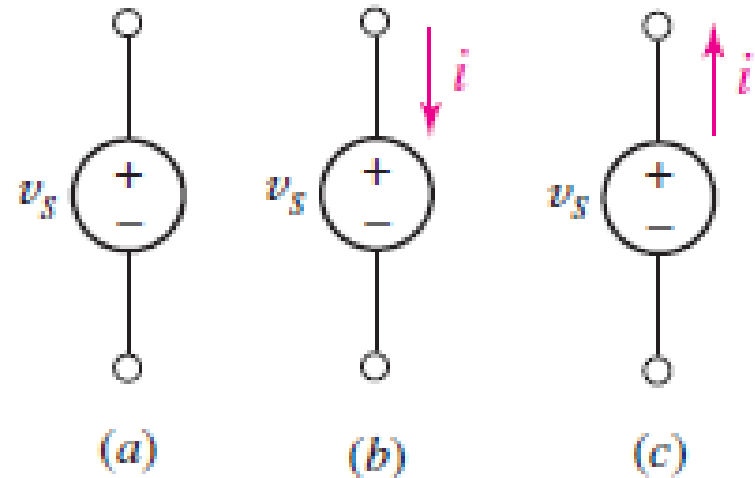- An **independent voltage source** is characterized by a terminal voltage which is completely independent of the current through it.
- The independent voltage source is an *ideal source* and does not represent exactly any real physical device.




Circuit symbol of the independent voltage source.



Independent Current Sources



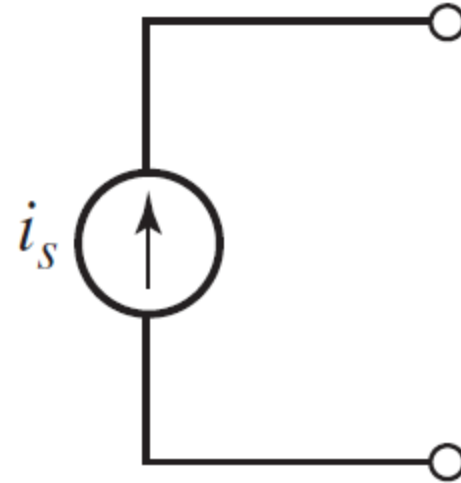- In the *independent current source*, the current through the element is completely independent of the voltage across it.
- In theory it can deliver *infinite power* from its terminals.
- It is, however, a *good approximation* for many practical sources, particularly in electronic circuits.



Circuit symbol for the independent current source.



Dependent Sources







- The *dependent, or controlled, source*, in which the source quantity is determined by a voltage or current existing at some other location in the system.
- To distinguish between dependent and independent sources, the diamond symbols are introduced.

- K is scaling constant.

- g is scaling factor (A/V),

- r is scaling factor (V/A).

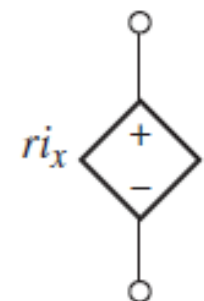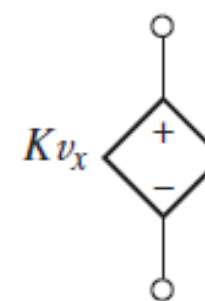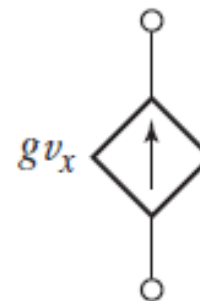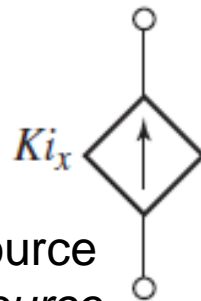

(a) *current-controlled current source*

(b) *voltage-controlled current source*

(c) *voltage-controlled voltage source*

(d) *Current controlled voltage source.*



Assessment

1. Which of the following is not an expression power?

- a) $P=VI$
- b) $P=I^2R$
- c) $P=V^2/R$
- d) $P=I/R$**

2. A 250V bulb passes a current of 0.3A. Calculate the power in the lamp.

- a) 75W**
- b) 50W
- c) 25W
- d) 90W

3. The symbol used for representing Independent sources

- a) Diamond
- b) Square
- c) Circle**
- d) Triangle



