



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35

An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++'(III Cycle) Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

23ECB101 – CIRCUIT ANALYSIS AND DEVICES

I YEAR/ II SEMESTER

UNIT 1 – MESH AND NODE ANALYSIS OF ELECTRIC CIRCUITS

TOPIC - Ohms Law



Introduction


- Electric Circuit : It is an interconnection of various elements in which there is at least one closed path in which current can flow.
- Electric circuit consists of two types of elements
 - i) active elements (or) sources
 - ii) Passive elements (or) sinks



Introduction



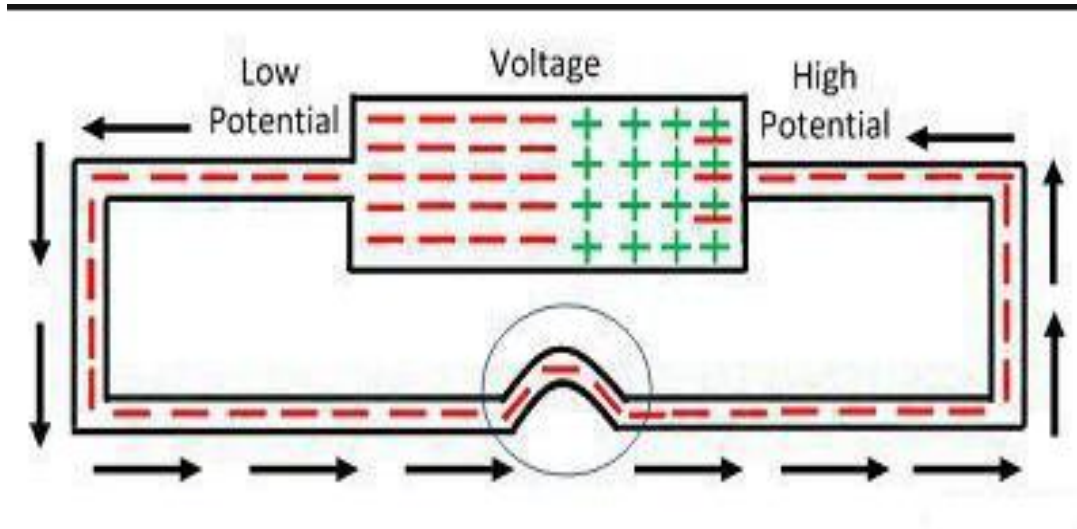- Active Elements: Elements of a circuit which possess energy of their own and can impart it to other elements of the circuit.
- Two types of active elements: voltage source & current source.



Current is the rate at which electric charge flows past a point in a circuit. In other words, **current** is the rate of flow of electric charge.

Voltage, also called electromotive force, is the potential difference in charge between two points in an electrical field.



Introduction

- A **current source** is an electronic circuit that delivers or absorbs an electric **current** which is independent of the **voltage** across it.
- A **current source** is the dual of a **voltage source**.
- A **voltage source** is a two terminal device which can maintain a fixed **voltage**.



Introduction



- **Passive Elements:** Elements of a circuit which do not possess energy of their own.
- The passive elements are the resistance, the inductance and the capacitance.

- **Resistance:** It's the property of a conductor by virtue of which, it opposes or limits the flow of current through it. The unit of resistance is ohm.



Resistors


- A *resistor* is a circuit element that dissipates electrical energy (usually as heat)
- Real-world devices that are modeled by resistors: incandescent light bulbs, heating elements (stoves, heaters, etc.), long wires
- Resistance is measured in Ohms



The CELL




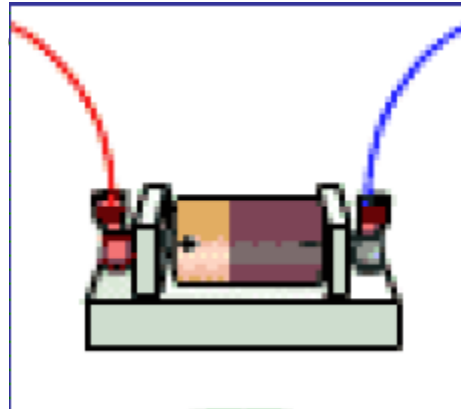- The cell stores **chemical energy** and **transfers it to** electrical energy when a circuit is connected.
- When two or more cells are connected together we call this a **Battery**.
- The cells' chemical energy is used up pushing a current round a





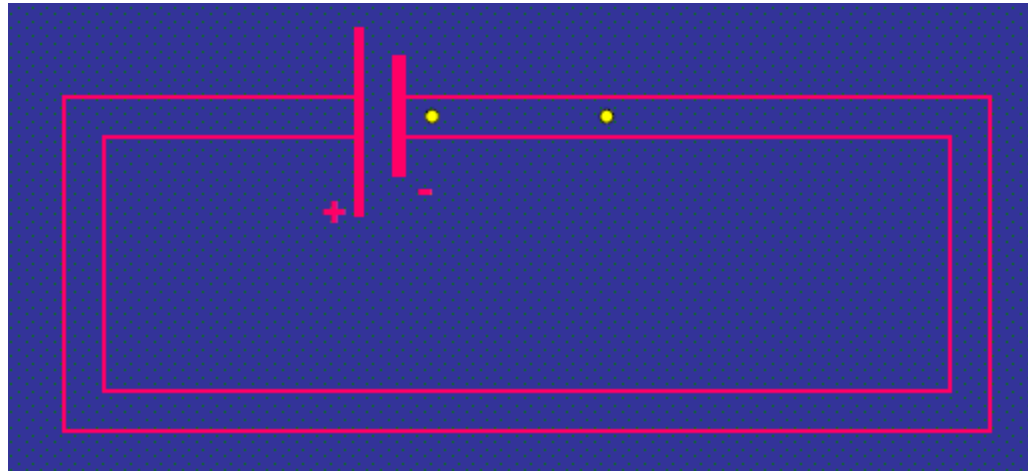
- In which direction does the current flow?
from the **Negative terminal to the Positive terminal** of a cell.





simple circuits

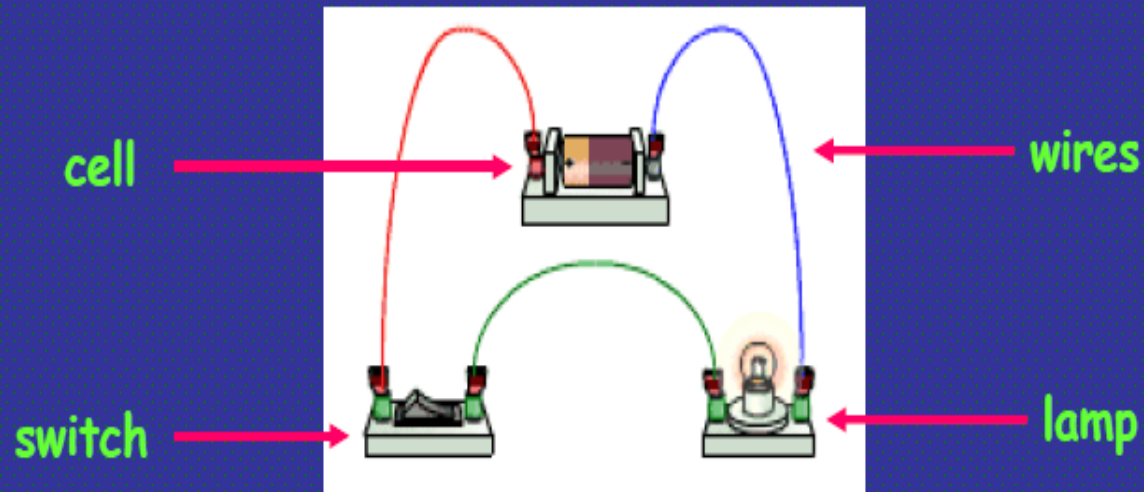
Here is a simple electric circuit. It has a cell, a lamp and a switch.





simple circuits

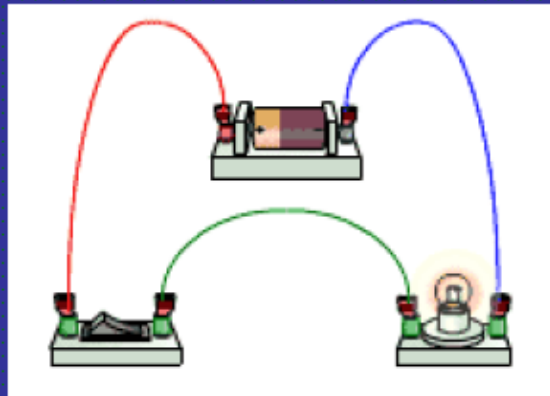When the switch is closed, the lamp lights up. This is because there is a continuous path of metal for the electric current to flow around.





If there were any breaks in the circuit, the current could not flow.



circuit diagram

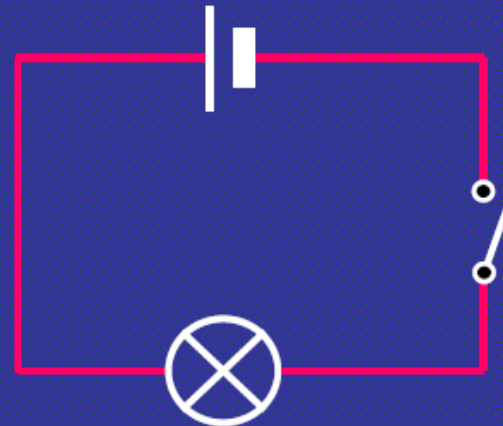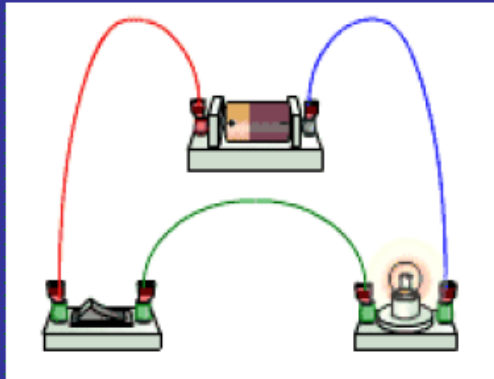Scientists usually draw electric circuits using symbols;



cell



lamp



switch




wires




circuit diagrams

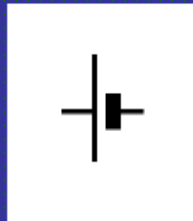In circuit diagrams components are represented by the following symbols;



cell

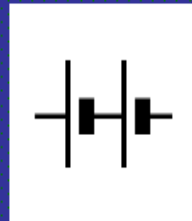

battery




switch




lamp




buzzer

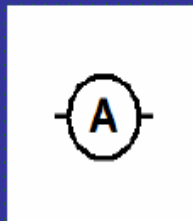


ammeter

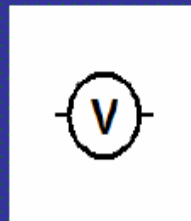


voltmeter

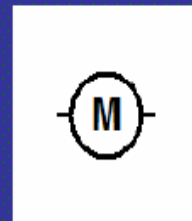

motor

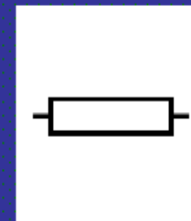

resistor

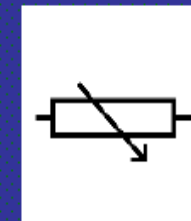

variable



Ohm's Law



- German physicist, **Georg Simon Ohm**, who published a pamphlet in 1827 that described the measure of currents and voltages, and to describe and relate them mathematically.
- One result was a statement of the fundamental relationship we now call ***Ohm's law***.
- Ohm's law states that the voltage across conducting materials is directly proportional to the current flowing through the material, or

$$v = Ri$$


where the constant of proportionality R is called the **resistance**.



Ohm's Law



□ $v(t) = i(t) R$ - or - $V = I R$

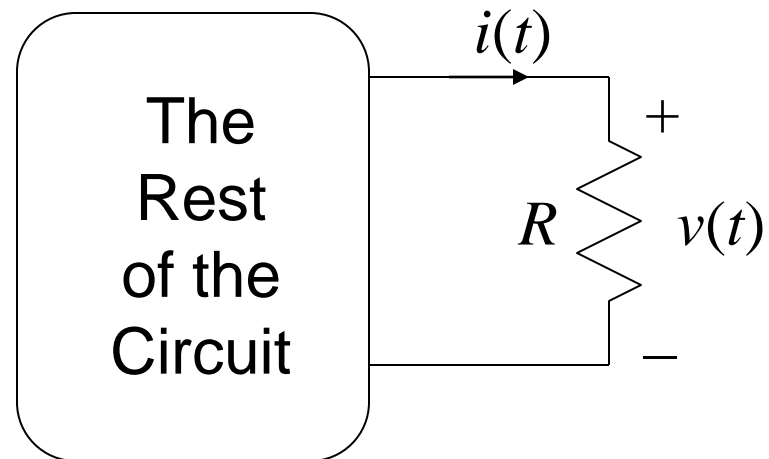



Ohm's Law



The temperature remaining constant, the current flowing through any conductor is directly proportional to the potential difference between the two ends of the conductor.

$I \propto V$, when temperature is constant

$$I = V / R$$

R is the resistance of the conductor

Ohm's law can be applied for both a.c and d.c circuits.



Limitations of Ohm's Law



- Ohm's law does not hold good for non metallic conductors such as silicon carbide.
- Ohm's law also does not hold good for non linear devices such as zener diodes, voltage regulators etc.




Resistance



- The unit of resistance is the *ohm*, which is 1 V/A and customarily abbreviated by a capital omega, Ω .
- Resistance is normally considered to be a positive quantity, although negative resistances may be simulated with special circuitry.

I (amperes)

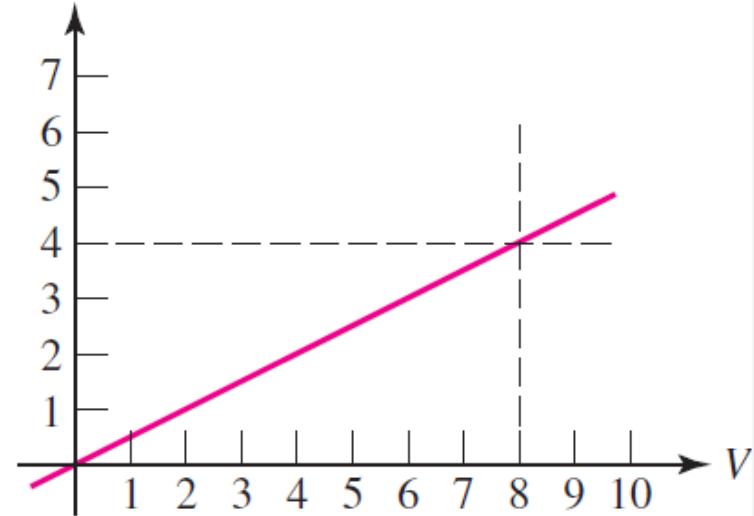

Current-voltage relationship for an example 2Ω *linear resistor*.



Power Absorption



- the *product of v and i* gives the power absorbed by the resistor.
- That is, *v and i are selected to satisfy the passive sign convention.*
- The absorbed power appears physically as heat and/or light and is always *positive*.
- A (positive) resistor is a passive element that cannot deliver power or store energy.
- Alternative expressions for the absorbed power are

$$p = vi = i^2R = v^2/R$$

