



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35

An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++'(III Cycle) Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

23ECB101 – CIRCUIT ANALYSIS AND DEVICES

I YEAR/ II SEMESTER

UNIT 1 – MESH AND NODE ANALYSIS OF ELECTRIC CIRCUITS

TOPIC - Kirchoff's Current Law



Introduction


- In general, circuits must be analyzed to determine a complete set of voltages and currents.
- Only two simple laws are needed in addition to Ohm's law.
- The new laws are
 - **Kirchhoff's current law (KCL)**
 - **Kirchhoff's voltage law (KVL)**
- They are simply restatements of *charge and energy conservation*, respectively.




Nodes, Paths, Loops And Branches



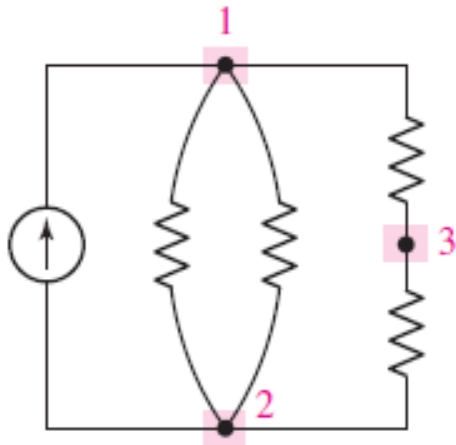- A point at which two or more elements have a common connection is called a **node**.



(a)

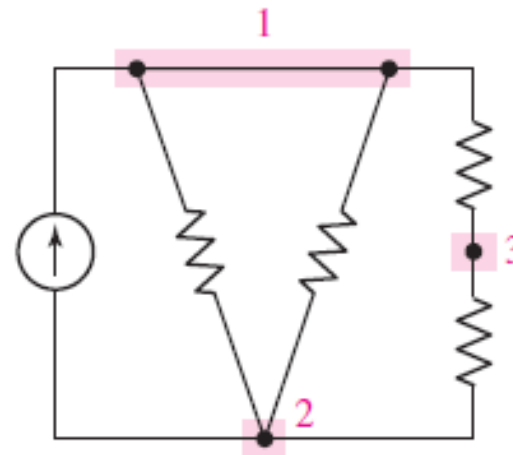


(b)



Nodes, Paths, Loops And Branches



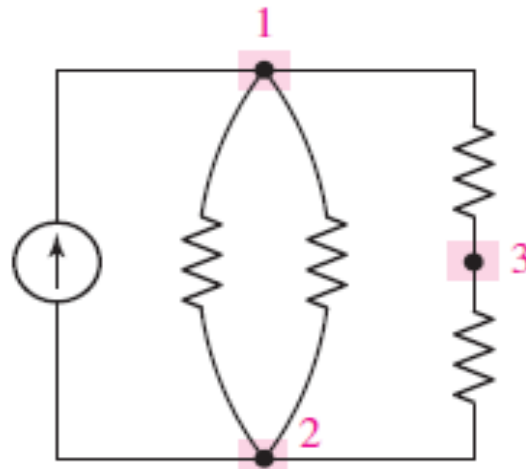- If no node was encountered more than once, then the set of nodes and elements that we have passed through is defined as a ***path***.
- ***If the node at which we started is the same as the node on which we ended, then the path is, by definition, a closed path or a loop.***






Nodes, Paths, Loops And Branches



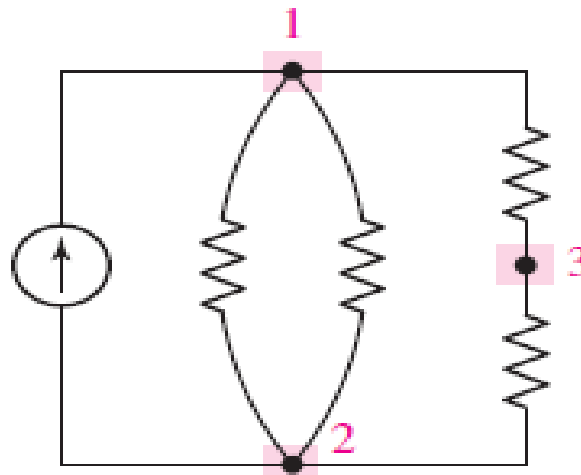- A **branch** as a single path in a network, composed of one simple element and the node at each end of that element.
- Thus, a path is a particular collection of branches.





Kirchhoff's Current Law (KCL)



- **Gustav Robert Kirchhoff**, a *German university professor who* was born about the time Ohm was doing his experimental work.
- Kirchhoff's current law (abbreviated KCL) states that **The algebraic sum of the currents entering any node is zero.**
- A compact expression for Kirchhoff's current law is

$$\sum_{n=1}^N i_n = 0$$



Kirchhoff's Current Law (KCL)



- This law represents a **mathematical statement** of the fact that charge cannot accumulate at a node.
- *A node is not a circuit element, and it certainly cannot store, destroy, or generate charge.*
- Hence, the currents must sum to **zero**.
- A hydraulic analogy : *three water pipes joined in the shape of a Y.*



Kirchhoff's Current Law (KCL)



- The sum of currents **entering** the node must be zero:

$$i_A + i_B + (-i_C) + (-i_D) = 0$$


- However, sum of currents **leaving** the node also zero:

$$(-i_A) + (-i_B) + i_C + i_D = 0$$

- We might also wish to equate

$$i_A + i_B = i_C + i_D$$

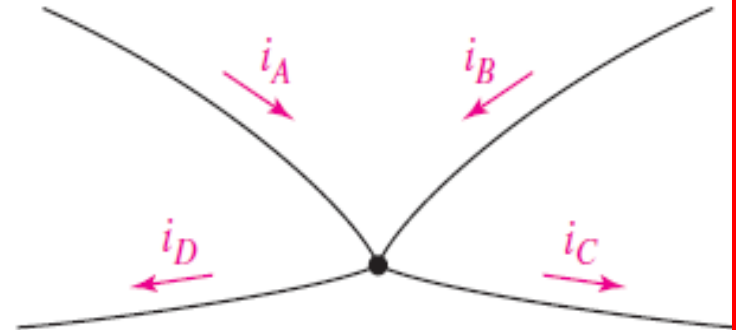- The sum of the currents going in **must equal** the sum of the currents going out.






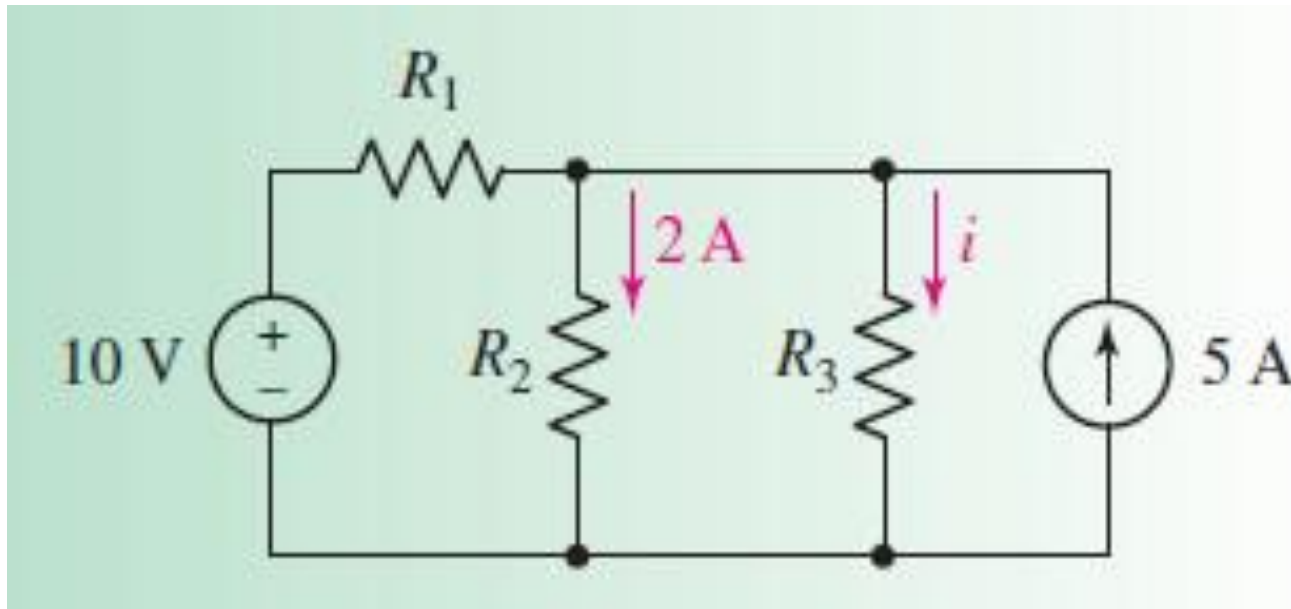Example





- For the circuit, compute the current through resistor R_3 if it is known that the voltage source supplies a current of 3 A.





Example

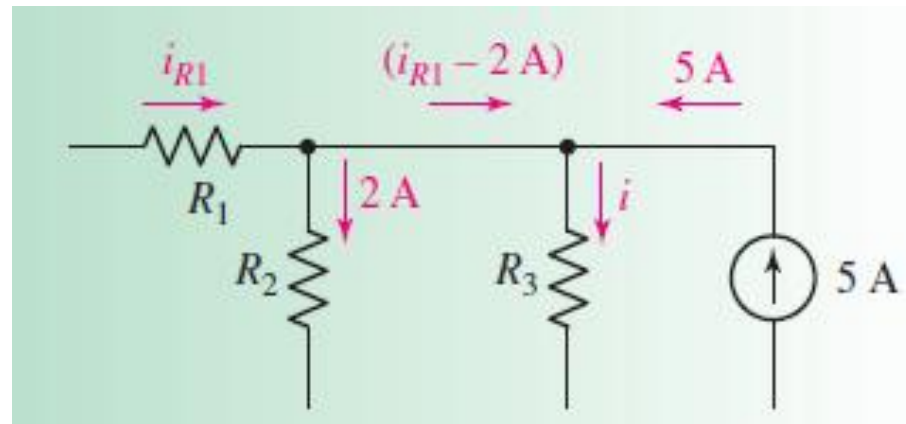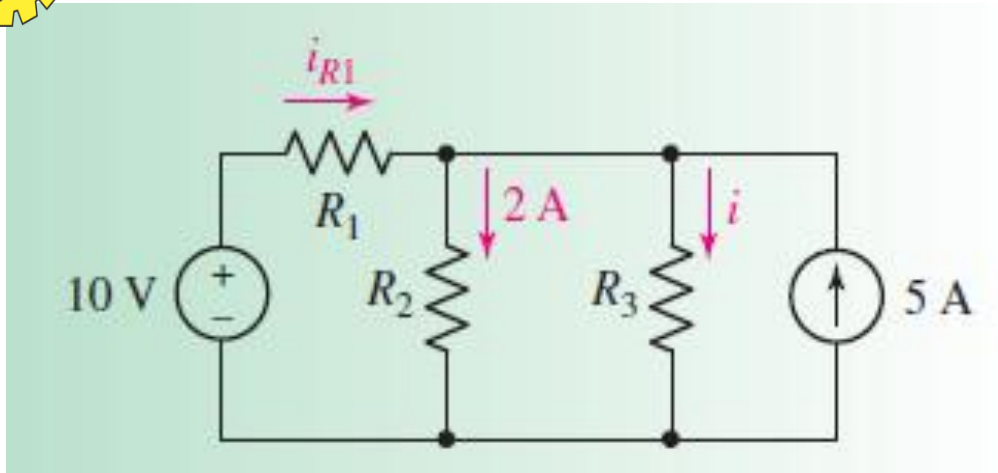



Example



- Summing the currents flowing into the node:

$$i_{R1} - 2 - i + 5 = 0$$

- We know the 10 V source is supplying 3 A.
- Substituting, we find that

$$i = 3 - 2 + 5 = 6 \text{ A.}$$



Procedures



- *Identify the goal of the problem*
- *Collect the known information*
- *Devise a plan*
- *Construct an appropriate set of equations*
- *Determine if additional information is required*
- *Attempt a solution*
- *Verify the solution. Is it reasonable or expected?*



Assessment

1. KCL deals with the conservation of?

- a) Momentum
- b) Mass
- c) Potential Energy
- d) Charge**

2. KCL is applied at _____

- a) Loop
- b) Node**
- c) Both loop and node
- d) Neither loop nor node

3. KCL can be applied for _____

- a) Planar networks
- b) Non-planar networks
- c) Both planar and non-planar**
- d) Neither planar nor non-planar



