



# **SNS COLLEGE OF TECHNOLOGY**

## **Coimbatore-35**

### **An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with ‘A++’(III Cycle) Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **23ECB101 – CIRCUIT ANALYSIS AND DEVICES**

I YEAR/ II SEMESTER

#### **UNIT 1 – MESH AND NODE ANALYSIS OF ELECTRIC CIRCUITS**

**TOPIC - Kirchoff's voltage law**



# Introduction


- In general, circuits must be analyzed to determine a complete set of voltages and currents.
- Only two simple laws are needed in addition to Ohm's law.
- The new laws are
  - **Kirchhoff's current law (KCL)**
  - **Kirchhoff's voltage law (KVL)**
- They are simply restatements of *charge and energy conservation*, respectively.



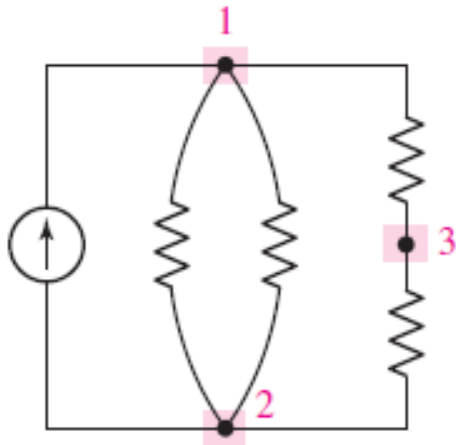
# Nodes, Paths, Loops And Branches



- A point at which two or more elements have a common connection is called a **node**.



(a)

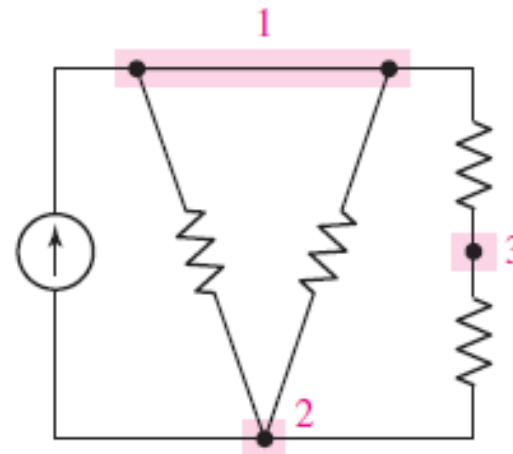


(b)


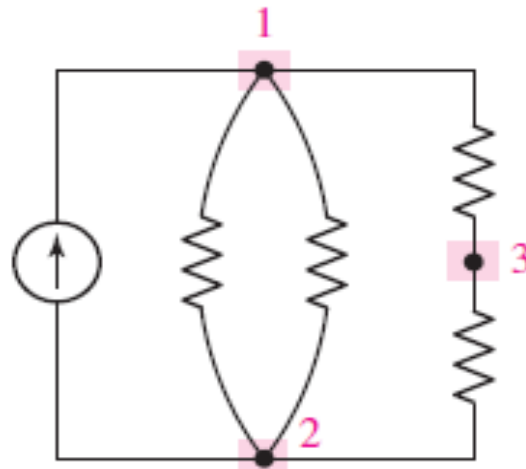
# Nodes, Paths, Loops And Branches



- If no node was encountered more than once, then the set of nodes and elements that we have passed through is defined as a ***path***.
- ***If the node at which we started is the same as the node on which we ended, then the path is, by definition, a closed path or a loop.***





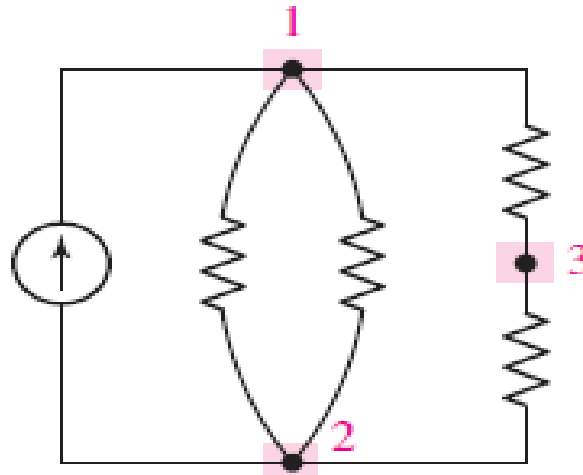
# Nodes, Paths, Loops And Branches



- A **branch** as a single path in a network, composed of one simple element and the node at each end of that element.
- Thus, a path is a particular collection of branches.





# Kirchhoff's Voltage Law (KVL)



- Kirchhoff's voltage law (abbreviated **KVL**):

**The algebraic sum of the voltages around any closed path is zero.**

- The algebraic sum of the voltages across the individual elements around it must be zero. Thus,


$$v_1 + v_2 + v_3 + \dots + v_N = 0$$

- or, more compactly,

$$\sum_{n=1}^N v_n = 0$$




# Kirchhoff's Voltage Law (KVL)

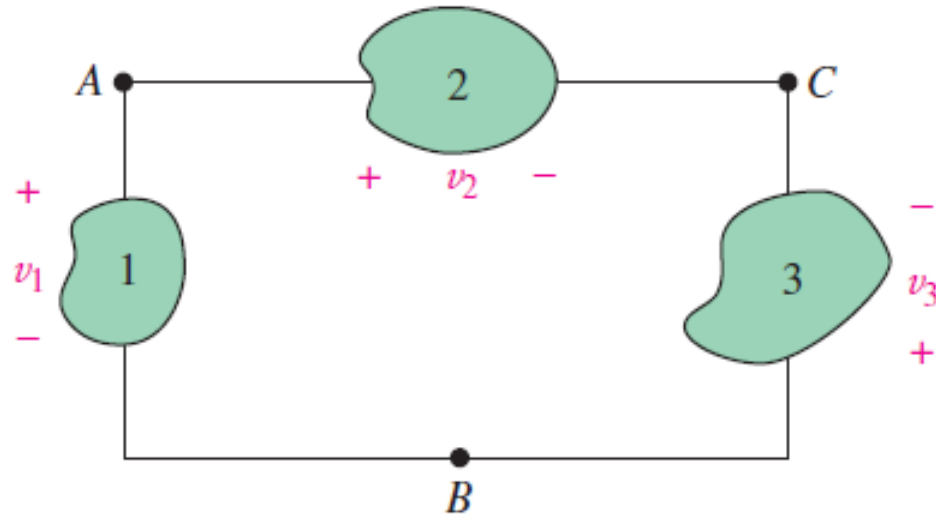

- If we carry a charge of 1 C from *A to B through element 1*, the reference polarity signs for  $v_1$  show that we do  $v_1$  joules of work.
- If we choose to proceed from *A to B via node C*, then we expend  $(v_2 - v_3)$  joules of energy.
- The work done, however, is independent of the path in a circuit, and so any route must lead to the same value for the voltage. In other words,  **$v_1 = v_2 - v_3$**



# Kirchhoff's Voltage Law (KVL)

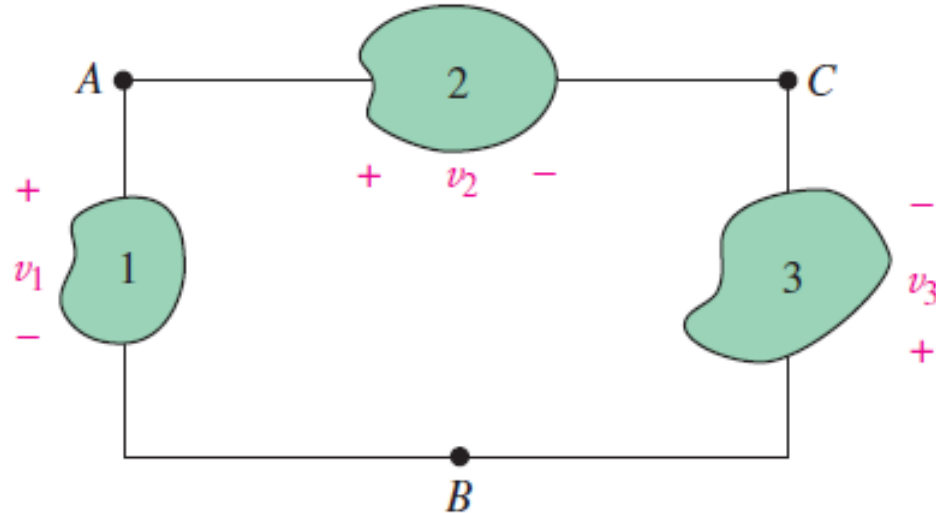

- Another method of applying KVL is moving mentally around the closed path in a clockwise direction
- Writing down directly the voltage of each element whose (+) terminal is entered, and writing down the negative of every voltage first met at the (-) sign.
- Applying this to the single loop, we have

$$-v_1 + v_2 - v_3 = 0$$





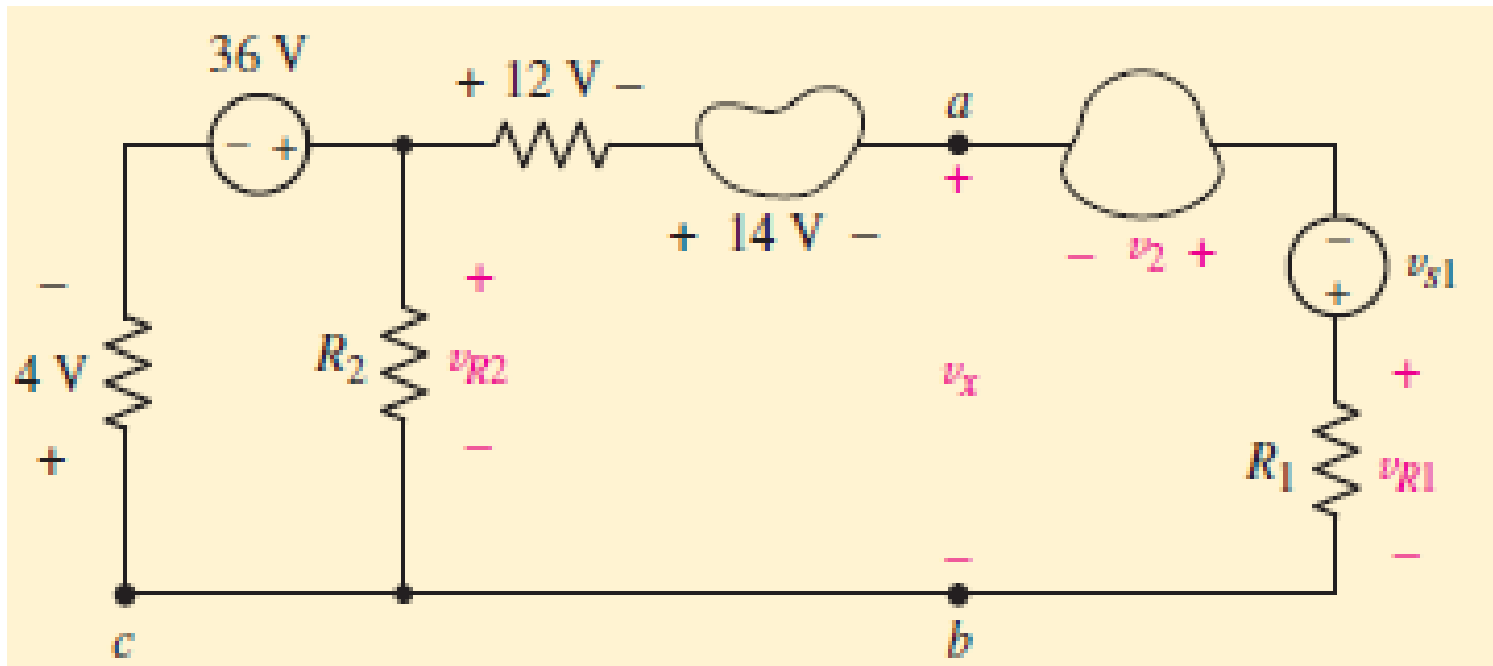
# Example



- In the circuit, there are eight circuit elements. Find  $v_{R2}$  (the voltage across  $R2$ ) and the voltage labelled  $V_x$ .





# Example



• we find  $v_{R2}$  by writing a KVL equation around the loop on the left, starting at point  $c$ :

$$4 - 36 + v_{R2} = 0$$

- which leads to  $v_{R2} = 32 \text{ V}$ .
- we apply KVL beginning at point  $c$ , moving up and across the top to  $a$ , through  $v_x$  to  $b$ , and through the conducting lead to the starting point:

$$+4 - 36 + 12 + 14 + v_x = 0$$

- so that  $v_x = 6 \text{ V}$
- **An alternative approach: Knowing  $v_{R2}$ ,** we might have taken the shortcut through  $R2$ :

$$-32 + 12 + 14 + v_x = 0$$

- yielding  $v_x = 6 \text{ V}$  once again.



# Assessment

1. KVL deals with the conservation of?

- a) Mass
- b) Momentum
- c) Charge
- d) Energy**

2. The sum of the voltages over any closed loop is equal to \_\_\_\_\_

- a) 0V**
- b) Infinity
- c) 1V
- d) 2V

3. What is the basic law that has to be followed in order to analyze the circuit?

- a) Newton's laws
- b) Faraday's laws
- c) Ampere's laws
- d) Kirchhoff's law**



