



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35

An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with ‘A++’(III Cycle) Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

23ECB101 – CIRCUIT ANALYSIS AND DEVICES

I YEAR/ II SEMESTER

UNIT 1 – MESH AND NODE ANALYSIS OF ELECTRIC CIRCUITS


TOPIC - Voltage and Current Division Rules



Current Division



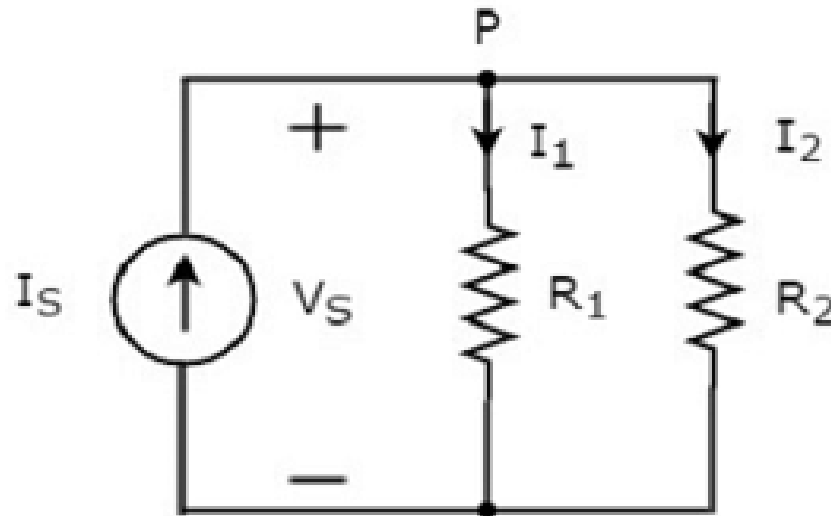- In a parallel circuit, current divides in all branches. Thus, a parallel circuit acts as a current divider.





- $I_1 = I_S (R_2 / R_1 + R_2)$
- $I_2 = I_S (R_1 / R_1 + R_2)$


- Thus current division rule states that current through any branch is given by the ratio of opposite branch resistance divided by total resistance multiplied by the total current.



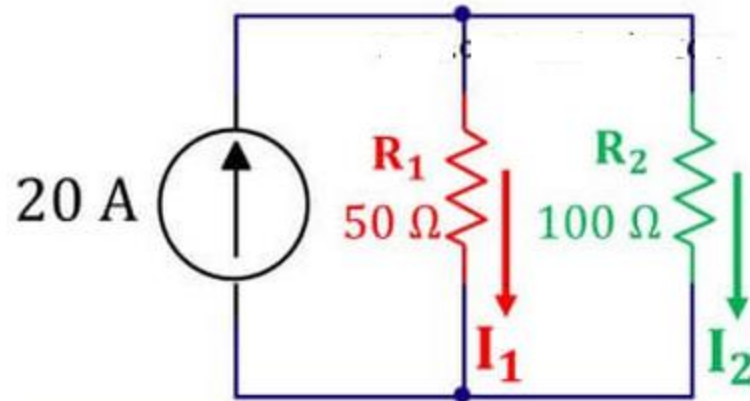Example



- *Two parallel resistors having their values 50 ohms and 100 ohms are connected in parallel. Find the current flowing through each when the connected source is of 20 A.*





Where $R_t = R_1 || R_2 = 33.33 \Omega$

$$I_1 = \frac{R_t}{R_1} * I_t$$

$$I_1 = \frac{33.33 \Omega}{50 \Omega} * 20 \text{ A}$$

$$I_1 = 13.33 \text{ A}$$

$$I_2 = \frac{R_t}{R_2} * I_t$$

$$I_2 = \frac{33.33 \Omega}{100 \Omega} * 20 \text{ A}$$


$$I_2 = 6.66 \text{ A}$$



Voltage Division



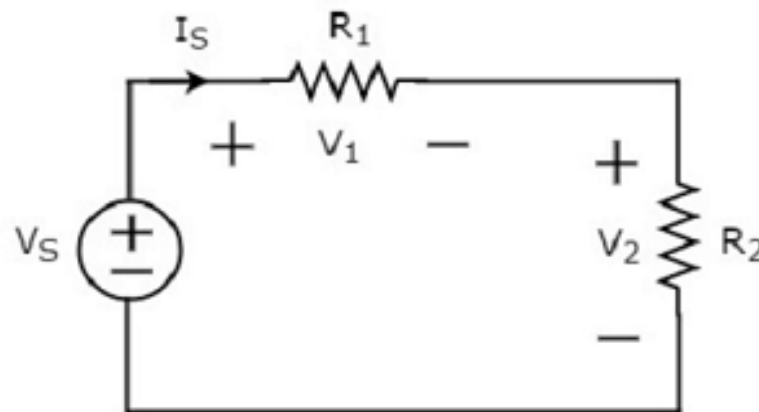- The series circuit acts as a voltage divider. Since the same current flows through each resistor, the voltage drops are proportional to the values of resistor.





- $V_1 = V_S(R_1/R_1 + R_2)$
- $V_2 = V_S(R_2/R_1 + R_2)$

- Voltage division rule states that the Voltage drop across any resistor in a series circuit is equal to the ratio of that resistance value to the total resistance, multiplied by the source voltage.



Example



- Three resistive elements of $6\text{k}\Omega$, $12\text{k}\Omega$ and $18\text{k}\Omega$ are connected together in series across a 36 volt supply. Calculate, the total resistance, the value of the current flowing around the circuit, and the voltage drops across each resistor.
- Data given: $V_S = 36$ volts, $R_1 = 6\text{k}\Omega$, $R_2 = 12\text{k}\Omega$ and $R_3 = 18\text{k}\Omega$



$$R_T = R_1 + R_2 + R_3 = 6k\Omega + 12k\Omega + 18k\Omega = 36k\Omega$$

$$I = \frac{V_S}{R_T} = \frac{36}{36000} = 1\text{mA}$$

$$V_{R1} = V_S \left(\frac{R_1}{R_T} \right) = 36 \left(\frac{6000}{36000} \right) = 6\text{volts}$$

$$V_{R2} = V_S \left(\frac{R_2}{R_T} \right) = 36 \left(\frac{12000}{36000} \right) = 12\text{volts}$$

$$V_{R3} = V_S \left(\frac{R_3}{R_T} \right) = 36 \left(\frac{18000}{36000} \right) = 18\text{volts}$$



Assessment

1. If there are 3 Resistors R_1 , R_2 and R_3 in series and V is total voltage and I is total current then Voltage across R_2 is

- a) $V R_3 / R_1 + R_2 + R_3$
- b) $V R_2 / R_1 + R_2 + R_3$**
- c) $V R_1 / R_1 + R_2 + R_3$
- d) V

2. For a parallel connected resistor R_1 , R_2 and a voltage of V volts. Current across the first resistor is given by

- a) $I R_1$
- b) $I R_2$
- c) $I R_1 / R_1 + R_2$
- d) $I R_2 / R_1 + R_2$**

3. Why is current division necessary?

- a) In series current is the same
- b) In parallel current differs**
- c) Because the voltage is also different
- d) Because of Kirchoff's laws.





THANK YOU