



SNS COLLEGE OF TECHNOLOGY
Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with ‘A++’(III Cycle) Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

23ECB101 – CIRCUIT ANALYSIS AND DEVICES

I YEAR/ II SEMESTER

UNIT 1 – MESH AND NODE ANALYSIS OF ELECTRIC CIRCUITS

TOPIC - Nodal Analysis



Nodal Analysis



- There are two basic methods that are used for solving any electrical network: **Nodal analysis** and **Mesh analysis**.
- In Nodal analysis, we will consider the node voltages with respect to Ground. Hence, Nodal analysis is also called as **Node-voltage method**.



- Follow these steps while solving any electrical network or circuit using **Nodal analysis**.

- **Step 1** – Identify the **principal nodes** and choose one of them as **reference node**. We will treat that reference node as the Ground.

- **Step 2** – Label the **node voltages** with respect to Ground from all the principal nodes except the reference node.



- **Step 3** – Write **nodal equations** at all the principal nodes except the reference node. Nodal equation is obtained by applying KCL first and then Ohm's law.

- **Step 4** – Solve the nodal equations obtained in Step 3 in order to get the node voltages.


- Now, we can find the current flowing through any element and the voltage across any element that is present in the given network by using node voltages.



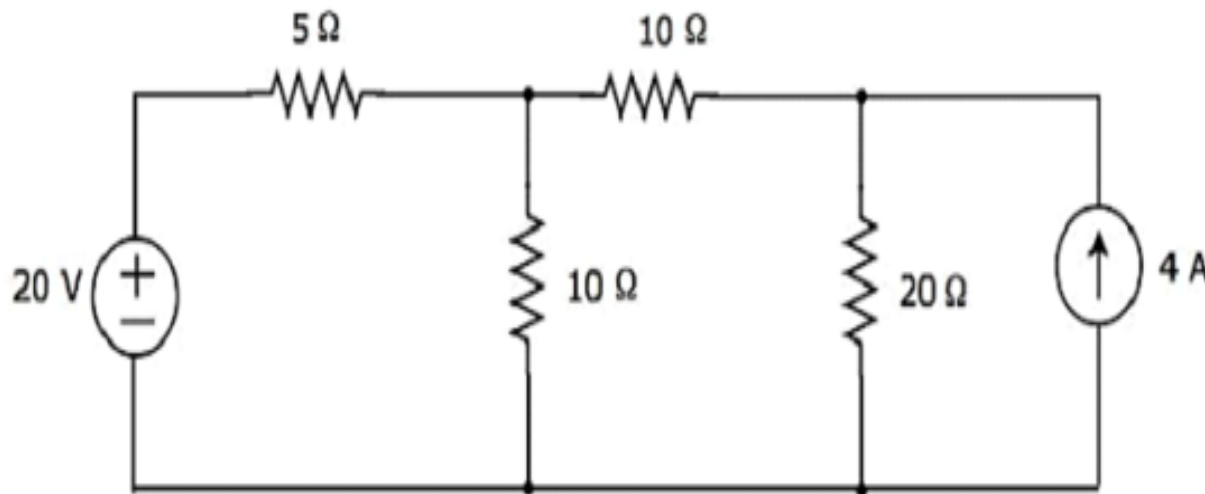Example




- Find the current flowing through $20\ \Omega$ resistor of the following circuit using **Nodal analysis**.





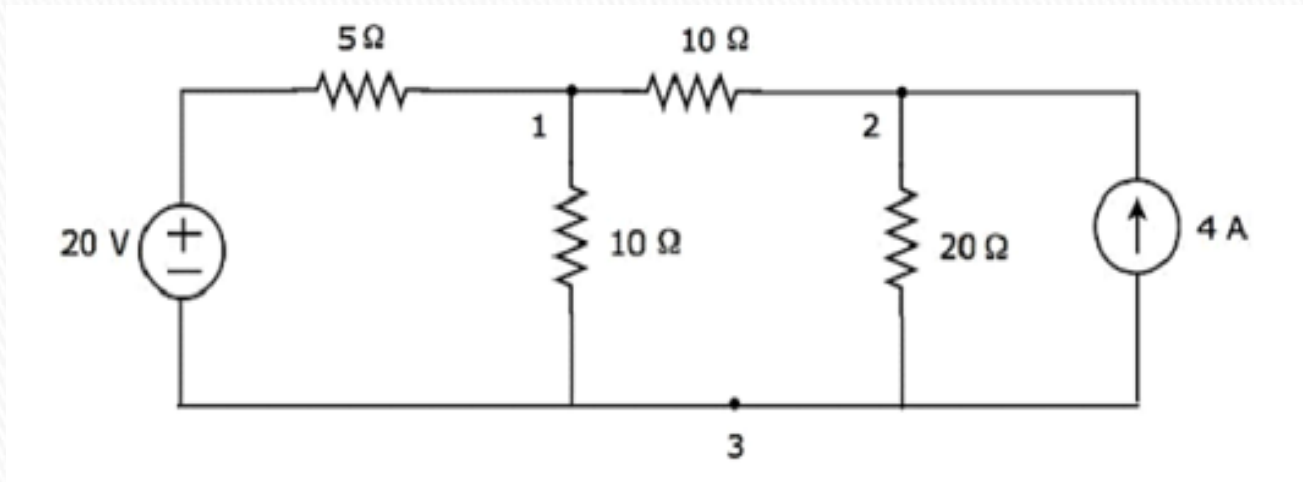
- **Step 1** – There are **three principle nodes** in the above circuit. Those are labelled as 1, 2, and 3 in the following figure.



In the above figure, consider **node 3** as reference node (Ground).



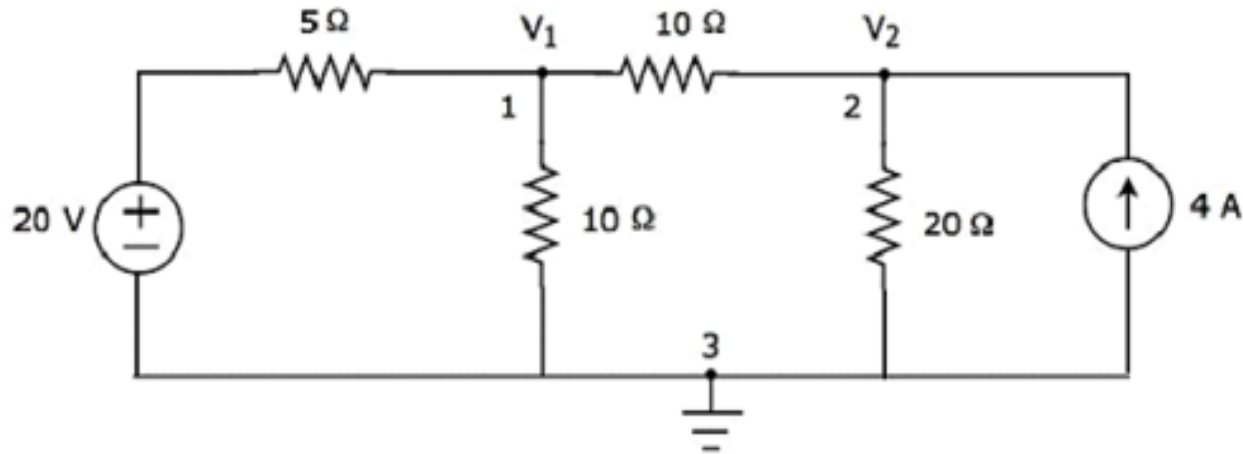Step 2 – The node voltages, V_1 and V_2 , are labelled in the following figure.



In the above figure, V_1 is the voltage from node 1 with respect to ground and V_2 is the voltage from node 2 with respect to ground.



Step 3 : The nodal equation at node 1 is

The **nodal equation** at node 1 is

$$\frac{V_1 - 20}{5} + \frac{V_1}{10} + \frac{V_1 - V_2}{10} = 0$$

$$\Rightarrow \frac{2V_1 - 40 + V_1 + V_1 - V_2}{10} = 0$$

$$\Rightarrow 4V_1 - 40 - V_2 = 0$$

$$\Rightarrow V_2 = 4V_1 - 40$$

Equation 1



The **nodal equation** at node 2 is

$$-4 + \frac{V_2}{20} + \frac{V_2 - V_1}{10} = 0$$

$$\Rightarrow \frac{-80 + V_2 + 2V_2 - 2V_1}{20} = 0$$

$$\Rightarrow 3V_2 - 2V_1 = 80$$

Equation 2



**Step 4 – Finding node voltages, V_1 and V_2 by solving Equation 1 and Equation 2.
substitute Equation 1 in Equation 2.**

$$3(4V_1 - 40) - 2V_1 = 80$$

$$\Rightarrow 12V_1 - 120 - 2V_1 = 80$$

$$\Rightarrow 10V_1 = 200$$

$$\Rightarrow V_1 = 20V$$

Substitute $V_1 = 20$ V in Equation 1.

$$V_2 = 4(20) - 40$$

$$\Rightarrow V_2 = 40V$$



- **Step 5** – The voltage across $20\ \Omega$ resistor is nothing but the node voltage V_2 and it is equal to $40\ \text{V}$. Now, we can find the current flowing through $20\ \Omega$ resistor by using Ohm's law.

- $I_{20\Omega} = V_2 / R$

- Substitute the values of V_2 and R in the above equation.

- $I_{20\Omega} = 40 / 20 \Rightarrow I_{20\Omega} = 2\ \text{A}$



Assessment

1. Nodal analysis is generally used to determine_____

- a) **Voltage**
- b) Current
- c) Resistance
- d) Power

2. If there are 10 nodes in a circuit, how many equations do we get?

- a) 10
- b) 9**
- c) 8
- d) 7

3. How many nodes are taken as reference nodes in a nodal analysis?

- a) 1**
- b) 2
- c) 3
- d) 4





THANK YOU