



SNS COLLEGE OF TECHNOLOGY
Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with ‘A++’(III Cycle) Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

23ECB101 – CIRCUIT ANALYSIS AND DEVICES

I YEAR/ II SEMESTER



UNIT 2 – NETWORK THEOREMS AND SOURCE TRANSFORMATION

TOPIC - Thevenin Theorem



THEVENIN THEOREM

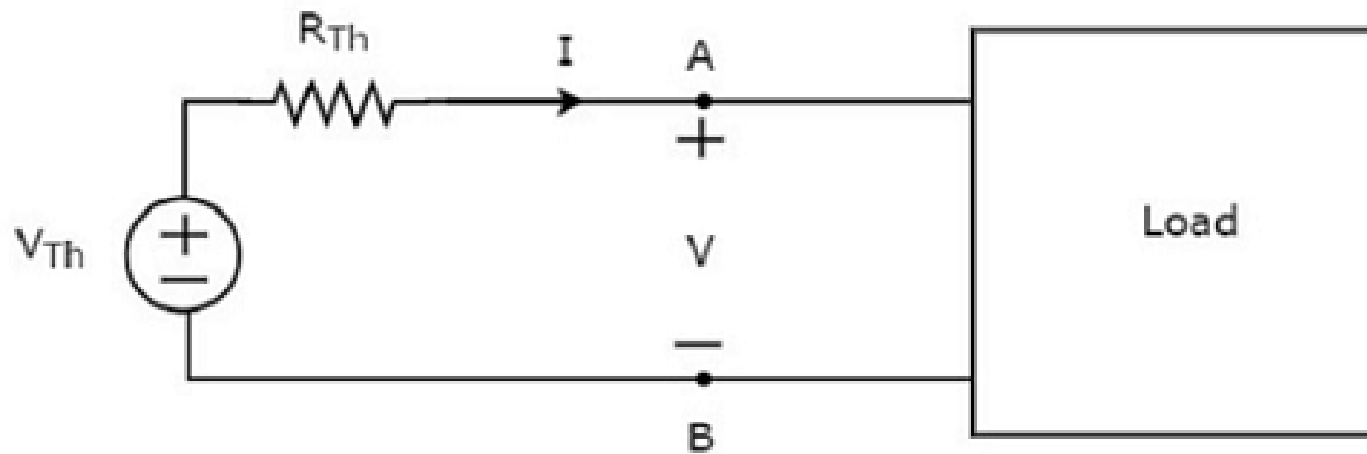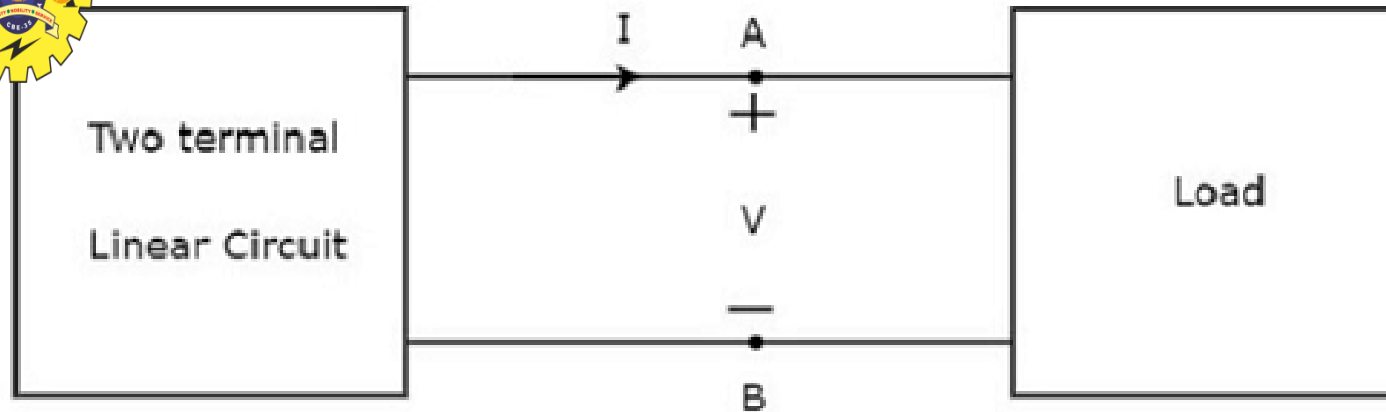Any linear, two terminal, bilateral active network can be replaced by a voltage source of thevenins voltage V_{th} in series with a thevenins resistance R_{th} . V_{th} is the open circuit voltage across the terminals & R_{th} is the effective resistance looking back from the terminals.



Thevenin Equivalent Circuit



Steps involved in solving a problem using thevenins theorem:

- **Step 1** – Consider the circuit diagram by opening the terminals with respect to which the Thevenin's equivalent circuit is to be found.
- **Step 2** – Find Thevenin's voltage V_{Th} across the open terminals of the above circuit.




- **Step 3** – Find Thevenin's resistance R_{Th} across the open terminals of the above circuit by eliminating the independent sources present in it.
- **Step 4** – Draw the **Thevenin's equivalent circuit** by connecting a Thevenin's voltage V_{Th} in series with a Thevenin's resistance R_{Th} .



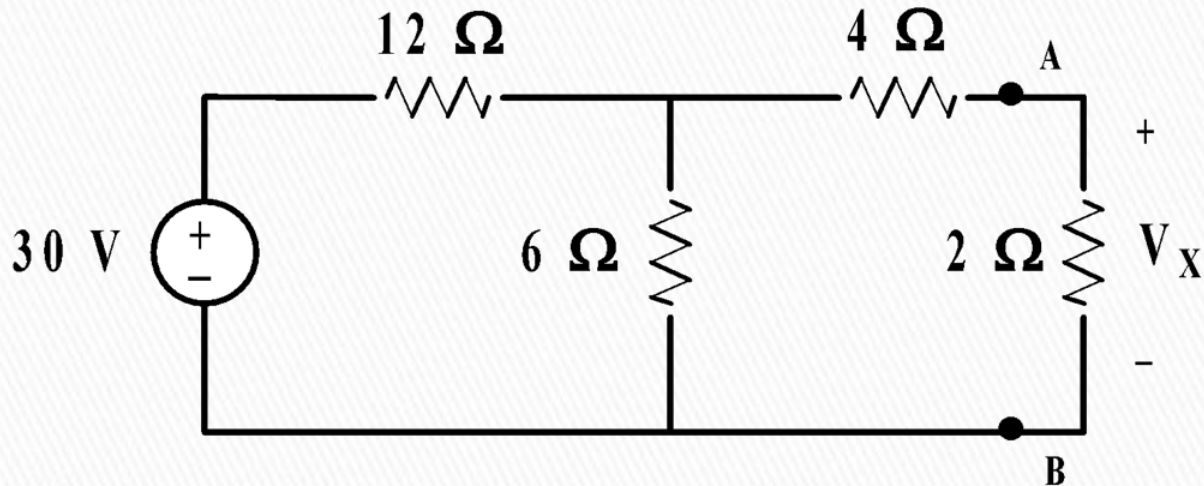
Example



Find V_X by first finding V_{TH} and R_{TH} to the left of A-B.




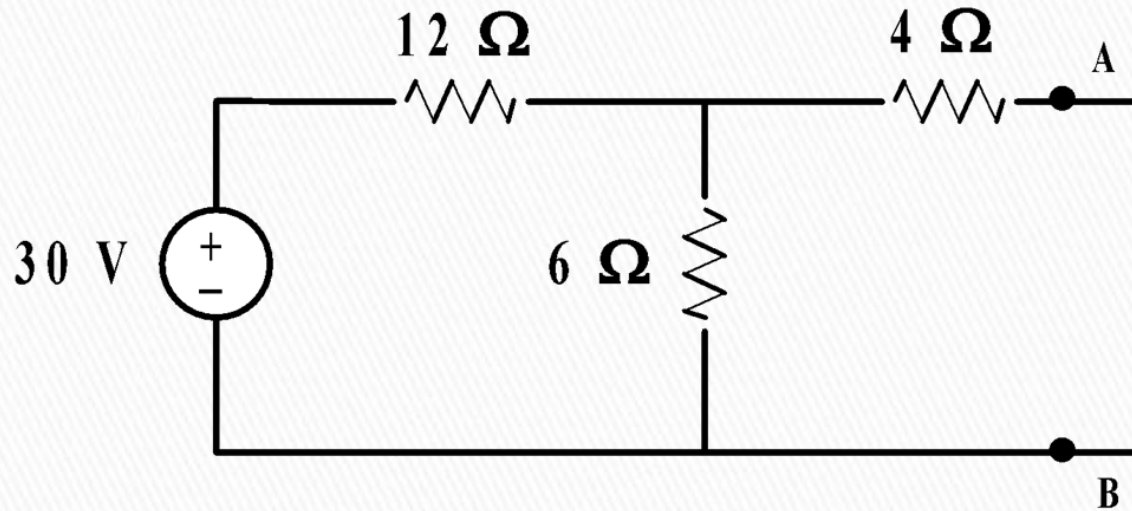First remove everything to the right of A-B.



Circuit for finding V_{TH}

$$V_{AB} = \frac{(30)(6)}{6+12} = 10V$$

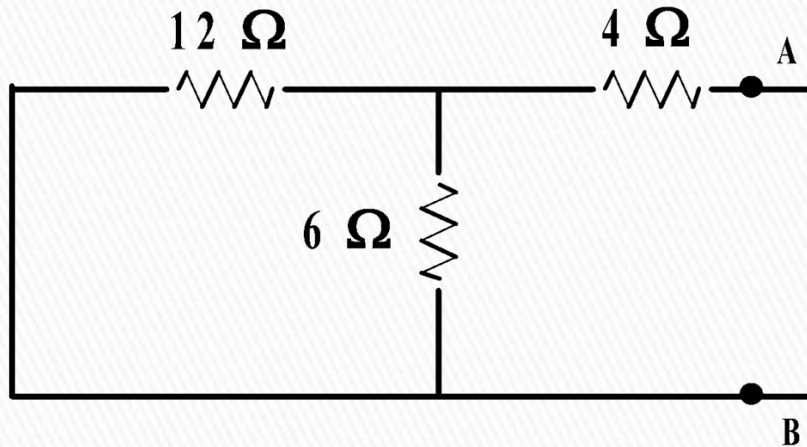


Circuit for finding R_{TH}

$$R_{TH} = 12 || 6 + 4 = 8 \Omega$$



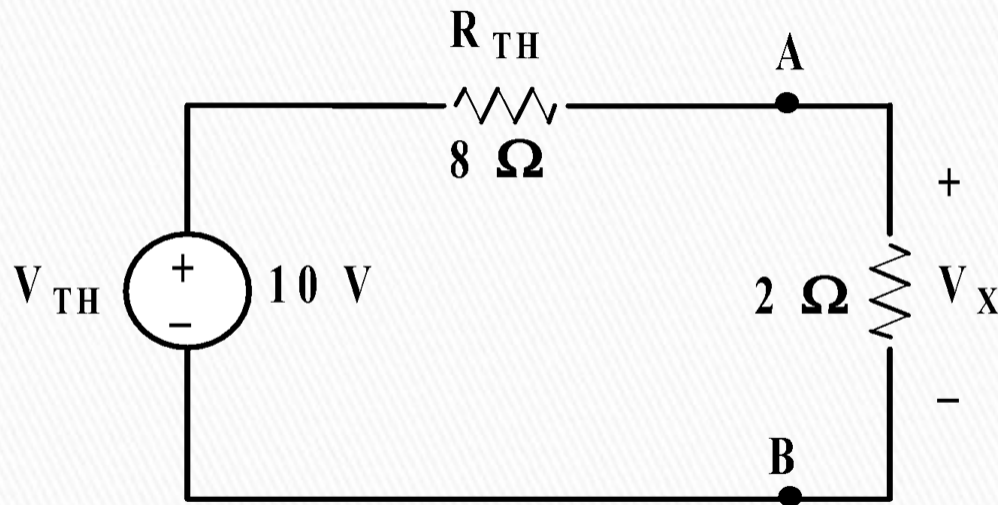After having found the Thevenin circuit connect this to the load in order to find V_X .








$$V_X = \frac{(10)(2)}{2+8} = 2V$$




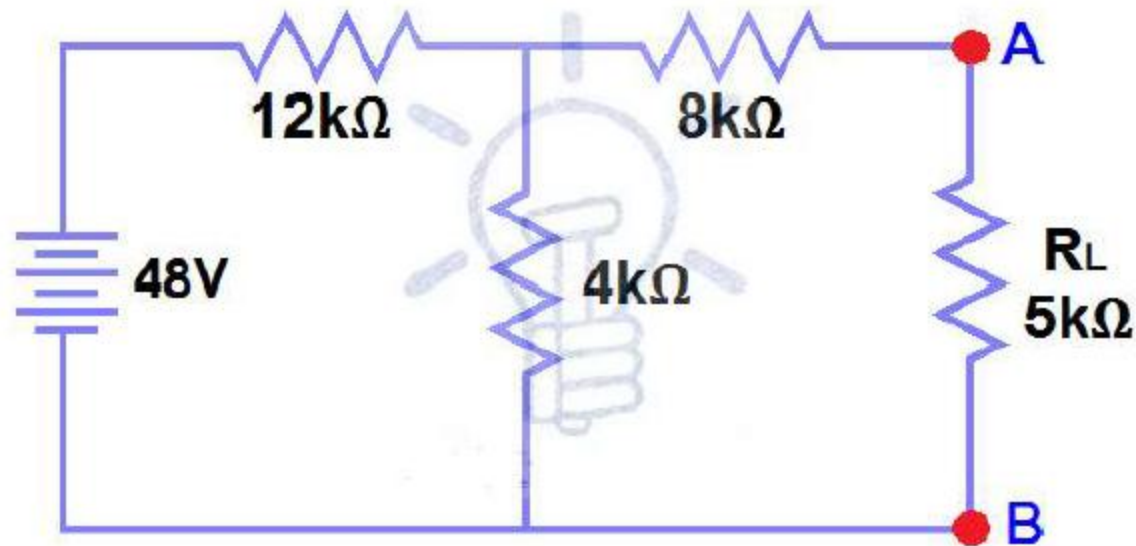Example

- Find V_{TH} , R_{TH} and the load current flowing through and load voltage across the load resistor using Thevenin's Theorem.



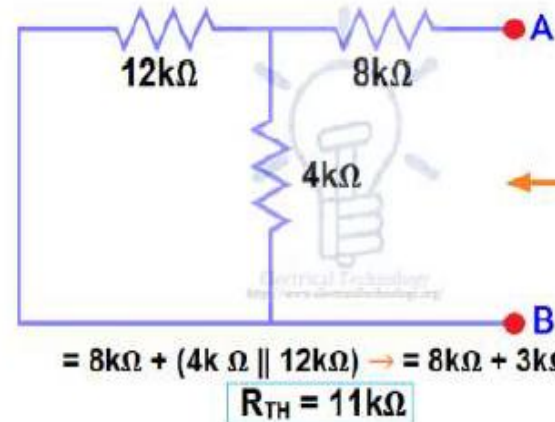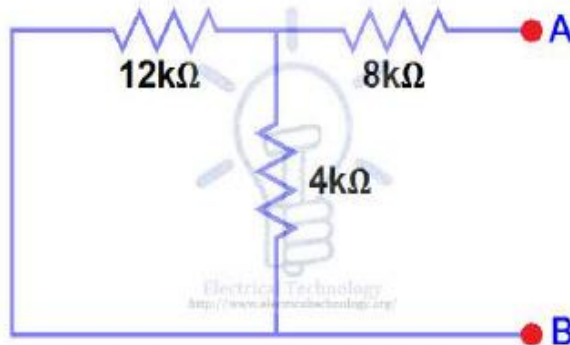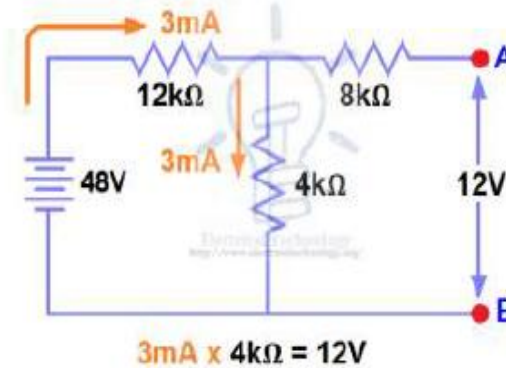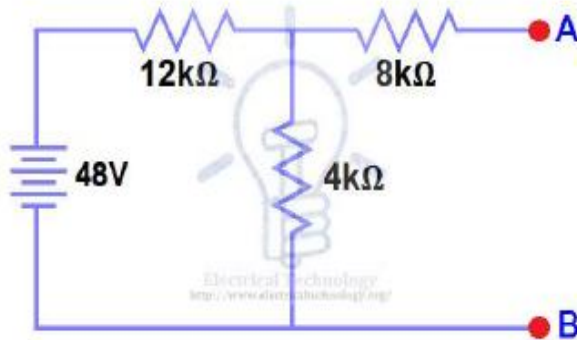

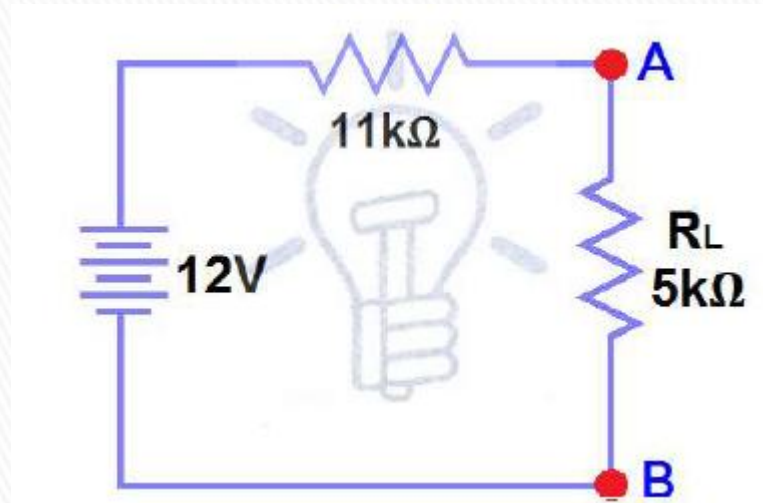

Now apply the last step. calculate the total load current & load voltage

$$I_L = V_{TH} / (R_{TH} + R_L)$$
$$= 12V / (11k\Omega + 5k\Omega) \rightarrow = 12/16k\Omega$$

$$I_L = 0.75mA$$

And

$$V_L = I_L \times R_L$$

$$V_L = 0.75mA \times 5k\Omega$$

$$V_L = 3.75V$$



THANK YOU