



SNS COLLEGE OF TECHNOLOGY
Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with ‘A++’(III Cycle) Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

23ECB101 – CIRCUIT ANALYSIS AND DEVICES

I YEAR/ II SEMESTER

UNIT 2 – NETWORK THEOREMS AND SOURCE TRANSFORMATION

TOPIC - Star-delta conversion Problems



Introduction




- Some resistor networks cannot be simplified using the usual series and parallel combinations. This situation can often be handled by trying the Δ -Y\Delta - Wye Y- Δ \Wye - delta transformation.
- The transformation allows us to replace three resistors in a Δ \Delta configuration by three resistors in a Y\Wye configuration, and the other way around.



Delta Wye Conversion

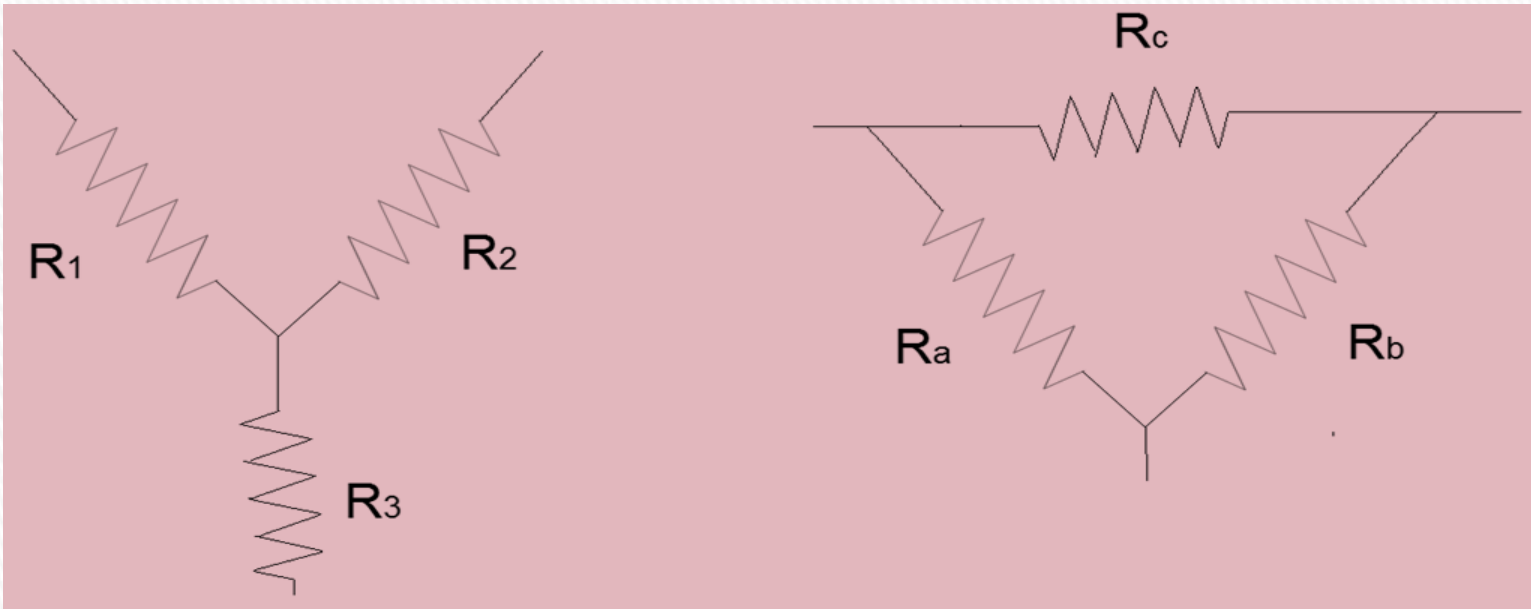- 3 terminal arrangements – commonly used in power systems



Wye (Y)


Delta (D)



delta has three nodes, while Y\Wye has four nodes (one extra in the center).



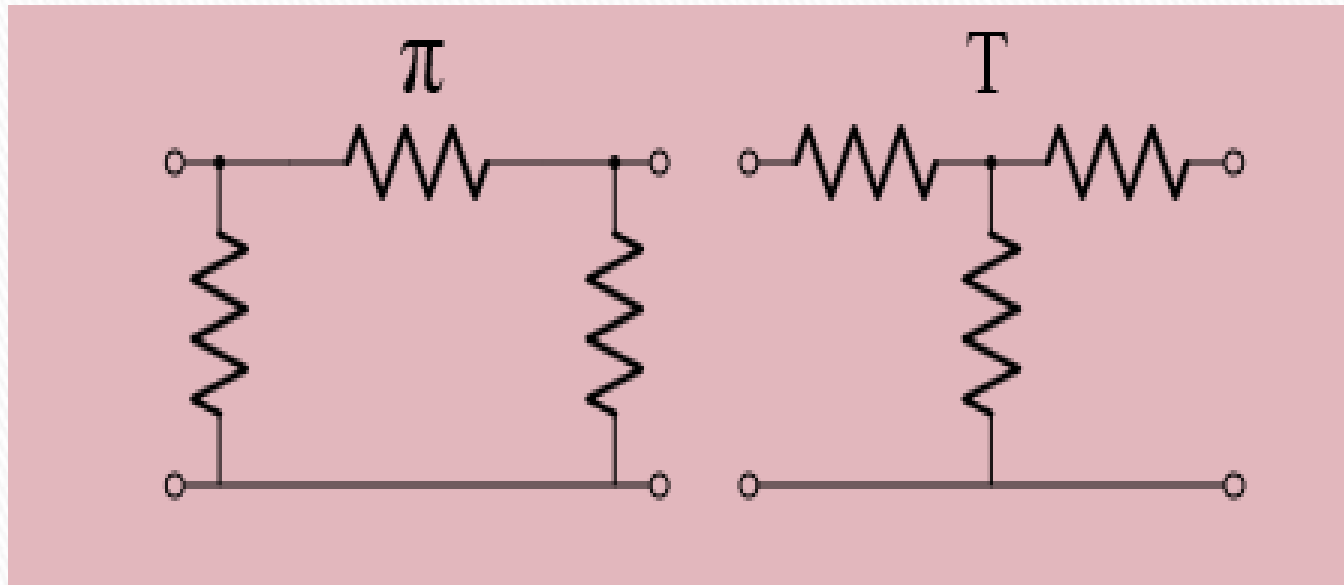- The configurations can be redrawn to square up the resistors. This is called a π - T





To transform a Delta into a Wye

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$



To transform a Wye into a Delta

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$



Simplification



- If $R_a = R_b = R_c = R'$, then $R_1 = R_2 = R_3 = R/3$
- If $R_1 = R_2 = R_3 = R$, then $R_a = R_b = R_c = 3R$



Example




- Assume we have a Δ 3 Ω resistors. Derive the Y equivalent by using the $\Delta \rightarrow Y$ equations.

$$R1 = \frac{Rb Rc}{Ra + Rb + Rc} = \frac{3 \cdot 3}{3 + 3 + 3} = 1 \Omega$$

$$R2 = \frac{Ra Rc}{Ra + Rb + Rc} = \frac{3 \cdot 3}{3 + 3 + 3} = 1 \Omega$$
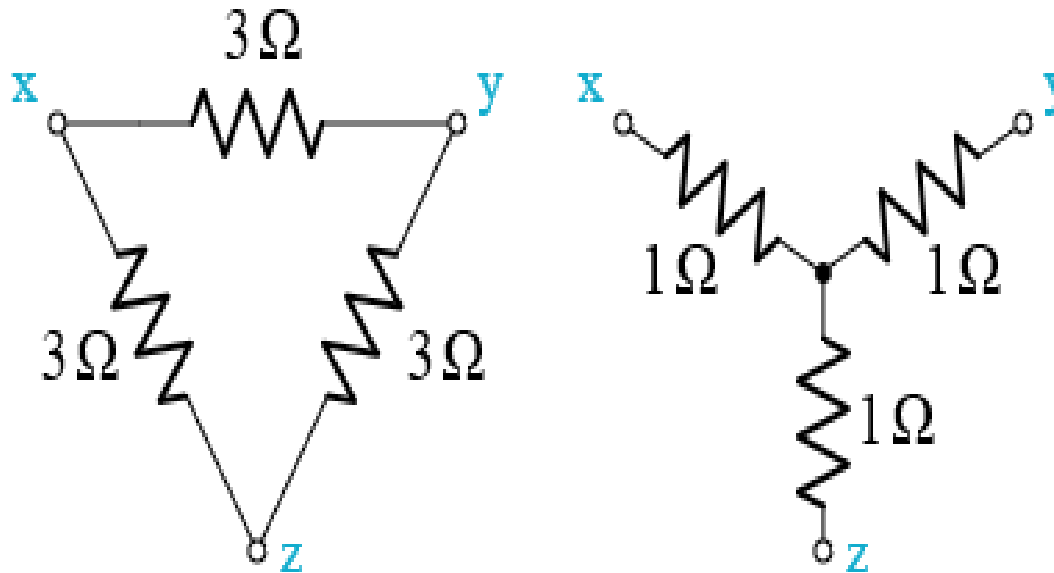
$$R3 = \frac{Ra Rb}{Ra + Rb + Rc} = \frac{3 \cdot 3}{3 + 3 + 3} = 1 \Omega$$



All the 3Ω resistors in delta connected network has been replaced By 1Ω resistor in Star connected network.



Going in the other direction, from Y \rightarrow Δ ,

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = \frac{1 \cdot 1 + 1 \cdot 1 + 1 \cdot 1}{1} = 3 \Omega$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = \frac{1 \cdot 1 + 1 \cdot 1 + 1 \cdot 1}{1} = 3 \Omega$$


$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{1 \cdot 1 + 1 \cdot 1 + 1 \cdot 1}{1} = 3 \Omega$$



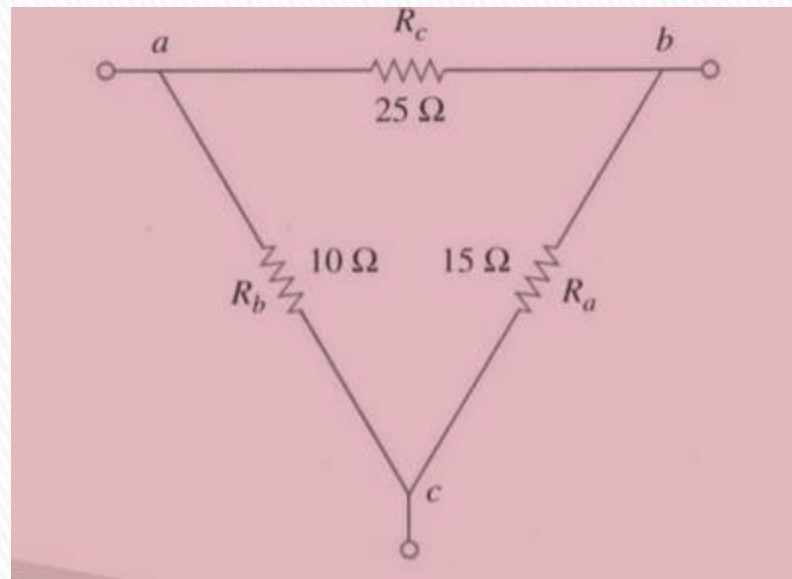Example



- Transform the delta network into its equivalent Wye network






Procedure



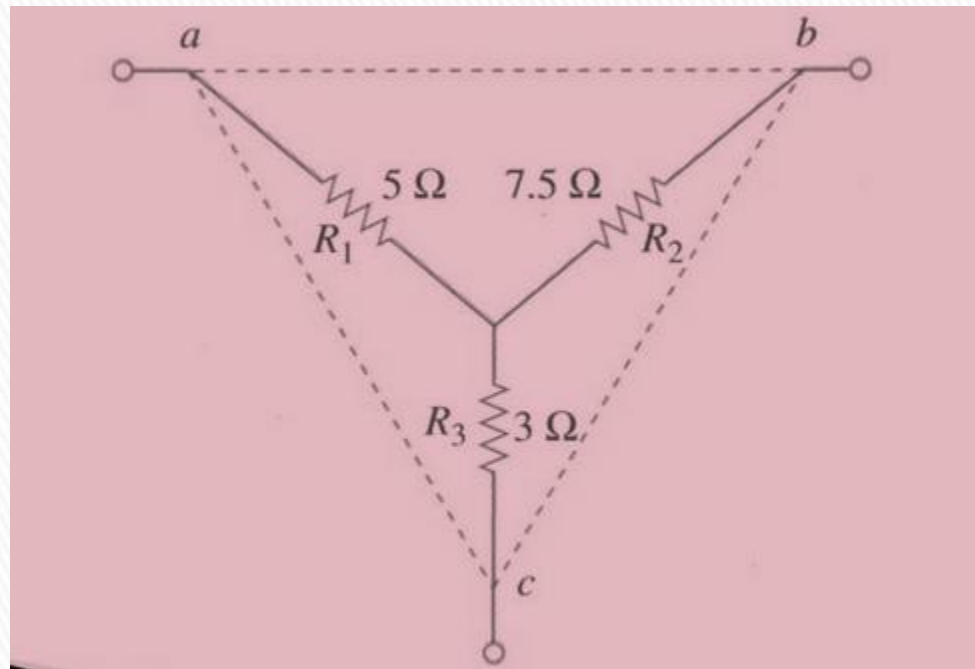- First transform your network into opposite network.
- Calculate the values of the new network.
- Erase the old network.







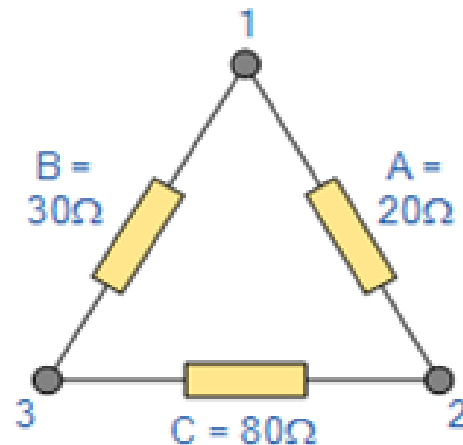Example



- Convert the following Delta Resistive Network into an equivalent Star Network.




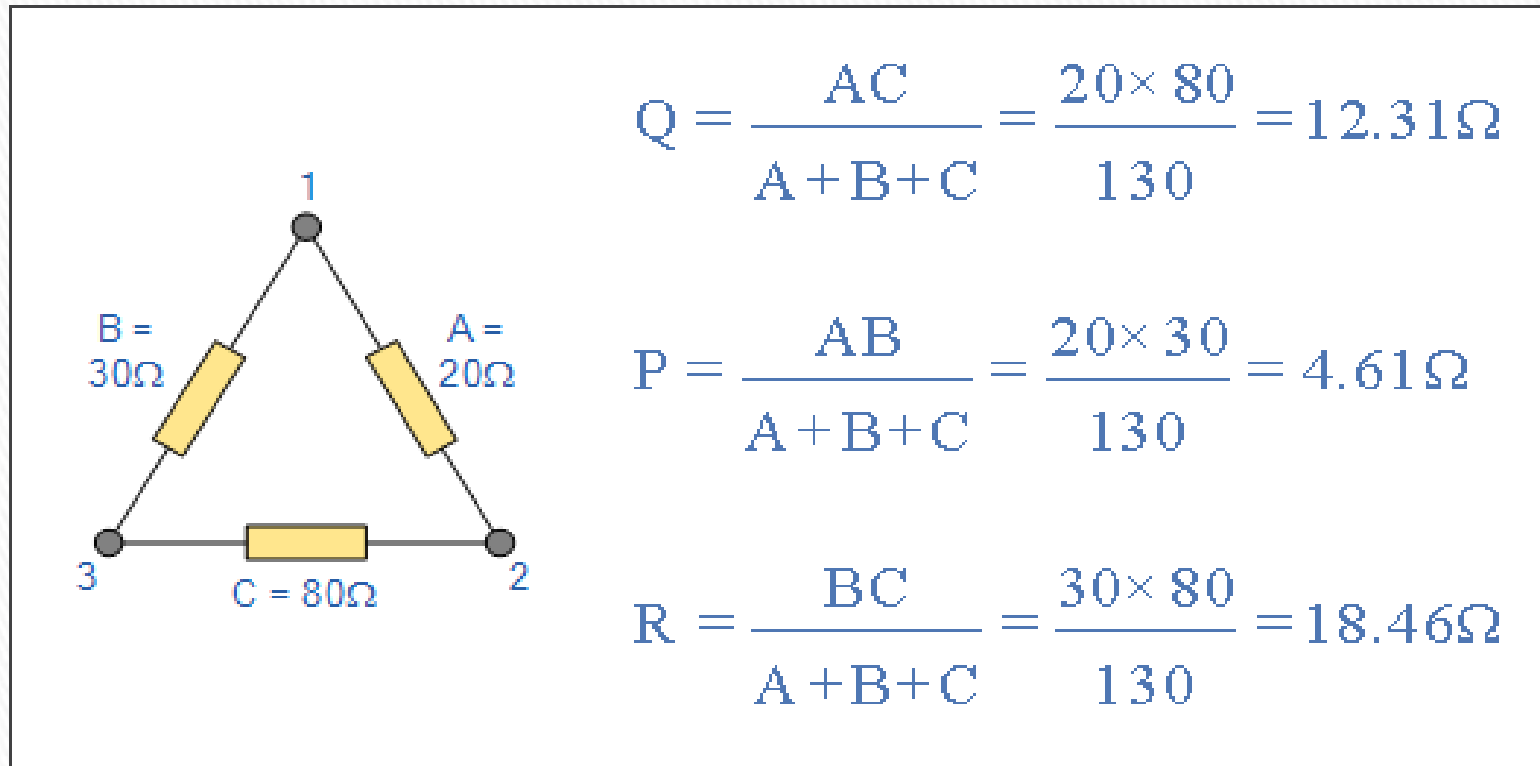




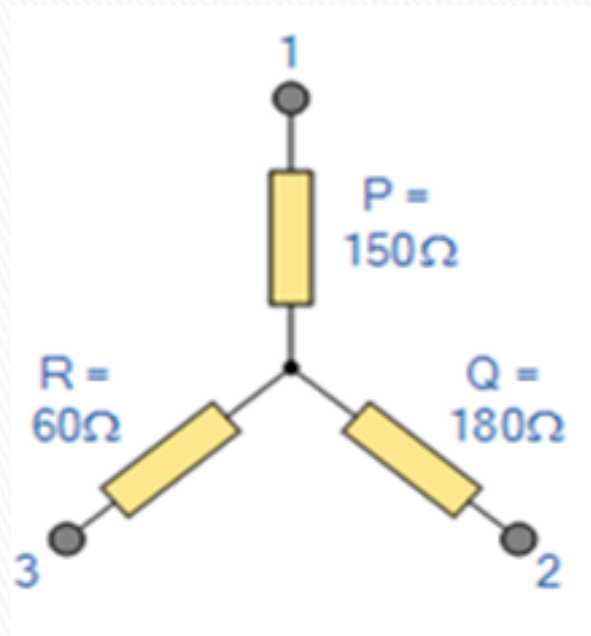Example

- Convert the following Star Resistive Network into an equivalent Delta Network.




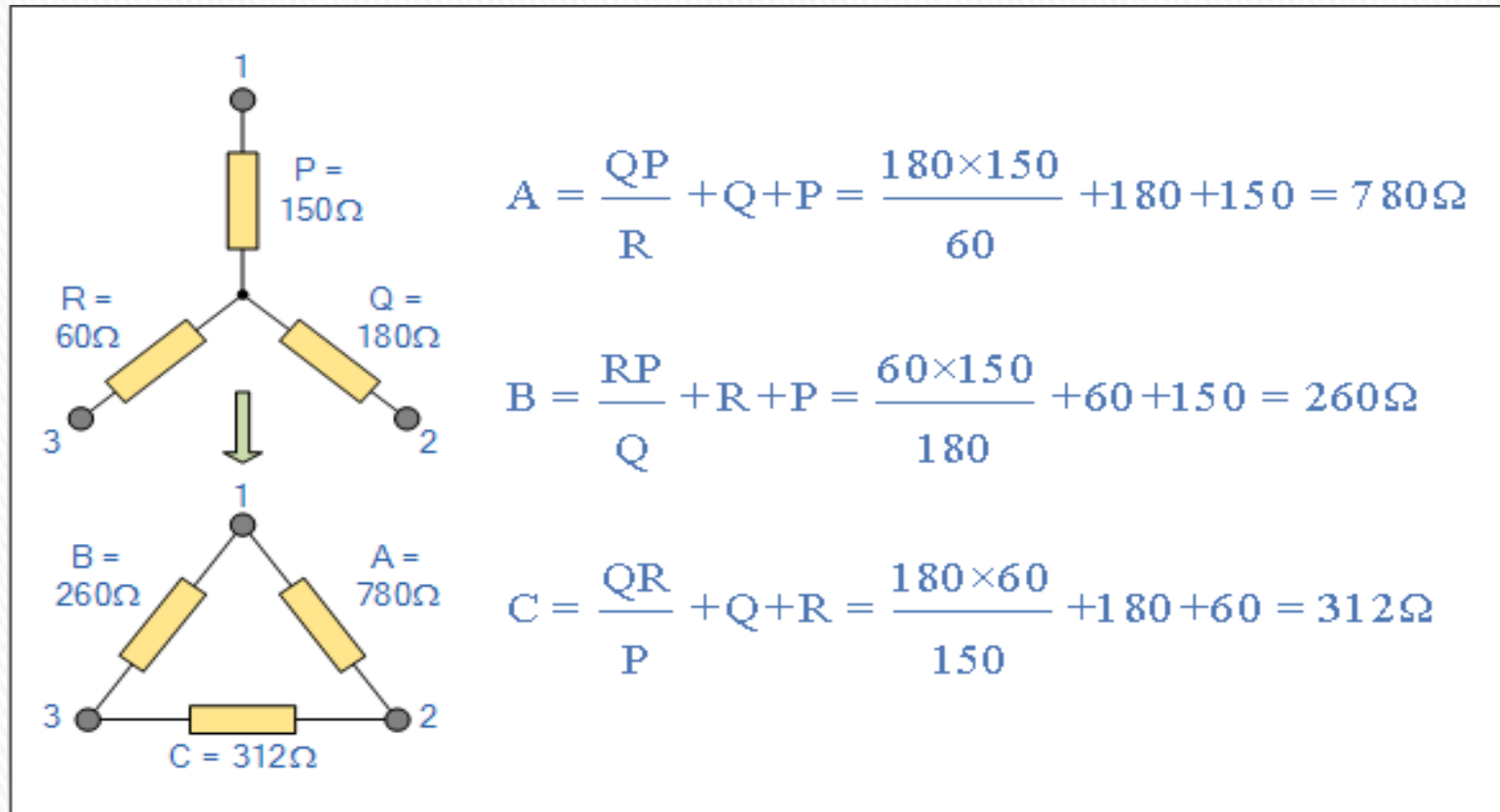




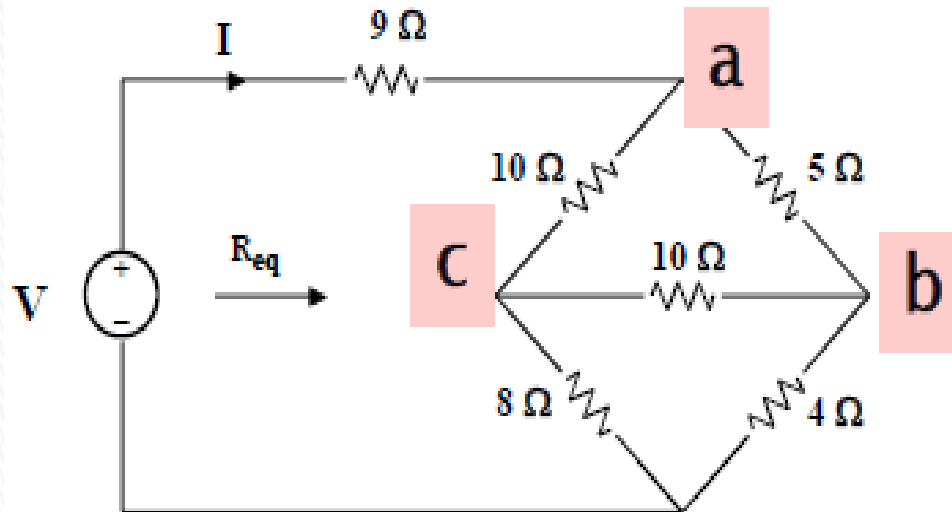Example

- Using the following circuit. Find R_{eq} .



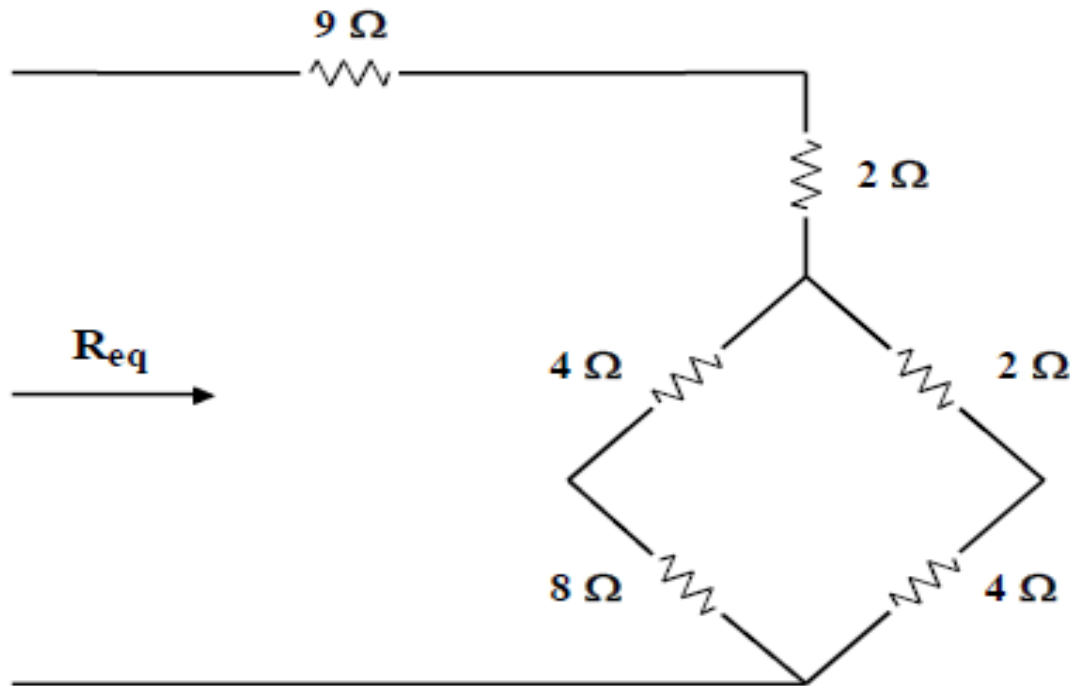Convert the delta around a – b – c to a wye.




$$R_{eq} = 15\ \Omega$$



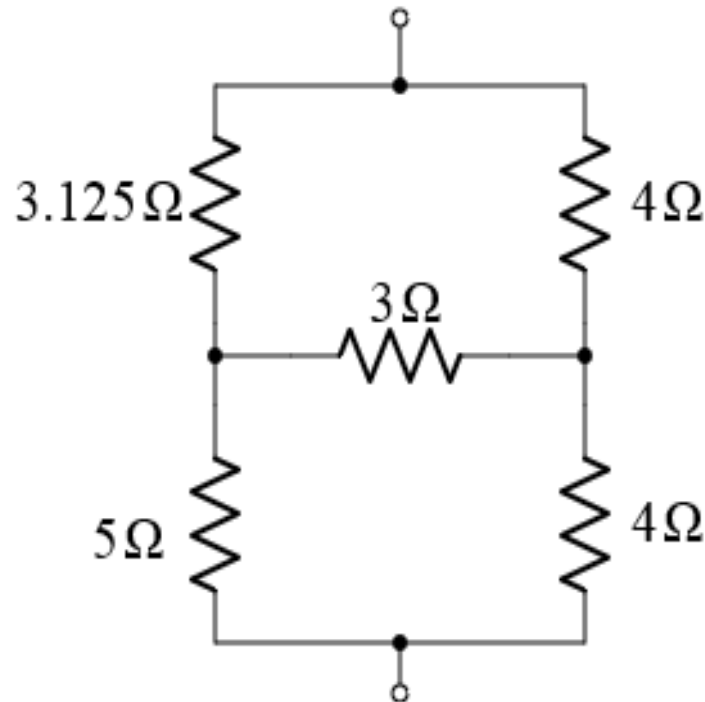
Example

- find the equivalent resistance between the top and bottom terminals.





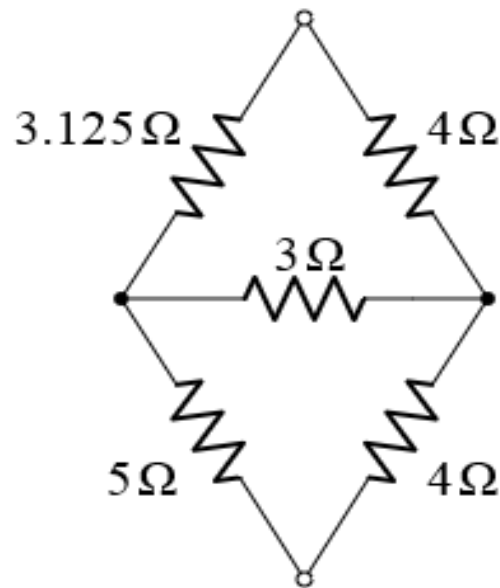
First, let's redraw the schematic to emphasize
we have two Δ (Delta) connections stacked
on the other.






*Now select one of the Δ \Delta to convert
1. We will perform a $\Delta \rightarrow Y$ transformation.*

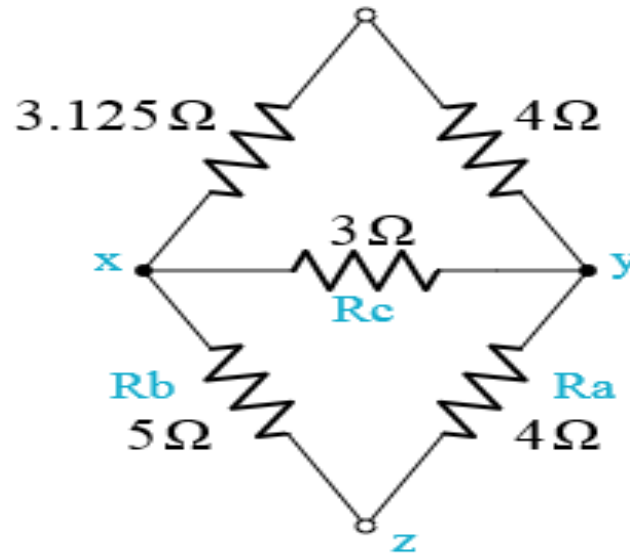- To get the right answers from the transformation equations, it is critical to keep the resistor names and node names straight.
- R_c must connect between nodes X and Y, and so on for the other resistors.



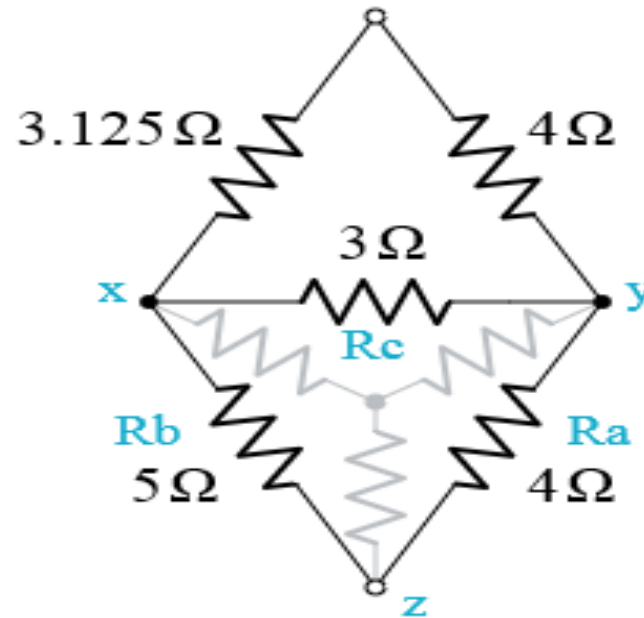
When we perform the transform on the lower Δ , the Δ resistors will be replaced by the new resistors,



Compute three new resistor values to convert the Δ to a Y, and draw the complete circuit.



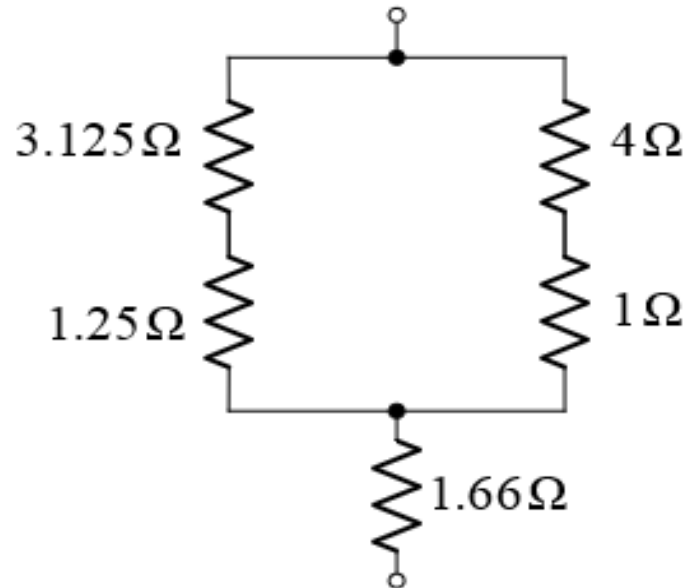
Continue simplification with series and parallel combinations until we get down to a single resistor between the terminals.






we proceed through the remaining simplification steps.

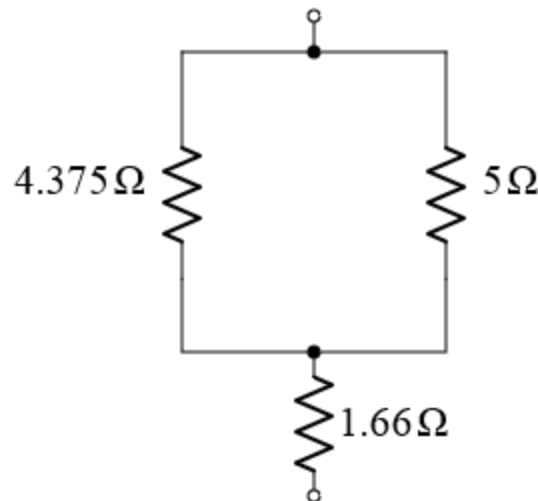- On the left branch, $3.125 + 1.25 = 4.375 \Omega$
- On the right branch, $4 + 1 = 5 \Omega$





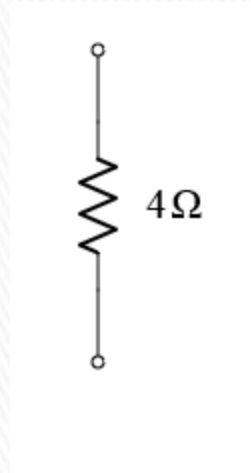- *The two parallel resistors combine as 2.33Ω .*
- *Requivalent= $2.33+1.66=4\Omega$*





THANK YOU