



SNS COLLEGE OF TECHNOLOGY
An Autonomous Institution
Coimbatore-35



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

IIYEAR/ III SEMESTER

**23ECT101 Basics of Electrical Engineering and
Instrumentation**


unit 5-MEASUREMENT SYSTEMS
BRIDGES-SCHERING'S BRIDGE



SCHERING 'S BRIDGE



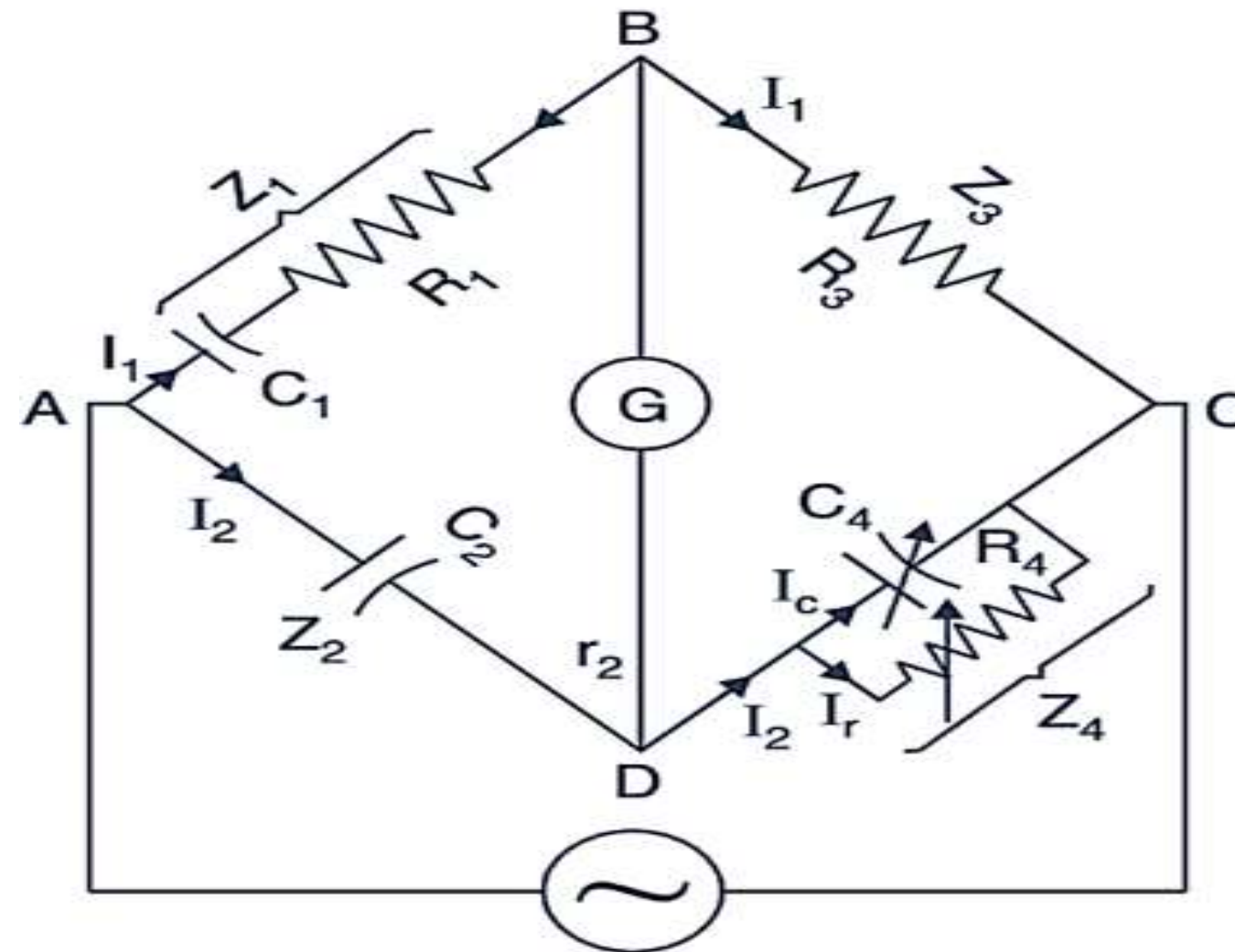A **Schering Bridge** is a bridge circuit used for measuring an unknown electrical capacitance and its dissipation factor. The dissipation factor of a capacitor is the ratio of its resistance to its capacitive reactance. The Schering Bridge is basically a four-arm alternating-current (AC) bridge circuit whose measurement depends on balancing the loads on its arms





The components of the circuit are:

C_1 = The unknown capacitor

R_1 = A series resistance representing dielectric loss in the capacitor C_1

Recall that power loss in an ideal capacitor is zero. This is the resistance contained in the capacitor, which causes power loss called dielectric loss.

R_3 = a non-inductive resistor

R_4 = a variable non-inductive resistor

C_2 = a standard capacitor, is an air capacitor and is loss free



C_4 = a variable capacitor parallel with R_4

The balance is obtained by varying R_3 (or R_4).

At balance condition:

$$Z_1 Z_4 = Z_2 Z_3$$

or

$$\left[R_1 + \frac{1}{j\omega C_1} \right] \left[\frac{R_4}{1 + j\omega C_4 R_4} \right] = \left[\frac{1}{j\omega C_2} \right] R_3$$

or

$$\left[R_1 + \frac{1}{j\omega C_1} \right] R_4 = \frac{R_3}{j\omega C_2} (1 + j\omega C_4 R_4)$$



or

$$R_1 R_4 + \frac{1}{j\omega C_1} R_4 = \frac{R_3}{j\omega C_2} + \frac{j\omega C_4 R_4 R_3}{j\omega C_2} \dots (1)$$

Since,

$$\left(\frac{1}{j} = -j \right)$$

Thus, Equation 1 written as

$$R_1 R_4 - \frac{jR_4}{\omega C_1} = -\frac{jR_3}{j\omega C_2} + \frac{C_4 R_4 R_3}{C_2}$$

Now equating real terms



$$R_1 R_4 = \frac{C_4 R_4 R_3}{C_2}$$

or

$$R_1 = \frac{R_3 C_4}{C_2}$$

Equating imaginary terms

$$-\frac{jR_4}{\omega C_1} = -\frac{jR_3}{\omega C_2}$$

or

$$C_1 = \frac{R_4 C_2}{R_3}$$

Dissipation factor (D) is given by

$$D = \omega r_1 C_1 = \omega \times \frac{R_3 C_4}{C_2} \times C_2 \frac{R_4}{R_3}$$
$$D = \omega C_4 R_4$$



ADVANTAGES

1. Balance equations are free from frequency.
2. The arrangement of the bridge is less costly as compared to the other bridges.

DRAWBACKS

There is a difficulty in obtaining balance as R_3 appears in both equations.

APPLICATIONS

Some of the applications of using Schering bridge are
Schering bridges used by generators
Used by power engines
Used in house industrial networks, etc