



# **SNS COLLEGE OF TECHNOLOGY**

## **Coimbatore-35**

### **An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with ‘A++’(III Cycle) Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **23ECB101 – CIRCUIT ANALYSIS AND DEVICES**

I YEAR/ II SEMESTER

#### **UNIT 4 – TRANSISTORS AND THEIR APPLICATIONS**



##### **TOPIC - Bipolar Junction Transistor**




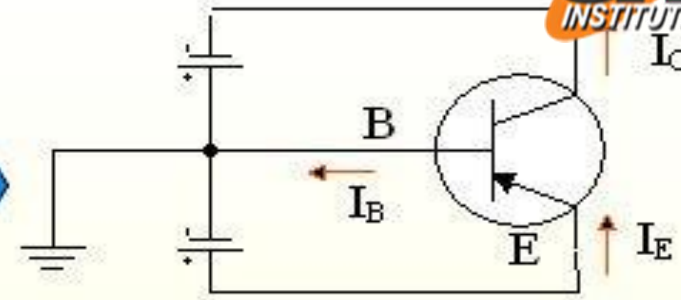
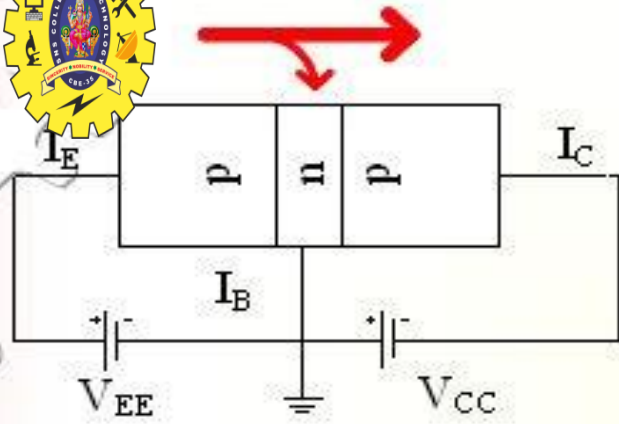
# Common-Base Configuration



- Common-base terminology is derived from the fact that the :
  - base is common to both input and output of the configuration.
  - base is usually the terminal closest to or at ground potential.
- All current directions will refer to **conventional** (hole) flow and the arrows in all electronic symbols have a direction defined by this convention.
- Note that the applied **biasing** (voltage sources) are such as to establish current in the direction indicated for each branch.



pnp

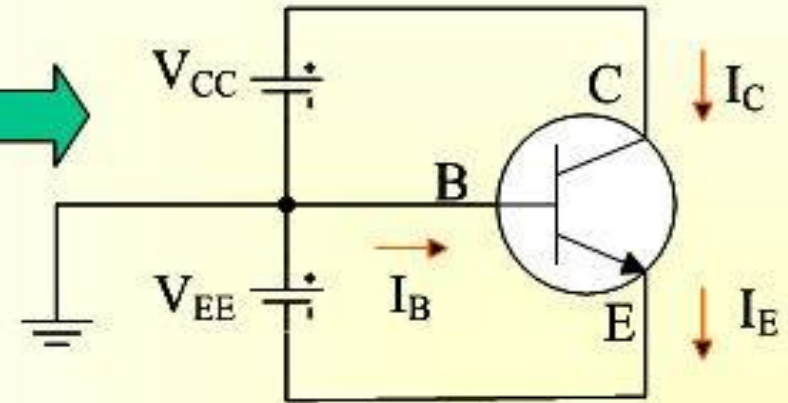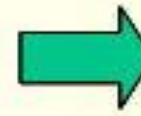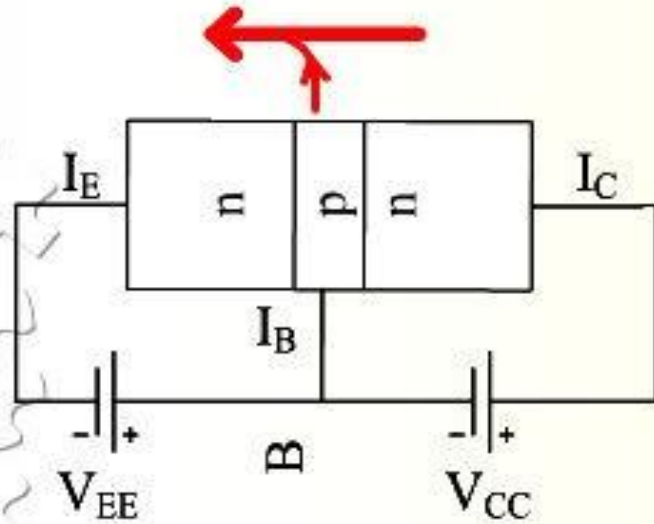

npn




To describe the behavior of common-base amplifiers requires two set of characteristics:

- Input or driving point characteristics.
- Output or collector characteristics



□ The output characteristics has 3 basic regions:

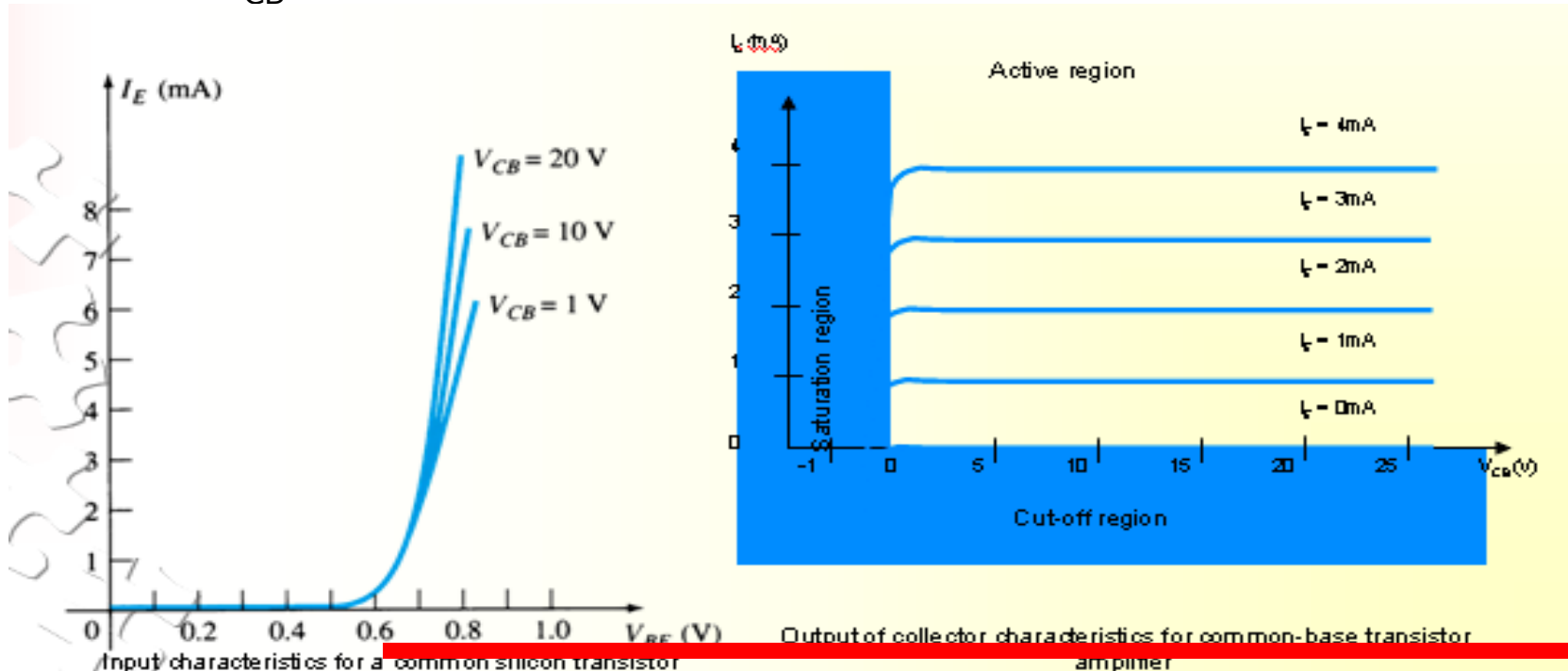- Active region – defined by the biasing arrangements
- Cutoff region – region where the collector current is 0A
- Saturation region- region of the characteristics to the left of  $V_{CB} = 0V$





<b>Active region</b>	<b>Saturation region</b>	<b>Cut-off region</b>
<ul style="list-style-type: none"><li>• <math>I_E</math> increased, <math>I_C</math> increased</li><li>• BE junction forward bias and CB junction reverse bias</li><li>• Refer to the <u>graf</u>, <math>I_C \approx I_E</math></li><li>• <math>I_C</math> not depends on <math>V_{CB}</math></li><li>• Suitable region for the transistor working as amplifier</li></ul>	<ul style="list-style-type: none"><li>• BE and CB junction is forward bias</li><li>• Small changes in <math>V_{CB}</math> will cause big different to <math>I_C</math></li><li>• The allocation for this region is to the left of <math>V_{CB} = 0</math> V.</li></ul>	<ul style="list-style-type: none"><li>• Region below the line of <math>I_E = 0</math> A</li><li>• BE and CB is reverse bias</li><li>• no current flow at collector, only leakage current</li></ul>




- The curves (output characteristics) clearly indicate that a first approximation to the relationship between  $I_E$  and  $I_C$  in the active region is given by

$$I_C \approx I_E$$

- Once a transistor is in the 'on' state, the base-emitter voltage will be assumed to be

$$V_{BE} = 0.7V$$

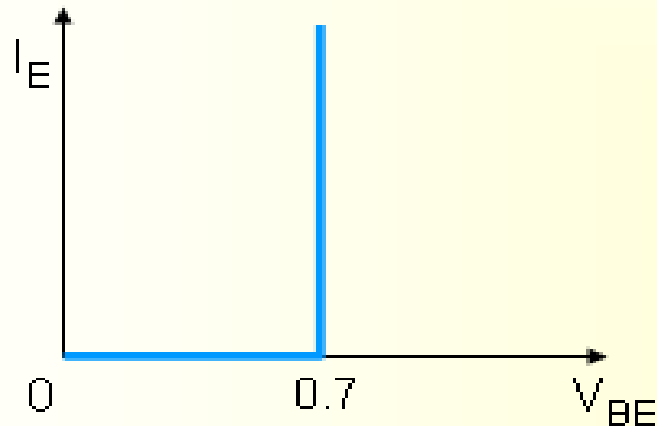



- In the dc mode the level of  $I_C$  and  $I_E$  due to the majority carriers are related by a quantity called alpha

$$\square = \frac{I_C}{I_E}$$

$$I_C = \square I_E + I_{CBO}$$

- It can then be summarized to  $I_C = \square I_E$  (ignore  $I_{CBO}$  due to small value)
- For ac situations where the point of operation moves on the characteristics curve, an ac alpha defined by



$$\square = \frac{\square I_C}{\square I_E}$$

- Alpha a common base current gain factor that shows the efficiency by calculating the current percent from current flow from emitter to collector. The value of  $\square$  is typical from  $0.9 \sim 0.998$ .


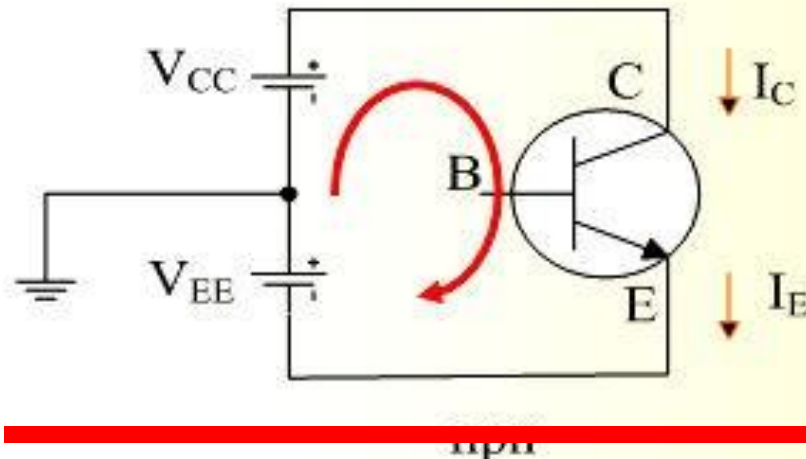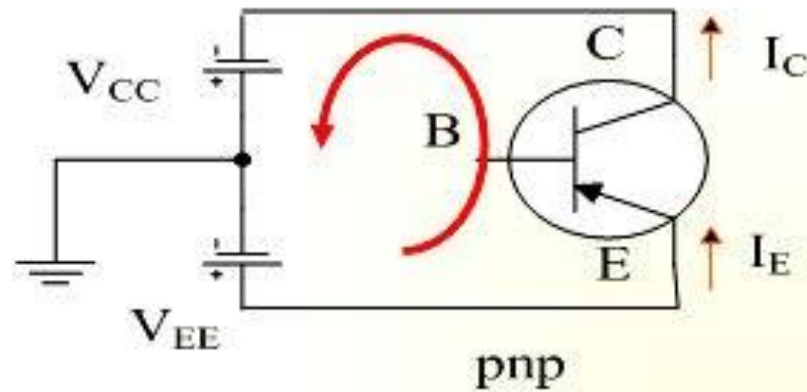
# Biassing

- Proper biasing CB configuration in active region by approximation  $I_C \approx I_E$  ( $I_B \approx 0 \mu A$ )









# Common-Emitter Configuration



- It is called common-emitter configuration since :
  - emitter is common or reference to both input and output terminals.
  - emitter is usually the terminal closest to or at ground potential.
- Almost amplifier design is using connection of CE due to the high gain for current and voltage.
- Two set of characteristics are necessary to describe the behavior for CE ;input (base terminal) and output (collector terminal) parameters.

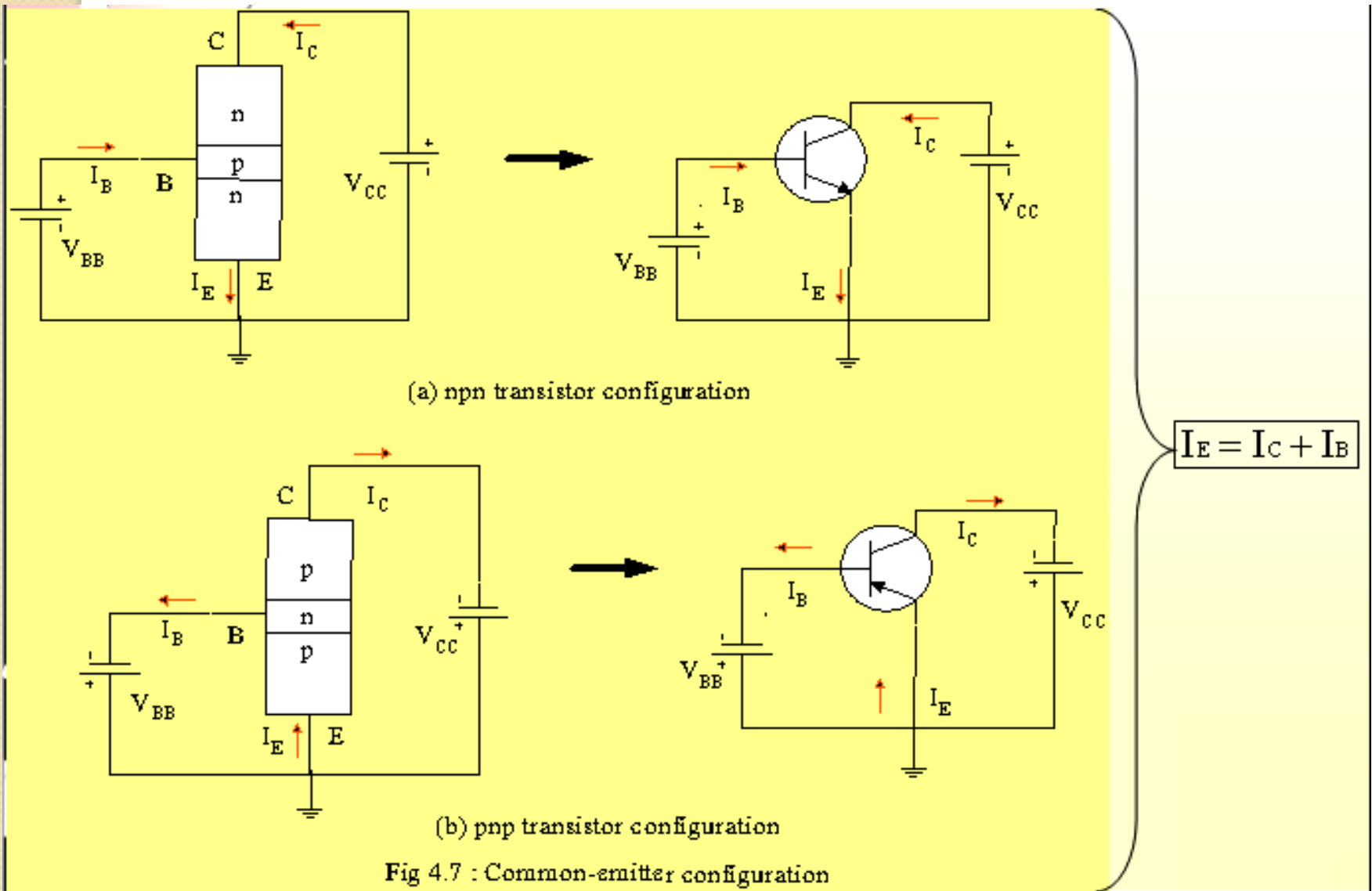
# Proper Biasing common-emitter configuration in active region



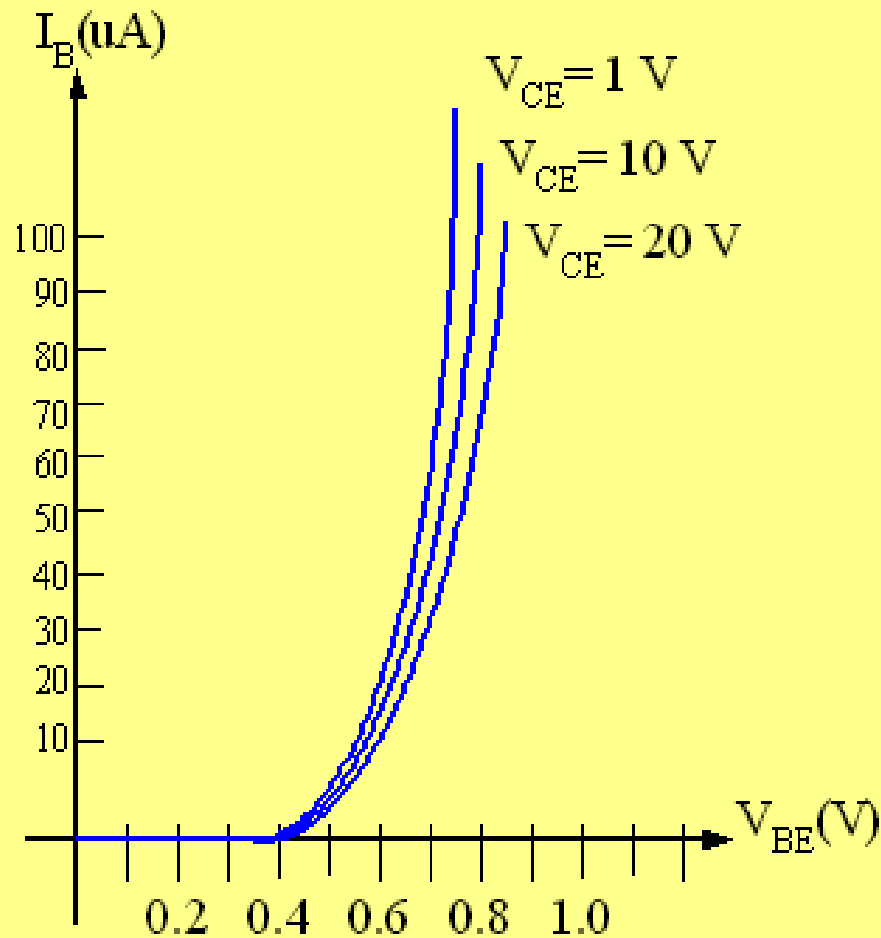

Input characteristics for a common-emitter NPN transistor

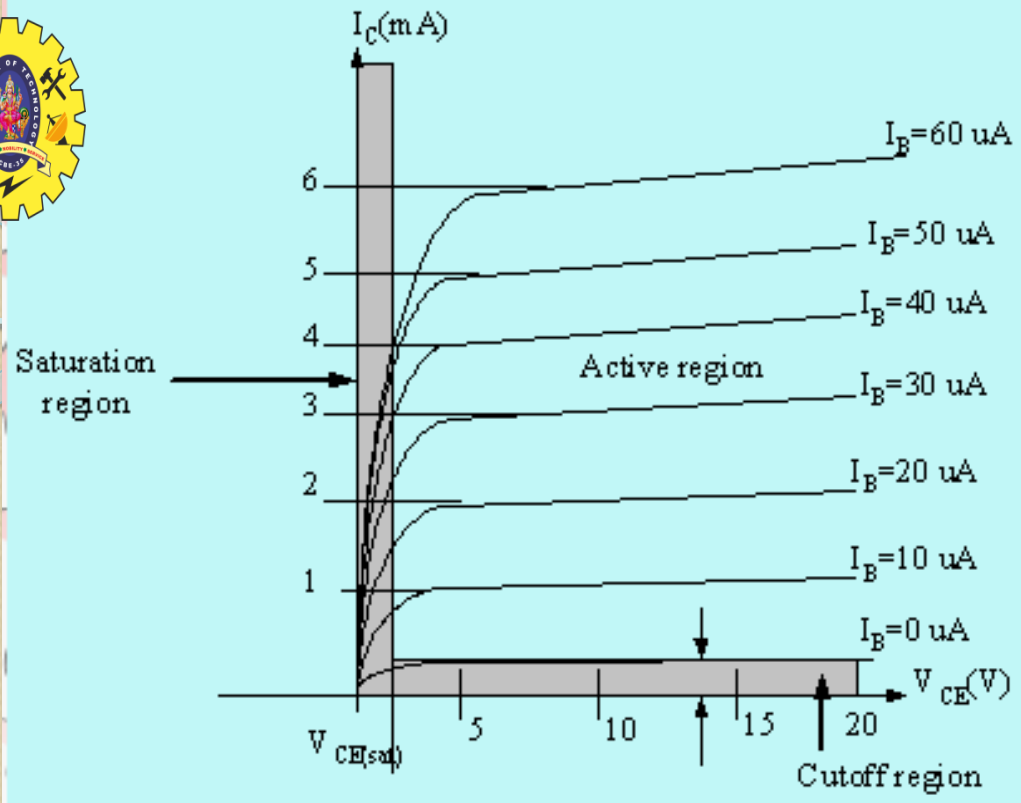- $I_B$  is microamperes compared to milliamperes of  $I_C$ .
- $I_B$  will flow when  $V_{BE} > 0.7\text{V}$  for silicon and  $0.3\text{V}$  for germanium
- Before this value  $I_B$  is very small and no  $I_B$ .
- Base-emitter junction is forward bias
- Increasing  $V_{CE}$  will reduce  $I_B$  for different values.





Output characteristics for a common-emitter npn transistor

- For small  $V_{CE}$  ( $V_{CE} < V_{CESAT}$ ),  $I_C$  increase linearly with increasing of  $V_{CE}$
- $V_{CE} > V_{CESAT}$   $I_C$  not totally depends on  $V_{CE}$  □ constant  $I_C$
- $I_B$  ( $\mu A$ ) is very small compare to  $I_C$  (mA). Small increase in  $I_B$  cause big increase in  $I_C$
- $I_B = 0 A$  □  $I_{CEO}$  occur.
- Noticing the value when  $I_C = 0A$ . There is still some value of current flows.



Active region	Saturation region	Cut-off region
<p>B-E junction is forward bias</p> <ul style="list-style-type: none"><li>• C-B junction is reverse bias</li><li>• can be employed for voltage, current and power amplification</li></ul>	<ul style="list-style-type: none"><li>• B-E and C-B junction is forward bias, thus the values of <math>I_B</math> and <math>I_C</math> is too big.</li><li>• The value of <math>V_{CE}</math> is so small.</li><li>• Suitable region when the transistor as a logic switch.</li><li>• NOT and avoid this region when the transistor as an amplifier.</li></ul>	<ul style="list-style-type: none"><li>• region below <math>I_{CE0}</math> is to be avoided if an undistorted o/p signal is required</li><li>• B-E junction and C-B junction is reverse bias</li><li>• <math>I_B=0</math>, <math>I_C</math> not zero, during this condition <math>I_C=I_{CE0}</math> where is this current flow when B-E is reverse bias.</li></ul>

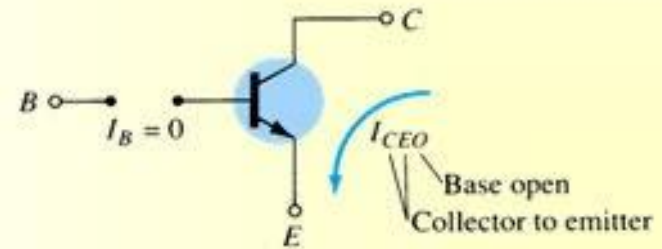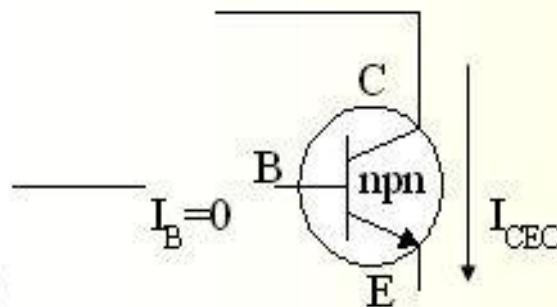




# Beta ( $\beta$ ) or amplification factor



The ratio of dc collector current ( $I_C$ ) to the dc base current ( $I_B$ ) is dc beta ( $\beta_{dc}$ ) which is dc current gain where  $I_C$  and  $I_B$  are determined at a particular operating point, Q-point (quiescent point).

It's define by the following equation:

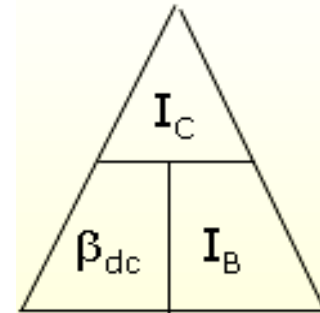
$$30 < \beta_{dc} < 300 \quad \square \quad 2N3904$$



On data sheet,  $\beta_{dc} = h_{FE}$  with  $h$  is derived from ac hybrid equivalent cct. FE are derived from forward-current amplification and common-emitter configuration respectively.



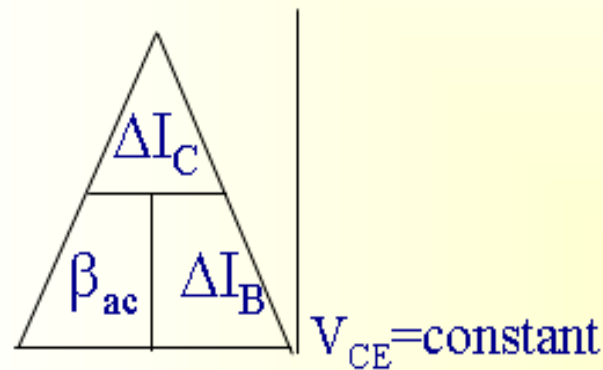
- For ac conditions an ac beta has been defined as the ratio of changes of collector current ( $I_C$ ) compared to the changes of base current ( $I_B$ ) where  $I_C$  and  $I_B$  are determined at operating point.
- On data sheet,  $\beta_{ac} = h_{fe}$
- It can be defined by the following equation:



# Common-Base

Although the Common-Base configuration is not the most common biasing type, it is often helpful in the understanding of how the BJT works.


Emitter - Current Curves

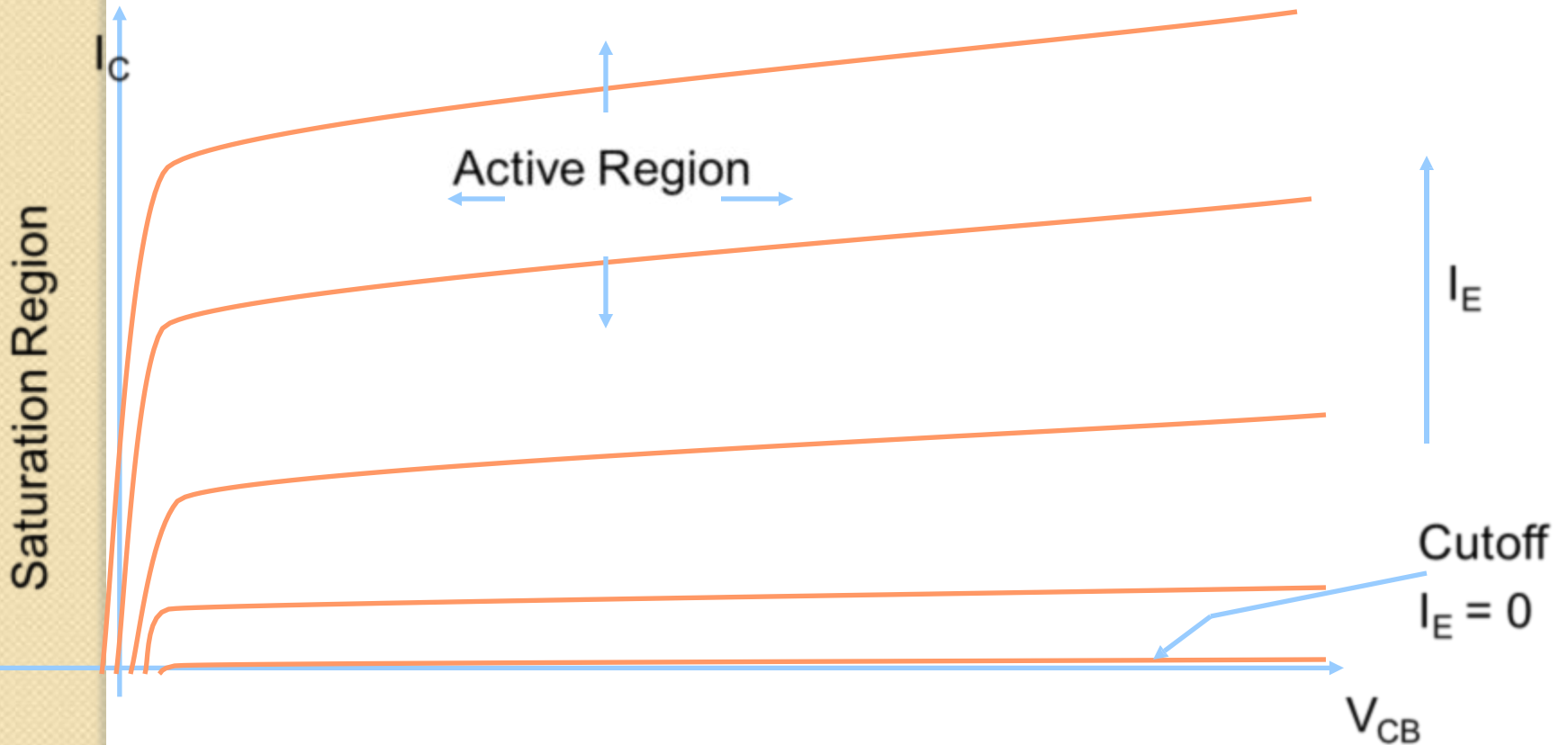



# Common-Base

Circuit Diagram: NPN Transistor

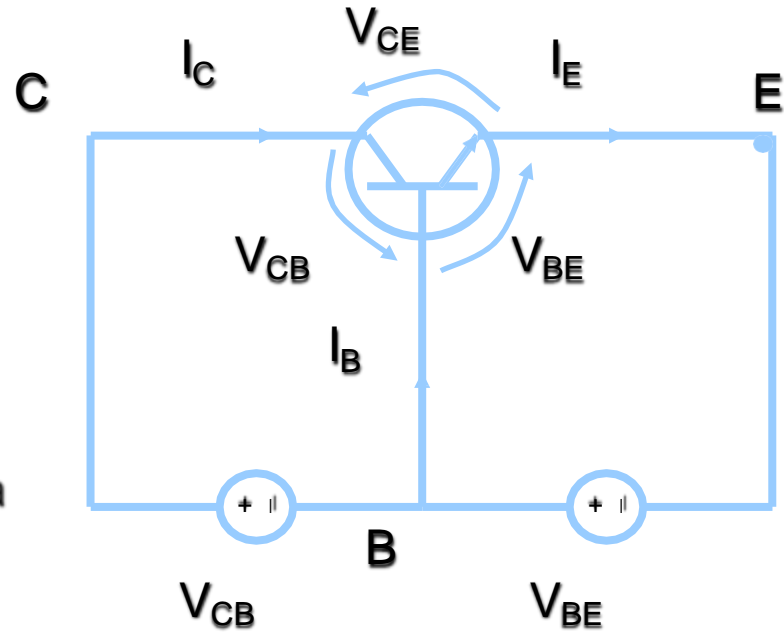


The Table Below lists assumptions that can be made for the attributes of the common-base biased circuit in the different regions of operation. Given for a Silicon NPN transistor.

Region of Operation	$I_C$	$V_{CE}$	$V_{BE}$	$V_{CB}$	C-B Bias	E-B Bias
Active	$\beta I_B$	$=V_{BE} + V_{CE}$	$\sim 0.7V$	$0V$	Rev.	Fwd.
Saturation	Max	$\sim 0V$	$\sim 0.7V$	$-0.7V < V_{CE} < 0$	Fwd.	Fwd.
Cutoff	$\sim 0$	$=V_{BE} + V_{CE}$	$0V$	$0V$	Rev.	None /Rev.

# Common-Collector


The Common-Collector biasing circuit is basically equivalent to the common-emitter biased circuit except instead of looking at  $I_C$  as a function of  $V_{CE}$  and  $I_B$  we are looking at  $I_E$ . Also, since  $\alpha \sim 1$ , and  $\alpha = I_C/I_E$  that means  $I_C \sim I_E$

Emitter-Current Curves

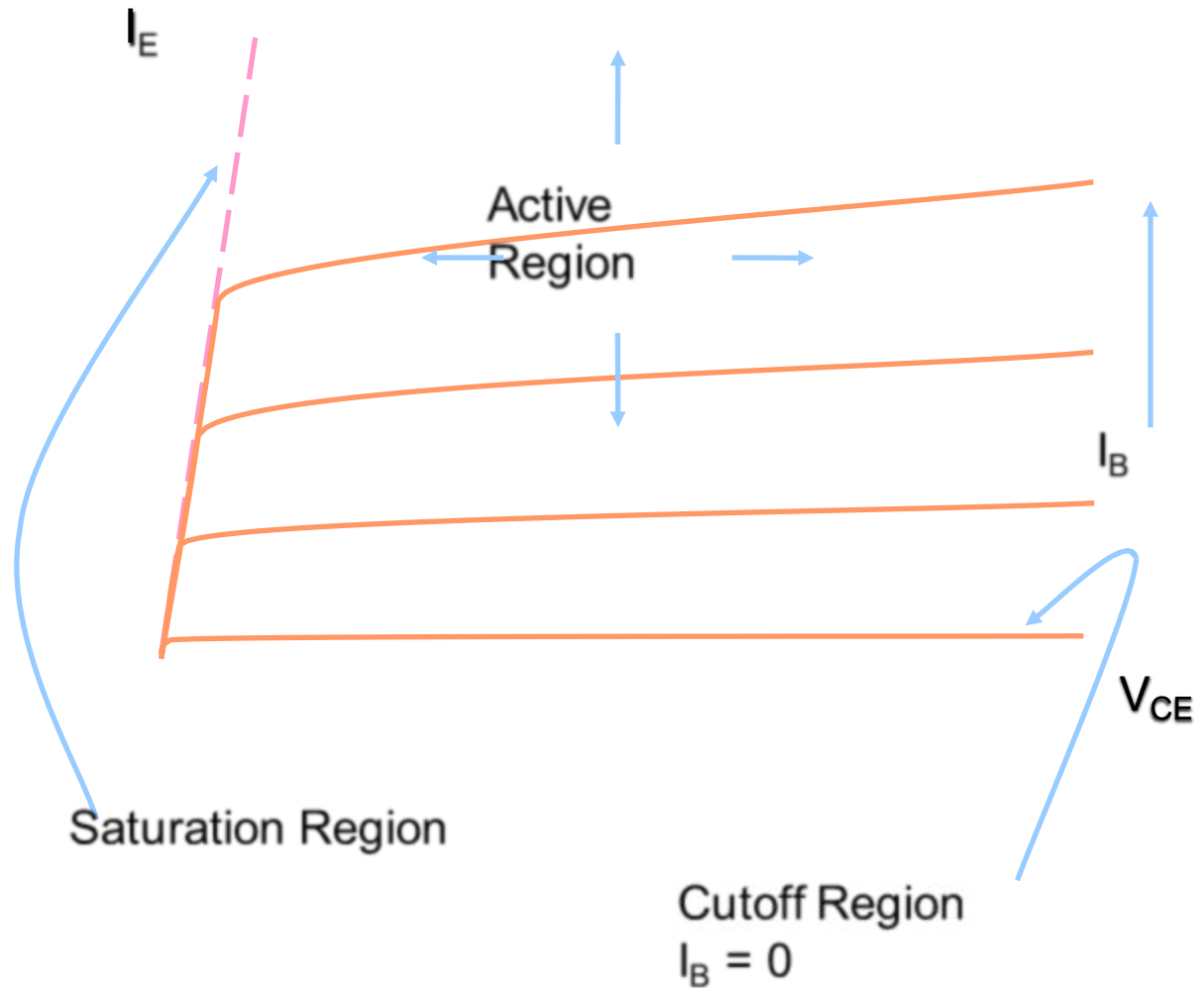


# Common-Emitter

Circuit Diagram

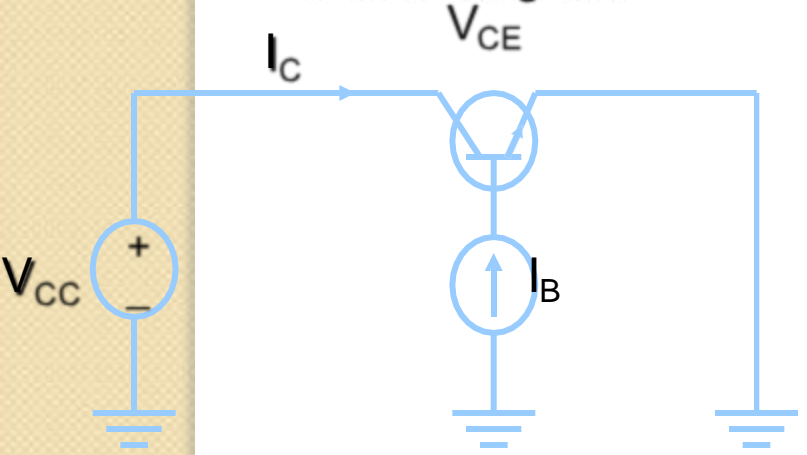

Collector-Current Curves

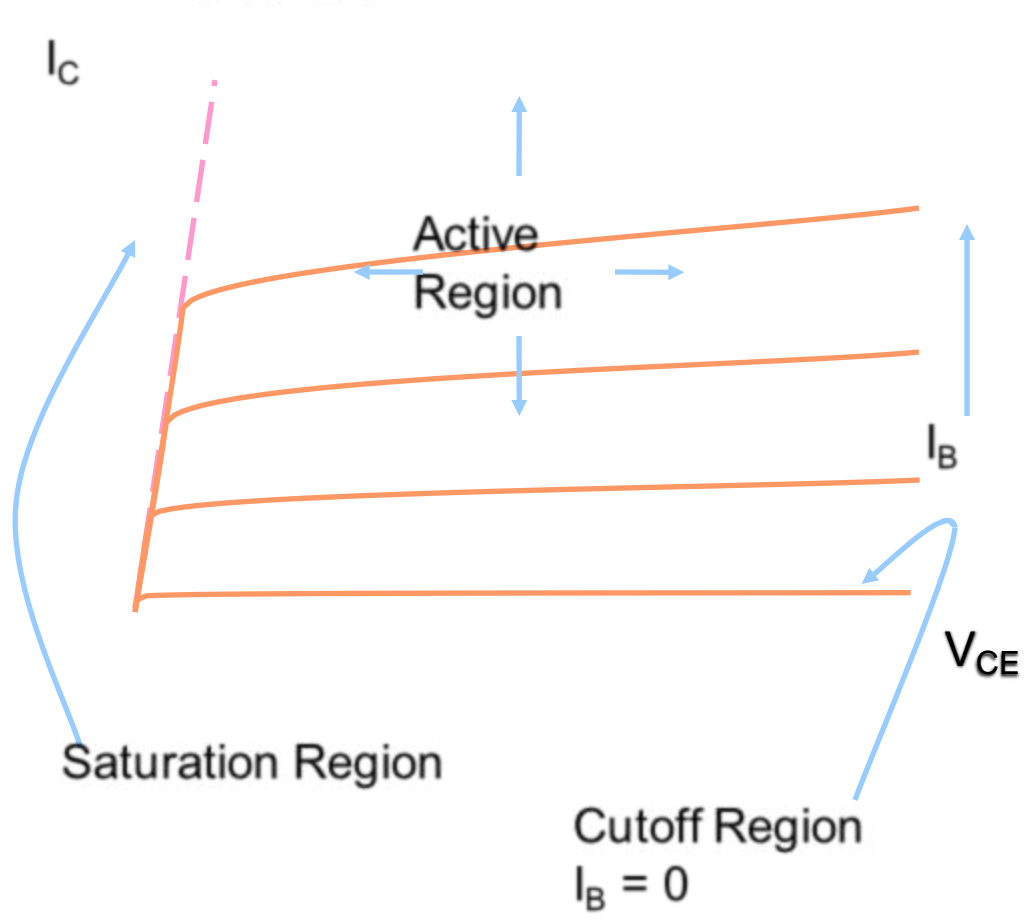

**Region of Operation**

**Active**

**Saturation**

**Cutoff**

**Description**

Small base current controls a large collector current

$V_{CE(sat)} \sim 0.2V$ ,  $V_{CE}$  increases with  $I_C$

Achieved by reducing  $I_B$  to 0, Ideally,  $I_C$  will also equal 0.



# Three Types of BJT Biasing



Biassing the transistor refers to applying voltage to get the transistor to achieve certain operating conditions.

Common-Base Biasing (CB) :      input =  $V_{EB}$  &  $I_E$   
output =  $V_{CB}$  &  $I_C$

Common-Emitter Biasing (CE):      input =  $V_{BE}$  &  $I_B$   
output =  $V_{CE}$  &  $I_C$

Common-Collector Biasing (CC): input =  $V_{BC}$  &  $I_B$   
output =  $V_{EC}$  &  $I_E$



# Configurations of Transistors Summary

**Transistor Configuration Summary Table**

Transistor Configuration	Common Base	Common Collector (Emitter Follower)	Common Emitter
Voltage Gain	High	Low	Medium
Current Gain	Low	High	Medium
Power Gain	Low	Medium	High
Input / Output Phase Relationship	0°	0°	180°
Input Resistance	Low	High	Medium
Output Resistance	High	Low	Medium

