



# **SNS COLLEGE OF TECHNOLOGY**

Kurumbapalayam (Po), Coimbatore – 641 107

**An Autonomous Institution**

Accredited by NBA – AICTE and Accredited by NAAC – UGC with ‘A’ Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



## **DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING**

**COURSE NAME : 23EET014-ANALOG ELECTRONIC CIRCUITS**

**I YEAR /II SEMESTER**

**Unit 4- OSCILLATORS & MULTIVIBRATOR CIRCUITS**

**Topic 3 : Astable multivibrator**





# Multivibrators




- Multivibrators are two-stage switching circuits in which the output of the first stage is fed to the input of the second stage and vice-versa.
- The outputs of two stages are complementary.
- Multivibrators are of three types, namely,
  - (i) Astable multivibrator,
  - (ii) Bistable multivibrator, and
  - (iii) Monostable multivibrator.


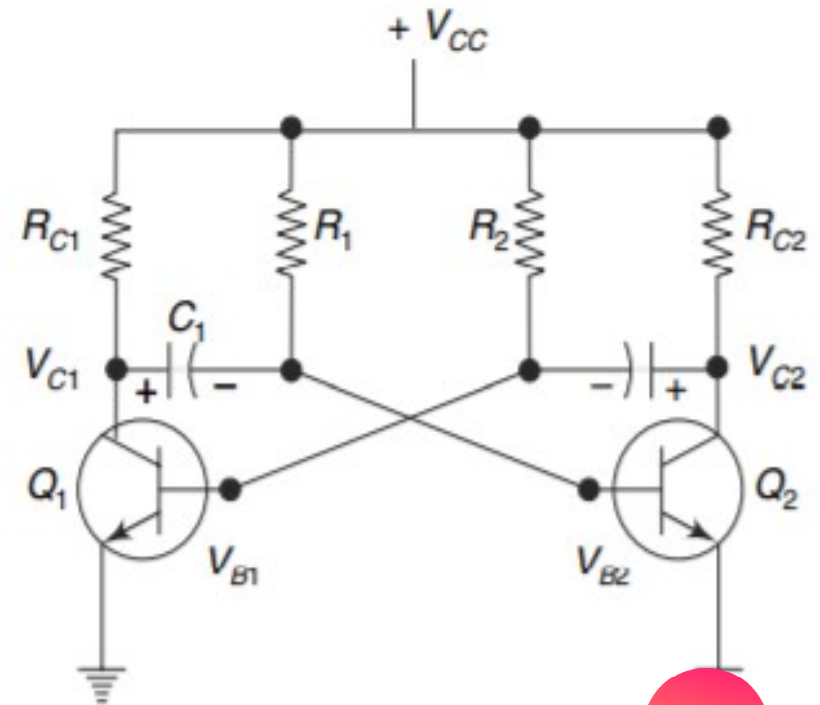
# Collector Coupled Astable Multivibrator


- The astable or free running multivibrator generates square wave without any external triggering pulse.
- It has no stable states, i.e. it has two quasi stable states.




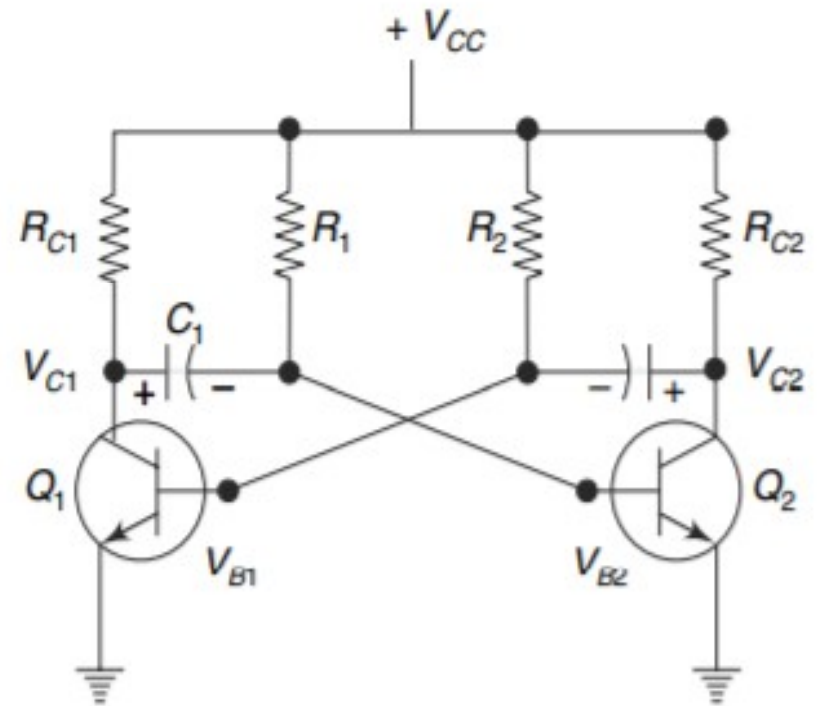
## Collector Coupled Astable Multivibrator

- It switches back and forth from one state to the other, remaining in each state for a time depending upon the discharging of a capacitive circuit.





## Working of Astable Multivibrator



- When the supply voltage  $+V_{CC}$  is applied, one transistor will conduct more than the other due to some circuit imbalance.
- Initially, let us assume that Q1 is conducting and Q2 is cut-off.
- Then  $V_{C1}$ , the output of Q1 is equal to  $V_{CE(sat)}$ , i.e. approximately zero volt and  $V_{C2} = +V_{CC}$ .
- At this instant, C1 charges exponentially with a time constant  $R_1C_1$  towards the supply voltage through R1 and correspondingly  $V_{B2}$  also increases exponentially towards  $V_{CC}$ .





## Working of Astable Multivibrator



- When  $V_{B2}$  crosses the cut-in voltage,  $Q2$  starts conducting and  $V_{C2}$  falls to  $V_{CE(sat)}$ .
- Also,  $V_{B1}$  falls due to capacitive coupling between collector of  $Q2$  and base of  $Q1$ , thereby driving  $Q1$ , into OFF state.
- Now, the rise in voltage  $V_{C1}$  is coupled through  $C1$  to the base of  $Q2$ , causing a small overshoot in voltage  $V_{B2}$ .
- Thus  $Q1$  is OFF and  $Q2$  is ON.
- At this instant, the voltage levels are:  $V_{B1}$  is negative,  $V_{C1} = V_{CC}$ ,  $V_{B2} = V_{BE(sat)}$  and  $V_{C2} = V_{CE(sat)}$ .





## Working of Astable Multivibrator



- When Q1 is OFF and Q2 is ON, the voltage  $V_{B1}$  increases exponentially with a time constant  $R_2C_2$  towards  $V_{CC}$ .
- Therefore, Q1 is driven into saturation and Q2 is cut-off.
- Now, the voltage levels are:  $V_{B1} = V_{BE(sat)}$ ,  $V_{C1} = V_{CE(sat)}$ ,  $V_{B2}$  is negative and  $V_{C2} = V_{CC}$ .





## Working of Astable Multivibrator



- It is clear that when Q2 is ON, the falling voltage VC2 permits the discharging of the capacitor C2 which drives Q1 into cut-off.
- The rising voltage of VC1 feeds back to the base of Q2 tending to turn it ON.
- This process is said to be regenerative.







## Time Period Calculation

ON time for  $Q_2$  is  $T_2 = 0.693 R_2 C_2$

ON time  $T_1$  for  $Q_1$  can be expressed as  $T_1 = 0.693 R_1 C_1$

Therefore, the total period of the waveform is

$$T = T_1 + T_2 = 0.69 (R_1 C_1 + R_2 C_2)$$

If  $R_1 = R_2 = R$  and  $C_1 = C_2 = C$ , we have a symmetrical multivibrator, with outputs at the two collectors having the same waveforms but out of phase with each other.

Therefore,  $T = 1.386 RC$  and  $f = \frac{1}{T} = \frac{1}{1.386 RC}$



# Applications of Astable Multivibrator

- The astable multivibrator is used as square wave generator, voltage to frequency convertor and in pulse synchronisation, as clock for binary logic signals, and so on.
- Since it produces square waves, it is a source of production of harmonic frequencies of higher order.
- It is used in the construction of digital voltmeter and SMPS.
- It can be operated as an oscillator over a wide range of audio and radio frequencies.



# References



Electronic Devices and Circuits By Salivahanan

# Thank You

