


Reg.No:

--	--	--	--	--	--	--	--



SNS College of Technology, Coimbatore-35.
(Autonomous)

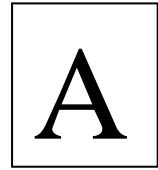B.E/B.Tech- Internal Assessment -I
Academic Year 2023-2024 (Even)



Second Semester

Electrical and Electronics Engineering

23EET102- ELECTRIC CIRCUIT ANALYSIS

Time: 1 ½ Hours

Maximum Marks: 50


Answer All Questions

PART - A (5x 2 = 10 Marks)

- | | | |
|--|-----|-----|
| 1. State Ohm's law. | CO1 | REM |
| 2. An Electric iron is rated 1000W, 240V. Find the current drawn & resistance of the heating element. | CO1 | REM |
| 3. Write down the expression of equivalent resistance for 'n' – number of resistors in series connection | CO1 | UND |
| 4. Distinguish between a Loop & Mesh of a circuit analysis. | CO1 | UND |
| 5. State Kirchoff's Current law | CO2 | REM |

PART - B (13+13+14 = 40 Marks)

- | | | | |
|--|----|-----|-----|
| 6. (a) Define i) charge ii) electric current iii) power iv) network & v) circuit | 13 | CO1 | APP |
| (OR) | | | |
| 6. (b) Derive the expression for Delta connected resistances in terms of Star connected resistances? | 13 | CO1 | UND |
| 7. (a) What are the types of sources? Explain them with suitable diagrams and Characteristics?. | 13 | CO1 | APP |
| (OR) | | | |
| 7. (b) Find the equivalent resistance between A & B in the given network | 13 | CO2 | APP |

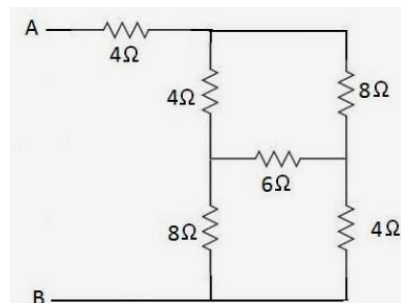

8. (a) Calculate the instantaneous value, peak value, average value, effective value of Indian standard single phase AC power supply with Waveforms 14 CO1 APP
- (OR)
8. (b) Provide a real-time classroom connected load example to illustrate the differences between KCL and KVL. 14 CO2 APP

Abbreviations:- REM-Remembering, UND-Understanding, APP-Appling, ANA-Analyzing, EVA-Evaluating, CRE-Creating

Reg.No:

--	--	--	--	--	--	--



SNS College of Technology, Coimbatore-35.
(Autonomous)

B.E/B.Tech- Internal Assessment -I
Academic Year 2023-2024 (Even)

B

Second Semester

Electrical and Electronics Engineering
23EET102- ELECTRIC CIRCUIT ANALYSIS

Time: 1 ½ Hours

Maximum Marks: 50


Answer All Questions

PART - A (5x 2 = 10 Marks)


1. Write down the expression of equivalent resistance for 'n'- number of resistors in parallel connection. CO1 REM
2. State Kirchoff's Voltage law CO1 REM
3. List the Difference Between Star and Delta Connection. CO1 UND
4. Identify the limitations of Ohms law. CO1 UND
5. Distinguish between network & circuit. CO2 REM

PART - B (13+13+14 = 40 Marks)

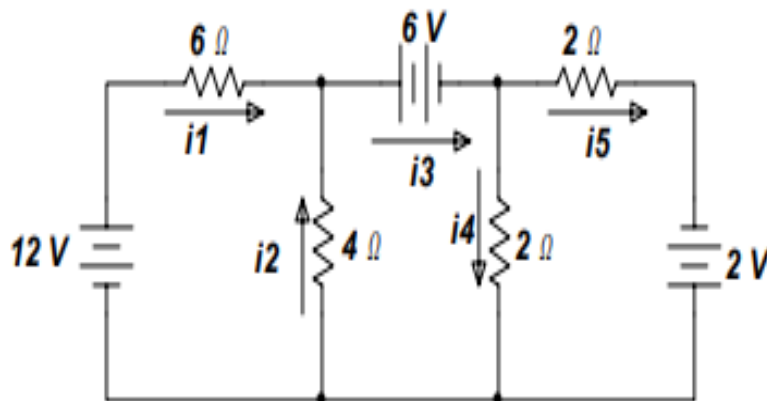6. (a) Define i) Waveforms ii) instantaneous value iii) peak value
iv) average value v) effective value. 13 CO1 APP
(OR)
6. (b) Find the current value flowing each resistor and also the find the voltage drops across 4-ohm resistor by using mesh or nodal analysis. 13 CO1 APP



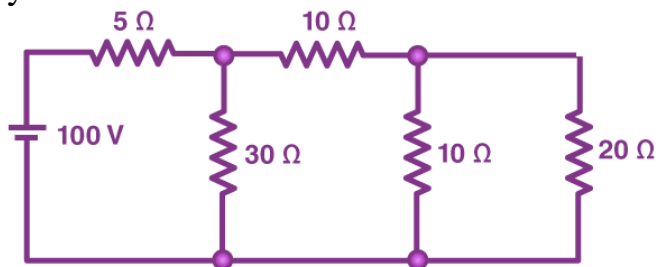7. (a) Determine the voltage at each node of the given circuit using nodal analysis. 13 CO1 APP




(OR)

7. (b) Utilizing voltage and current division rules and a real-time example, conclude by discussing network reduction approaches. 13 CO2 APP

8. (a) Derive the expression for Delta to Star transformation with proper example 14 CO2 UND

(OR)

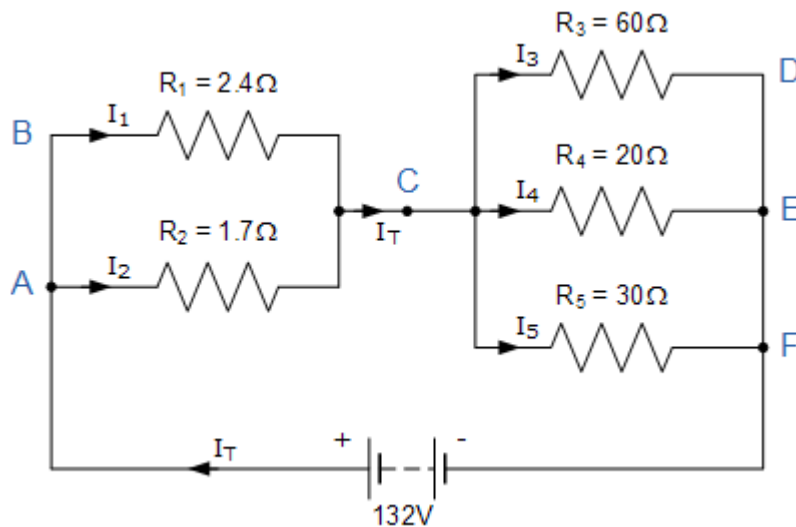8. (b) Find the Kirchhoff's Current Law Equivalent Circuit for the below network. 14 CO2 APP



Abbreviations:- **REM**-Remembering, **UND**-Understanding, **APP**-Applying, **ANA**-Analyzing, **EVA**-Evaluating, **CRE**-Creating