

Reg.No:

--	--	--	--	--	--	--	--



SNS College of Technology, Coimbatore-35.
(Autonomous)

B.E/B.Tech- Internal Assessment -II

Academic Year 2023-2024 (Even)

Second Semester

Electrical and Electronics Engineering

23EET102- ELECTRIC CIRCUIT ANALYSIS



Time: 1 ½ Hours

Maximum Marks: 50


Answer All Questions

PART - A (5x 2 = 10 Marks)

- | | | |
|---|-----|-----|
| 1. List the advantages of Maximum power transfer theorem. | CO2 | REM |
| 2. What is the difference between Thevenin and superposition theorem? | CO2 | REM |
| 3. Derive the maximum power Transfer theorem equation. | CO3 | UND |
| 4. Distinguish between RL & RC circuit analysis. | CO3 | APP |
| 5. Sketch the phasor diagrams of three phase four wire system. | CO3 | UND |


PART - B (13+13+14 = 40 Marks)

- | | | | |
|--|----|-----|-----|
| 6. (a) Obtain Thevenin's equivalent circuit with respect to the terminals of AB of the network shown in the circuit, also How to Apply Thevenin's Theorem? | 13 | CO2 | APP |
|--|----|-----|-----|

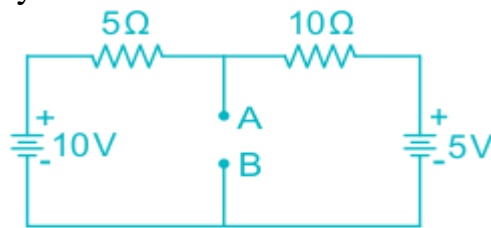


(OR)

- | | | | |
|---|----|-----|-----|
| 6. (b) Find the current through 9Ω resistor of the network shown in figure by using Norton's Theorem. | 13 | CO2 | APP |
|---|----|-----|-----|

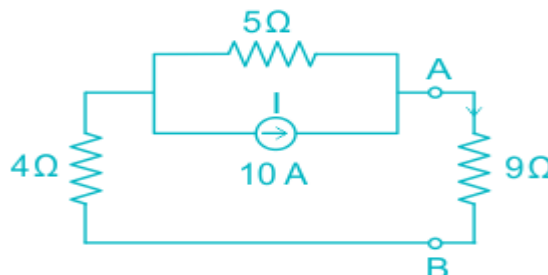


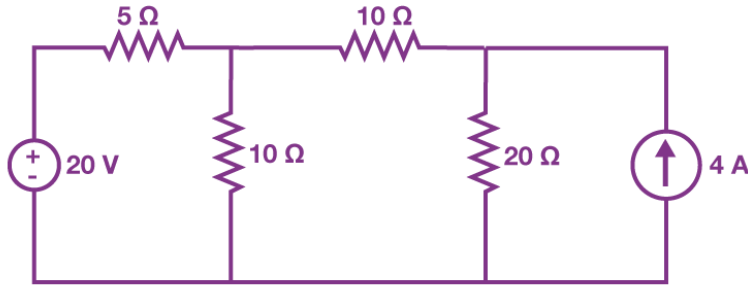7. (a) Find the current flowing through $20\ \Omega$ using the superposition theorem. 13 CO3 APP theorem.



(OR)

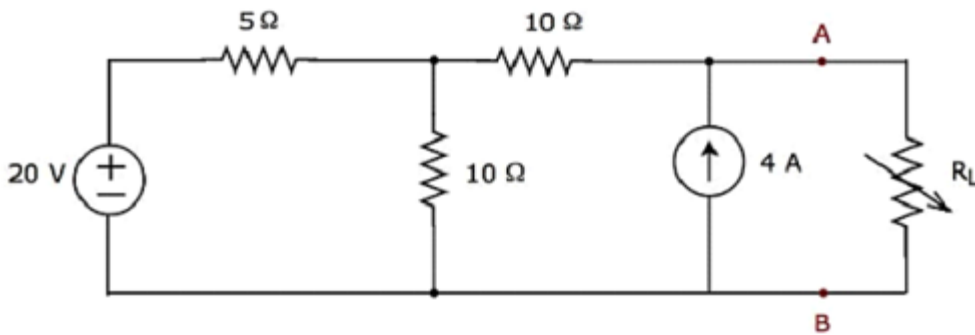7. (b) Find the maximum power that can be delivered to the load resistor R_L of the circuit shown in the following figure. 13 CO3 APP



8. (a) Find the reasons with proper explanation of three phase 3-wire and 4-wire circuits with unbalanced loads used in real time. 14 CO2 APP

(OR)

8. (b) Provide a phasor diagrams of classroom connected load example to illustrate the differences between Phase and line values. 14 CO3 APP

Abbreviations:- REM-Remembering, UND-Understanding, APP-Appling, ANA-Analyzing, EVA-Evaluating, CRE-Creating

Reg.No:

--	--	--	--	--	--	--	--



SNS College of Technology, Coimbatore-35.
(Autonomous)

B.E/B.Tech- Internal Assessment -II

Academic Year 2023-2024 (Even)

Second Semester

Electrical and Electronics Engineering

23EET102- ELECTRIC CIRCUIT ANALYSIS

B

Time: 1 ½ Hours

Maximum Marks: 50


Answer All Questions

PART - A (5x 2 = 10 Marks)

- | | | |
|---|-----|-----|
| 1. List the advantages of Superposition Theorem. | CO2 | REM |
| 2. What is the duality between Thevenin and Norton theorem? | CO2 | REM |
| 3. List the Difference Between Star and Delta Connection. | CO3 | UND |
| 4. Identify the usage of Reactive Power in Loads. | CO3 | UND |
| 5. Distinguish between Phase and line values of three phase circuits. | CO3 | REM |


PART - B (13+13+14 = 40 Marks)

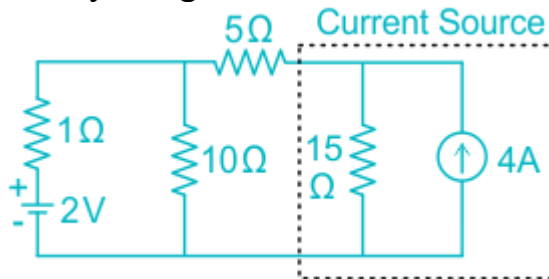6. (a) Find the current flowing through 5Ω resistor of the circuit shown here. By using Thevenin's Theorem. 13 CO2 APP




(OR)

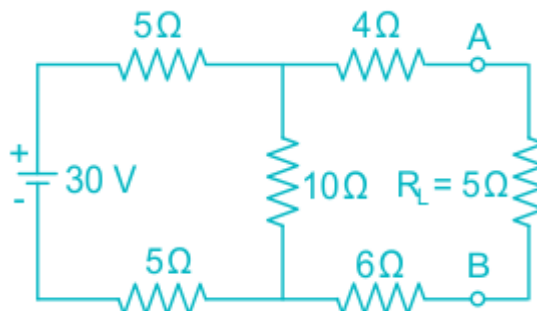6. (b) In the network shown in figure, calculate the current through the load resistor R_L by using Norton's Theorem. 13 CO2 APP




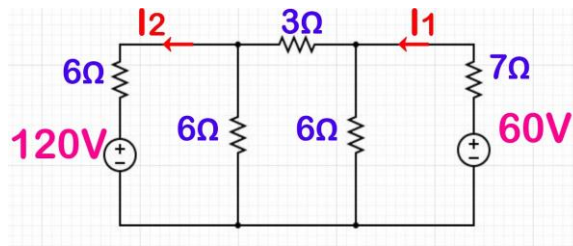7. (a) Find the current flowing through $3\ \Omega$ using the superposition theorem. 13 CO3 APP theorem.



(OR)

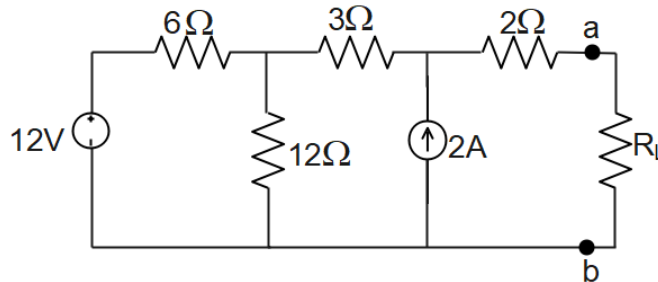7. (b) Find the value of R_L for maximum power transfer in the circuit and find the maximum power. 13 CO3 APP



8. (a) Derive the expression for Power factor calculations with Real time example by using your residential loads, 14 CO2 APP

(OR)

8. (b) Find the reasons with proper explanation of three phase 3-wire and 4-wire circuits with balanced loads used in real time. 14 CO3 APP

Abbreviations:- REM-Remembering, UND-Understanding, APP-Aplying, ANA-Analyzing, EVA-Evaluating, CRE-Creating