

Circuit Puzzles

Predict whether each circuit will light all the LEDs. Then build the circuits. If the circuit doesn't work make changes! Add or remove copper tape. Add more or different LEDs.

LEDs have a positive and negative lead (wire). Typically the longer lead is positive and the shorter lead is negative, check each LED before placing it in your circuit. In this activity the picture shows the tightly wound lead as positive, and the loosely wound lead as negative.



1.) Will all three LEDs light?

2.) Will all three LEDs light?

3.) Will all three LEDs light?

4.) Will all four LEDs light?

Predict:

Predict:

Predict:

Predict:

ALL? TWO? ONE? NONE?

ALL? TWO? ONE? NONE?

ALL? TWO? ONE? NONE?





ALL? THREE? TWO? ONE? NONE?

What actually happens?

What actually happens?

What actually happens?

What actually happens?

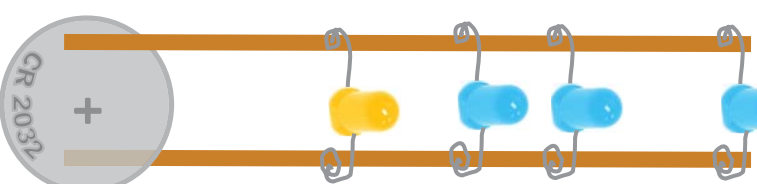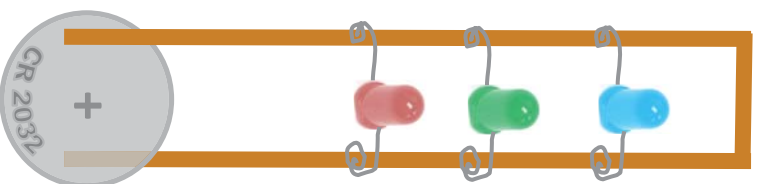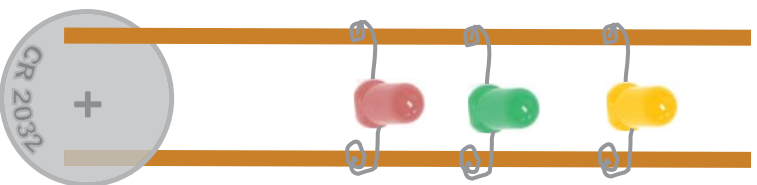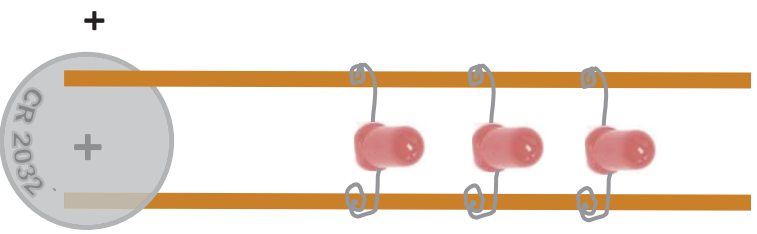


Will all four LEDs light?

Predict:

ALL? THREE? TWO? ONE? NONE?

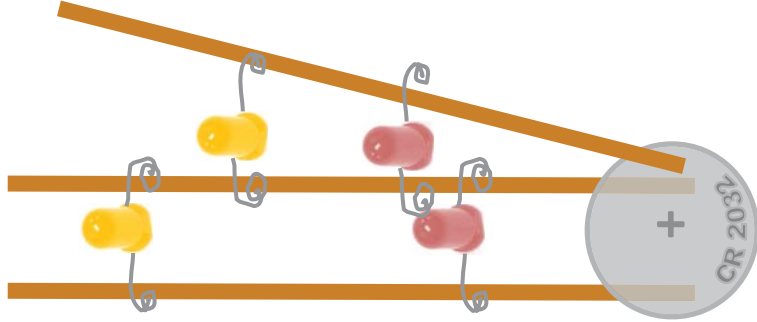What actually happens? Add two more LEDs so all six light.




6.) Will all three LEDs light?

Predict:

ALL? TWO? ONE? NONE?

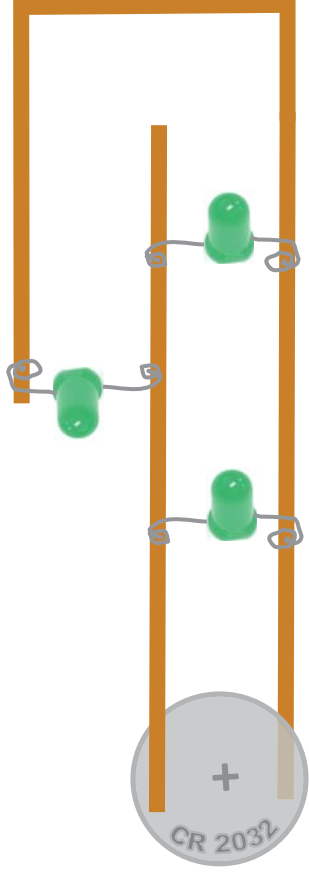What actually happens? Add three more LEDs so all six light.



7.) Place four LEDs so that they all light.

Use at least two different colors


8.) Will all five LEDs light?

Predict:

ALL? SOME? NONE?

What actually happens?

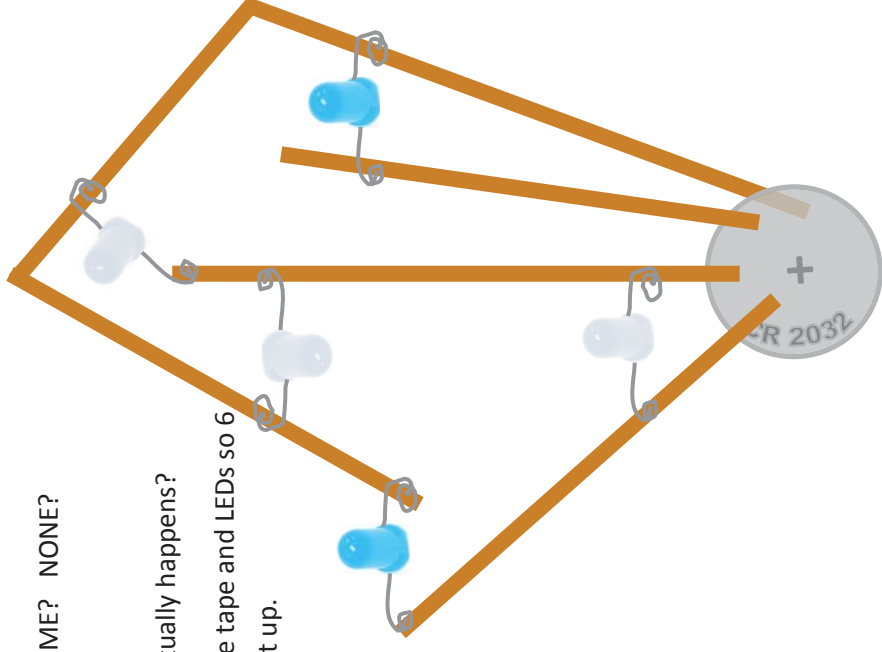Add more tape and LEDs so 6 LEDs light up.



9.) Design a circuit that will light the five corners of the star and use LEDs of at least two different colors.

