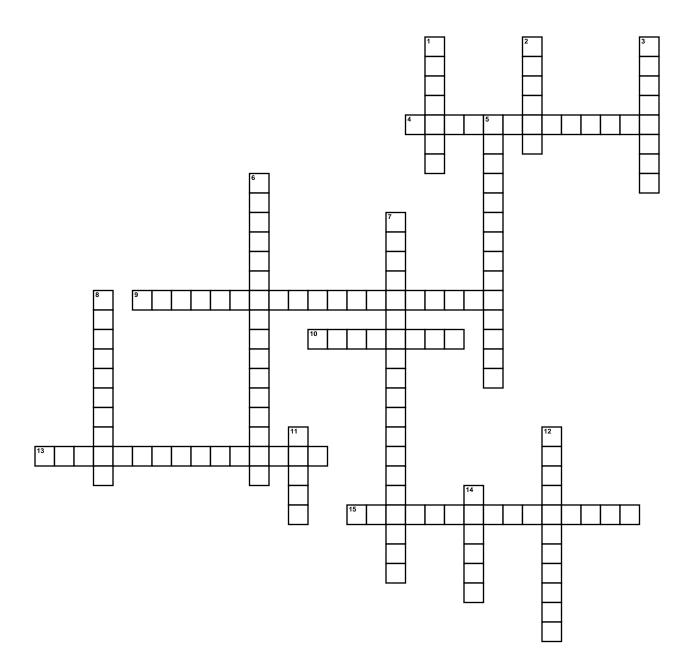
## **Electric Circuit - Series and Parallel**



## Across

- [4] There is one path for the charge to follow
- [9] It's supplied from the battery
- [10] The charge of the smaller side of the battery
- [13] A pathway for charges to flow
- [15] There is more than one path for the charge to follow

## Down

- [1] A component of a circuit
- [2] It allows the current to flow if it is closed
- [3] The charge of the longer side of the battery
- [5] A component of a circuit
- [6] It converts electrical energy in other forms of energy
- [7] It flows from positive side to negative side of the battery
- [8] It represents an electric device
- [11] A kind of an electrical device
- [12] A component of a circuit
- [14] A kind of an electrical device

## Solution

