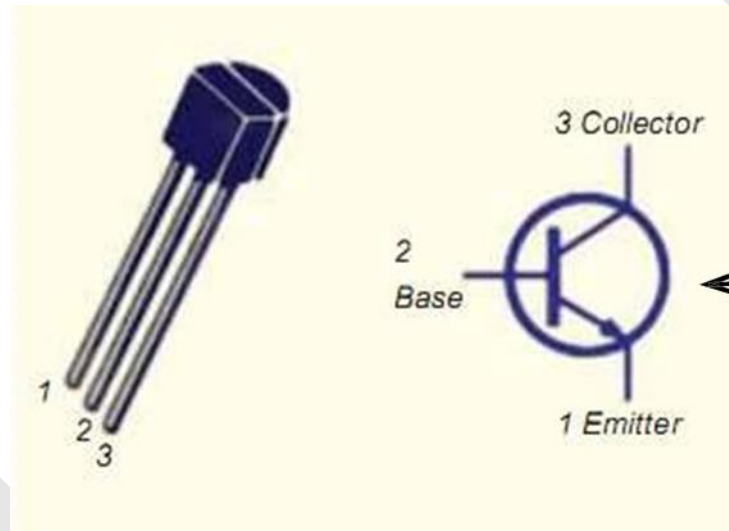




# UNIT IV



## BIPOLAR JUNCTION TRANSISTORS



# Bipolar Junction Transistors

- The transistor is a three-layer semiconductor device consisting of either two n- and one p- type layers of material or two p- and one n- type layers of material.
- The former is called an npn transistor, while the latter is called a pnp transistor
- So, there are two types of BJT-
  - i) pnp transistor
  - ii) npn transistor



# Bipolar Junction Transistors




In each transistor following points to be noted-

- i) There are two junction, so transistor can be considered as two diode connected back to back.
- ii) There are three terminals.
- iii) The middle section is thin than other.


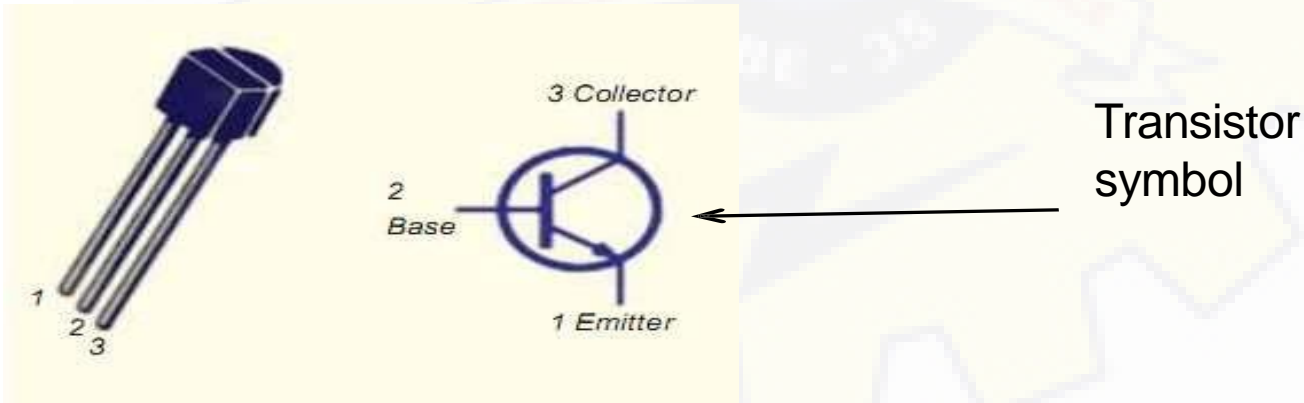
# Naming of Transistor Terminals

- Transistor has three section of doped semiconductor.
- The section one side is called “emitter” and the opposite side is called “collector”.
- The middle section is called “base”.





# Naming of Transistor Terminals

## 1) Emitter:

→ The section of one side that supplies carriers is called emitter.

→ Emitter is always forward biased wr to base so it can supply carrier.

→ For “npn transistor” emitter supply holes to its junction.

→ For “pnp transistor” emitter supply electrons to its junction.



# Naming of Transistor Terminals

## 2) Collector:

- The section on the other side that collects carrier is called collector.
- The collector is always reversed biased wr to base.

## 3) Base:

- The middle section which forms two pn junction between emitter and collector is called Base.



Some important factors to be remembered-

- The transistor has three region named emitter, base and collector.
- The Base is much thinner than other region.
- Emitter is heavily doped so it can inject large amount of carriers into the base.
- Base is lightly doped so it can pass most of the carrier to the collector.
- Collector is moderately doped.



Some important factors to be remembered-


- The junction between emitter and base is called emitter-base junction(emitter diode) and junction between base and collector is called collector-base junction(collector diode).
- The emitter diode is always forward biased and collector diode is reverse biased.
- The resistance of emitter diode is very small(forward) and resistance of collector diode is high(reverse).





# Transistor Operation

## 1) Working of npn transistor:

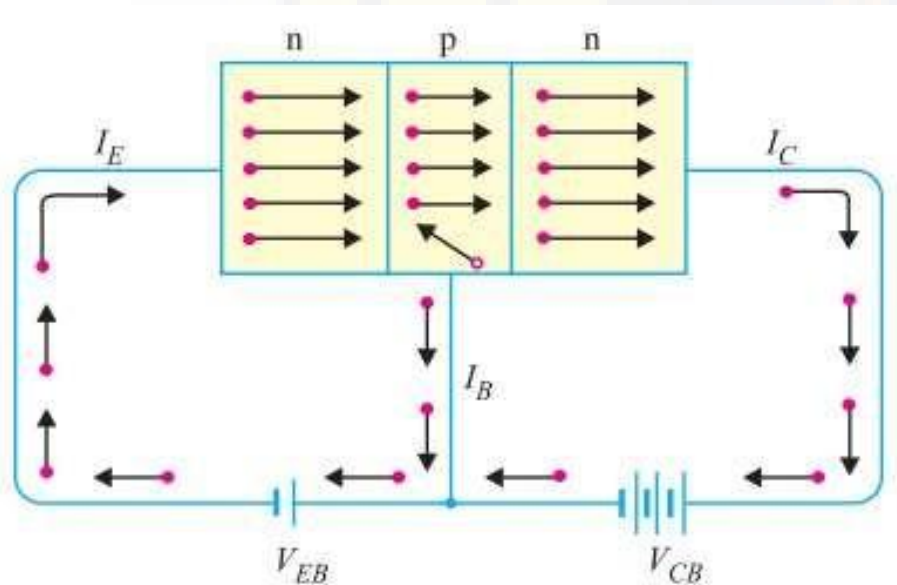

✓ Forward bias is applied to emitter-base junction and reverse bias is applied to collector-base junction.

✓ The forward bias in the emitter-base junction causes electrons to move toward



# Transistor Operation


## 1) Working of npn transistor:

- ✓ As this electrons flow toward p-type base, they try to recombine with holes. As base is lightly doped only few electrons recombine with holes within the base.
- ✓ These recombined electrons constitute small base current.
- ✓ The remainder electrons crosses base and constitute  $I_E = I_B + I_C$  current.



# Transistor Operation

## 2) Working of pnp transistor:

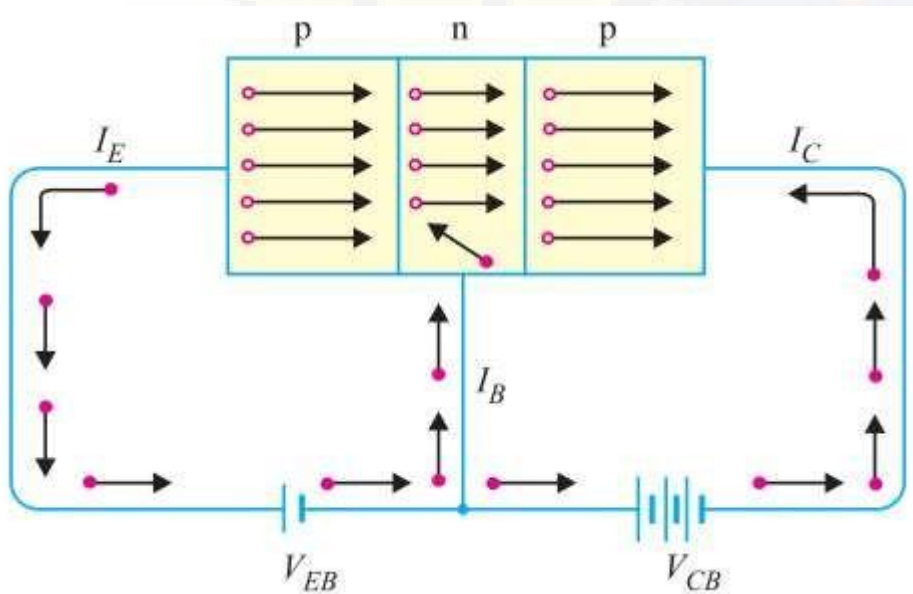

✓ Forward bias is applied to emitter- base junction and reverse bias is applied to collector- base junction.

✓ The forward bias in the emitter-base junction causes holes to move toward







# Transistor Operation

## 2) Working of pnp transistor:

- ✓ As this holes flow toward n-type base, they try to recombine with electrons. As base is lightly doped only few holes recombine with electrons within the base.
- ✓ These recombined holes constitute small base current.
- ✓ The remainder holes crosses base and constitute collector current.



# Transistor Symbol

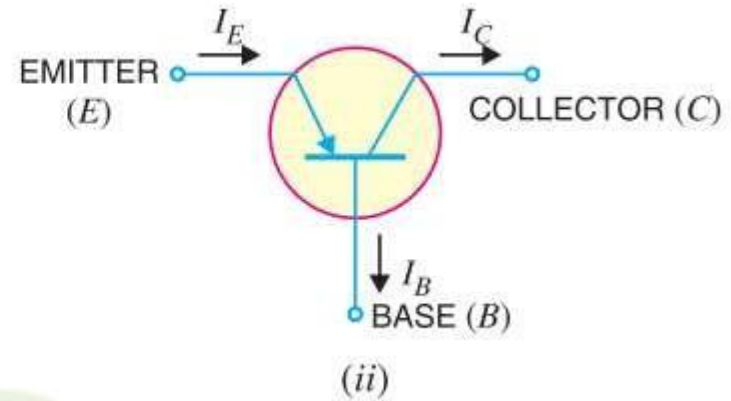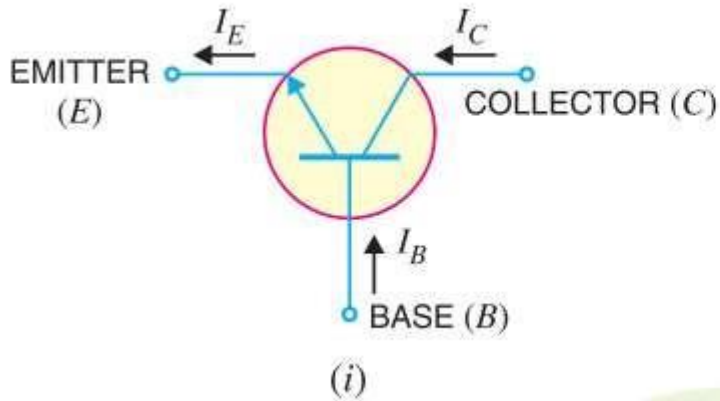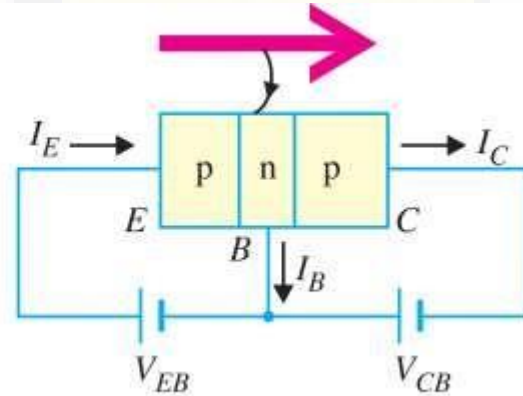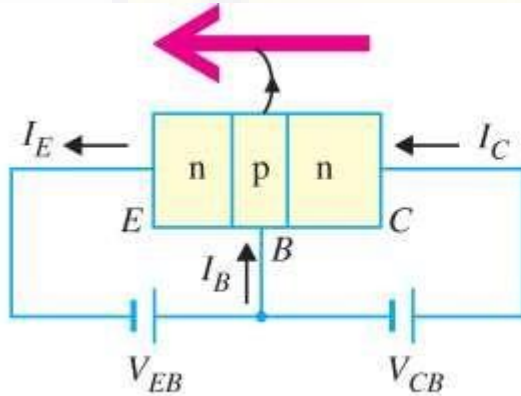



# Transistor Connection

- Transistor can be connected in a circuit in following three ways-
- 1) Common Base
  - 2) Common Emitter
  - 3) Common Collector



# Transistor Connection


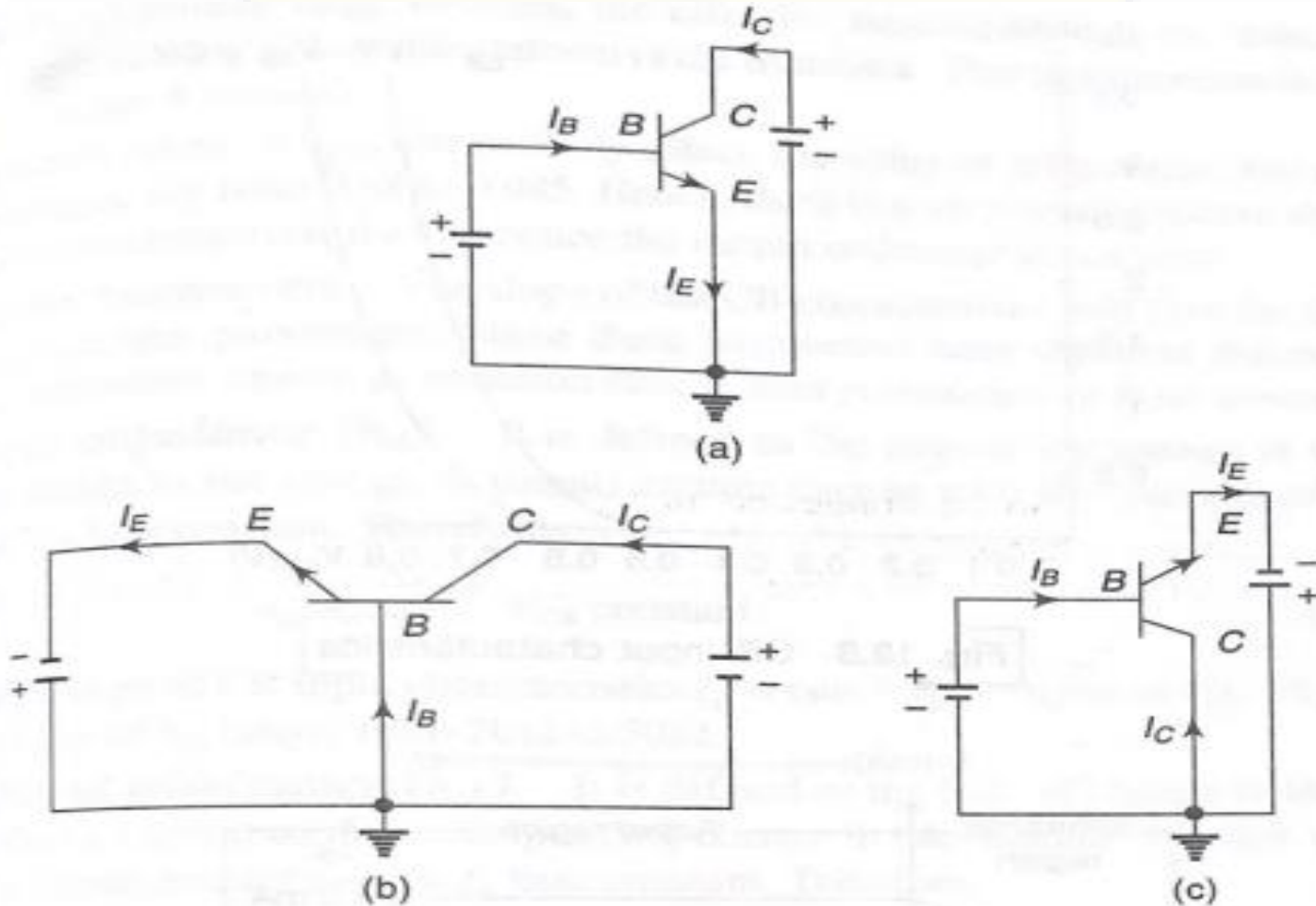


Fig. 13.6 Transistor configuration: (a) common base (b) common emitter and (c) common collector

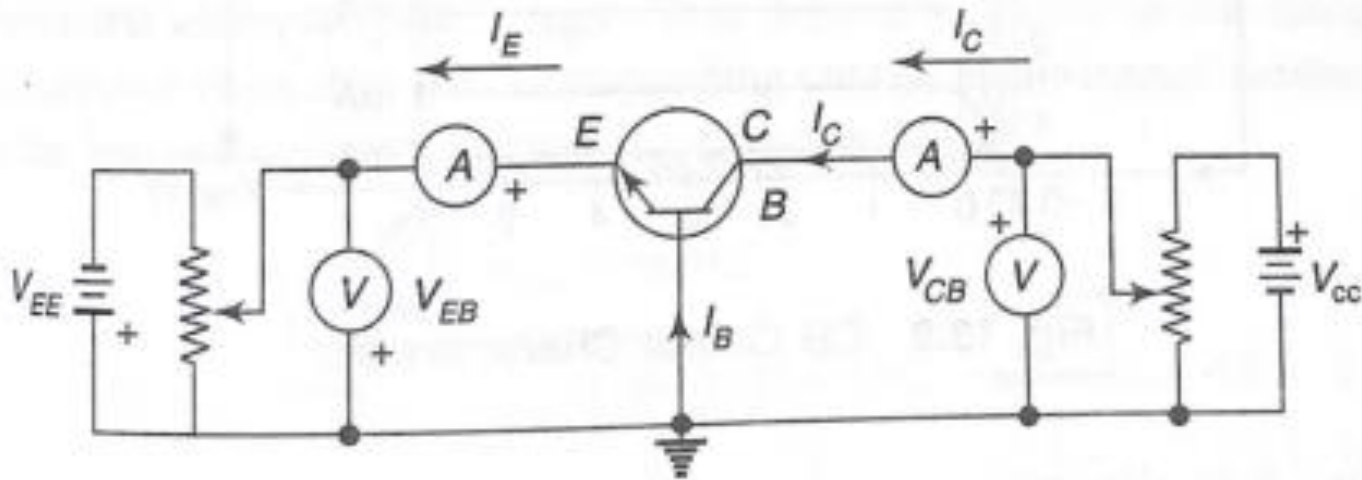

# Common Base Connection

- The common-base terminology is derived from the fact that the base is common to both the input and output sides of the configuration.



**Fig. 13.7** Circuit to determine CB static characteristics





# Common Base Connection

- Current amplification factor ( $\alpha$ ) :

The ratio of change in collector current to change in emitter current at constant  $V_{CB}$  is known

$$\alpha = \frac{\Delta I_C}{\Delta I_E} \text{ at constant } V_{CB}$$

→ Practical value of  $\alpha$  is less than unity, but in the range of 0.9 to 0.99



# Expression for Collector Current

→ Total emitter current does not reach the collector terminal, because a small portion of it constitute base current. So,

$$I_E = I_C + I_B$$

▪



# Characteristics of common base configuration

- Input Characteristics:

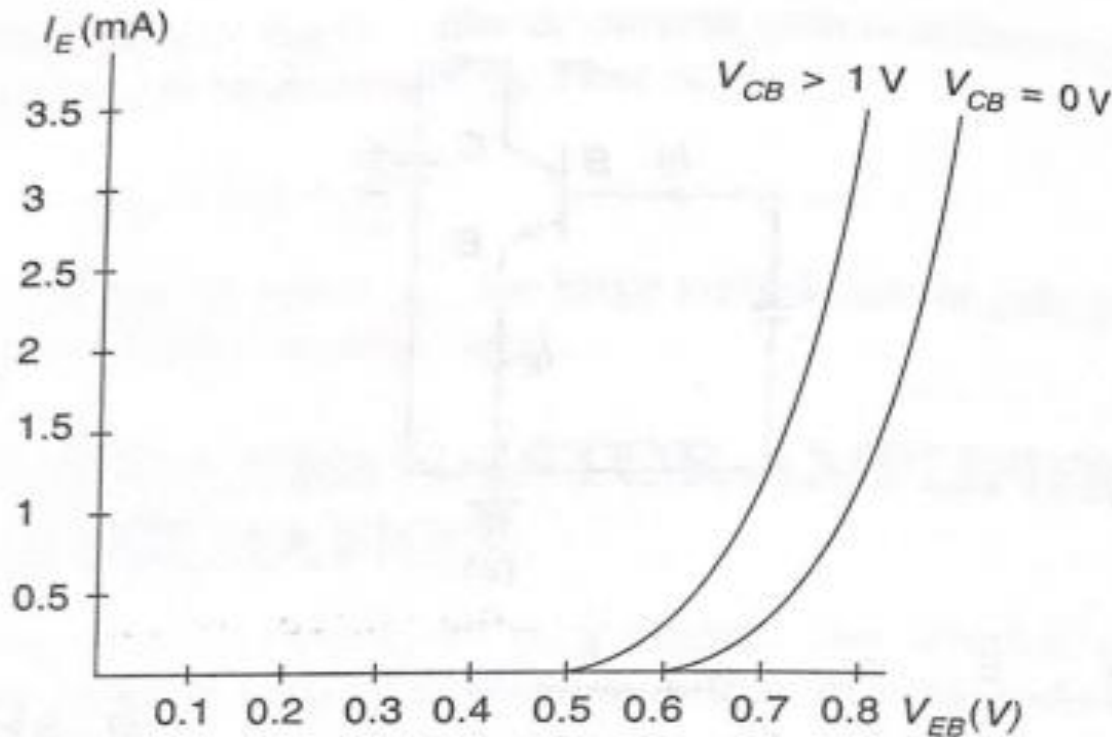



Fig. 13.8 CB Input characteristics



# Characteristics of common base configuration

Output

Characteristics:

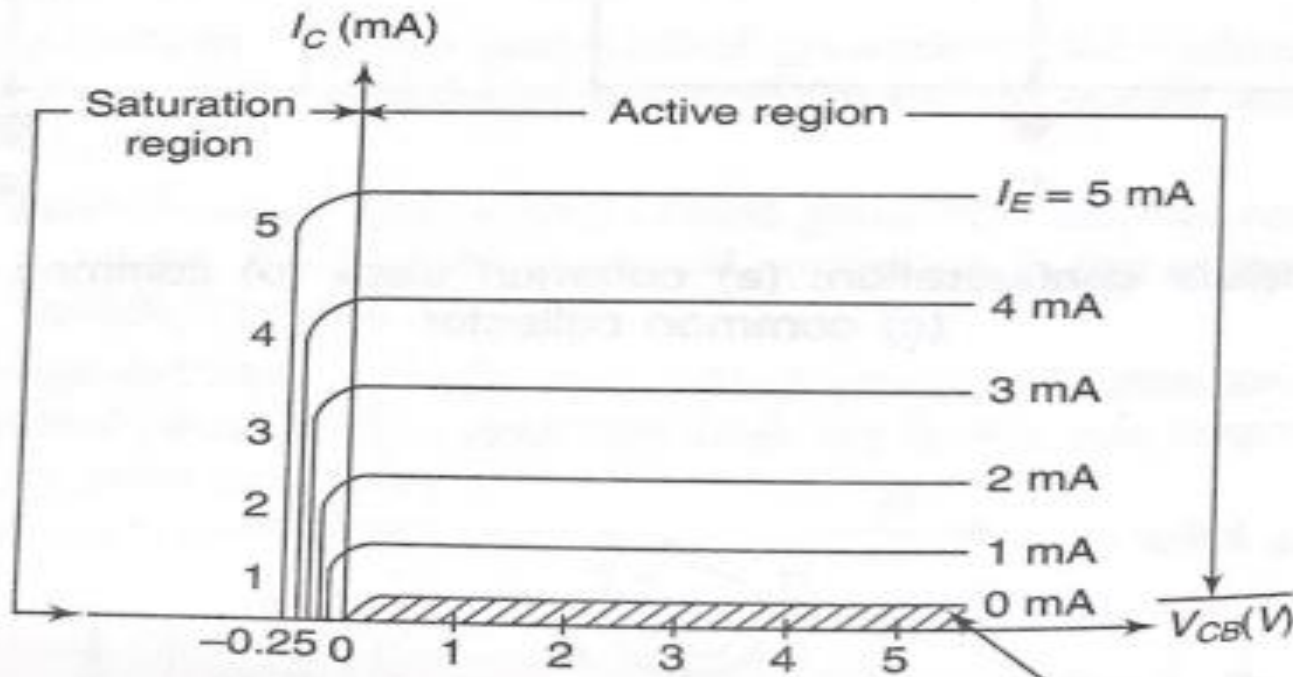

**Fig. 13.9** CB Output Characteristics



# Common Emitter Connection

- The common-emitter terminology is derived from the fact that the emitter is common to both the input and output sides of the configuration.

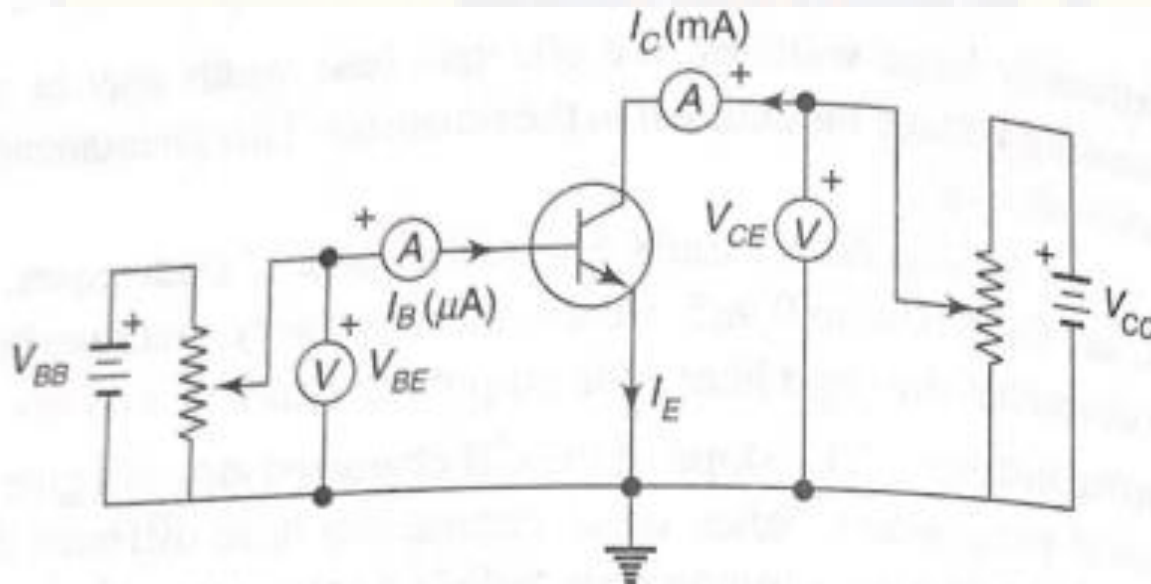


Fig. 13.10 Circuit to determine CE static characteristics



# Common Emitter Connection

- Base Current amplification factor ( $\beta$ ) :
- The ratio of change in collector current to the change in base current is known as base current

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

- Usually this range varies from 20 to 500.



# Relation Between $\beta$ and $\alpha$

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$


$$\beta = \frac{\Delta I_C}{\Delta I_E - \Delta I_C}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$



# Characteristics of common emitter configuration

- Input Characteristics:

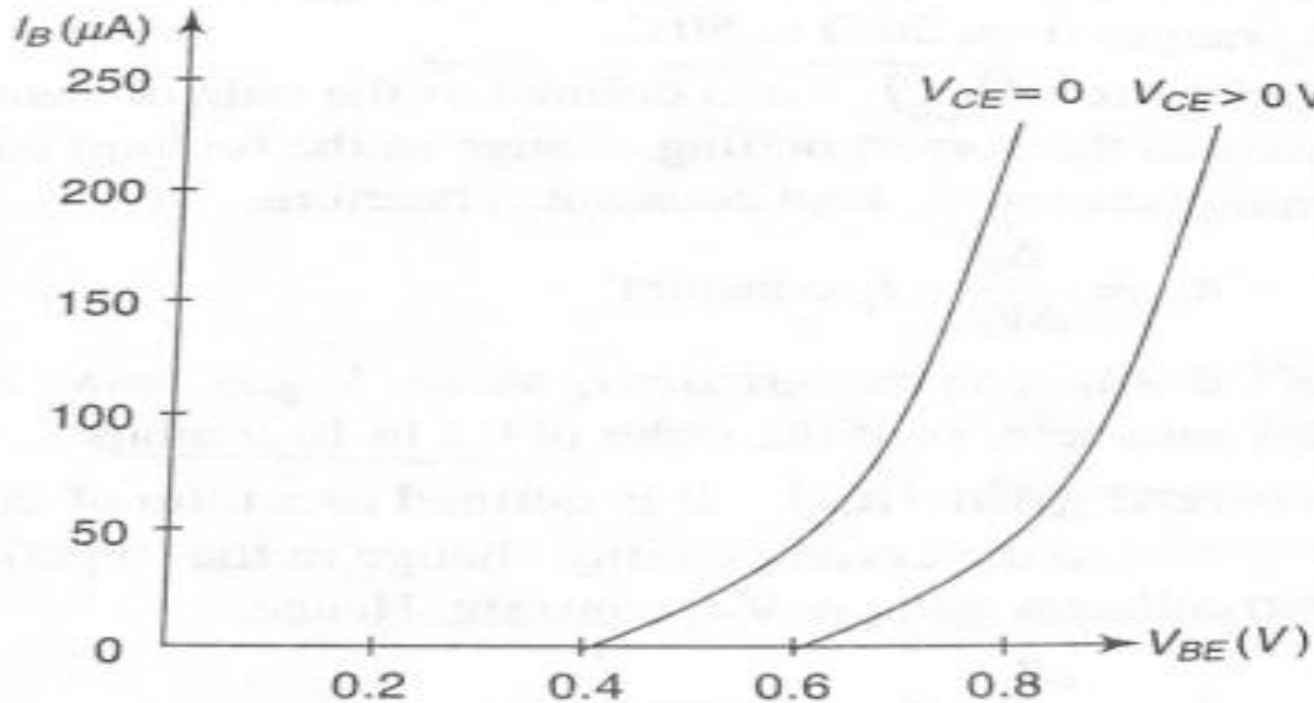






# Characteristics of common emitter configuration

- Output Characteristics:

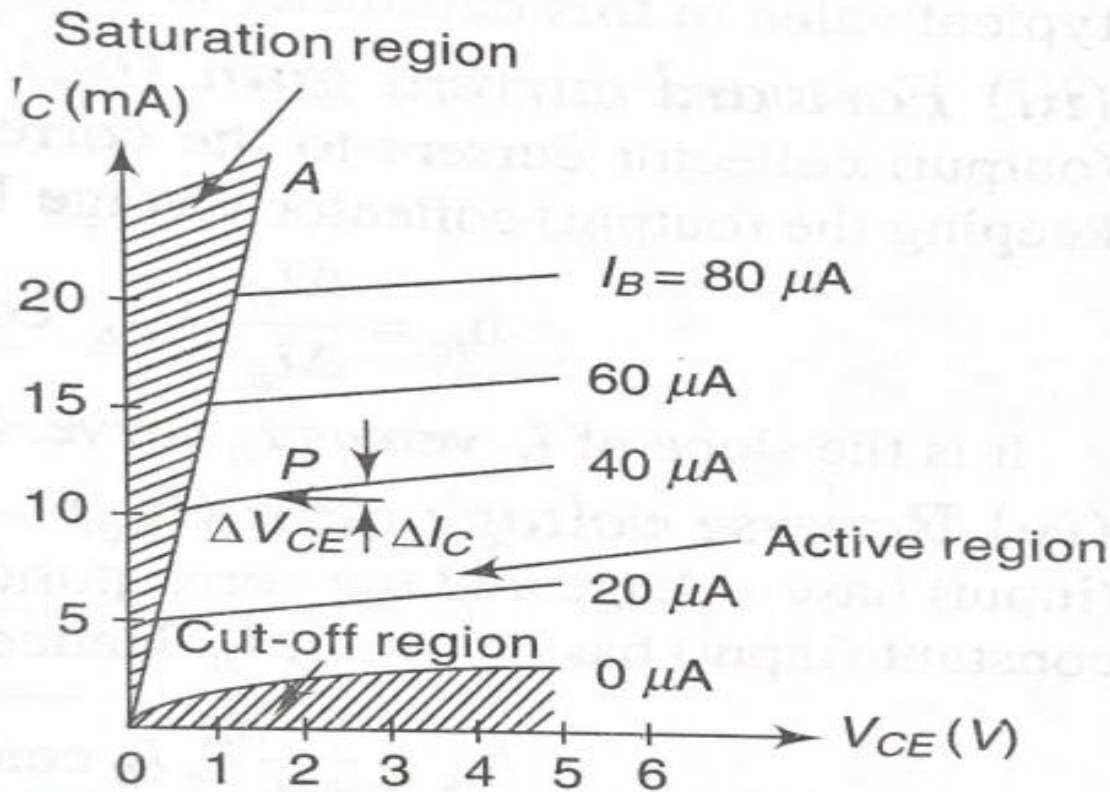


**Fig. 13.12** CE output characteristics



# Common Collector Configuration


- The common-collector terminology is derived from the fact that the collector is common to both the input and output sides of the configuration.

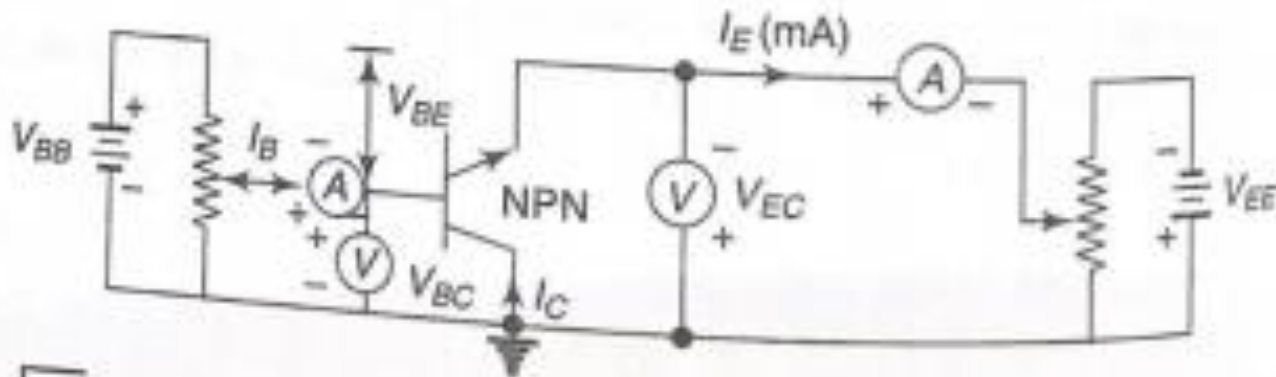


**Fig. 13.13** Circuit to determine CC static characteristics



# Common Collector Configuration

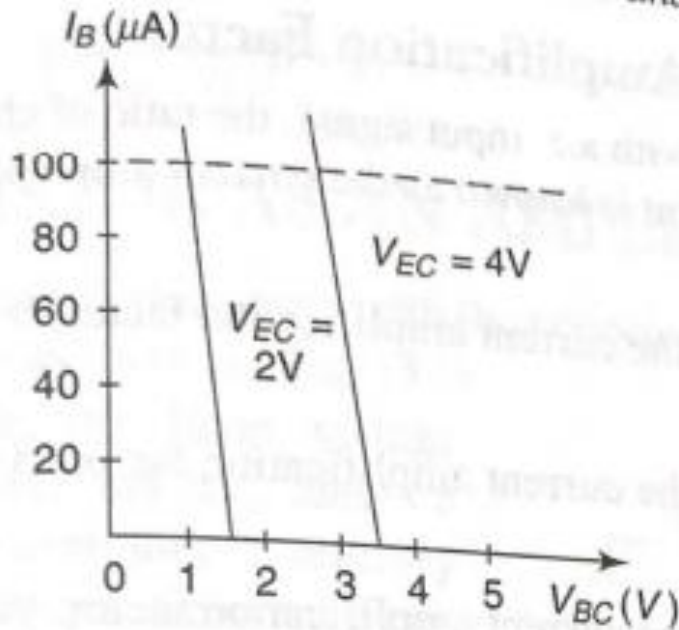

**Fig. 13.14** CC input characteristics

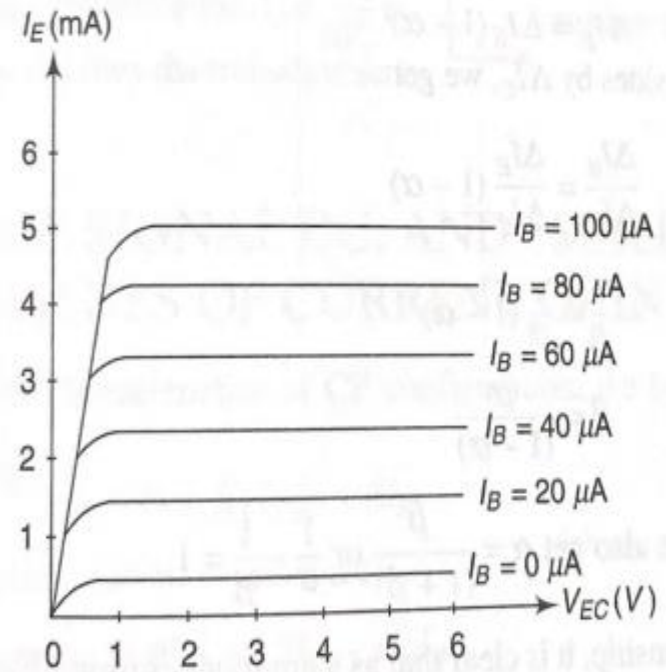

**Fig. 13.15** CC output characteristics



# Common Collector Configuration

- Current amplification factor ( $\gamma$ ) :
- In common emitter connection input current is base current and output current is emitter current.
- The ratio of change in emitter current to the change in base current is known as current amplification

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$



# Comparison of Transistor Connection

S. No.	Characteristic	Common base	Common emitter	Common collector
1.	Input resistance	Low (about 100 $\Omega$ )	Low (about 750 $\Omega$ )	Very high (about 750 k $\Omega$ )
2.	Output resistance	Very high (about 450 k $\Omega$ )	High (about 45 k $\Omega$ )	Low (about 50 $\Omega$ )
3.	Voltage gain	about 150	about 500	less than 1
4.	Applications	For high frequency applications	For audio frequency applications	For impedance matching
5.	Current gain	No (less than 1)	High ( $\beta$ )	Appreciable