



# SNS COLLEGE OF TECHNOLOGY

## (AN AUTONOMOUS INSTITUTION)

Approved by AICTE & Affiliated to Anna University  
Accredited by NBA & Accredited by NAAC with 'A+' Grade,  
Recognized by UGC saravanampatti (post), Coimbatore-641035.



## Department of Biomedical Engineering

Course Name: **23BMB101-Electron Devices and Circuits**

**I Year : II Semester**

**Unit II -Transistors**

**Topic : Bipolar Junction Transistor<sup>1</sup>**




# INTRODUCTION



- When a p-type semiconductor is joined with the n-type semiconductor, a p-n junction is formed between them. This p-n junction forms a most popular device known as a semiconductor diode. Vision Tit 2
- An addition of another layer to a p-n junction diode forms a three terminal device called a transistor that amplifies the electronic signals. The term transistor normally refers to a Bipolar Junction Transistor (BJT). Vision Title 3
- The transistor that is made up of one p-type and two n-type semiconductor layers is known as n-p-n transistor whereas the transistor that is made up of one n-type and two p-type semiconductor layers is known as p-n-p transistor.



# Classification of Transistors

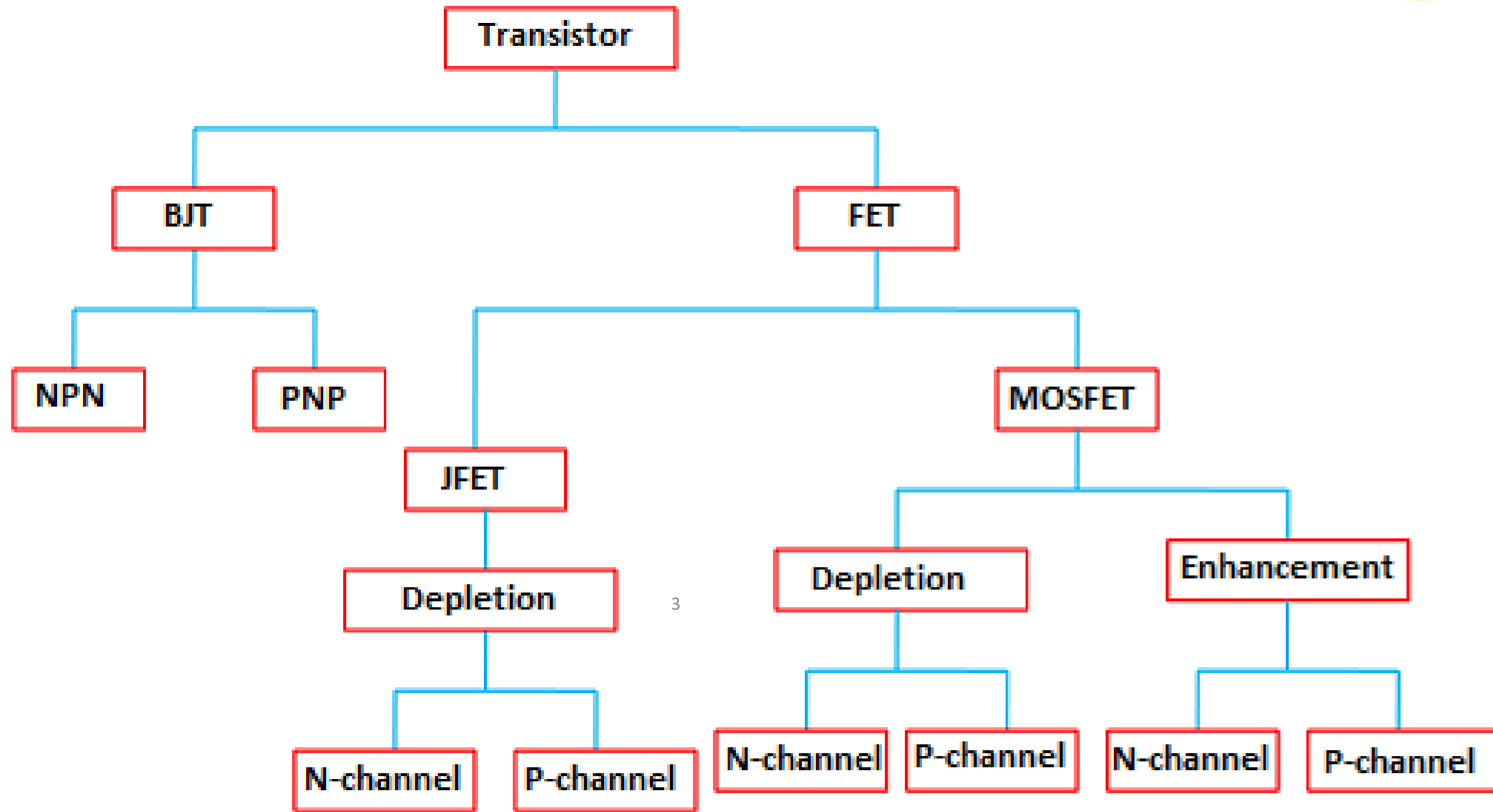

## Classification of transistors



# Bipolar Junction Transistor




- A bipolar junction transistor or BJT is a three terminal electronic device that amplifies the flow of current.
- It is a current controlled device. In bipolar junction transistor, electric current is conducted by both free electrons and holes.
- Bipolar junction transistors are classified into two types based on their construction: They are
  - ✓ NPN transistor
  - ✓ PNP transistor

4





# Bipolar Junction Transistor

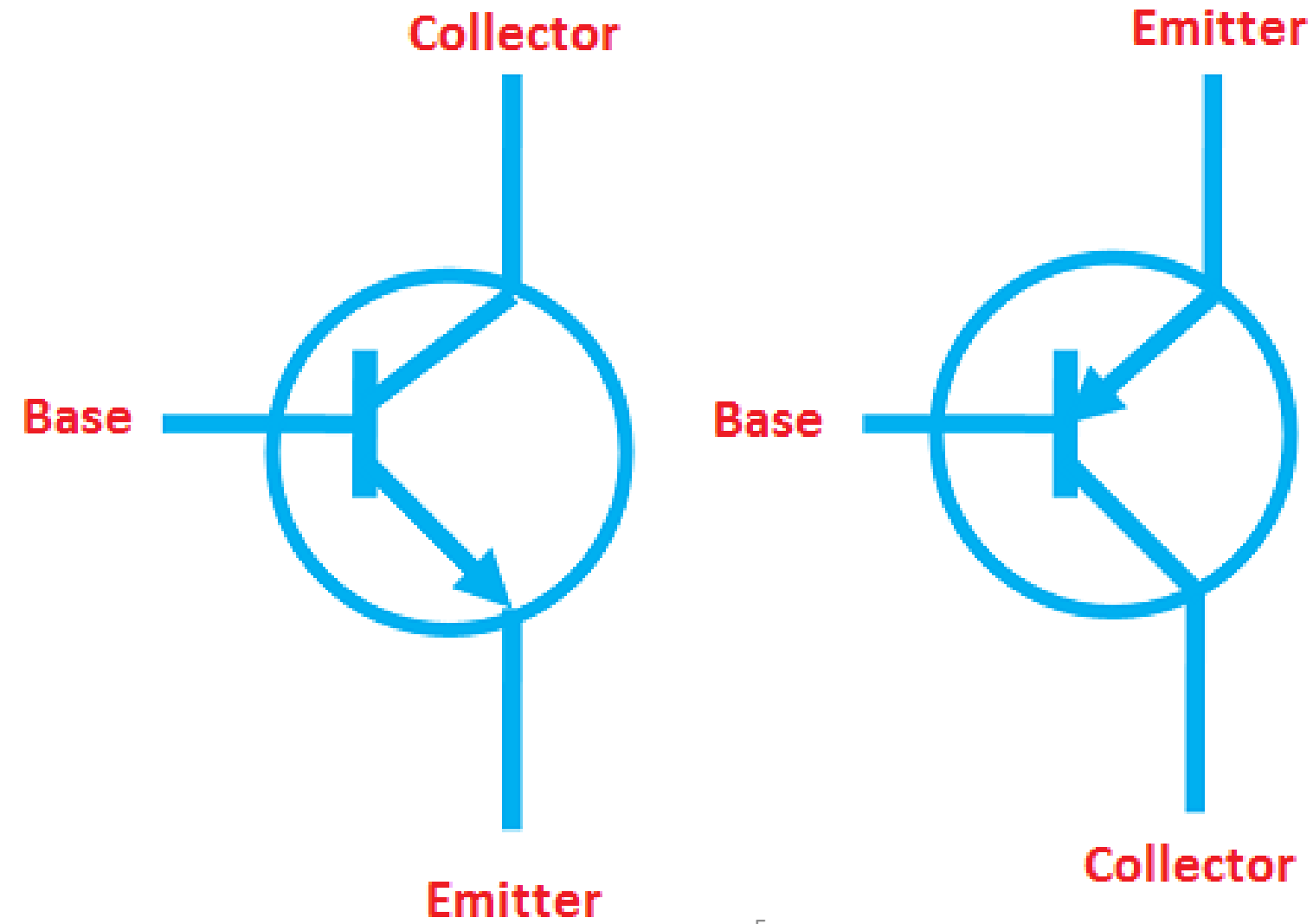

5

NPN Transistor

PNP Transistor

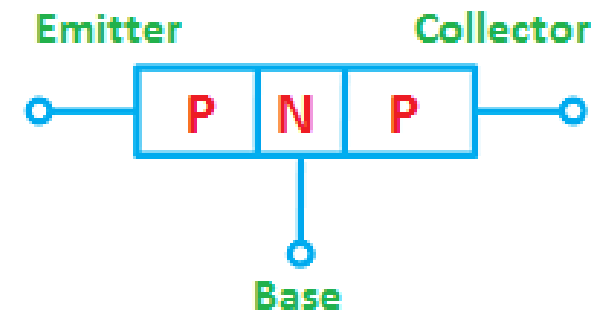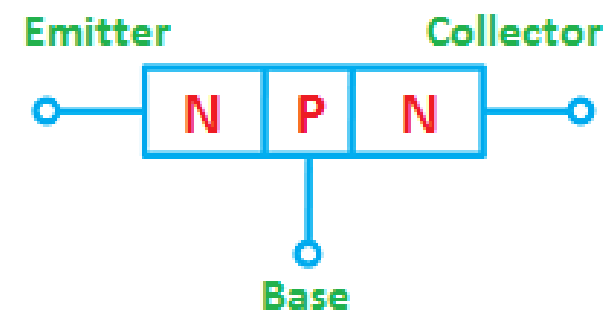



# Bipolar Junction Transistor



- **Emitter:** As the name suggests, the emitter section supplies the charge carriers. The emitter section is heavily doped so that it can inject a large number of charge carriers into the base. The size of the emitter is always greater than the base.
- **Base:** The middle layer is called base. The base of the transistor is very thin as compared to emitter and collector. It is very lightly doped.
- **Collector:** The function of the collector is to collect charge carriers. It is moderately doped. The size of the collector is always greater than emitter and base.





## BJT operation modes

- **The transistor can be operated in three modes:**
  - ✓ **Cut-off mode**
  - ✓ **Saturation mode**
  - ✓ **Active mode**
- Applying dc voltage to the transistor is nothing but the biasing of transistor.
- In order to operate transistor in one of these regions, we have to supply dc voltage to the npn or pnp transistor.
- Based on the polarity of the applied dc voltage, the transistor operates in any one of these regions.

Vision Tit 2



# Cut-off mode

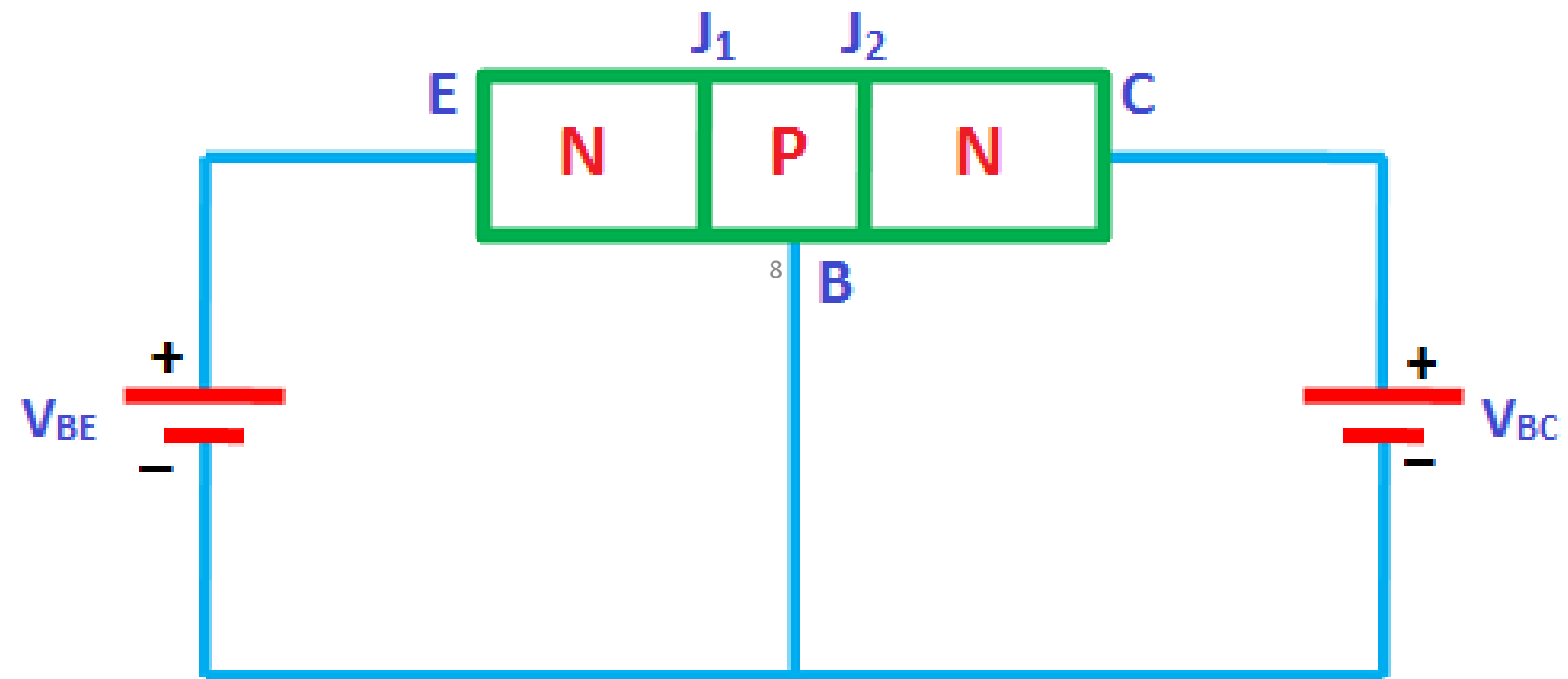
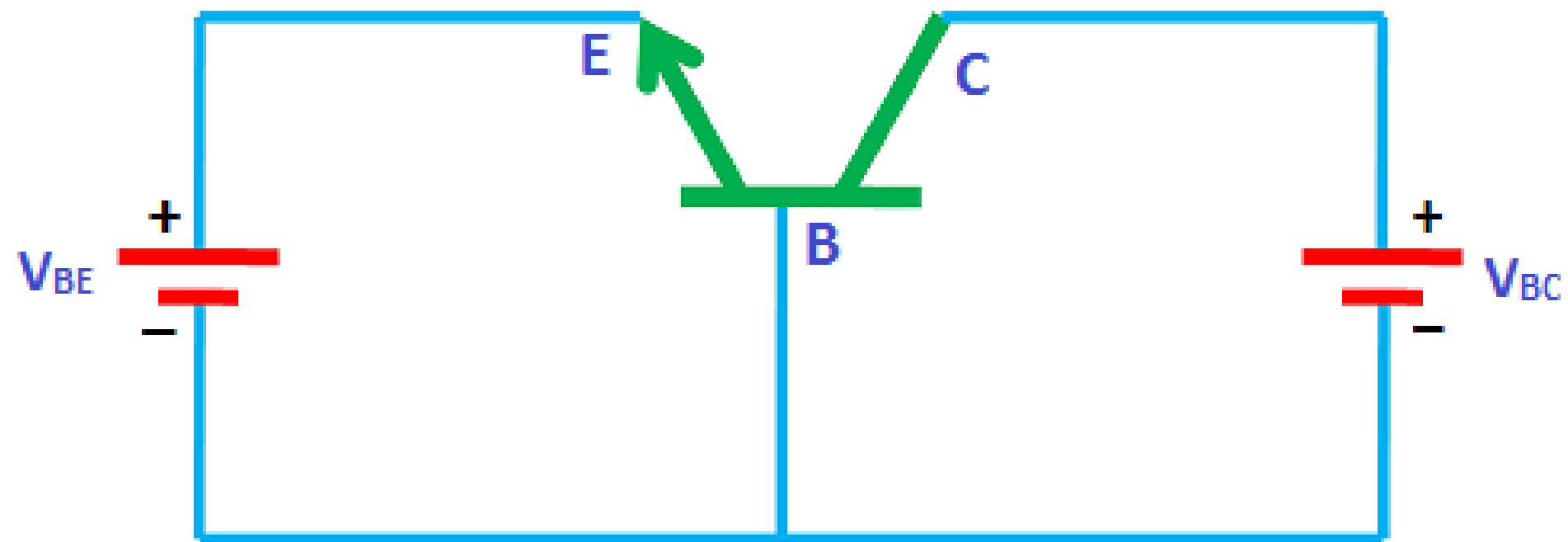


# Cutoff mode







# Saturation mode

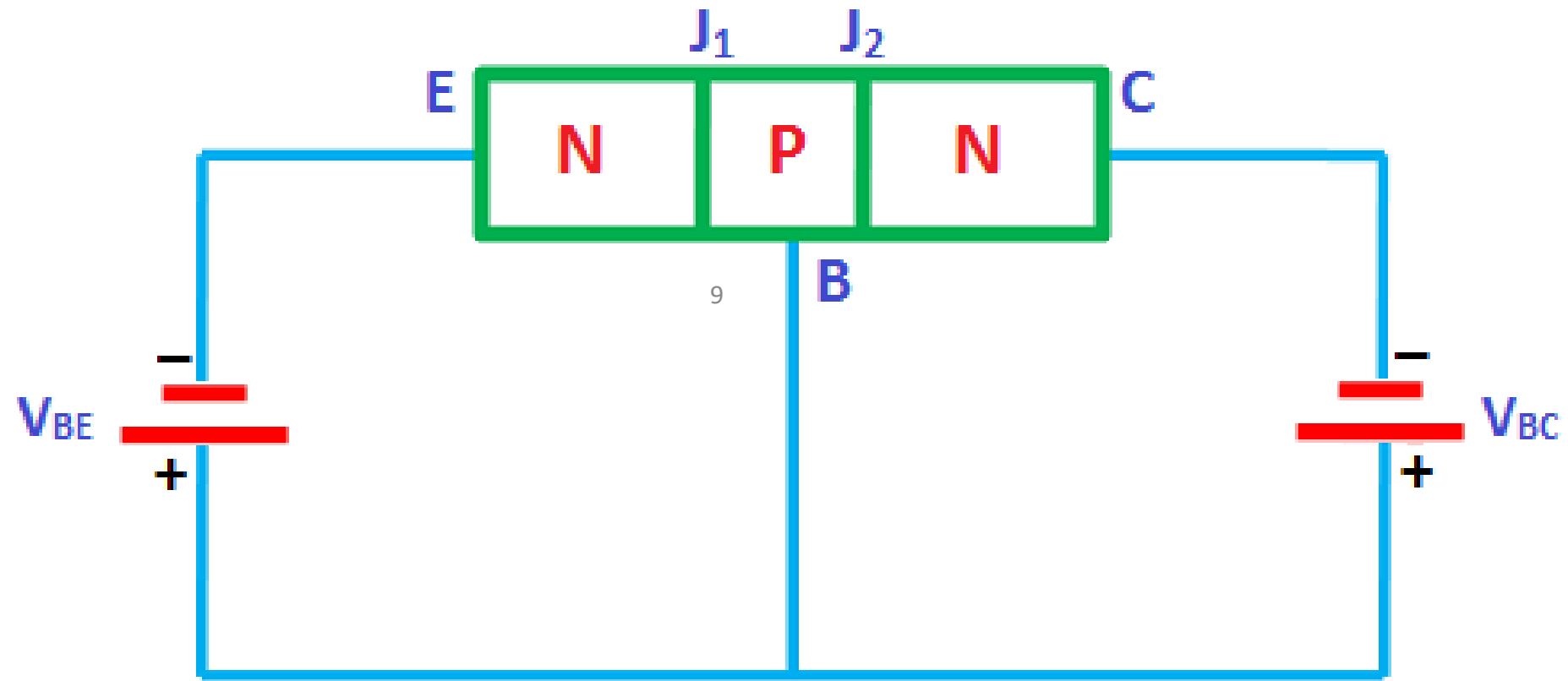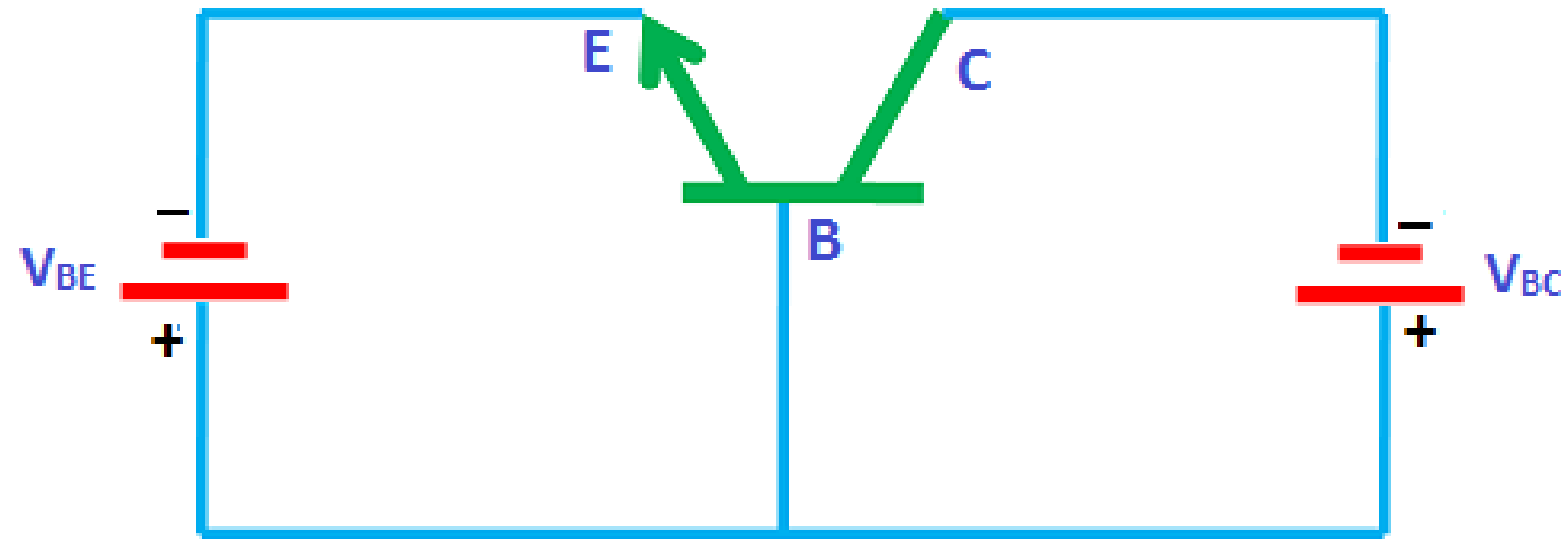

Saturation mode





# Active mode

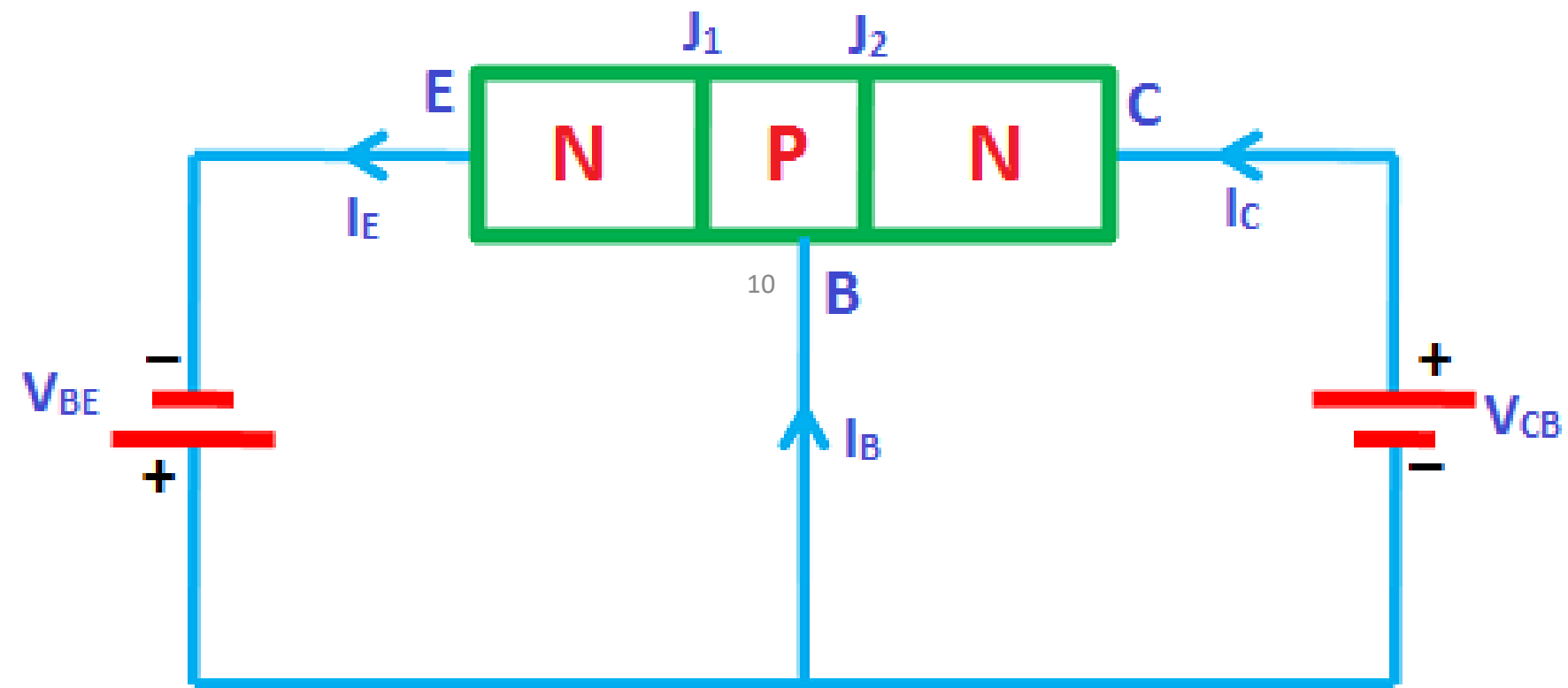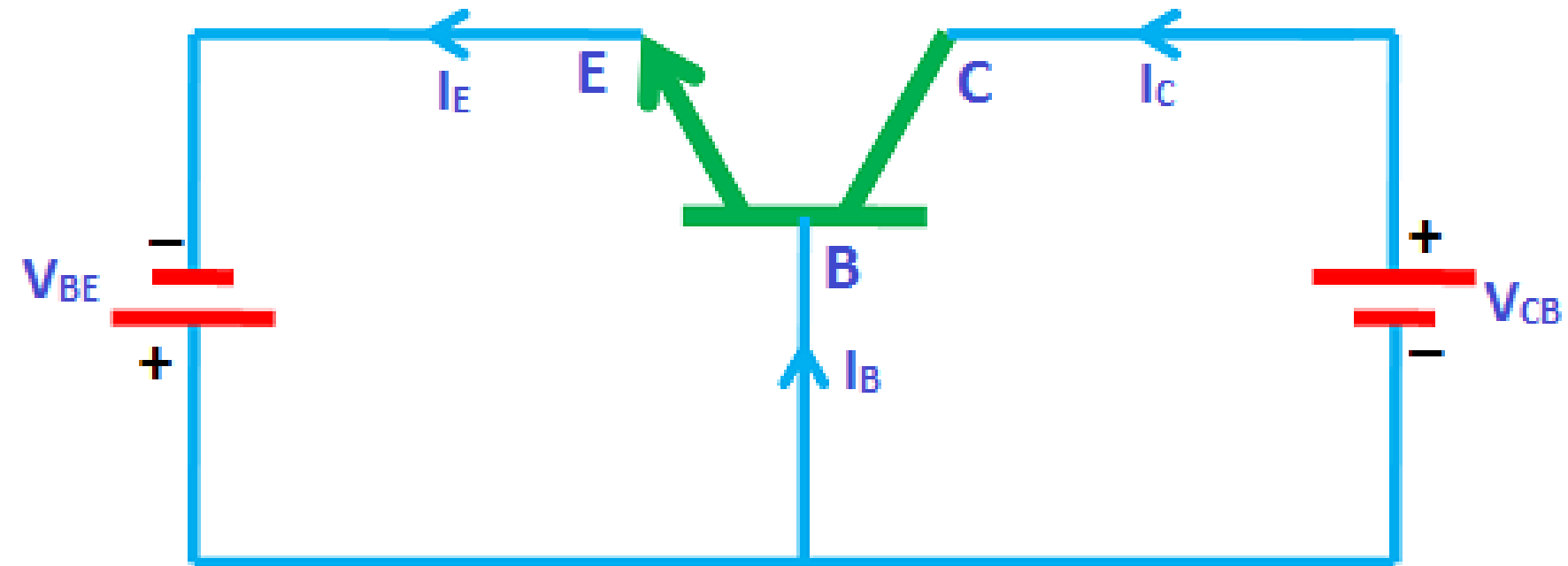

# Active mode



# NPN transistor

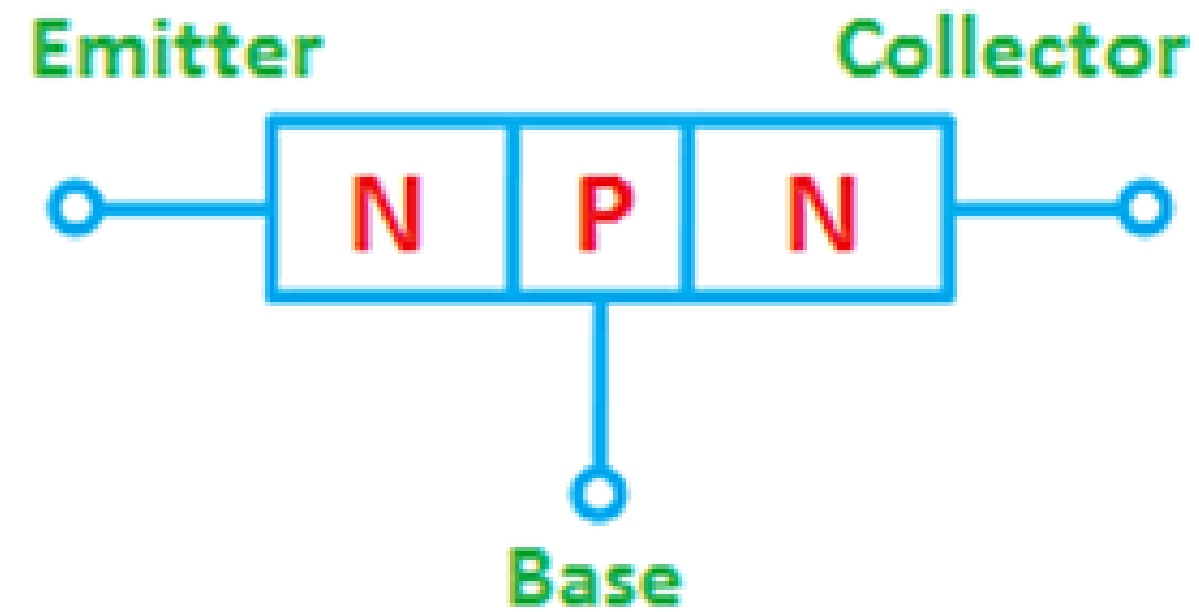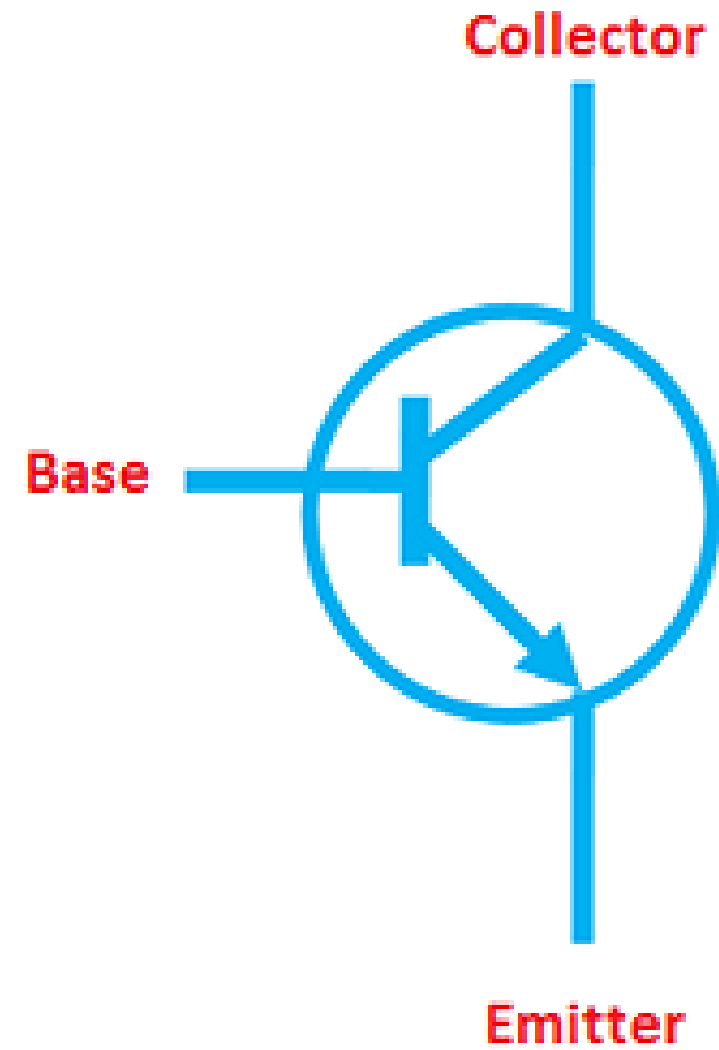


11

NPN transistor symbol




# Working of NPN transistor- Unbiased

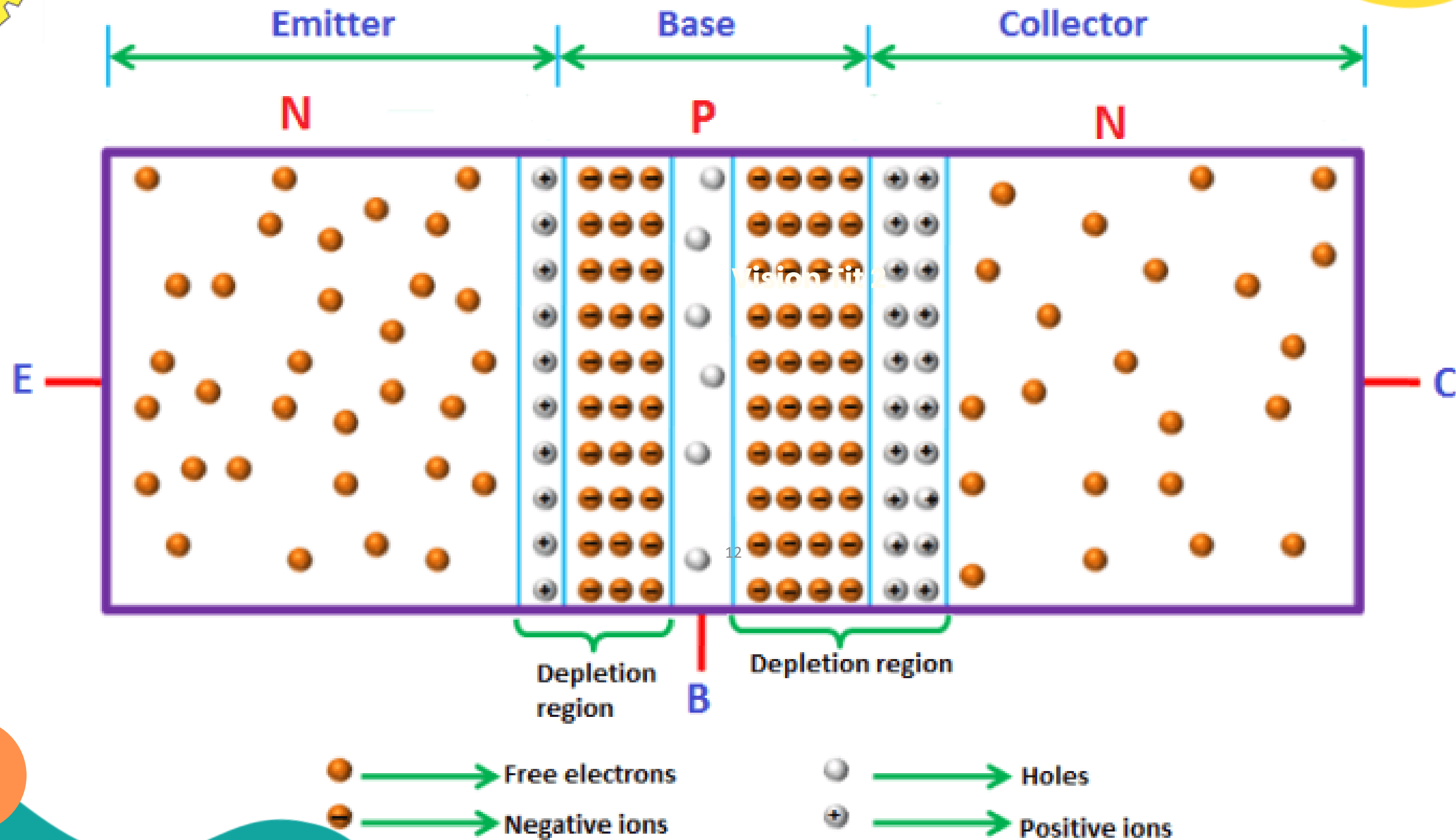





# Working of NPN transistor- Biased

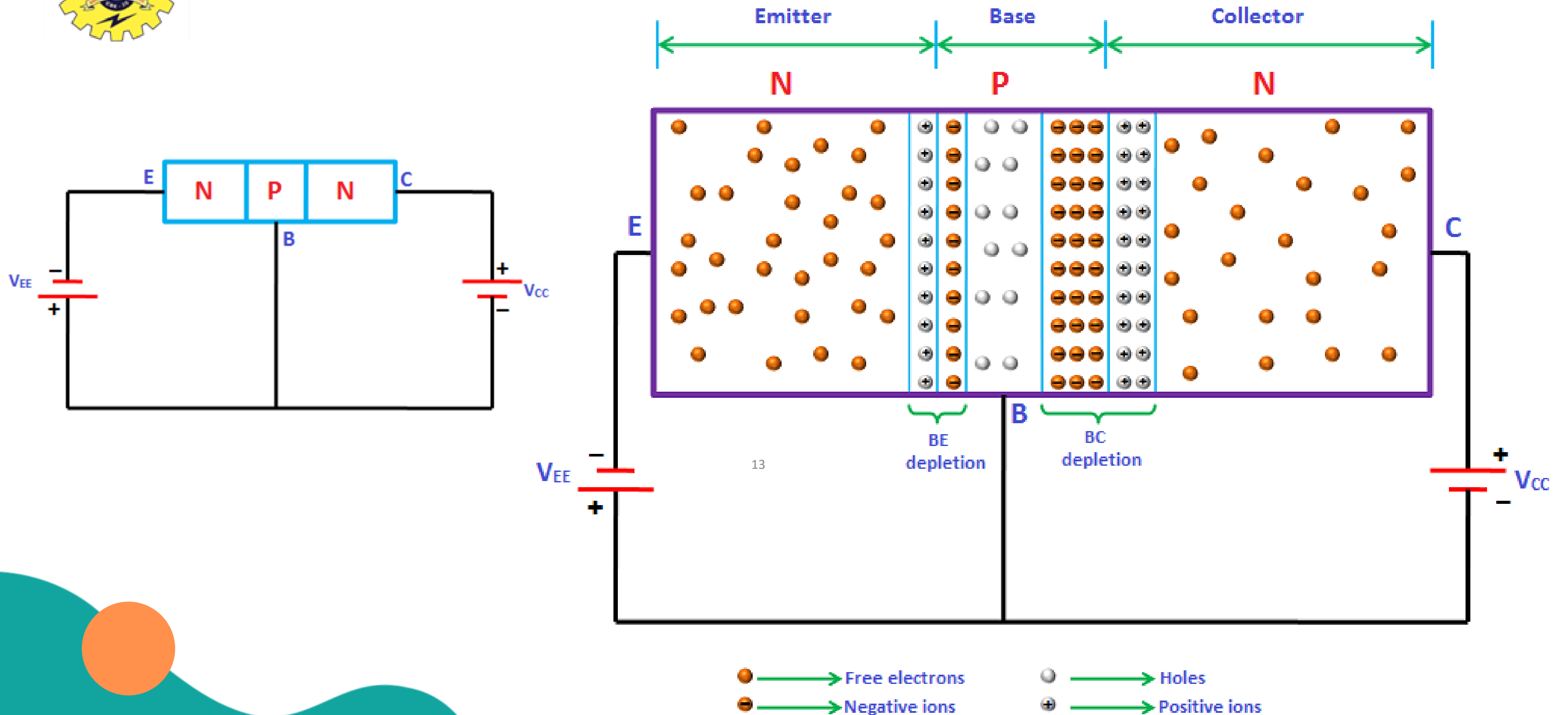





# Current direction in NPN transistor

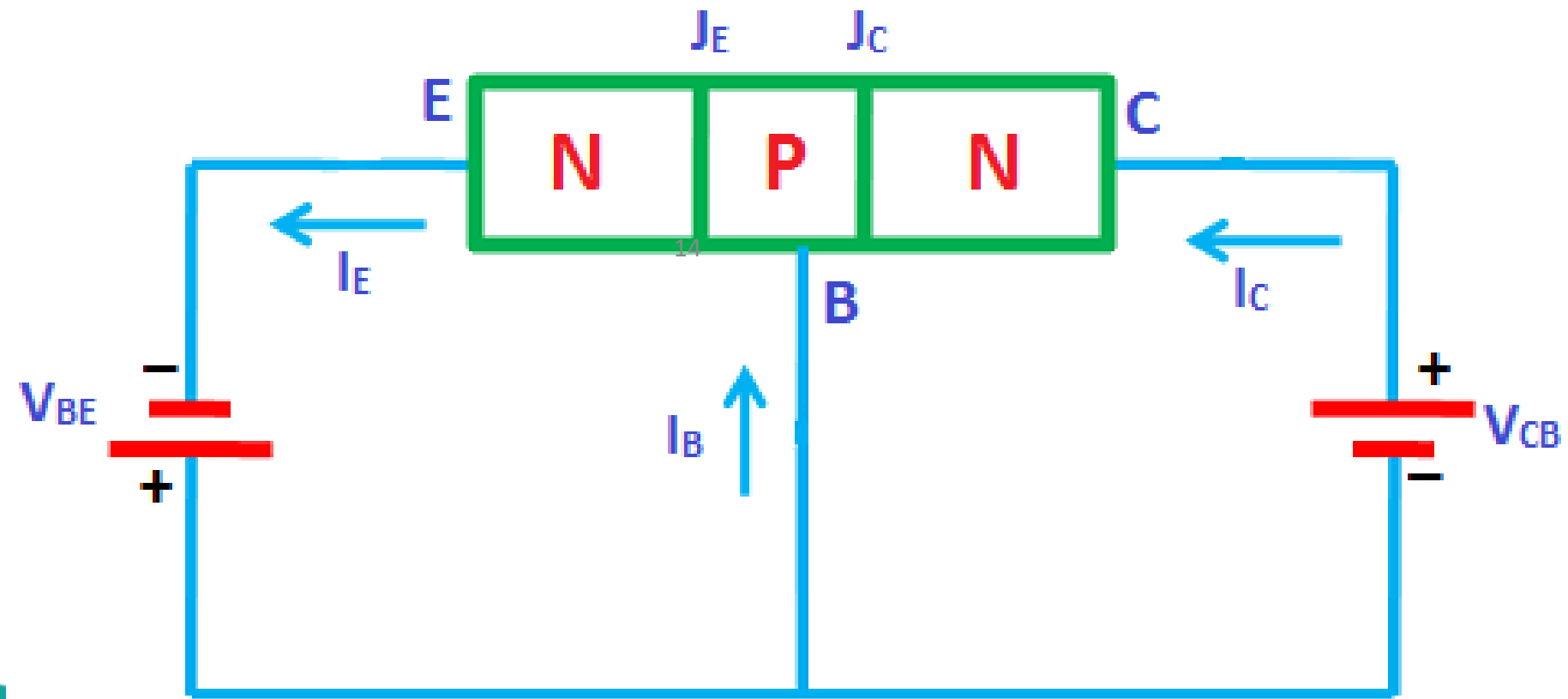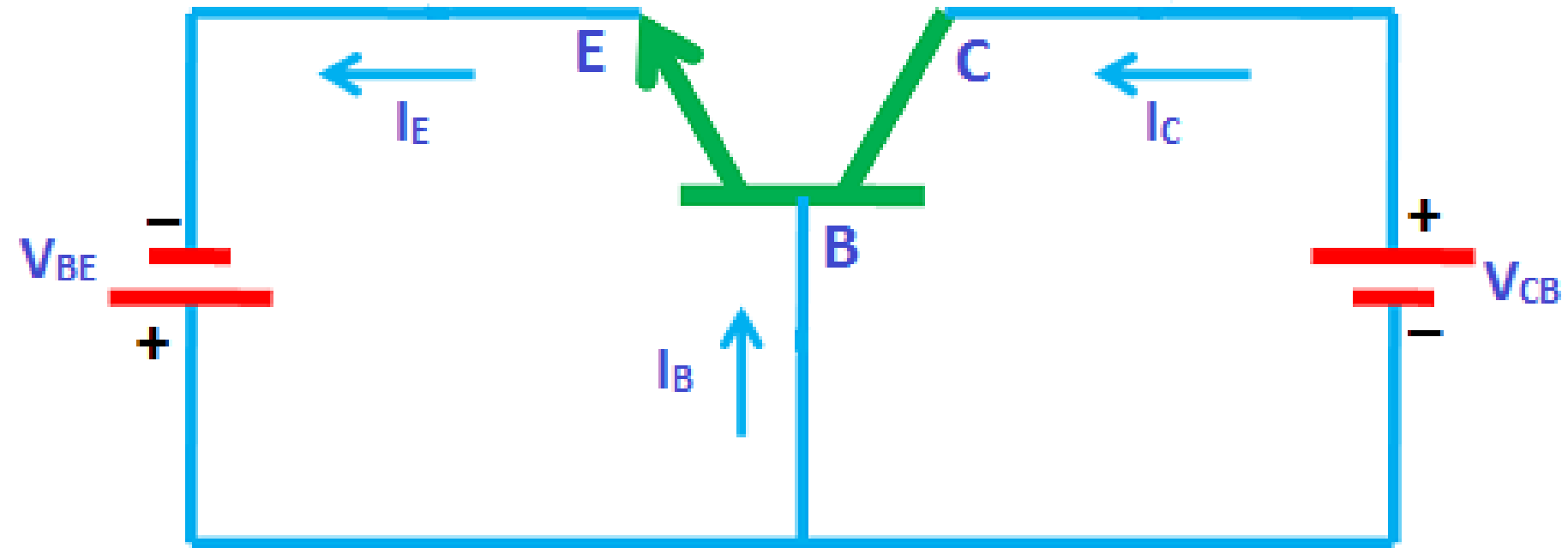



# PNP Transistor

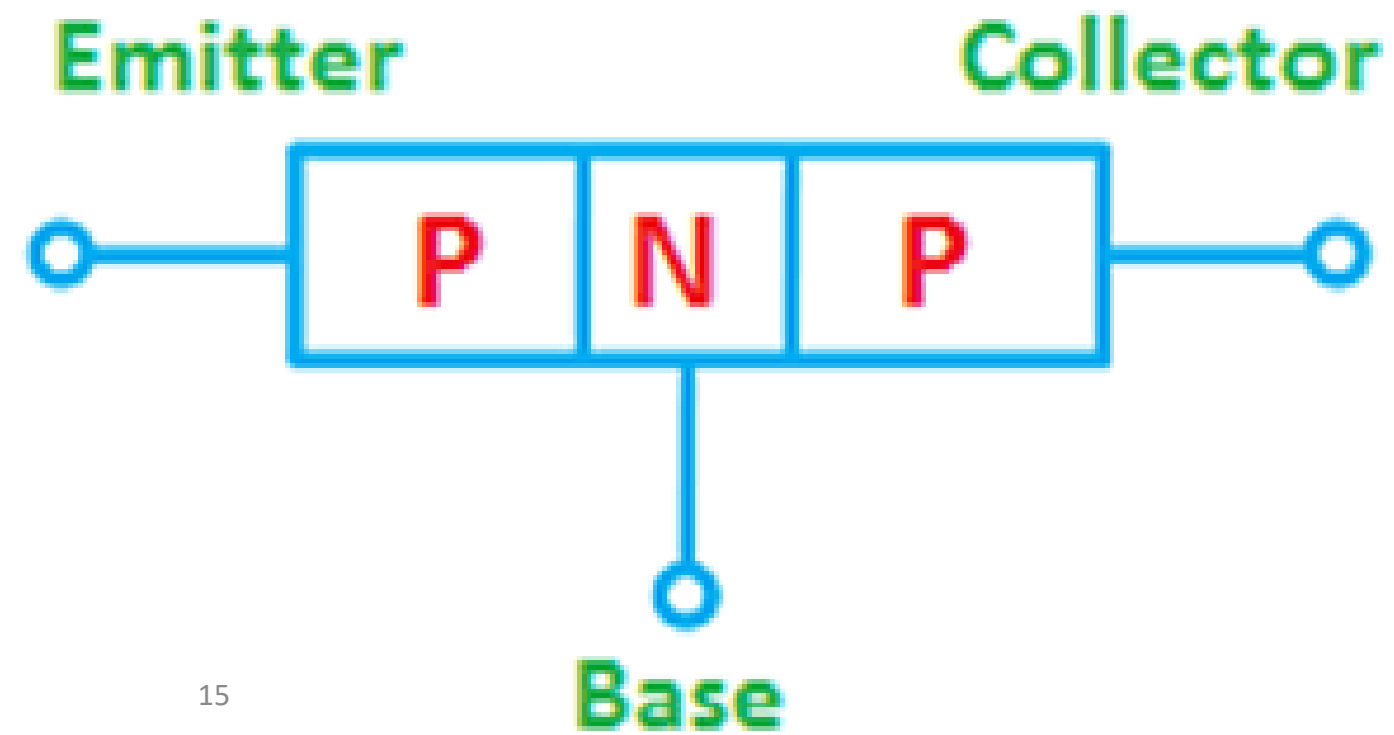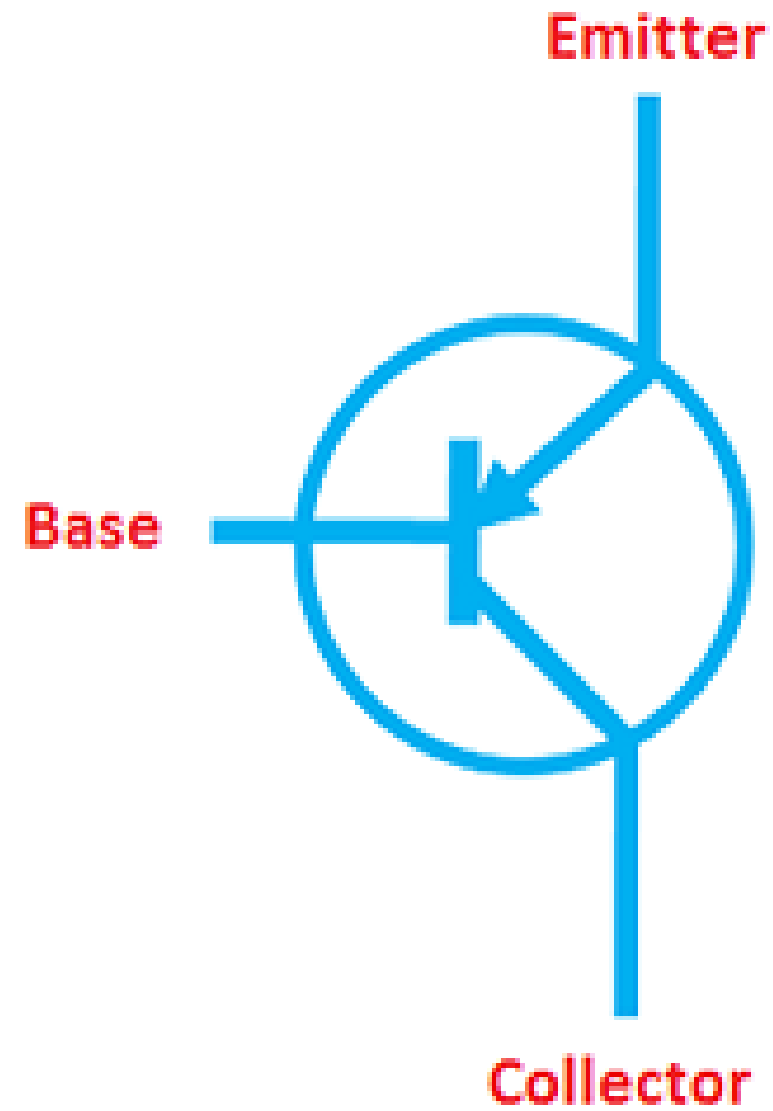


15

PNP transistor symbol




# Working of NPN transistor- Unbiased

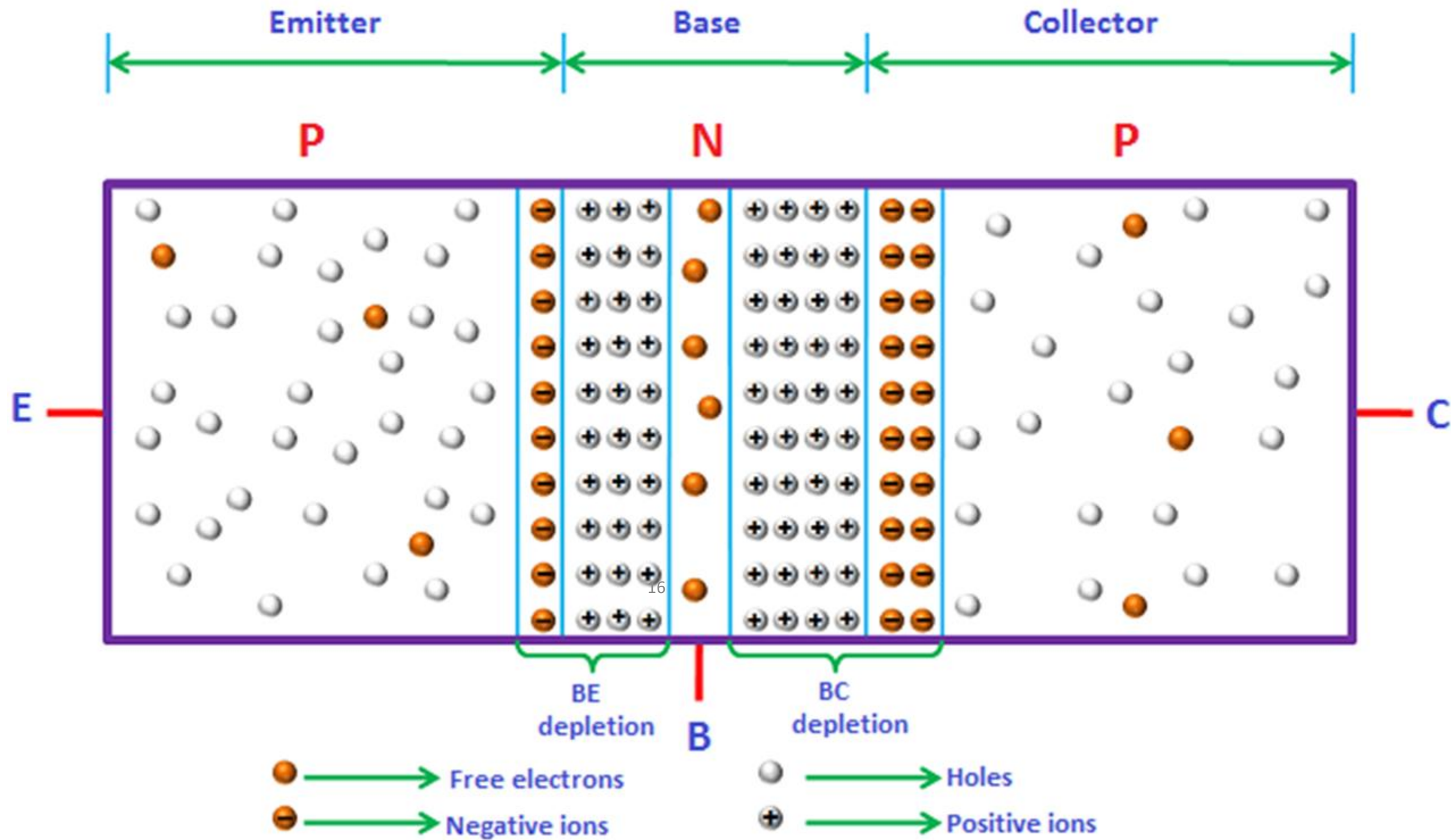







# Working of NPN transistor- Biased

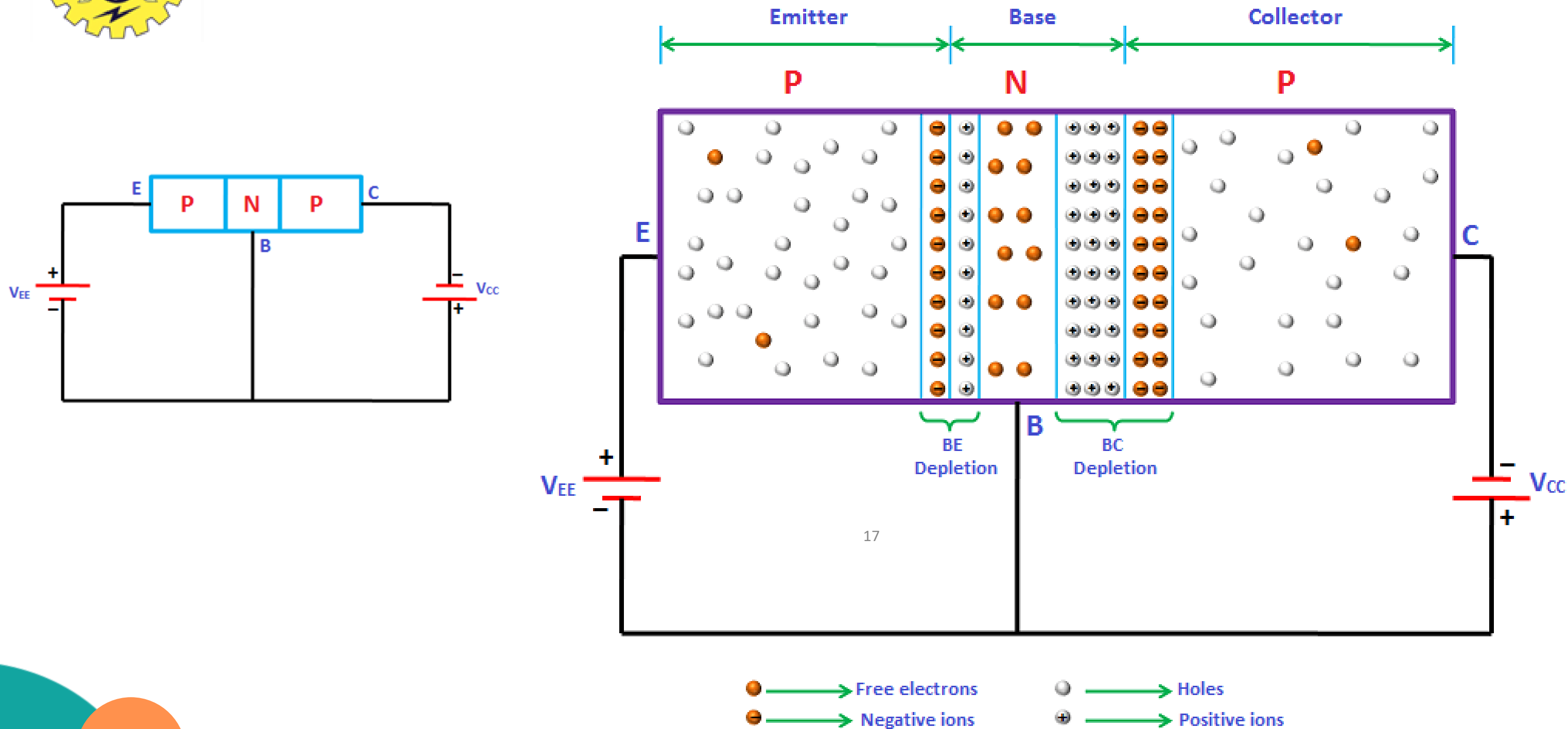



# Current direction in PNP transistor

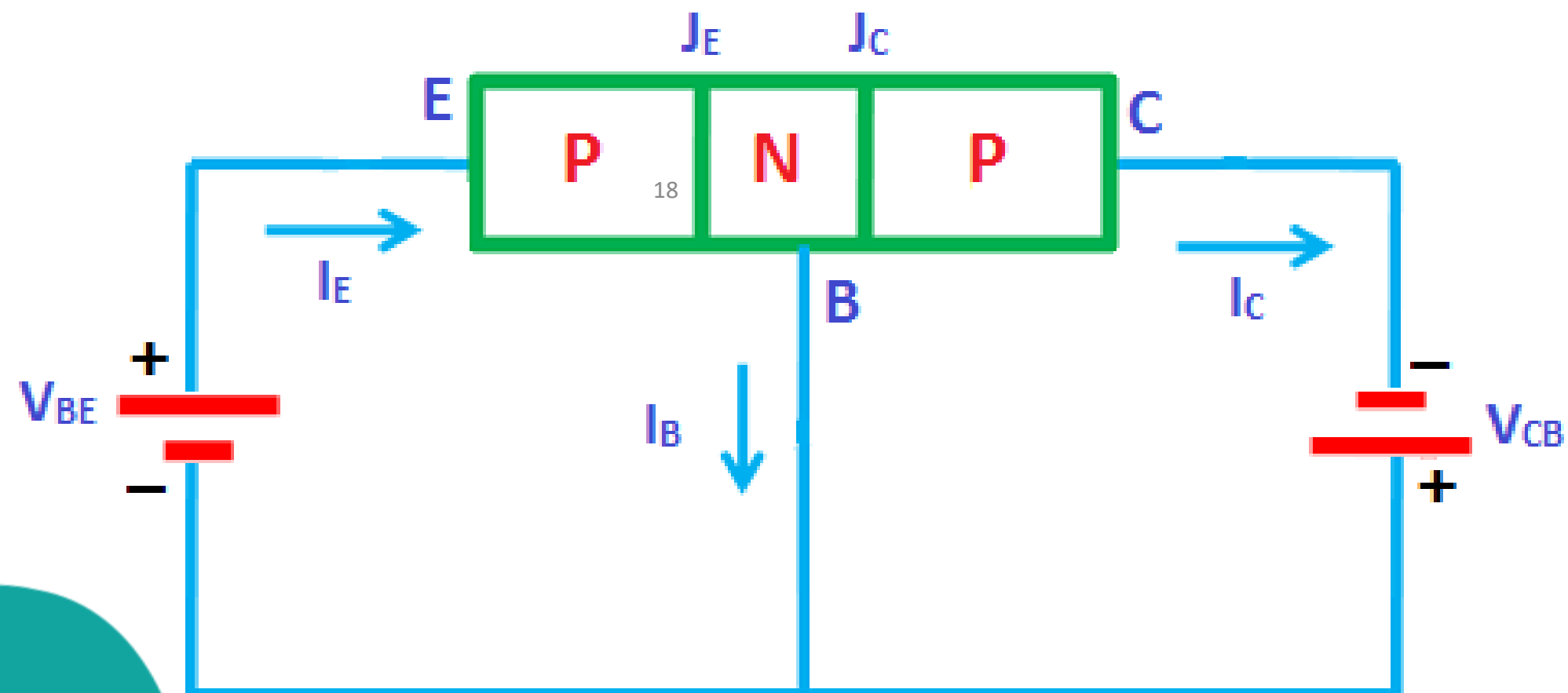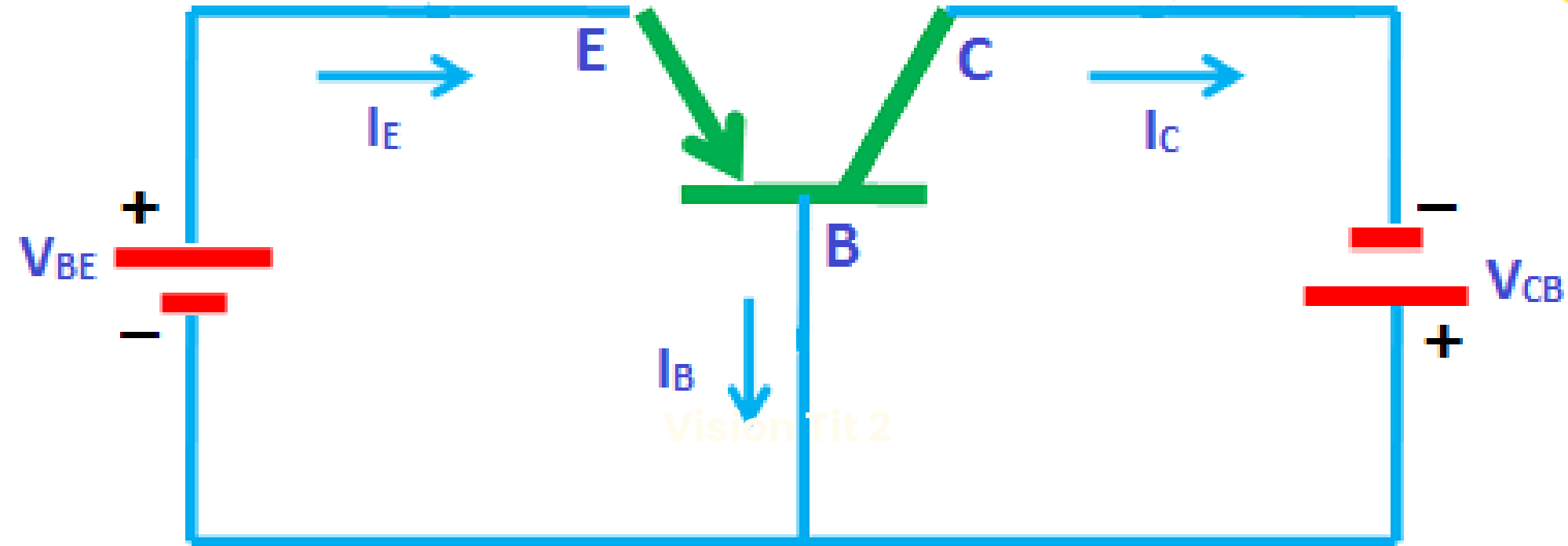




# Types of Transistor Configuration


- We know that transistor has three terminals namely emitter (E), base (B), and collector (C). But to connect a transistor in the circuit, we need four terminals: two terminals for input and other two terminals for output.
- When a transistor is to be connected in a circuit, one terminal is used as the input terminal, the other terminal is used as the output terminal and the third terminal is common to the input and output.
- Depending upon the terminal which is used as a common terminal to the input and output terminals, the transistor can be connected in the following three configurations. They are:
  - ✓ **Common base (CB) configuration**
  - ✓ **Common emitter (CE) configuration**
  - ✓ **Common collector (CC) configuration**



# Common base (CB) configuration

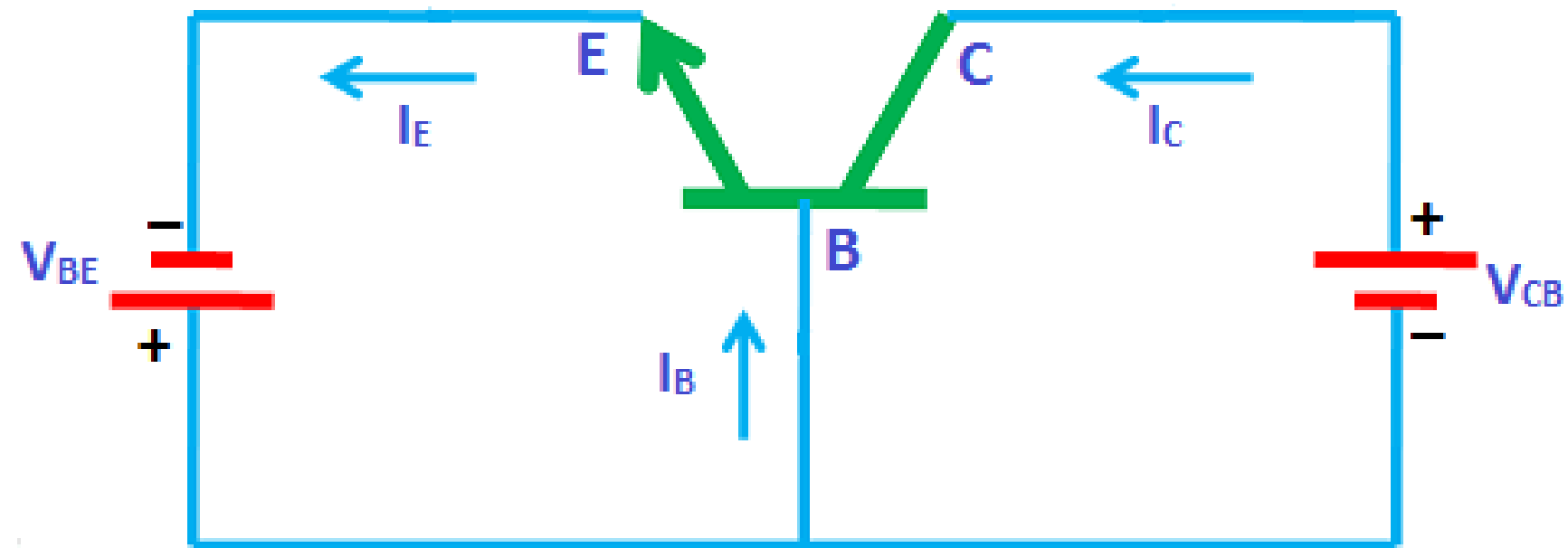


$$I_E = I_B + I_C$$

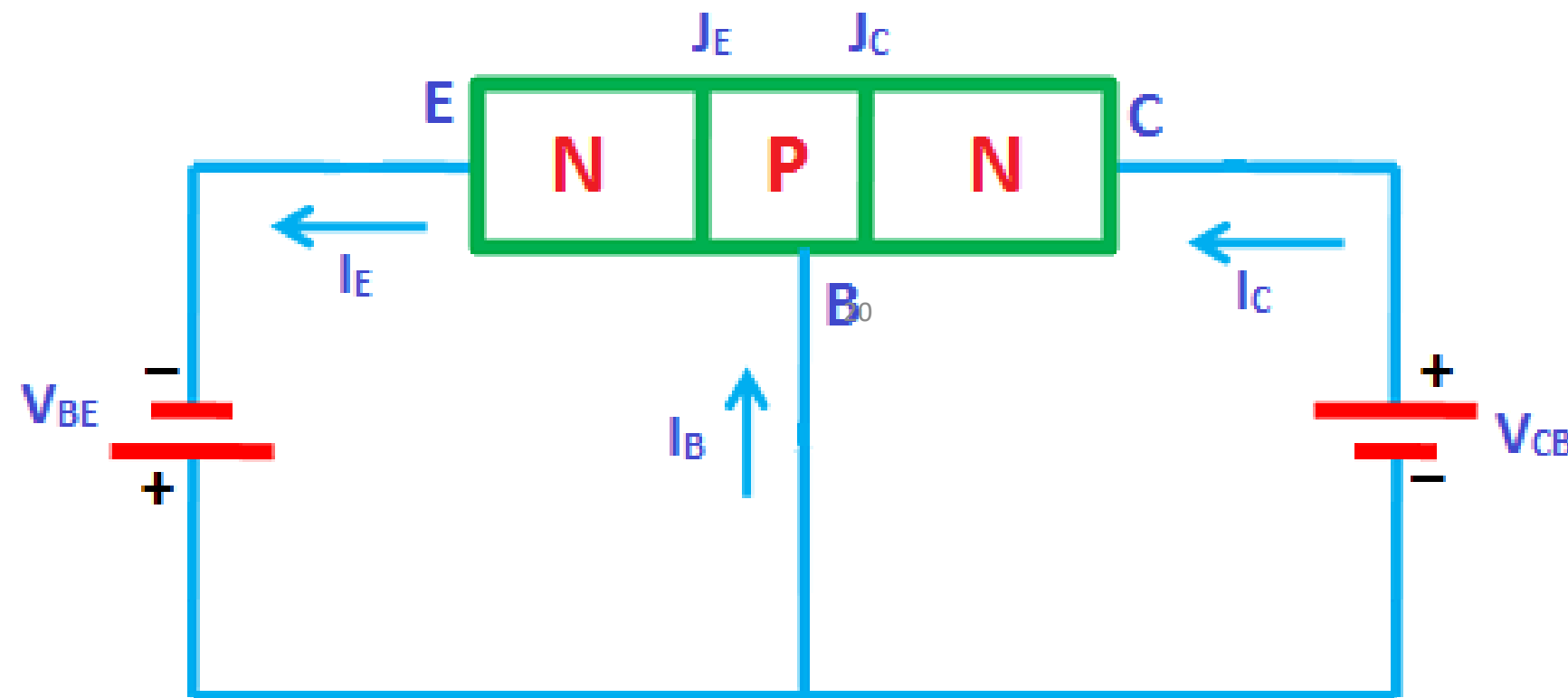


Common base configuration



# Transistor Characteristics

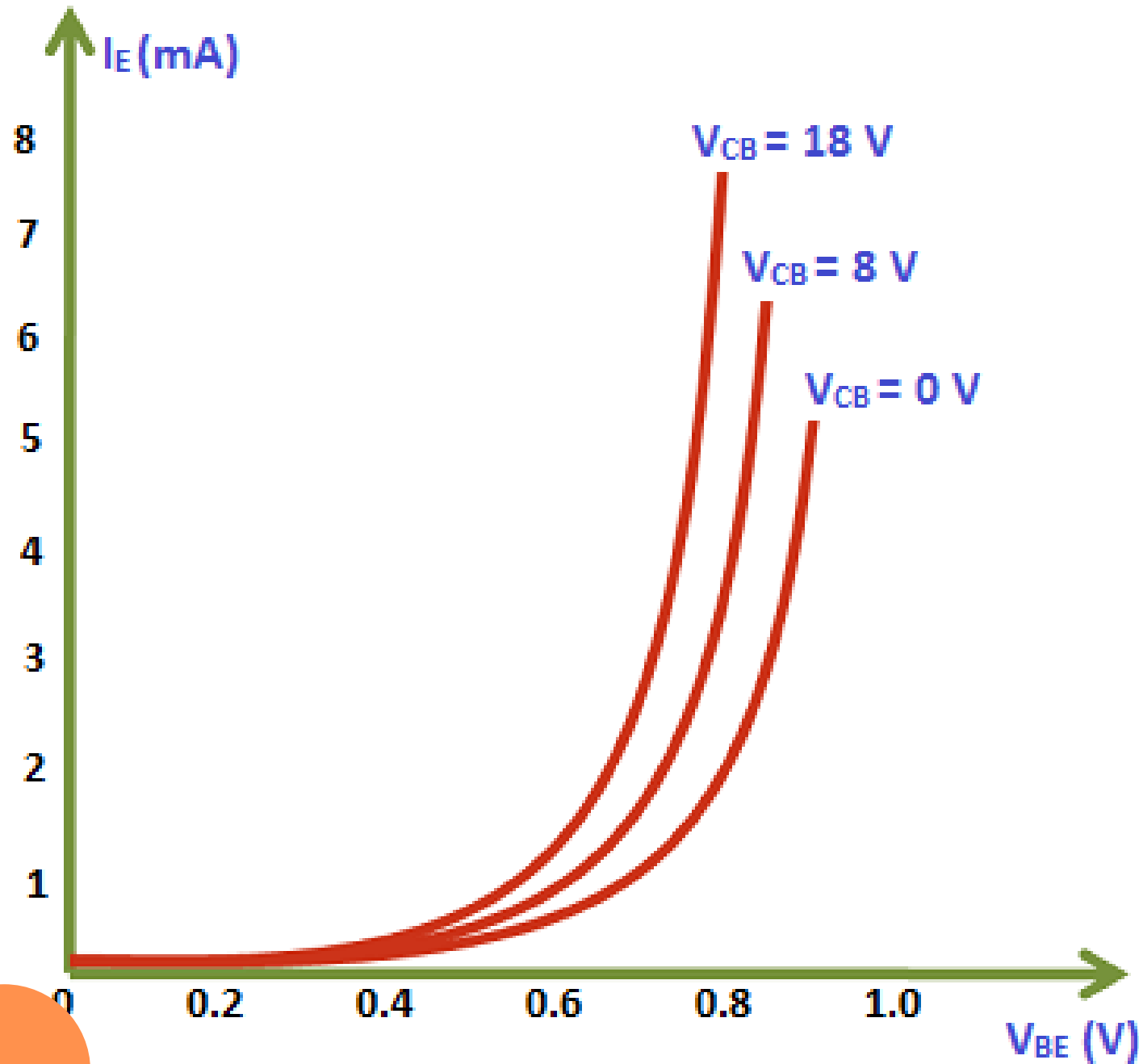

I/p characteristics CB configuration

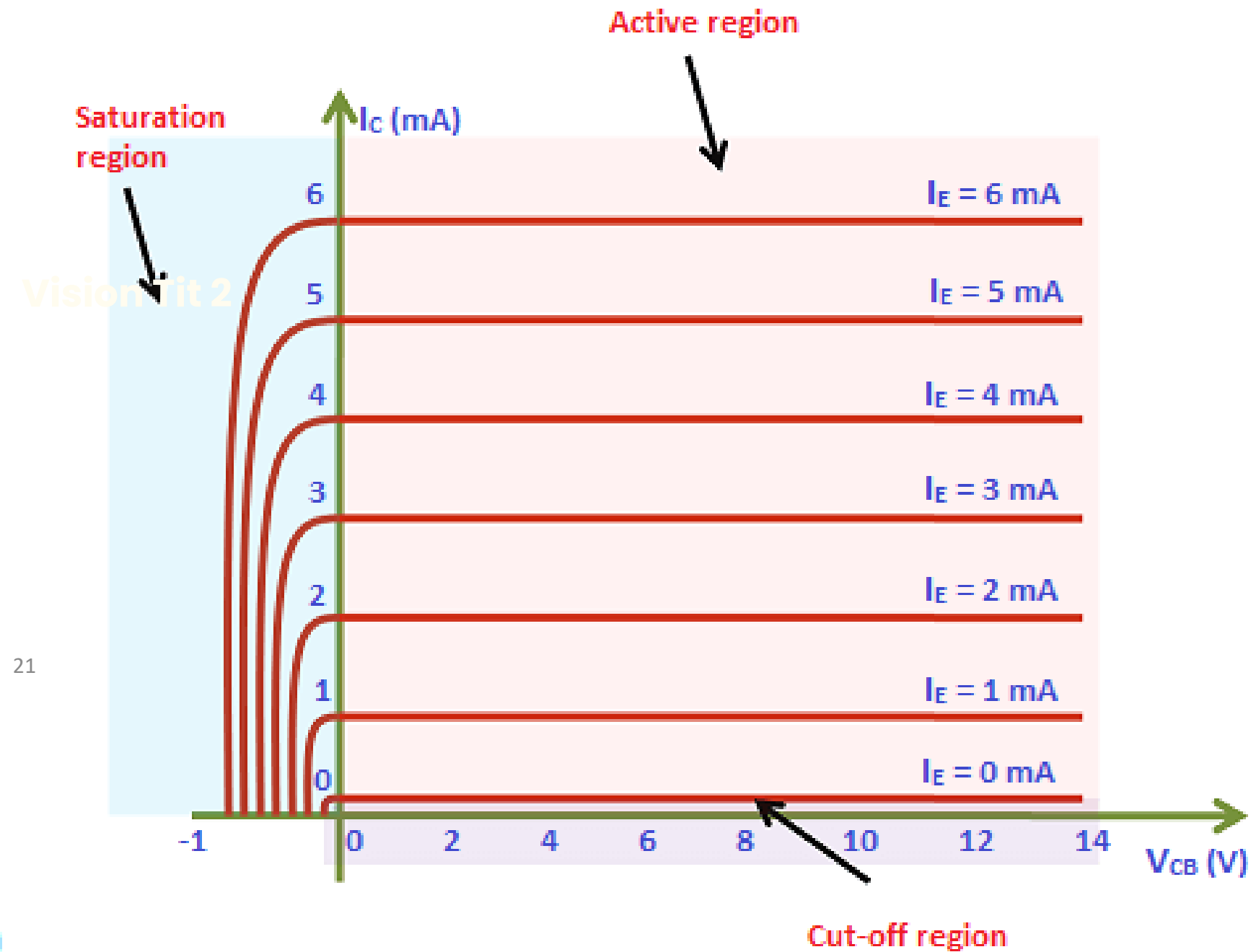

O/P characteristics CB configuration




# Transistor Parameters




Dynamic input resistance ( $r_i$ )	Dynamic output resistance ( $r_o$ )	Current gain ( $\alpha$ )
<p>Dynamic input resistance is defined as the ratio of change in input voltage or emitter voltage (<math>V_{BE}</math>) to the corresponding change in input current or emitter current (<math>I_E</math>), with the output voltage or collector voltage (<math>V_{CB}</math>) kept at constant.</p> $r_i = \frac{\Delta V_{BE}}{\Delta I_E},$ $V_{CB} = \text{Constant}$	<p>Dynamic output resistance is defined as the ratio of change in output voltage or collector voltage (<math>V_{CB}</math>) to the corresponding change in output current or collector current (<math>I_C</math>), with the input current or emitter current (<math>I_E</math>) kept at constant.</p> $r_o = \frac{\Delta V_{CB}}{\Delta I_C},$ $I_E = \text{Constant}$	<p>The current gain of a transistor in CB configuration is defined as the ratio of output current or collector current (<math>I_C</math>) to the input current or emitter current (<math>I_E</math>).</p> $\alpha = \frac{I_C}{I_E}$



# Common Emitter Configuration

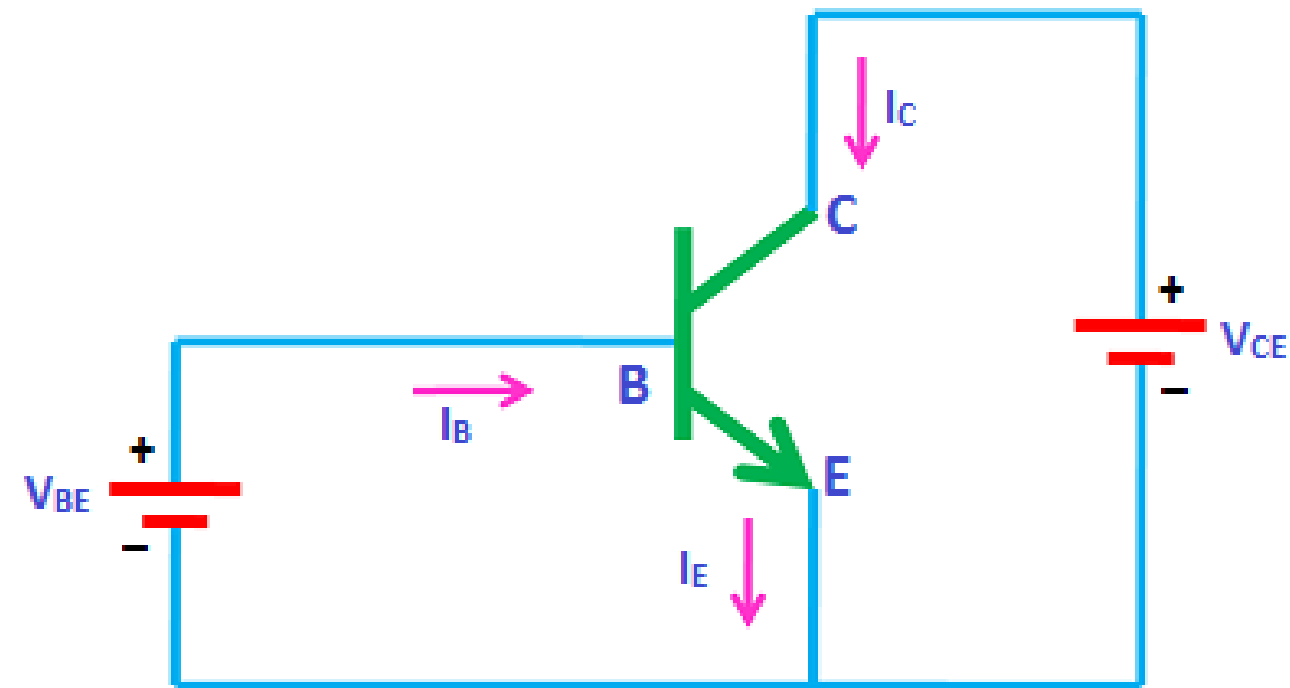


$$I_E = I_B + I_C$$

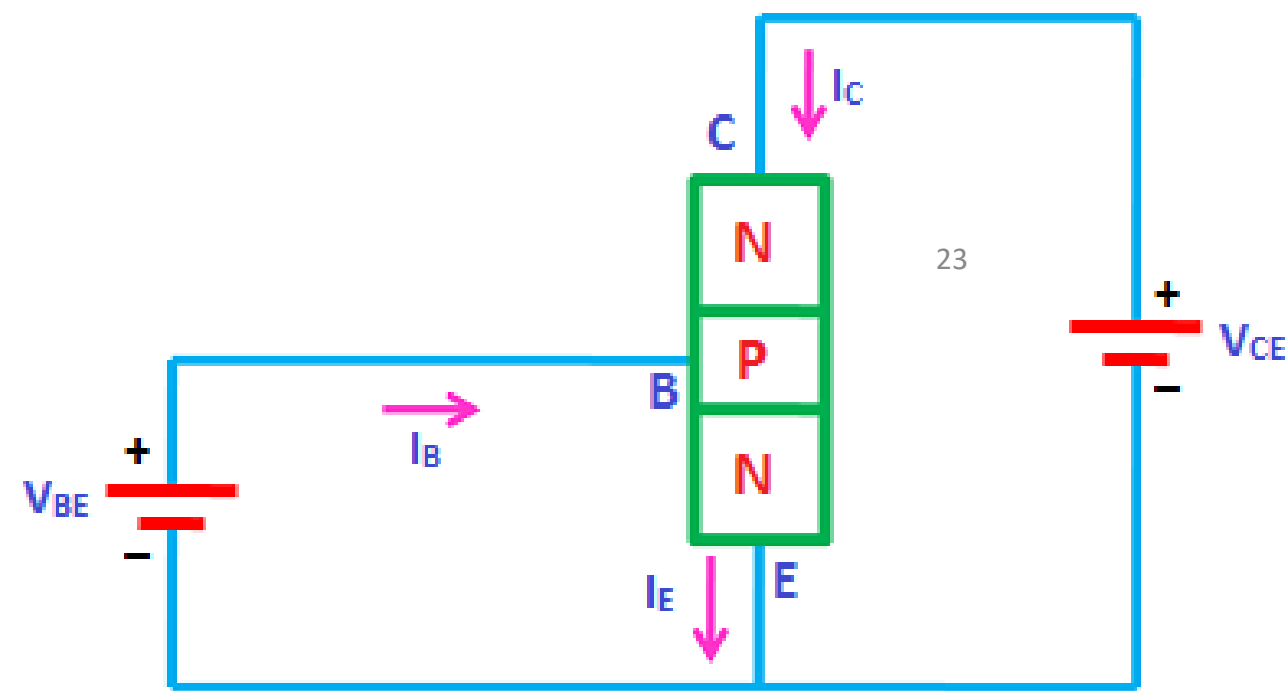

Common emitter configuration




# Transistor Characteristics

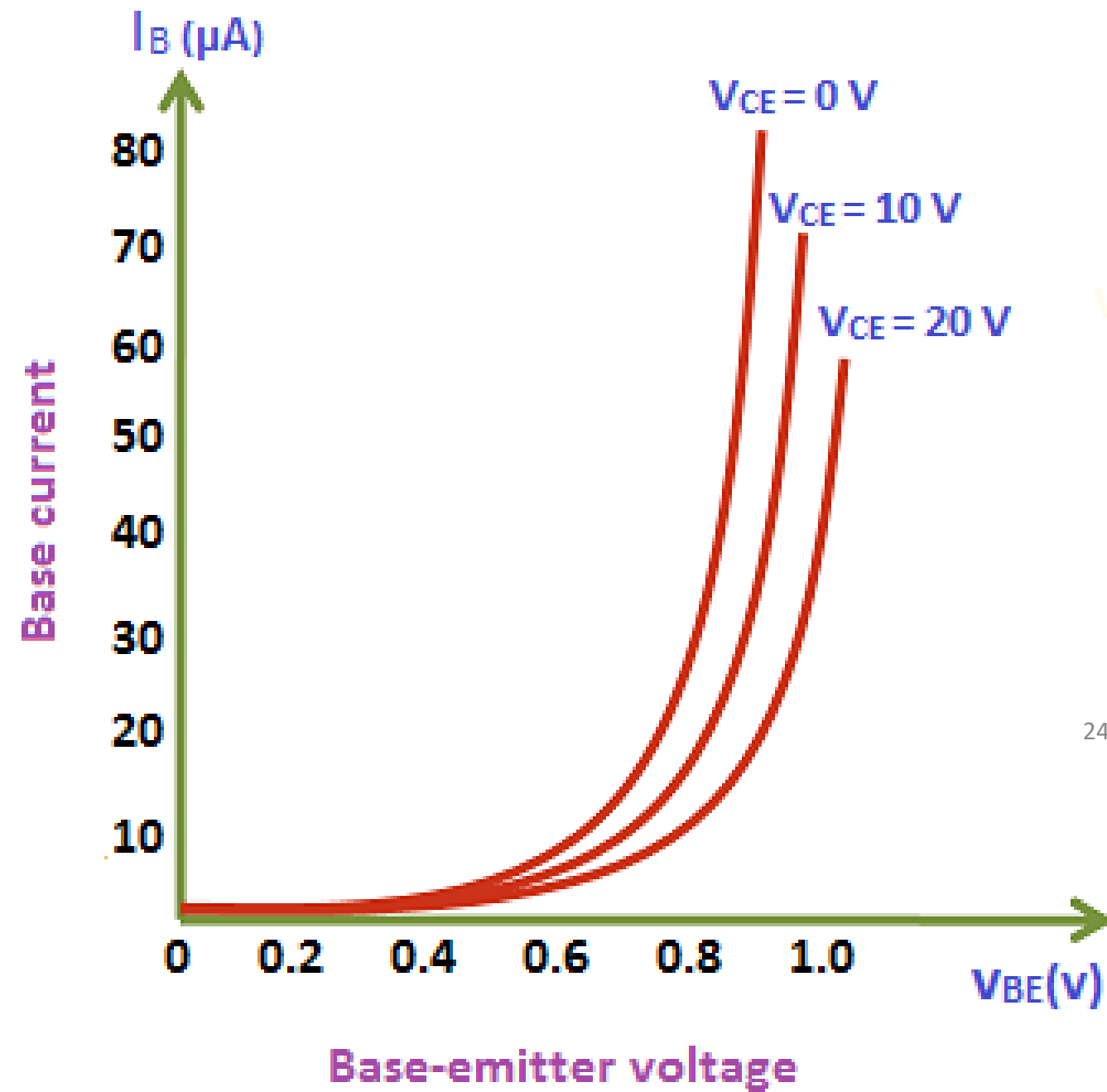

I/P Characteristics CE configuration

24

Vision Tip 2

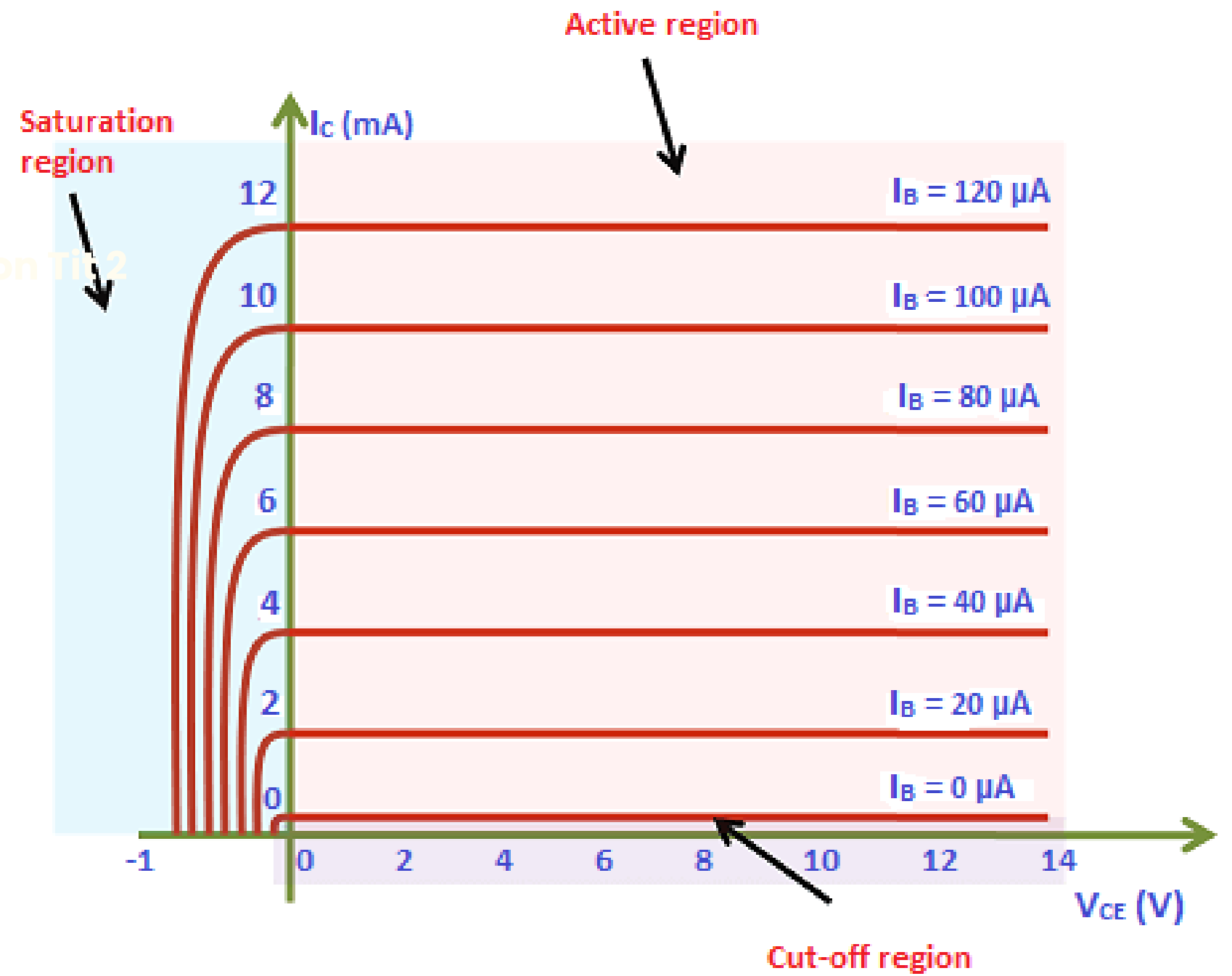

O/P Characteristics CE Configuration







# Transistor Parameters



Dynamic input resistance ( $r_i$ )	Dynamic output resistance ( $r_o$ )	Current gain ( $\alpha$ )
<p>Dynamic input resistance is defined as the ratio of change in input voltage or base voltage (<math>V_{BE}</math>) to the corresponding change in input current or base current (<math>I_B</math>), with the output voltage or collector voltage (<math>V_{CE}</math>) kept at constant.</p> $r_i = \frac{\Delta V_{BE}}{\Delta I_B},$ $V_{CE} = \text{Constant}$	<p>Dynamic output resistance is defined as the ratio of change in output voltage or collector voltage (<math>V_{CE}</math>) to the corresponding change in output current or collector current (<math>I_C</math>), with the input current or base current (<math>I_B</math>) kept at constant.</p> $r_o = \frac{\Delta V_{CE}}{\Delta I_C},$ $I_B = \text{Constant}$	<p>The current gain of a transistor in CE configuration is defined as the ratio of output current or collector current (<math>I_C</math>) to the input current or base current (<math>I_B</math>).</p> $\alpha = \frac{I_C}{I_B}$




# Common Collector Configuration

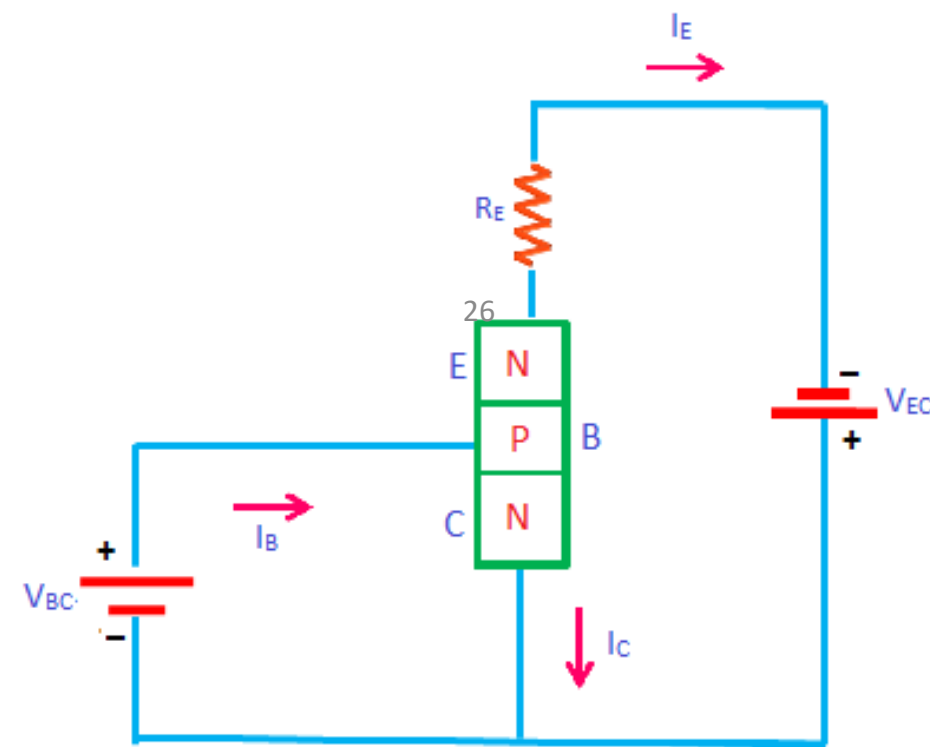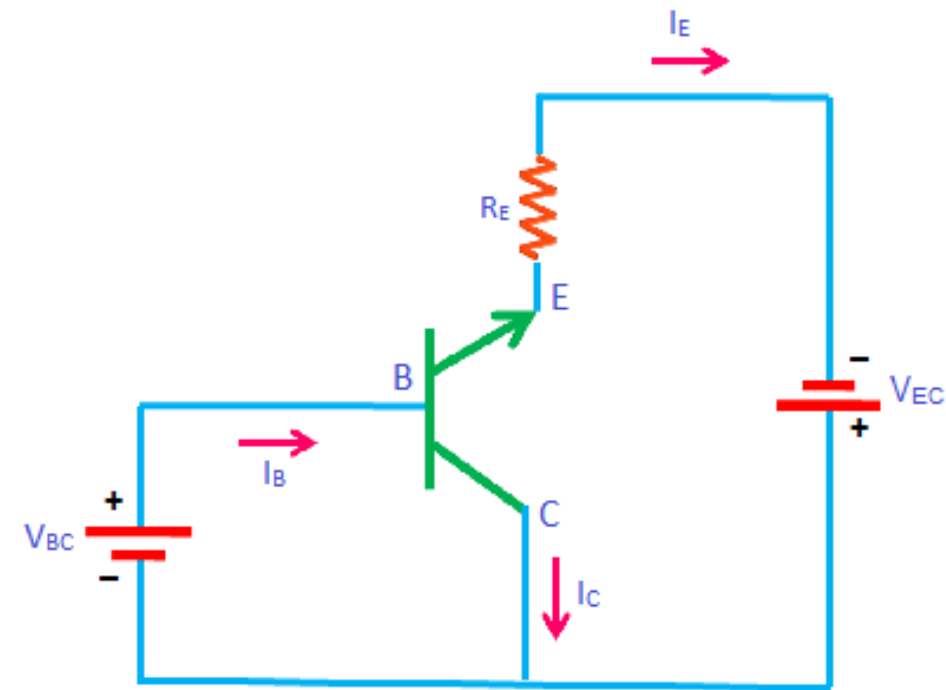


Common collector configuration



# Transistor Characteristics

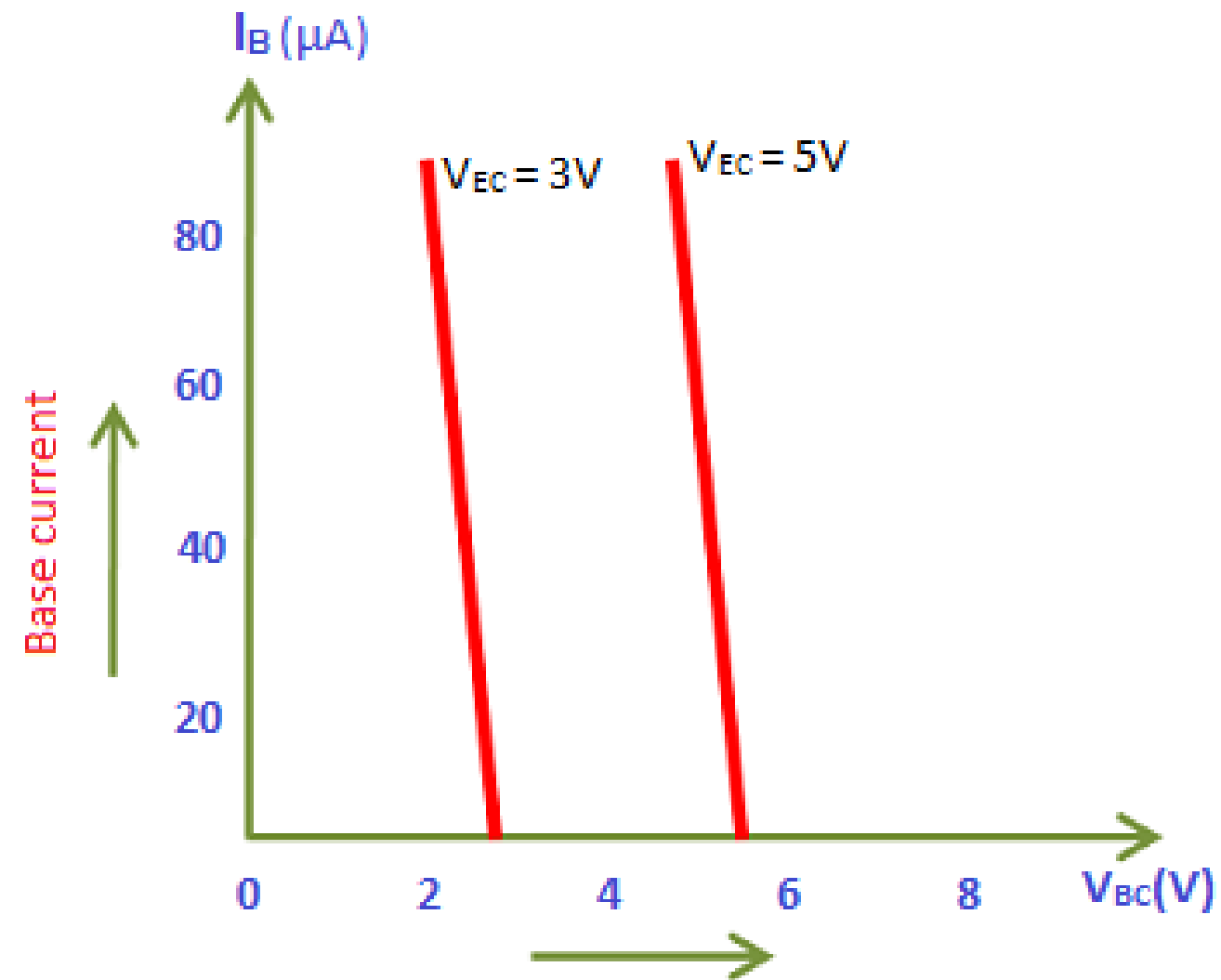

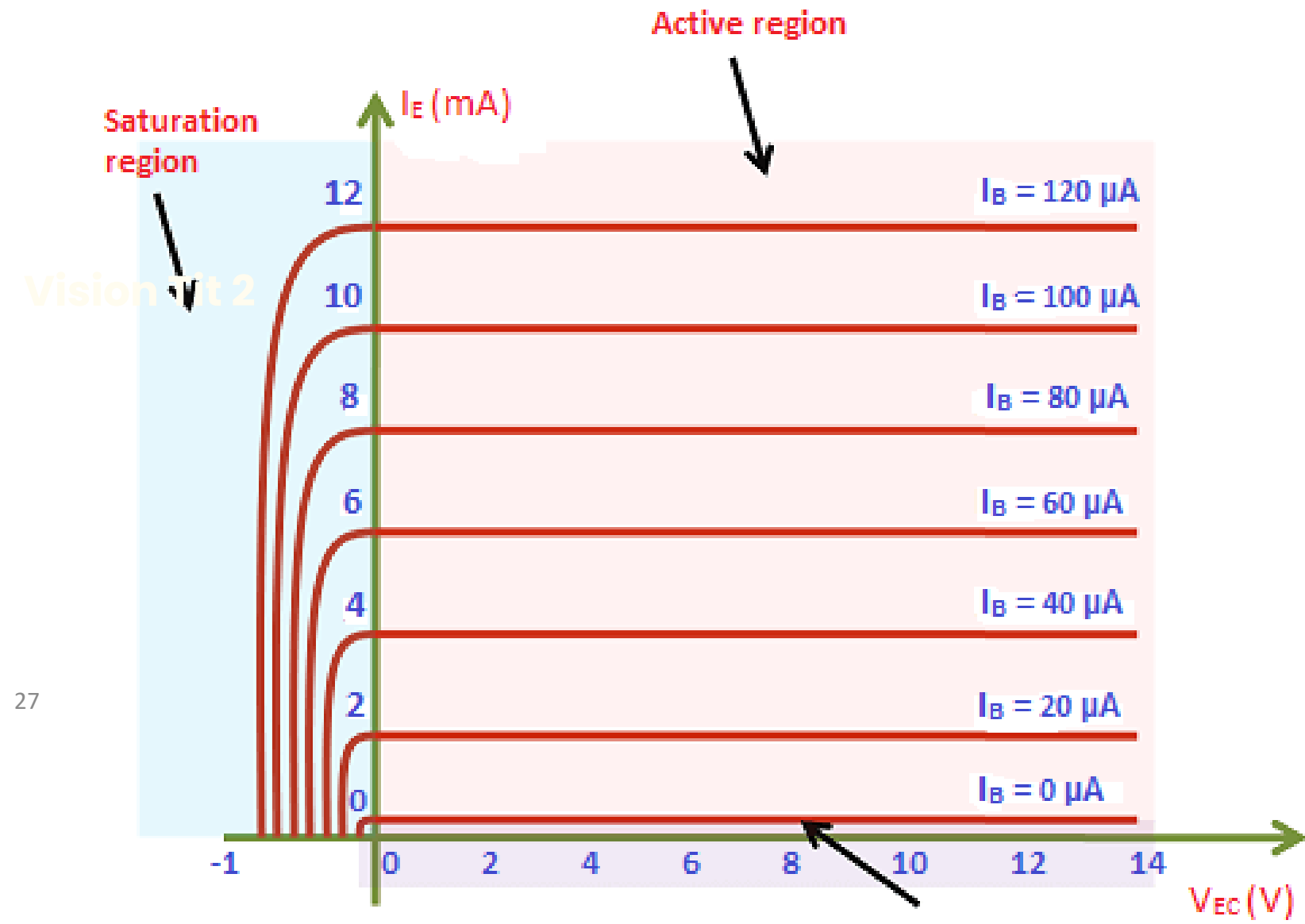Base-collector voltage  
**Input characteristics**



**Output characteristics**



# Transistor Parameters



Dynamic input resistance ( $r_i$ )	Dynamic output resistance ( $r_o$ )	Current gain ( $\alpha$ )
<p>Dynamic input resistance is defined as the ratio of change in input voltage or base voltage (<math>V_{BC}</math>) to the corresponding change in input current or base current (<math>I_B</math>), with the output voltage or emitter voltage (<math>V_{EC}</math>) kept at constant.</p> $r_i = \frac{\Delta V_{BC}}{\Delta I_B},$ $V_{CE} = \text{Constant}$	<p>Dynamic output resistance is defined as the ratio of change in output voltage or emitter voltage (<math>V_{EC}</math>) to the corresponding change in output current or emitter current (<math>I_E</math>), with the input current or base current (<math>I_B</math>) kept at constant.</p> $r_o = \frac{\Delta V_{CE}}{\Delta I_E},$ $I_B = \text{Constant}$	<p>The current gain of a transistor in CE configuration is defined as the ratio of output current or collector current (<math>I_C</math>) to the input current or base current (<math>I_B</math>).</p> $\gamma = \frac{\Delta I_E}{\Delta I_B}$