



SNS COLLEGE OF TECHNOLOGY

(AN AUTONOMOUS INSTITUTION)

Approved by AICTE & Affiliated to Anna University
Accredited by NBA & Accredited by NAAC with 'A+' Grade,
Recognized by UGC saravanampatti (post), Coimbatore-641035.



Department of Biomedical Engineering

Course Name: **23BMB101-Electron Devices and Circuits**

I Year : II Semester

Unit II -Transistors

Topic : Unijunction¹ Transistors




INTRODUCTION



- Unijunction Transistor is a semiconductor switching device having 2 layers and 3 terminals and is abbreviated as UJT.
- It is called so because of the presence of only one junction.
- It has the ability to limit large power with a small input signal and is also known as a double base diode.
- UJT is a device that possesses negative resistance characteristic that means its emitter current rises regeneratively when triggered. Thus an emitter supply is needed in order to restrict it.




Construction of Unijunction Transistors

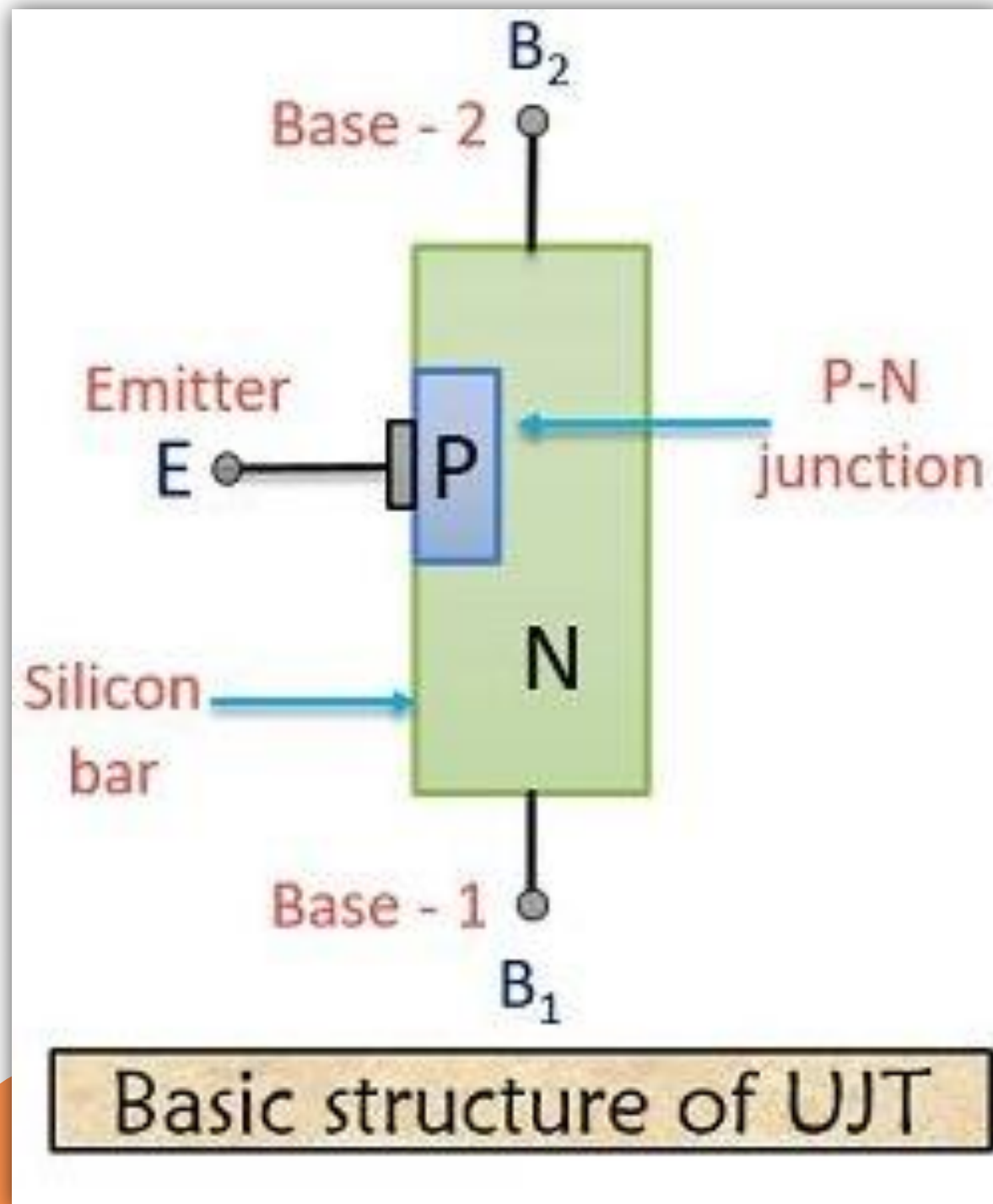

- Its structure is almost similar to an N-channel JFET. UJT consists of a lightly doped N-type silicon bar in which a P-type material is diffused thus producing PN junction.
- Due to the existence of a single PN junction, it is termed as a Unijunction device.
- It consists of two ohmic contacts at the end of the bar which is labelled as base 1 (B1) and base 2 (B2).
- Emitter region is closer to B2 in order to have the optimum electrical characteristic.




Basic arrangement of a UJT

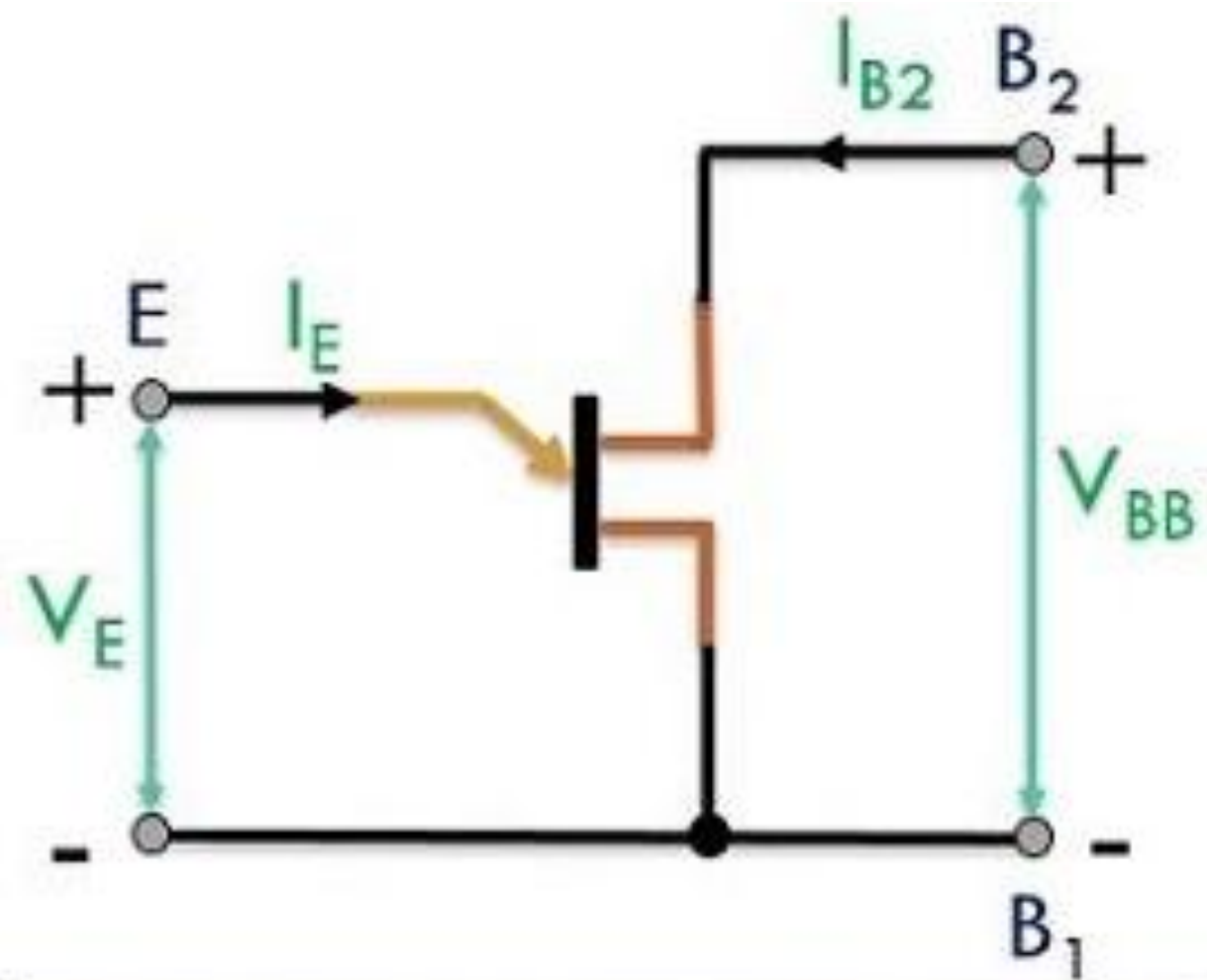


Basic UJT arrangement

Visid

4

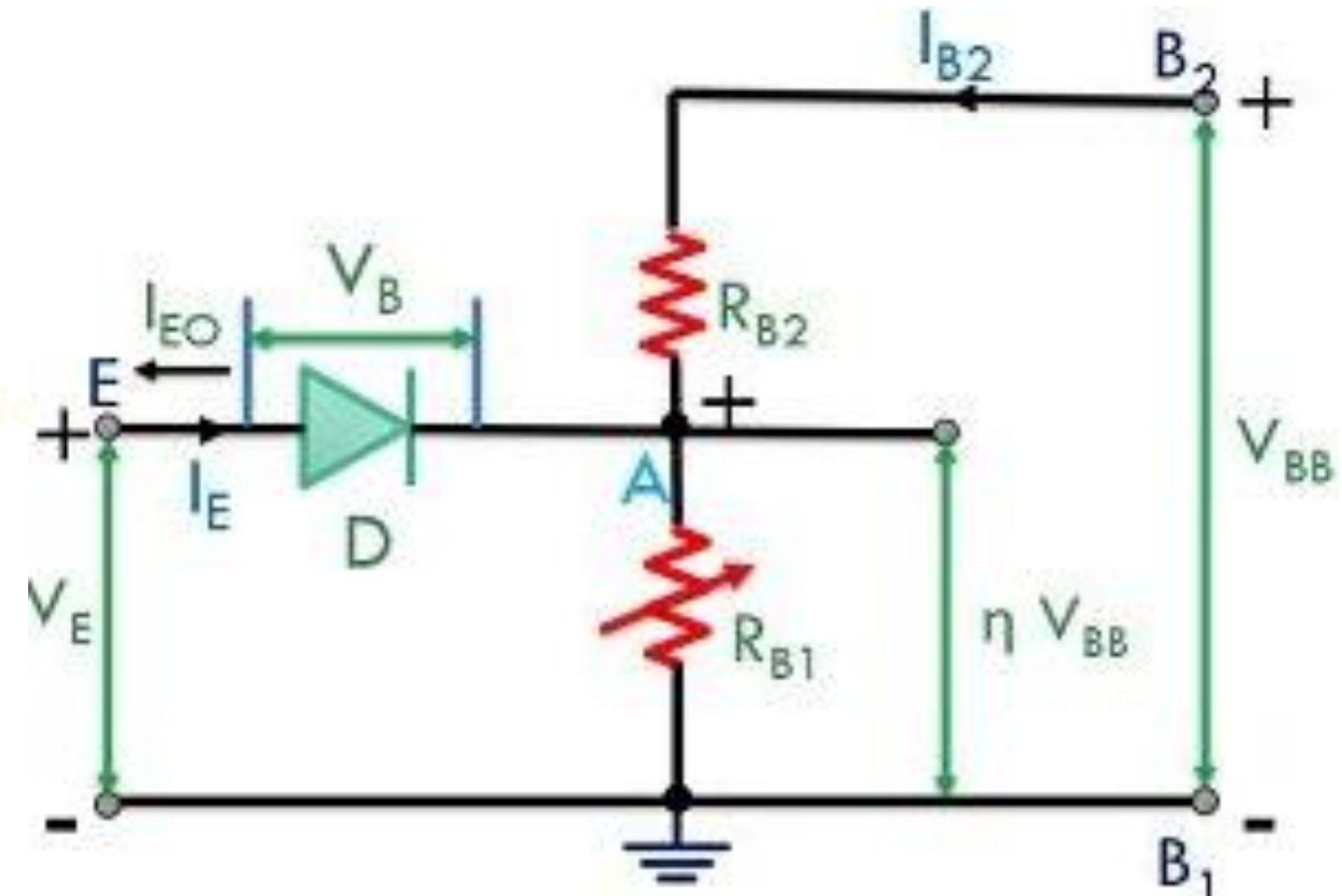

Equivalent circuit of UJT

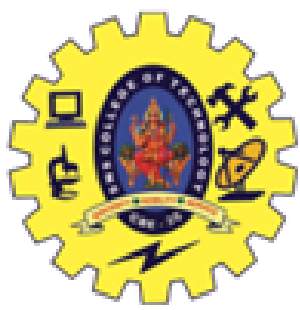

Working of a UJT

- The two resistors of the circuit together constitute the total resistance which is the resistance between B2 and B1 where the emitter is kept open is known as **Interbase resistance R_{BB}** .

Vision Tit 2

$$R_{BB} = R_{B1} + R_{B2}$$

- Normally the value of R_{B1} is greater than that of R_{B2} .

$$V_A = V_{BB} \times \frac{R_{B1}}{R_{B1} + R_{B2}}$$

$$V_A = \eta V_{BB}, \quad \text{where } \eta \text{ is the intrinsic standoff ratio}$$



Working of a UJT

- Consider a condition when there is no emitter potential supplied to the circuit. In such a case the diode gets reverse biased.

$$V_A + V_B = \eta V_{BB} + V_B$$

Vision Tit 2

- On proceeding further, if the emitter potential is increased more, the diode will now get forward biased. The emitter potential that puts the diode in forward biased condition is known as **peak point voltage** and is denoted by V_p .
- The minimum value of I_E to trigger the device is known as **peak point current** of the emitter terminal denoted by I_p .

6



Characteristics of Unijunction transistor

