



SNS COLLEGE OF TECHNOLOGY

(AN AUTONOMOUS INSTITUTION)

Approved by AICTE & Affiliated to Anna University
Accredited by NBA & Accredited by NAAC with 'A+' Grade,
Recognized by UGC saravanampatti (post), Coimbatore-641035.



Department of Biomedical Engineering

Course Name: **23BMB101-Electron Devices and Circuits**

I Year : II Semester

Unit II -Transistors

Topic : Differential Amplifier¹



INTRODUCTION





- The amplifier which amplifies the difference between two input signals is called as Differential amplifier.
- The differential amplifier configuration is very much popular and it is used in variety of analog circuits. It is basic building in operational amplifiers.
- It has both good bias stability and good voltage gain without the use of large bypass capacitors.
- The circuit is also known as an emitter-coupled amplifier, because the transistors are coupled at the emitter terminals.

2



Differential Amplifier

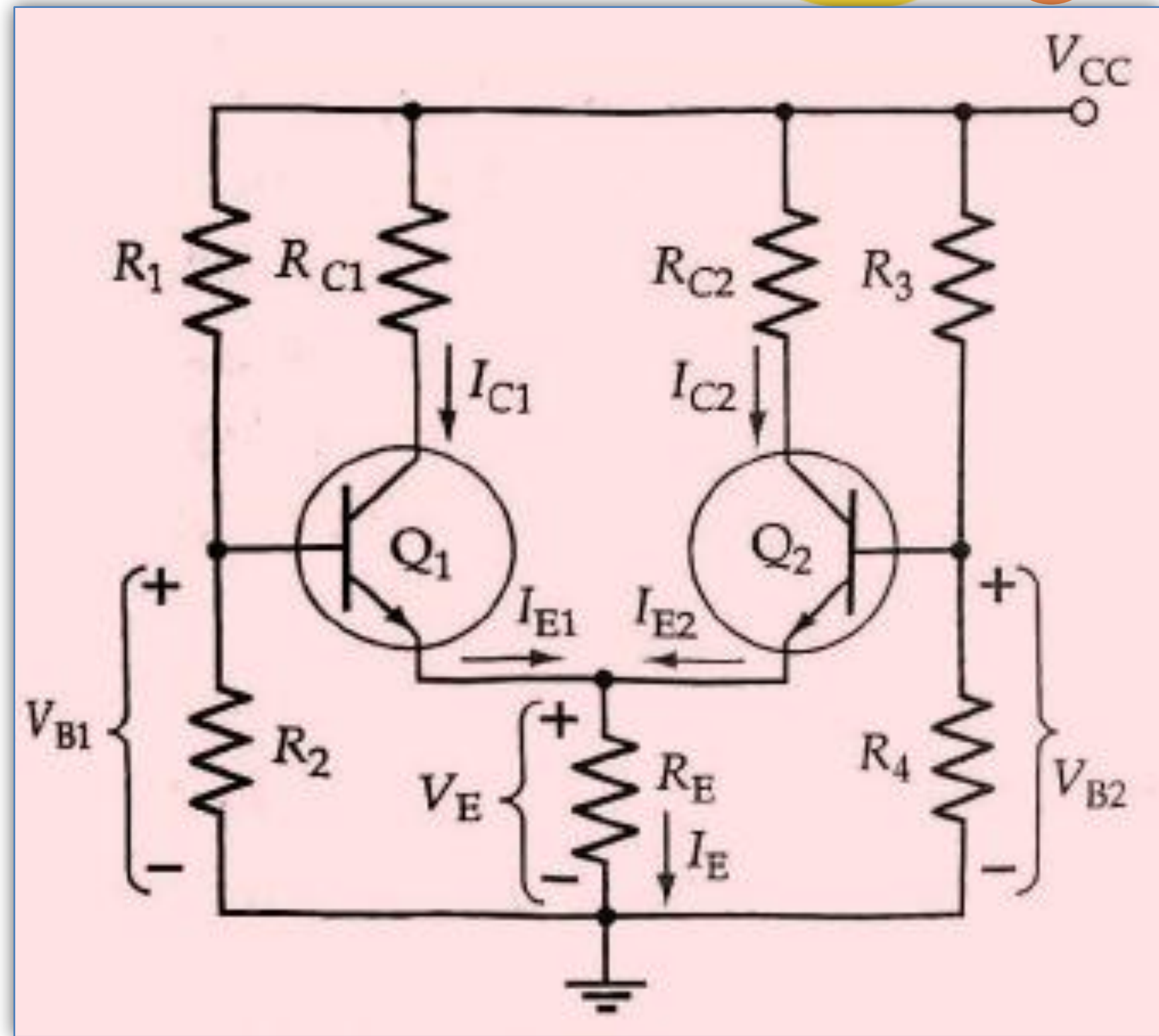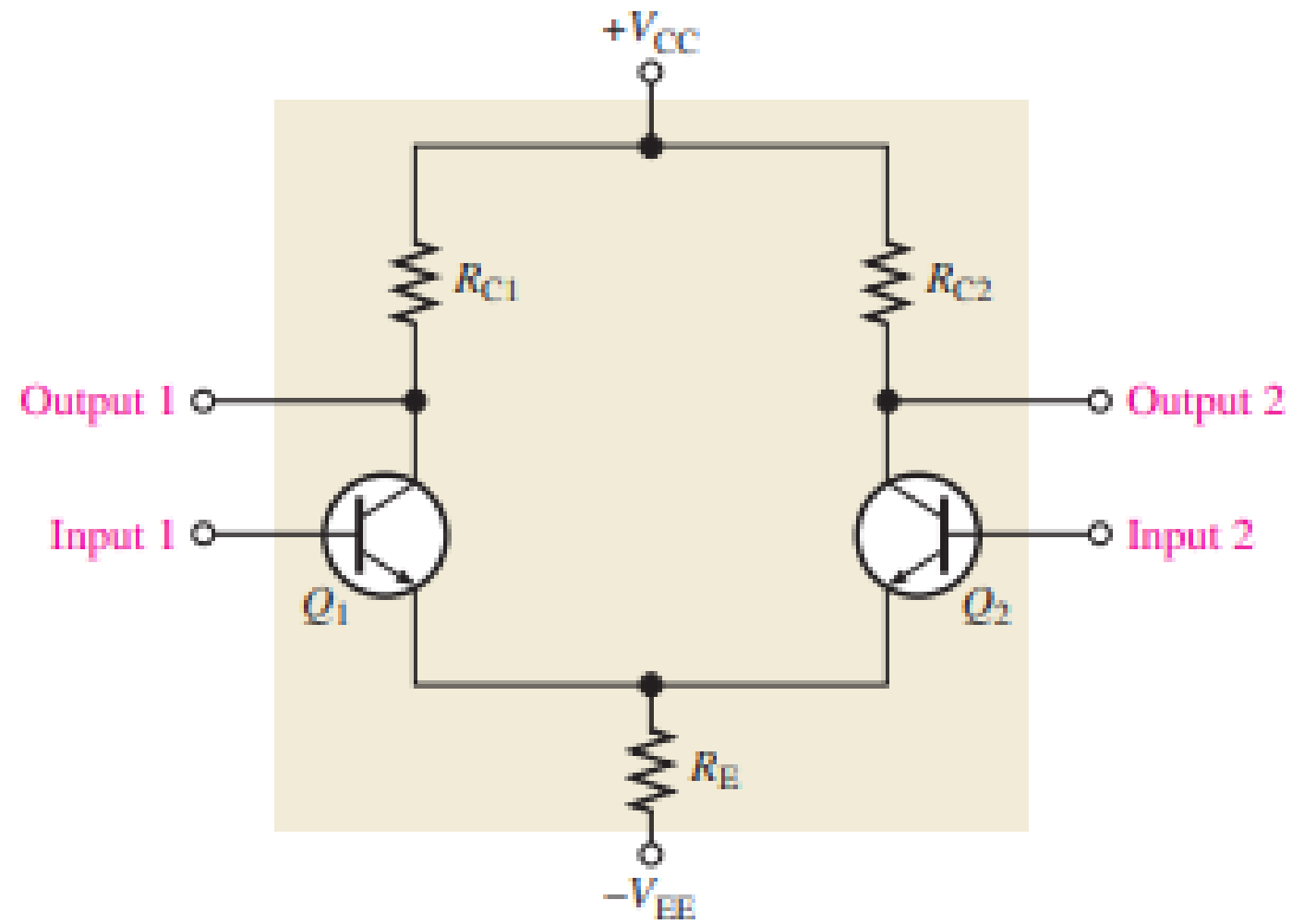



Differential Amplifier



- Fig shows that a basic differential amplifier circuit consists of two voltage-divider bias circuits with a single emitter resistor. The circuit is also known as an emitter-coupled amplifier, because the transistors are coupled at the emitter terminals.
- If transistors Q_1 and Q_2 are assumed to be identical in all respects, and if $V_{B1} = V_{B2}$, then the emitter currents are equal and the total emitter current is

$$I_E = I_{E1} + I_{E2}$$

$$V_E = V_B - V_{BE}$$

4

$$I_E = \frac{V_B - V_{BE}}{R_E}$$

$$I_{E1} = I_{E2} = \frac{I_E}{2}$$



Differential Amplifier




- Like the emitter current in a single-transistor voltage-divider bias circuit, I_E in the differential amplifier remains virtually constant regardless of the transistor h_{FE} value.
- As a result, I_{E1} , I_{E2} , I_{C1} and I_{C2} all remain substantially constant, and the constant collector current levels keep V_{c1} and V_{c2} stable.
- So, the differential amplifier has the same excellent bias stability as a single transistor voltage-divider bias circuit.


5




Differential Amplifier

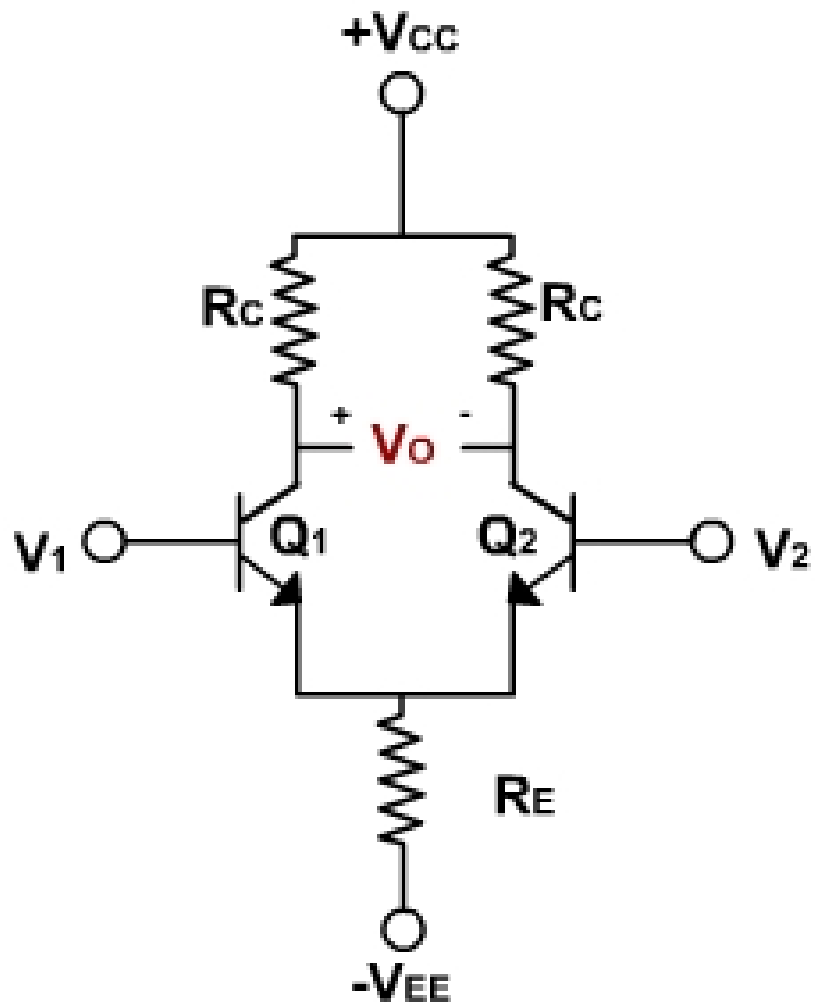

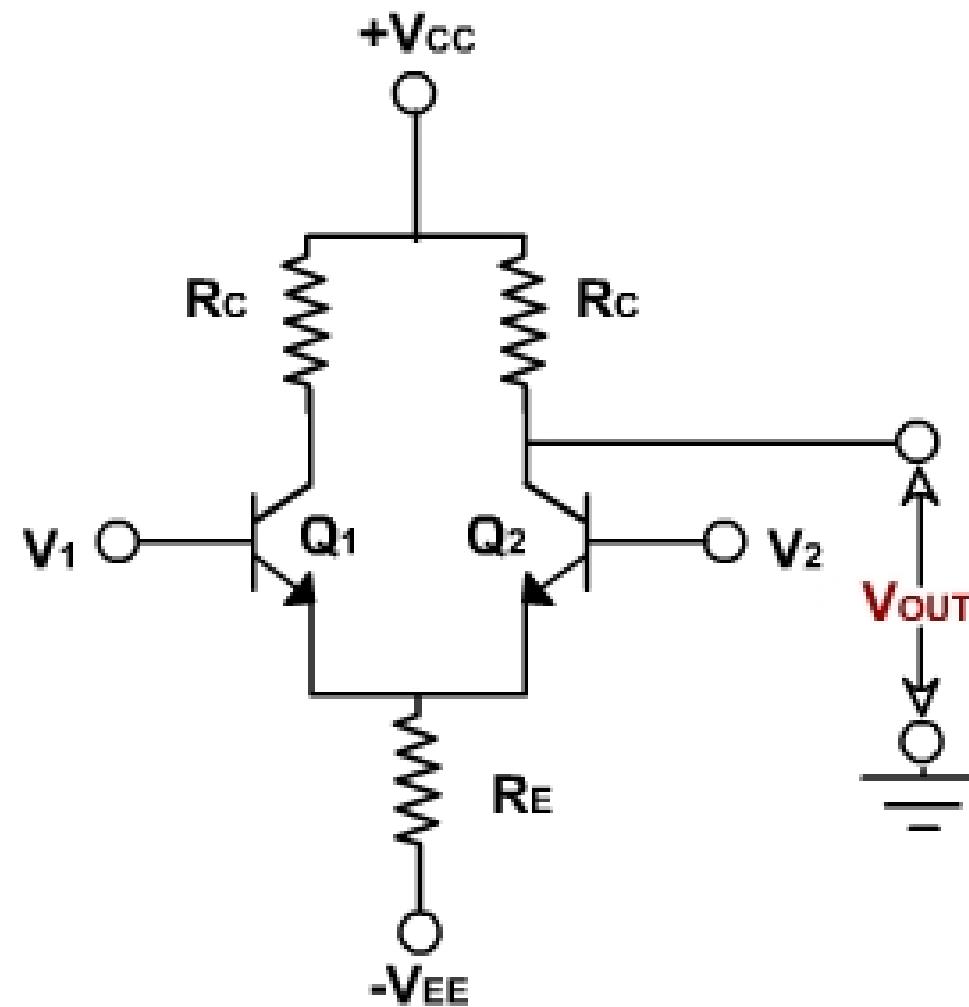
Dual input, balanced output differential amplifier.



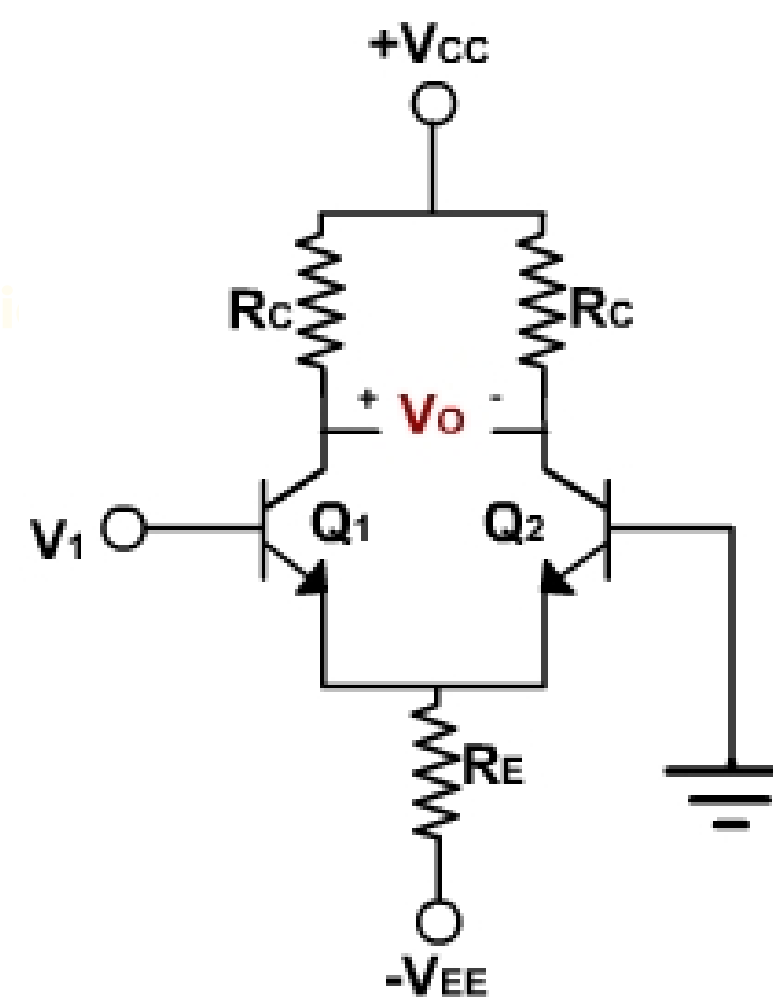Dual input, unbalanced output differential amplifier.



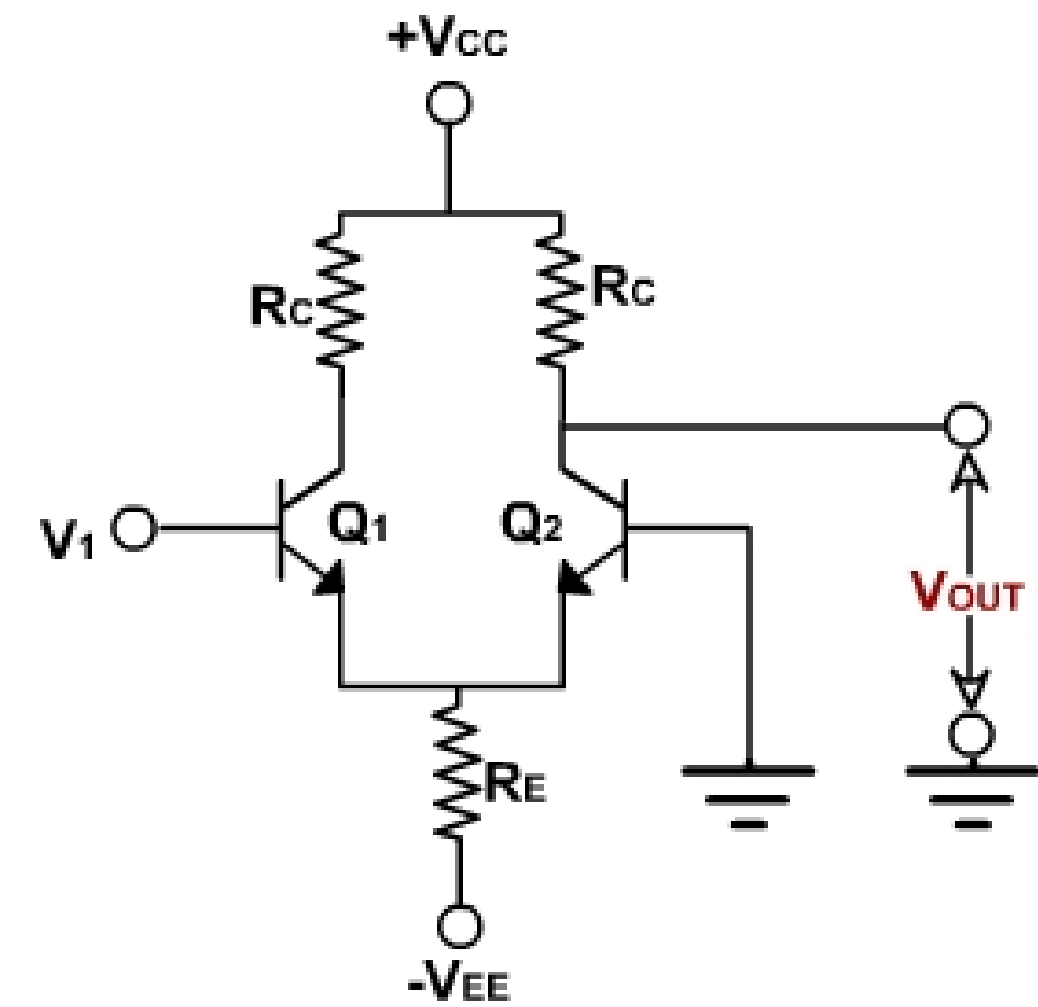Single input balanced output differential amplifier



Single input unbalanced output differential amplifier.



Differential Mode of operation

- In differential mode, the two input signals are equal in magnitude but opposite in phase, the differential input voltage V_d is,


$$\text{➤ } V_d = V_1 - V_2 = V_{in}/2 - (-V_{in}/2) = V_{in}$$

- Hence the differential gain is given by,

$$\text{➤ } A_d = V_{out}/V_d = V_{out}/V_{in}$$

- So,

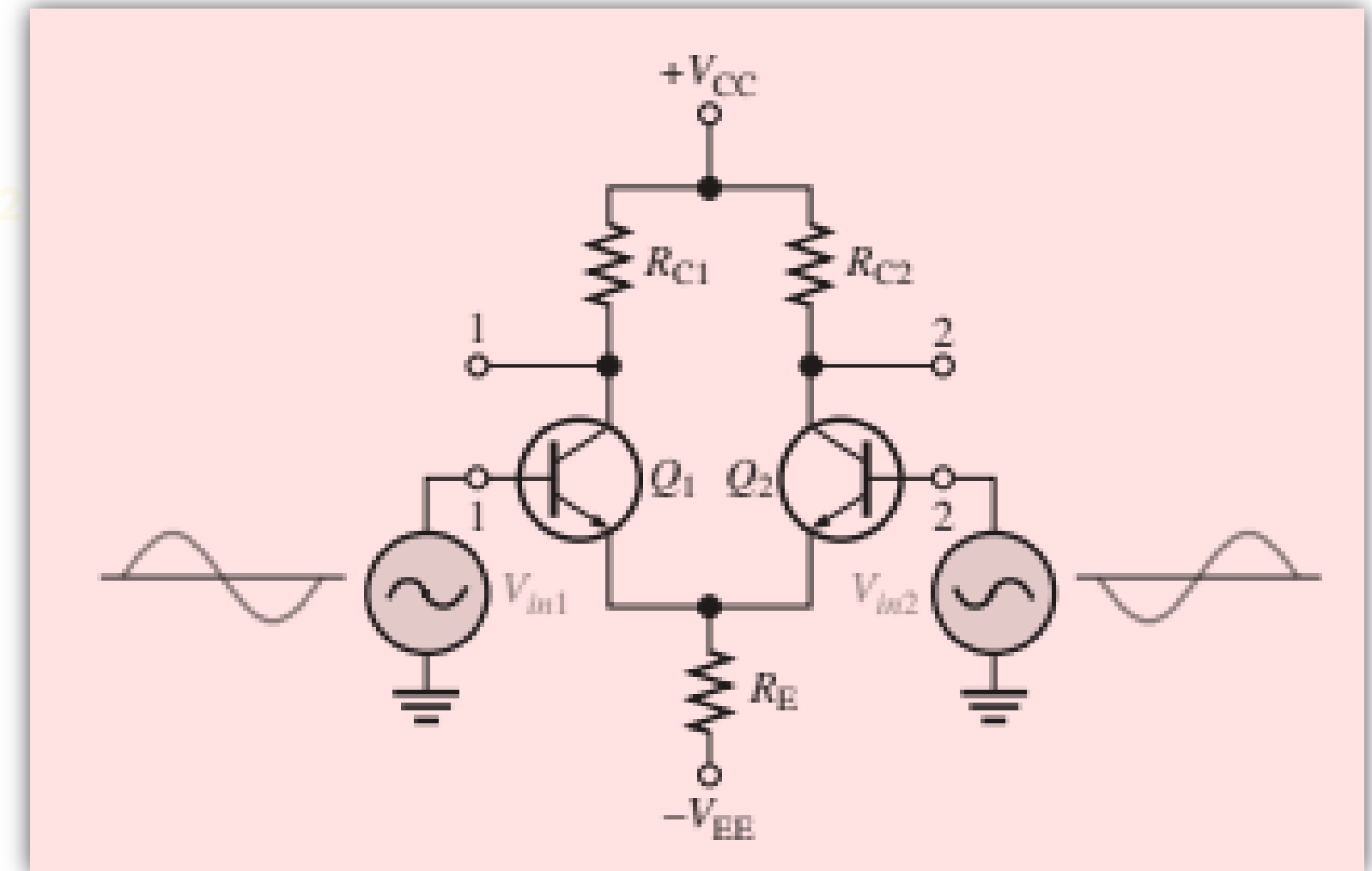
$$\text{➤ } A_d = -h_{fe} * R_c / (2(h_{ie} + R_s))$$





Common Mode of operation

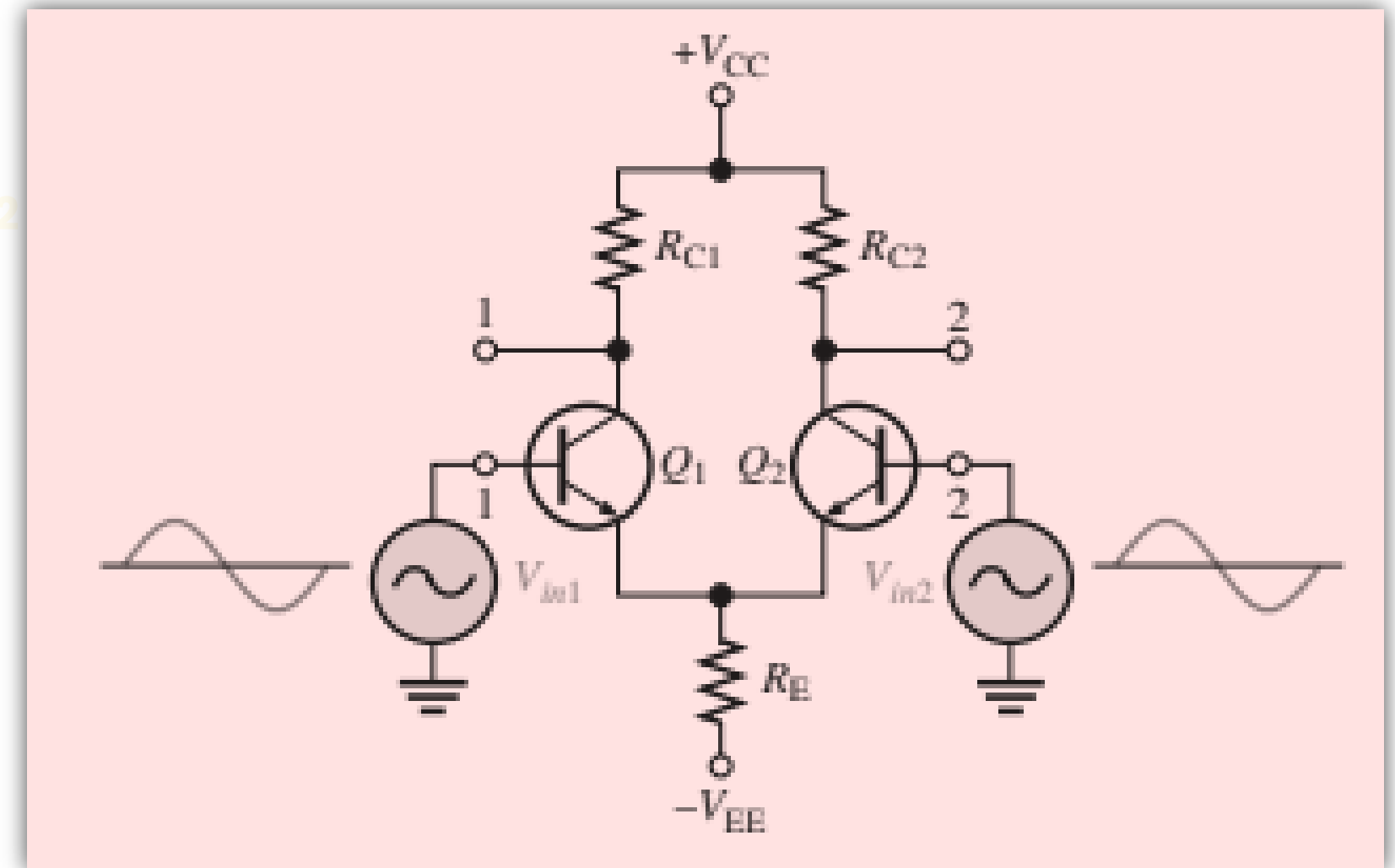- One of the most important aspects of the operation of a diff-amp can be seen by considering the common-mode condition where two signal voltages of the same phase, frequency, and amplitude are applied to the two inputs.
- When the input signals are applied to both inputs, the outputs are superimposed and they cancel, resulting in a zero output voltage.



This action is called **common-mode rejection**.



Common Mode of operation

- In common mode differential amplifier mode, the two inputs are of same magnitude and in phase, so we have,

$$\checkmark V_1 = V_2 = V_{in}$$

- The common mode signal V_{cm} is the average of the two input signals i.e,


$$\checkmark V_{cm} = (V_1 + V_2) / 2 = (V_{in} + V_{in}) / 2 = V_{in}$$

- The output voltage in common mode is given by,

$$\checkmark V_{out} = A_{cm} * V_{in}$$

$$\checkmark \text{or, } A_{cm} = V_{out} / V_{in}$$

Vision Tit 2

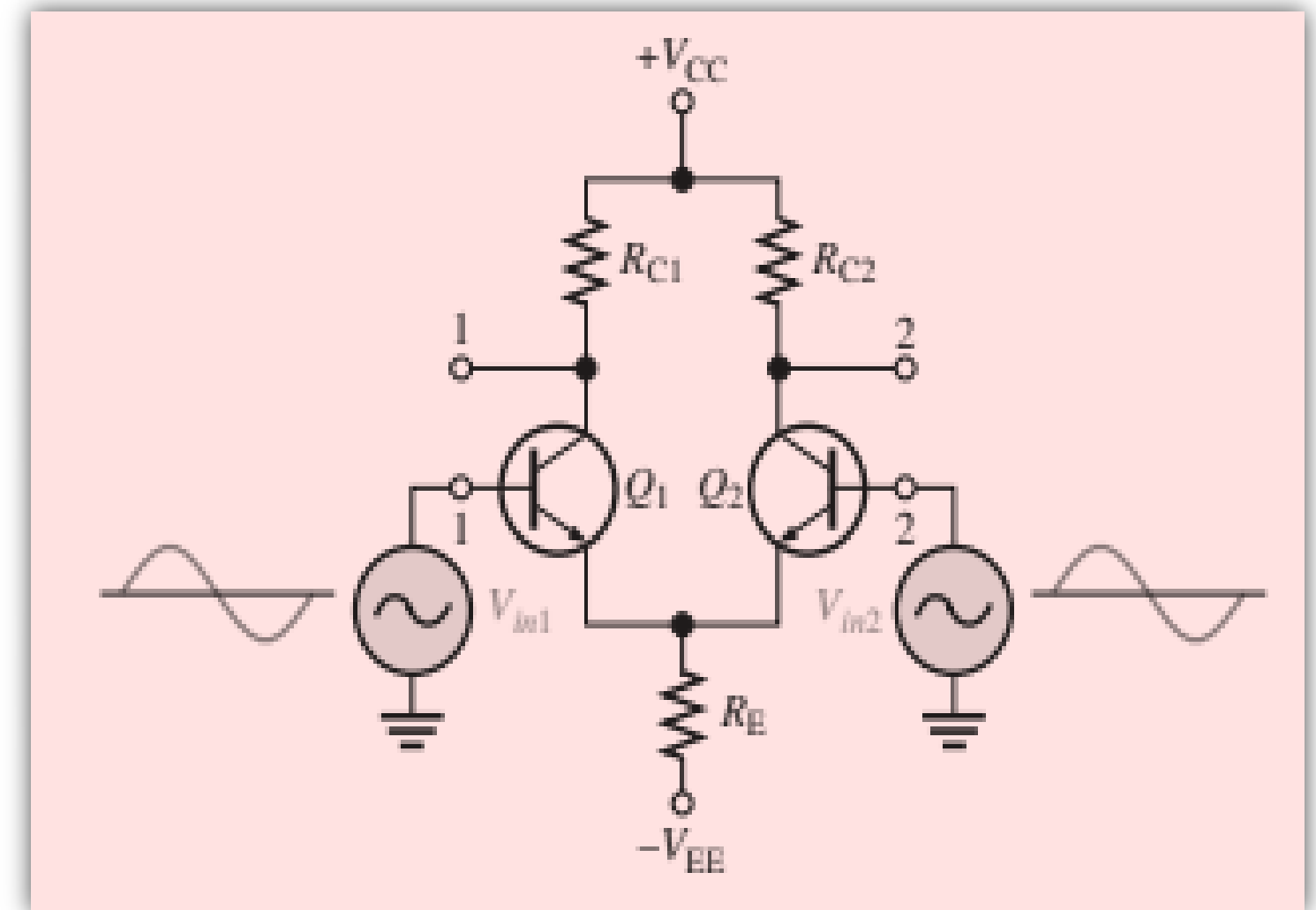



Common-Mode Rejection Ratio



- Unwanted signals (noise) appearing with the same polarity on both input lines are essentially cancelled by the diff-amp and do not appear on the outputs.
- The measure of an amplifier's ability to reject common-mode signals is a parameter called the **CMRR (Common Mode Rejection Ratio)**.
- Ideally, a diff-amp provides a very high gain for desired signals (differential) and zero gain for common-mode signals. . The higher the differential gain with respect to the common-mode gain, the better the performance of the diff-amp in terms of rejection of common-mode signals.
- This suggests that a good measure of the diff-amp's performance in rejecting unwanted common-mode signals is the ratio of the differential voltage gain $A_{v(d)}$ to the common-mode gain, A_{cm}

$$\text{CMRR} = \frac{A_{v(d)}}{A_{cm}}$$