



# SNS COLLEGE OF TECHNOLOGY

## (AN AUTONOMOUS INSTITUTION)

Approved by AICTE & Affiliated to Anna University  
Accredited by NBA & Accredited by NAAC with 'A+' Grade,  
Recognized by UGC saravanampatti (post), Coimbatore-641035.



## Department of Biomedical Engineering

Course Name: **23BMB101-Electron Devices and Circuits**

I Year : II Semester


Unit IV – **Power Amplifiers & Switching Circuits**

Topic : Multivibrators - Astable<sup>1</sup>


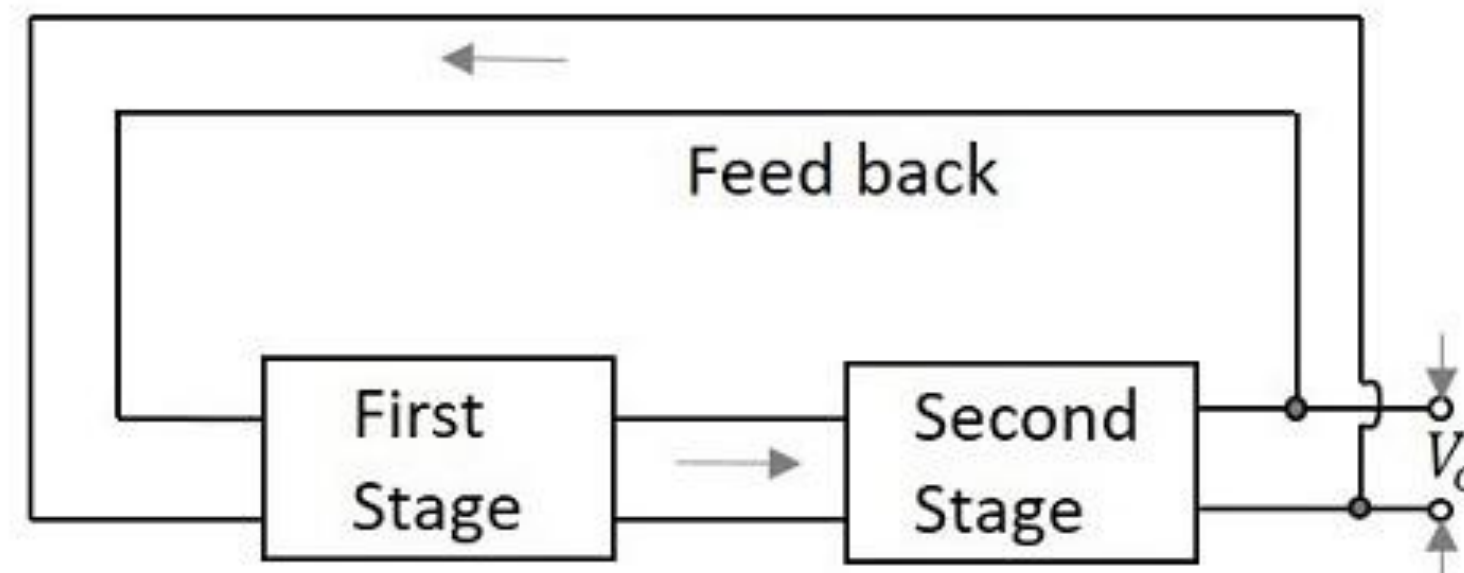
# INTRODUCTION

- A MULTIVIBRATOR is an electronic circuit that generates square, rectangular, pulse waveforms, also called nonlinear oscillators or function generators.
- Multivibrator is basically a two amplifier circuits arranged with regenerative feedback.
- A Multivibrator is a two-stage resistance coupled amplifier with positive feedback from the output of one amplifier to the input of the other.
- Two transistors are connected in feedback so that one controls the state of the other. Hence the ON and OFF states of the whole circuit, and the time periods for which the transistors are driven into saturation or cut off are controlled by the conditions of the circuit.





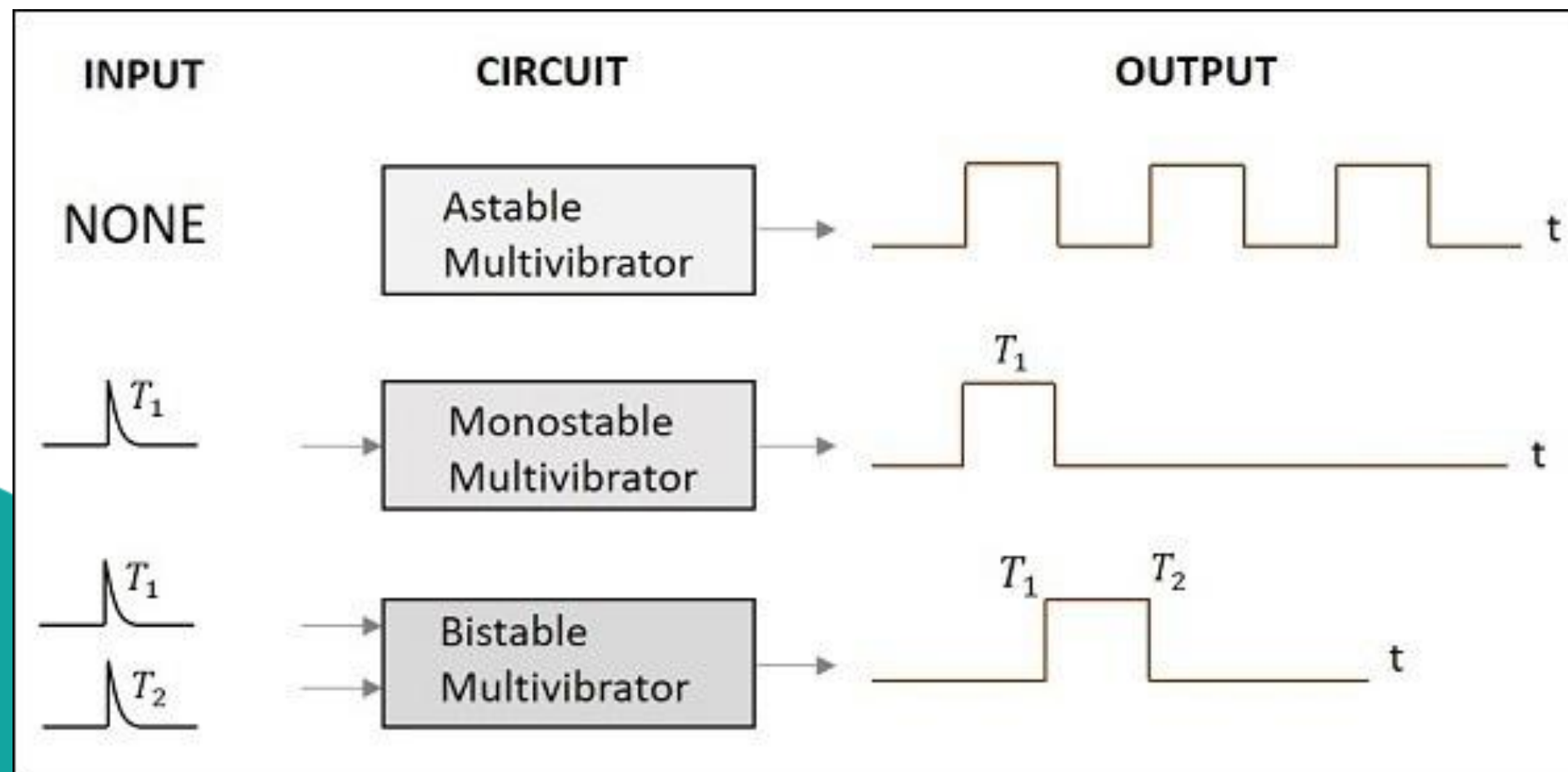
# Multivibrators

There are two possible states of a Multivibrator. In first stage, the transistor Q1 turns ON while the transistor Q2 turns OFF. In second stage, the transistor Q1 turns OFF while the transistor Q2 turns ON.

- Depending upon the manner in which these two states are interchanged, the Multivibrators are classified into three types.



Circuit is not stable in either state—it continuously oscillates from one state to the other. (Oscillators)

One of the state is stable but the other is not. (Timer)

Circuit is stable in both the state and will remain in either state indefinitely. (Flip flop)



# Astable Multivibrator


- An astable multivibrator has no stable states. Once the Multivibrator is ON, it just changes its states on its own after a certain time period which is determined by the RC time constants.

- Two transistors named Q1 and Q2 are connected in feedback to one another.

- The collector of transistor Q1 is connected to the base of transistor Q2 through the capacitor C1 and vice versa.

- The emitters of both the transistors are connected to the ground.

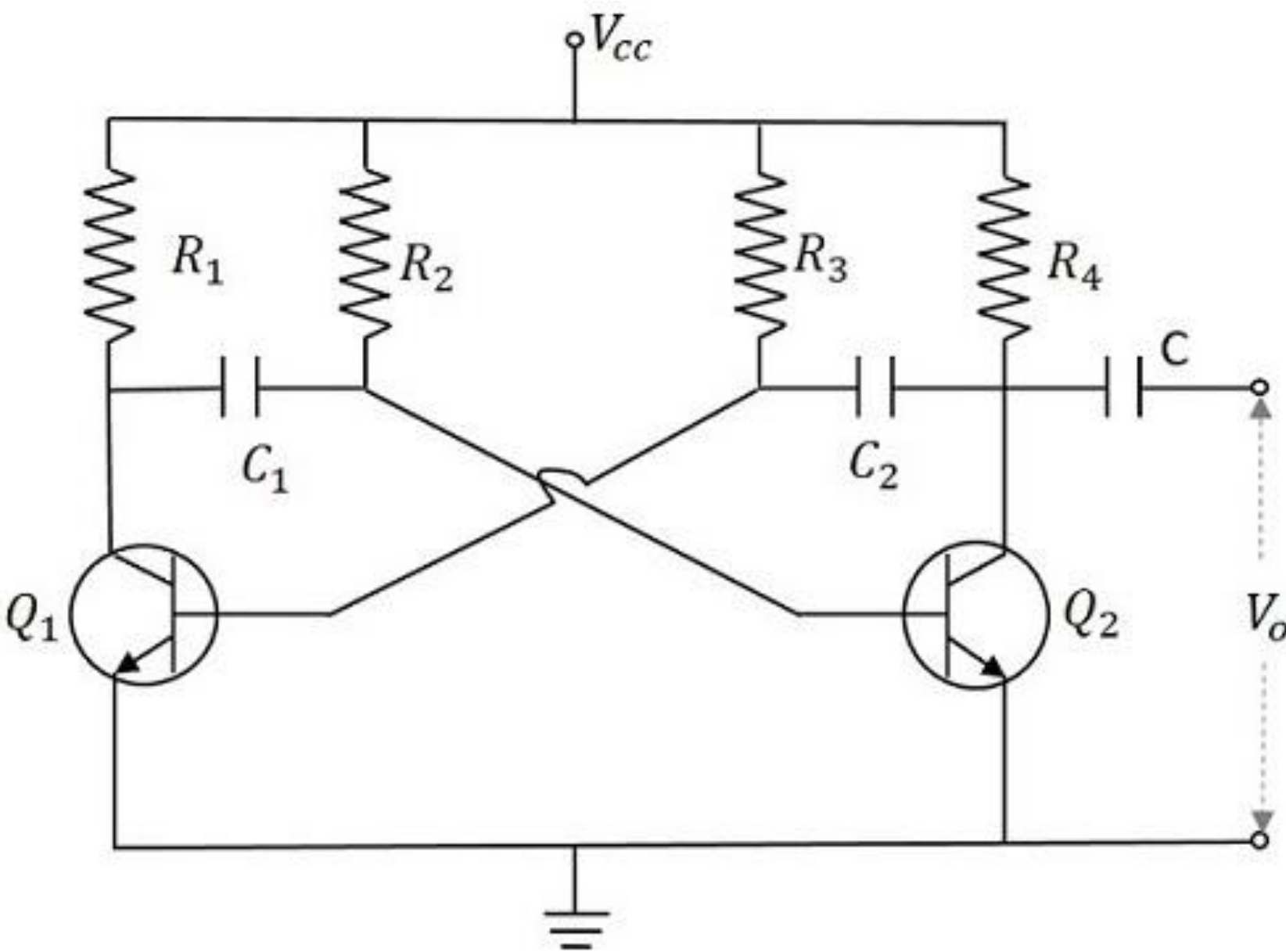- The collector load resistors R1 and R4 and the biasing resistors R2 and R3 are of equal values. The capacitors C1 and C2 are of equal values.






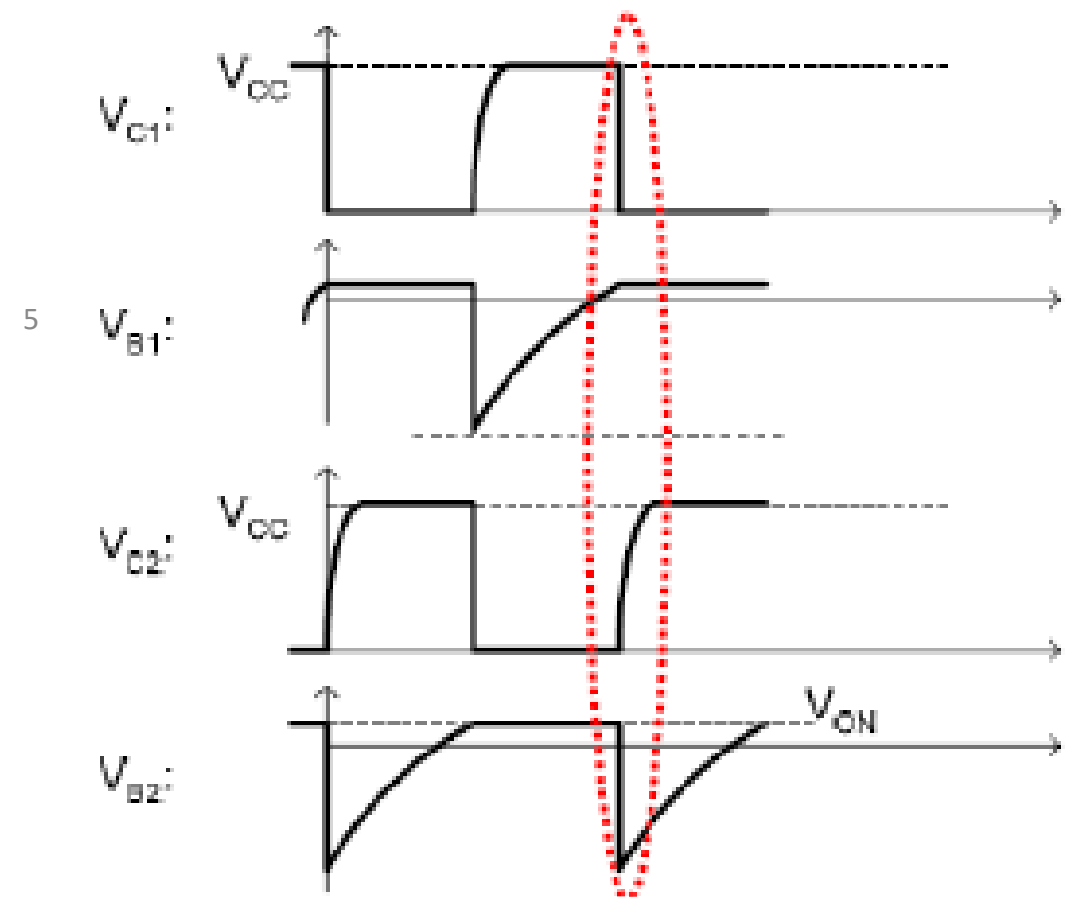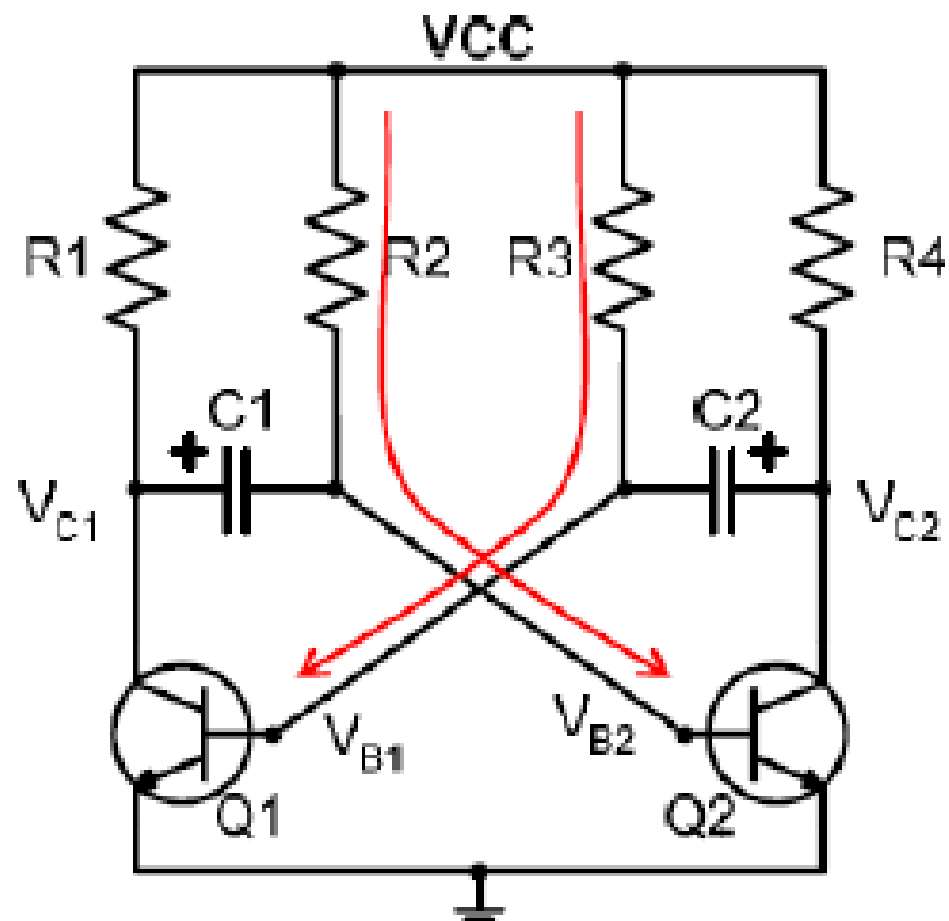
# Astable Multivibrator



- When the circuit is first powered up, neither transistor is ON.
- Both  $V_{B1}$  and  $V_{B2}$  rise via base resistor  $R3$  and  $R2$  respectively. Any one of the transistor will conduct faster than other due to some circuit imbalance. We can not say which transistor will turn on first so for analysis purpose we assume  $Q1$  conducts first and  $Q2$  off ( $C1$  is fully charged).
- Since  $Q1$  conducts and  $Q2$  off hence  $V_{C1} = 0V$  and  $V_{C2} = V_{CC}$ . - state 1








# Astable Multivibrator

- Due to higher voltage at  $V_{C2}$ , capacitor  $C2$  will be charged via  $R4$  (low resistance path because  $R4 < R2$ ).  $C1$  (which was charged earlier, and can not hold the charge for indefinite period) starts discharging via  $R2$  (high resistance path because  $R2 > R1$ ). Time taken to discharge  $C1$  ( $T1 = R2C1$ )  $>$  time taken to charge  $C2$  ( $T2 = R4C2$ ).
- When  $C2$  is fully charged then left plate of  $C2$  will be at  $-V_{CC}$  which switch off the  $Q1$ . When  $C1$  is fully discharged then left plate of  $C1$  will be at  $+V_{CC}$  which switch on the  $Q2$ . – State 2

Vision Tit 2

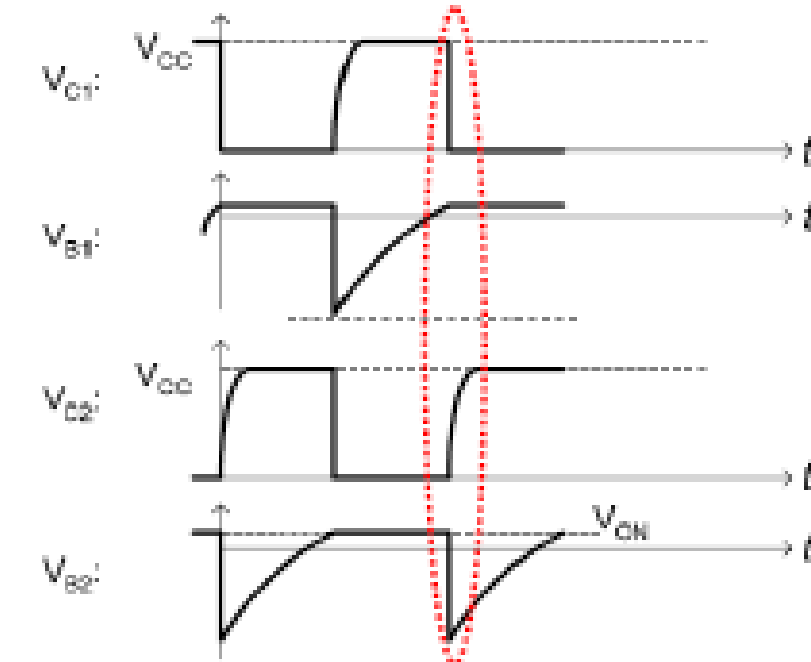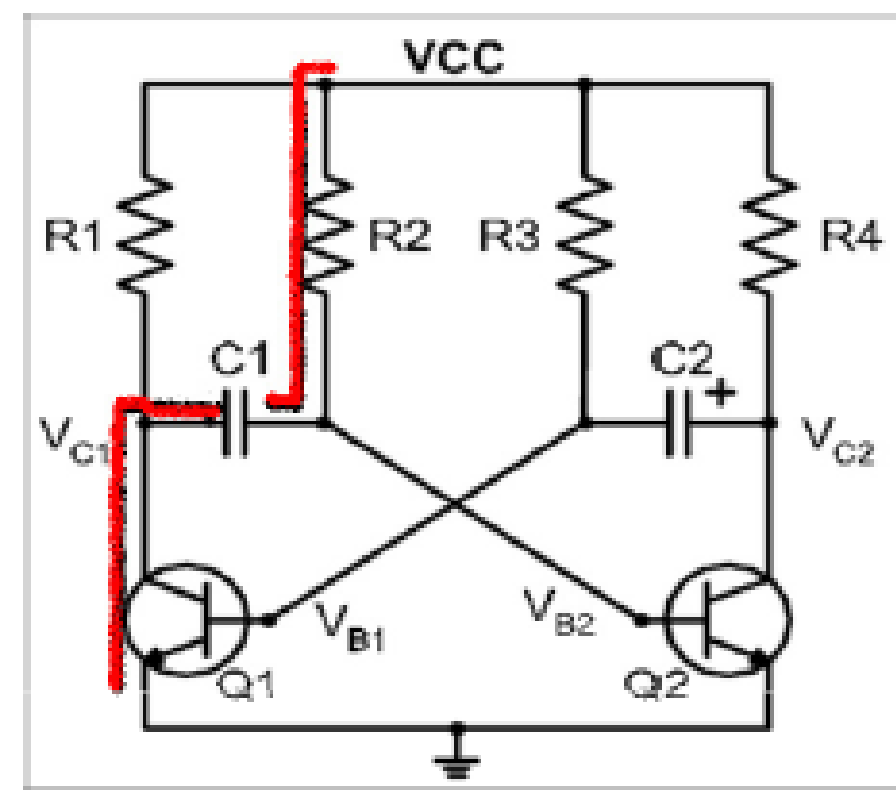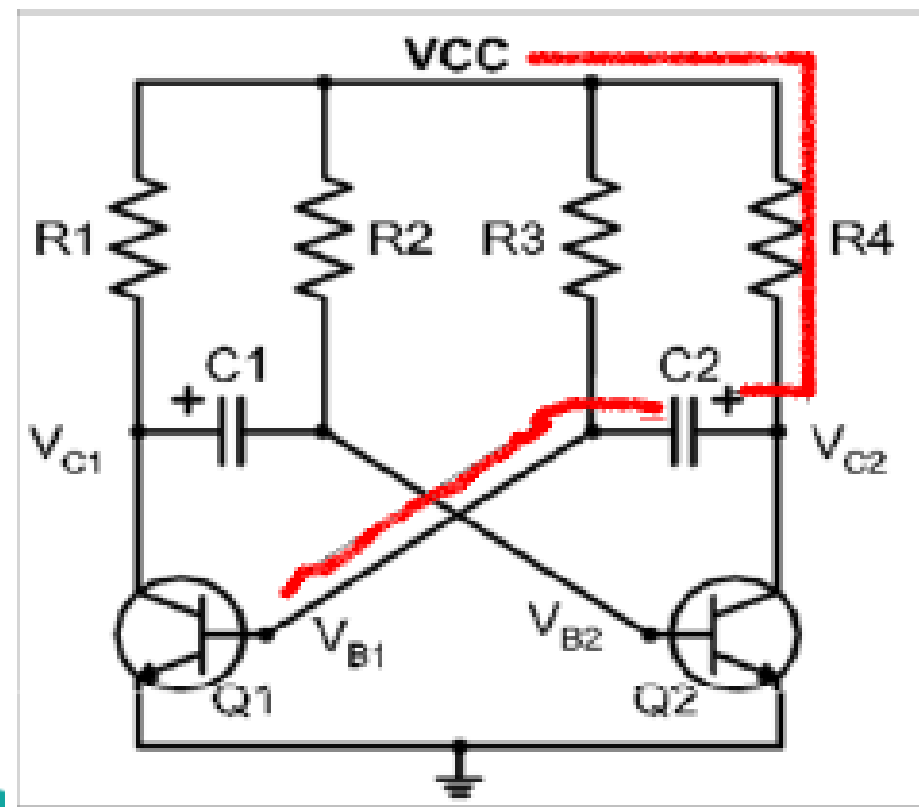



## Astable Multivibrator

- The ON time of transistor  $Q_1$  or the OFF time of transistor  $Q_2$  is given by

$$t_1 = 0.69R_1C_1$$

- Similarly, the OFF time of transistor  $Q_1$  or ON time of transistor  $Q_2$  is given by

$$t_2 = 0.69R_2C_2$$

- Hence, total time period of square wave

$$t = t_1 + t_2 = 0.69(R_1C_1 + R_2C_2)$$

- As  $R_1 = R_2 = R$  and  $C_1 = C_2 = C$ , the frequency of square wave will be

$$f = \frac{1}{t} = \frac{1}{1.38RC} = \frac{0.7}{RC}$$