



# **SNS COLLEGE OF TECHNOLOGY**

## **(AN AUTONOMOUS INSTITUTION)**

Approved by AICTE & Affiliated to Anna University  
Accredited by NBA & Accredited by NAAC with 'A+' Grade,  
Recognized by UGC saravanampatti (post), Coimbatore-641035.



## **Department of Biomedical Engineering**

**Course Name: 23BMB101-Electron Devices and Circuits**

**I Year : II Semester**

**Unit IV –Power Amplifiers & Switching Circuits**

**Topic : Schmitt Trigger<sup>1</sup>**



# INTRODUCTION




- Schmitt Trigger is an electronic circuit that adds hysteresis to the input-output transition threshold with the help of positive feedback.
- Hysteresis here means it provides two different threshold voltage levels for rising and falling edge.
- Essentially, a Schmitt Trigger is a Bi-stable Multivibrator and its output remains in either of the stable states indefinitely. For the output to change from one stable state to other, the input signal must change (or trigger) appropriately.
- This Bistable operation of the Schmitt Trigger requires an amplifier with positive feedback (or regenerative feedback) with a loop gain greater than one. Hence, Schmitt Trigger is also known as Regenerative Comparator.

Vision Tit 2

Vision Title 3




# Schmitt Trigger

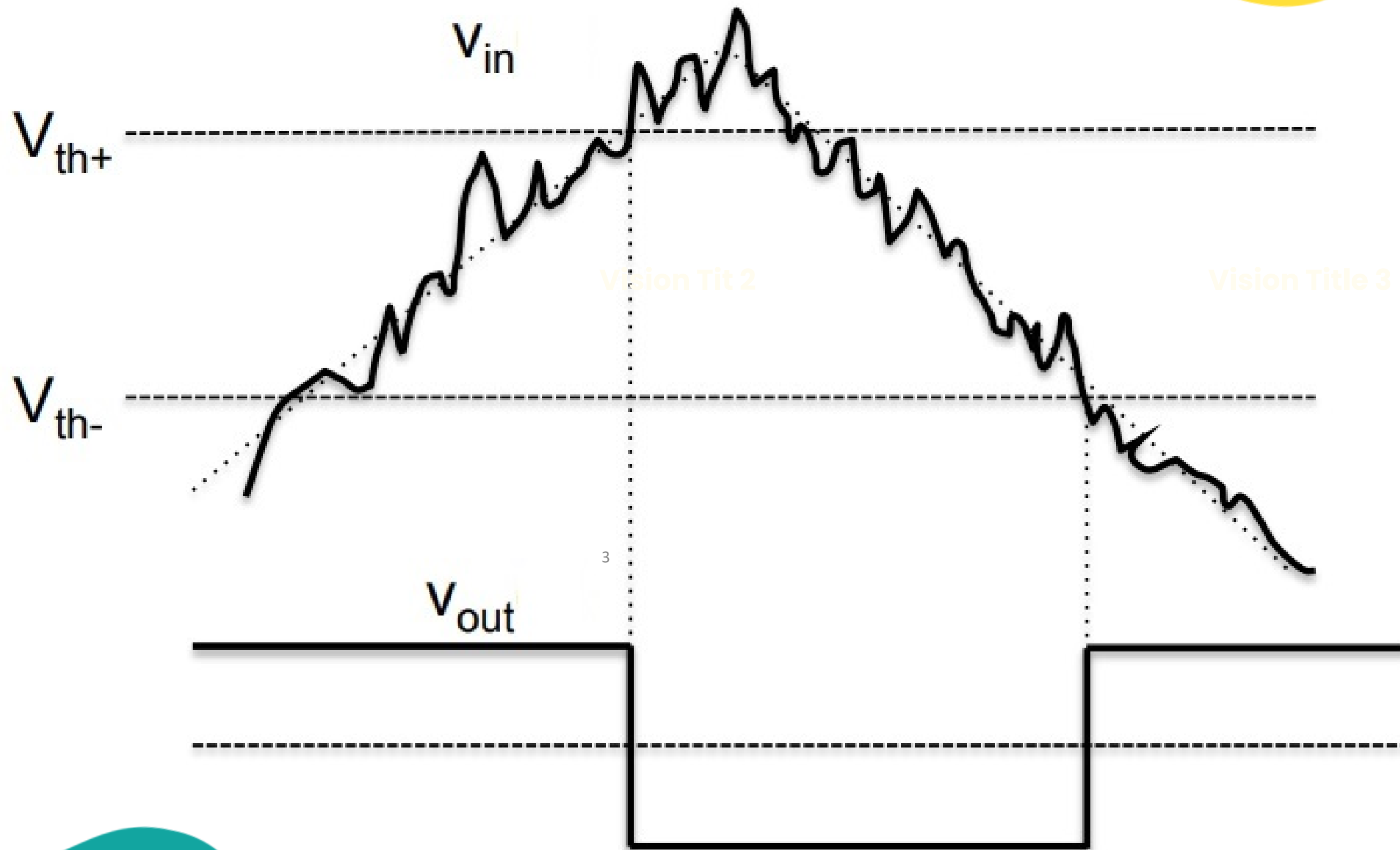



# Construction of Schmitt Trigger

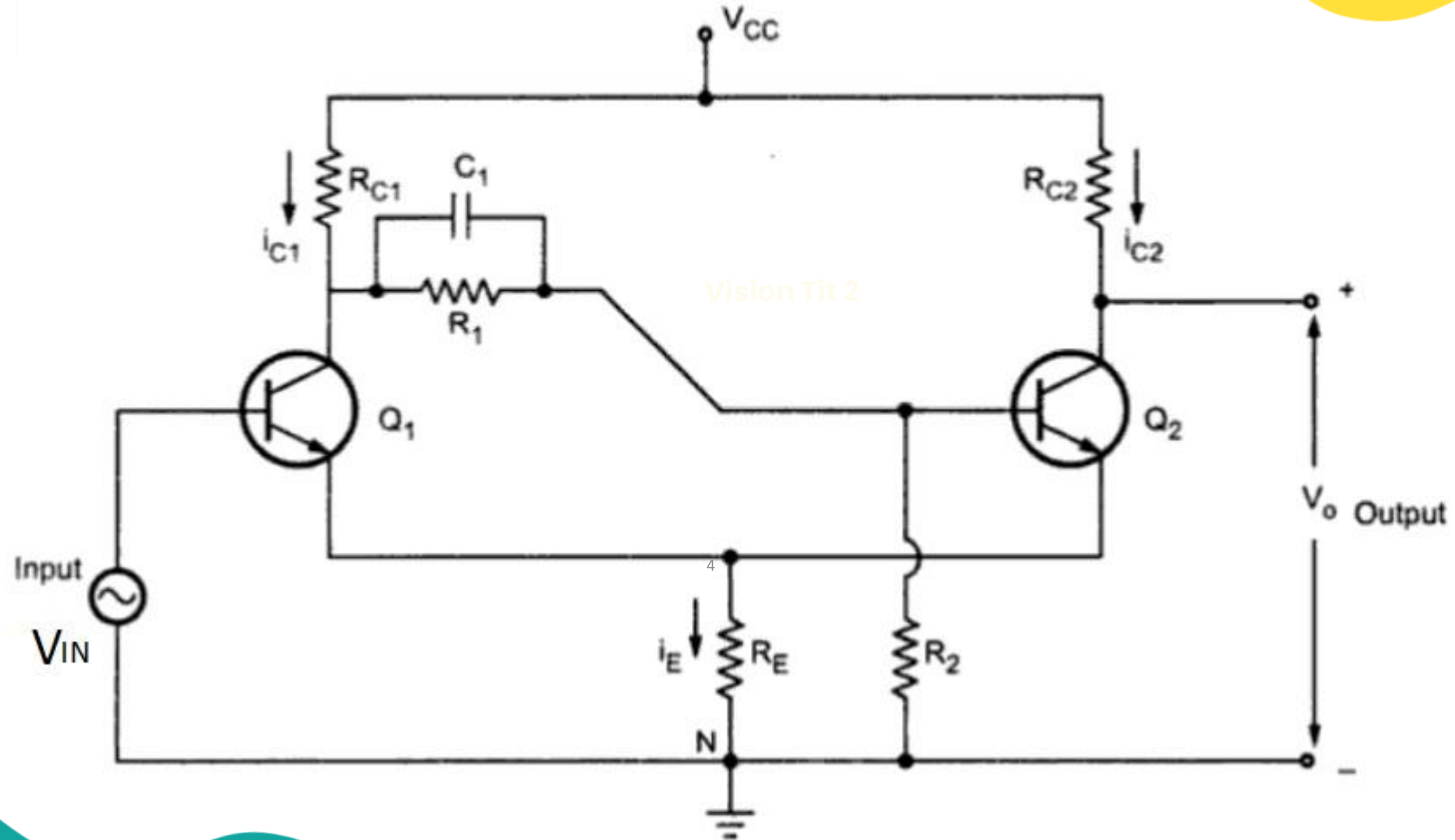



## Operation of Schmitt Trigger

- When  $V_{IN}$  is zero, Q1 is cut-off and Q2 is in saturation. As a result, the output voltage  $V_O$  is LOW. If

$V_{CE(SAT)}$  is assumed to be 0, then the voltage across  $R_E$  is given by:

- $$(V_{CC} * R_E) / (R_E + R_{C2})$$

- This voltage is also the emitter voltage of Q1. So, for Q1 to conduct, the input voltage  $V_{IN}$  must be greater than the sum of the emitter voltage and 0.7 V i.e.

- $$V_{IN} = [(V_{CC} * R_E) / (R_E + R_{C2})] + 0.7$$

- When the  $V_{IN}$  is greater than this voltage, Q1 starts conducting and Q2 is cut-off due to regenerative action. As a result, the output  $V_O$  goes HIGH. Now the voltage across the  $R_E$  changes to a new value and is given by:

- $$(V_{CC} * R_E) / (R_E + R_{C1})$$



# Operation of Schmitt Trigger

- Transistor Q1 will conduct as long as the input voltage  $V_{IN}$  is greater than or equal to the following:
- $$V_{IN} = [(V_{CC} * R_E) / (R_E + R_{C1})] + 0.7$$
- If  $V_{IN}$  falls below this value, then Q1 comes out of saturation and the rest of the circuit operates due to regenerative action of Q1 going to cut-off and Q2 to saturation.

