



# SNS COLLEGE OF TECHNOLOGY

## (AN AUTONOMOUS INSTITUTION)

Approved by AICTE & Affiliated to Anna University  
Accredited by NBA & Accredited by NAAC with 'A+' Grade,  
Recognized by UGC saravanampatti (post), Coimbatore-641035.



## Department of Biomedical Engineering

Course Name: **23BMB101-Electron Devices and Circuits**

**I Year : II Semester**

**Unit V – Feedback Amplifiers and Oscillators**


**Topic : RC Phase Shift Oscillator<sup>1</sup>**


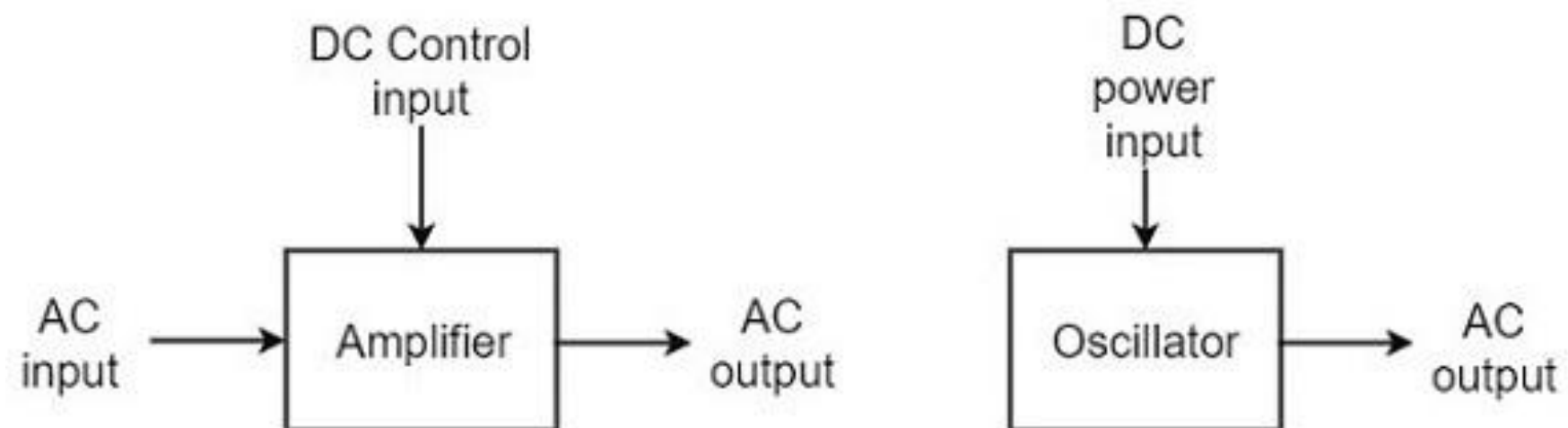
# INTRODUCTION




- An electronic oscillator is an electronic circuit that produces a periodic, oscillating electronic signal, often a sine wave or a square wave or a triangle wave.
- Oscillators convert direct current (DC) from a power supply to an alternating current (AC) signal.
- They are widely used in many electronic devices ranging from simplest clock generators to digital instruments (like calculators) and complex computers and peripherals etc.







# Oscillators

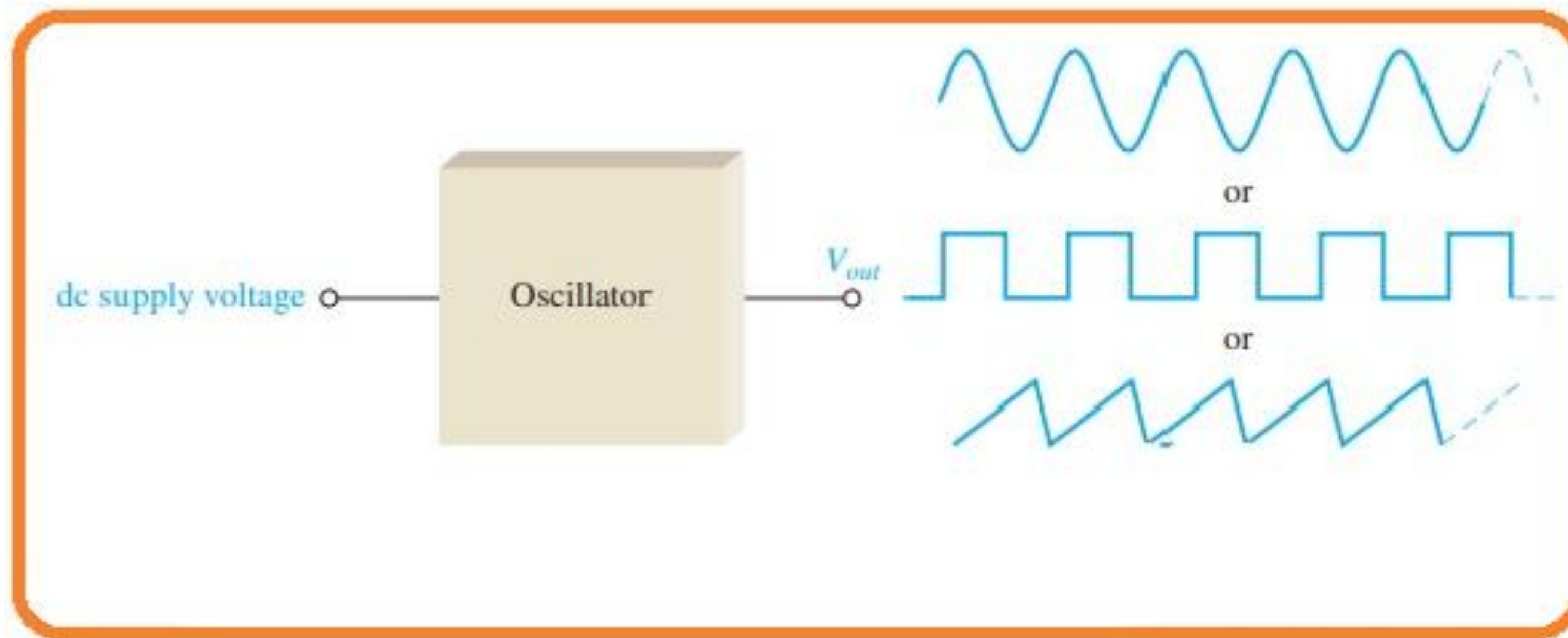

itle 3






# Oscillators

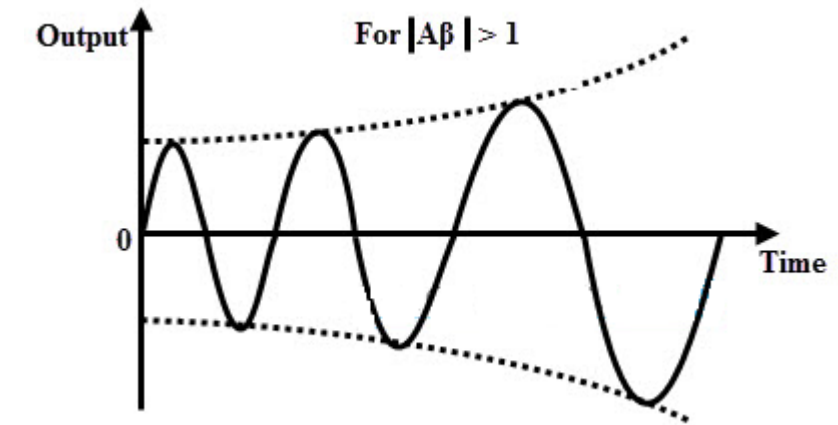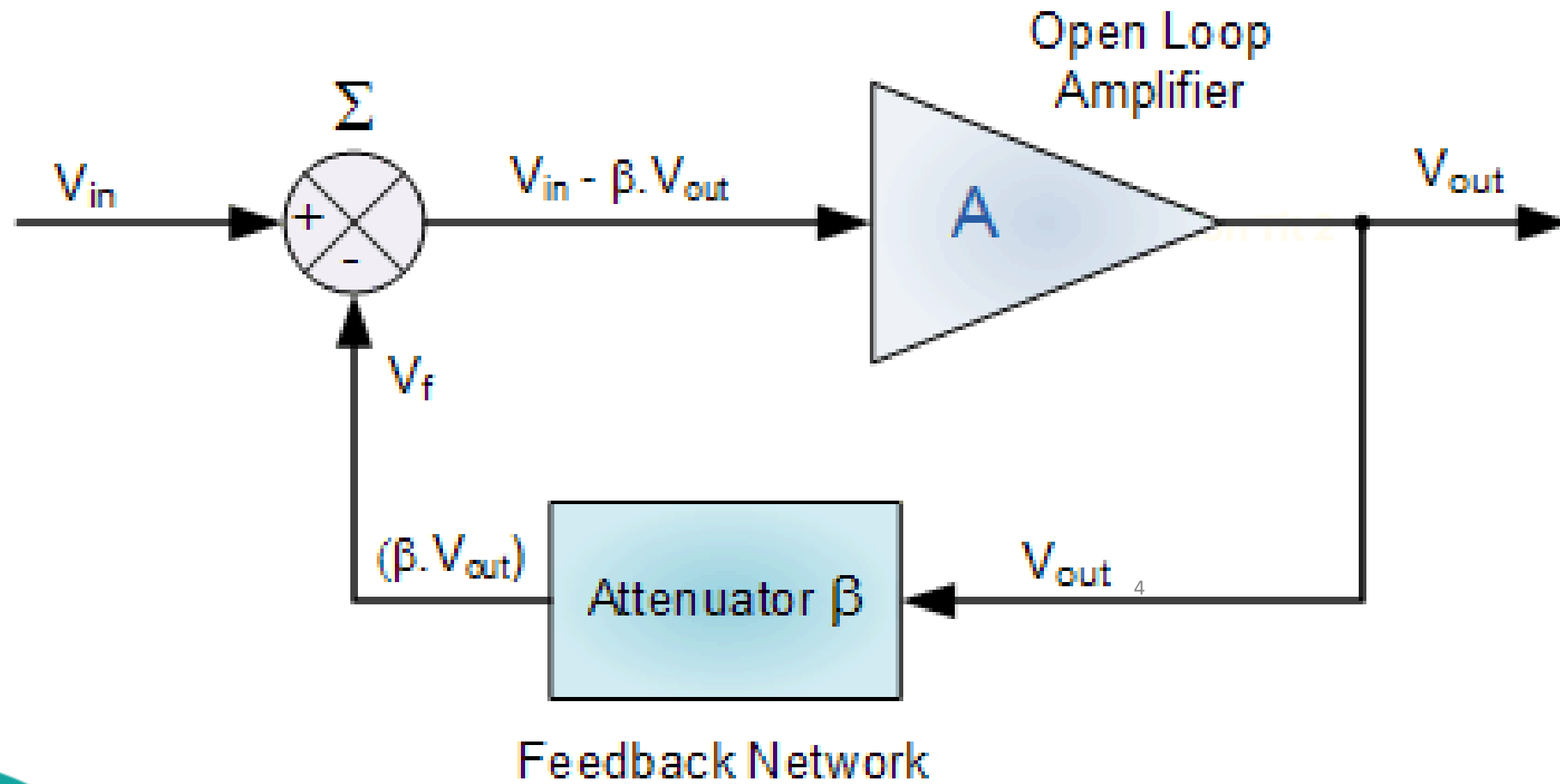




# Oscillators

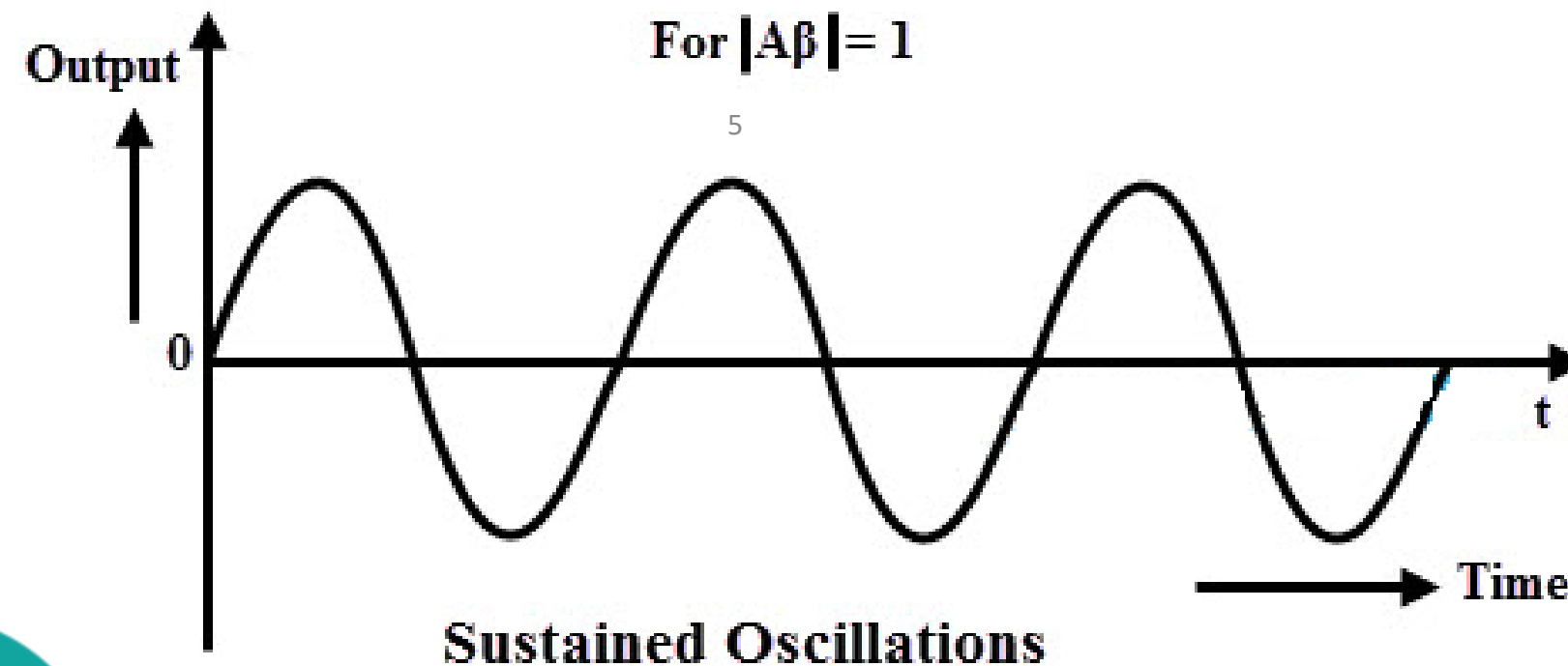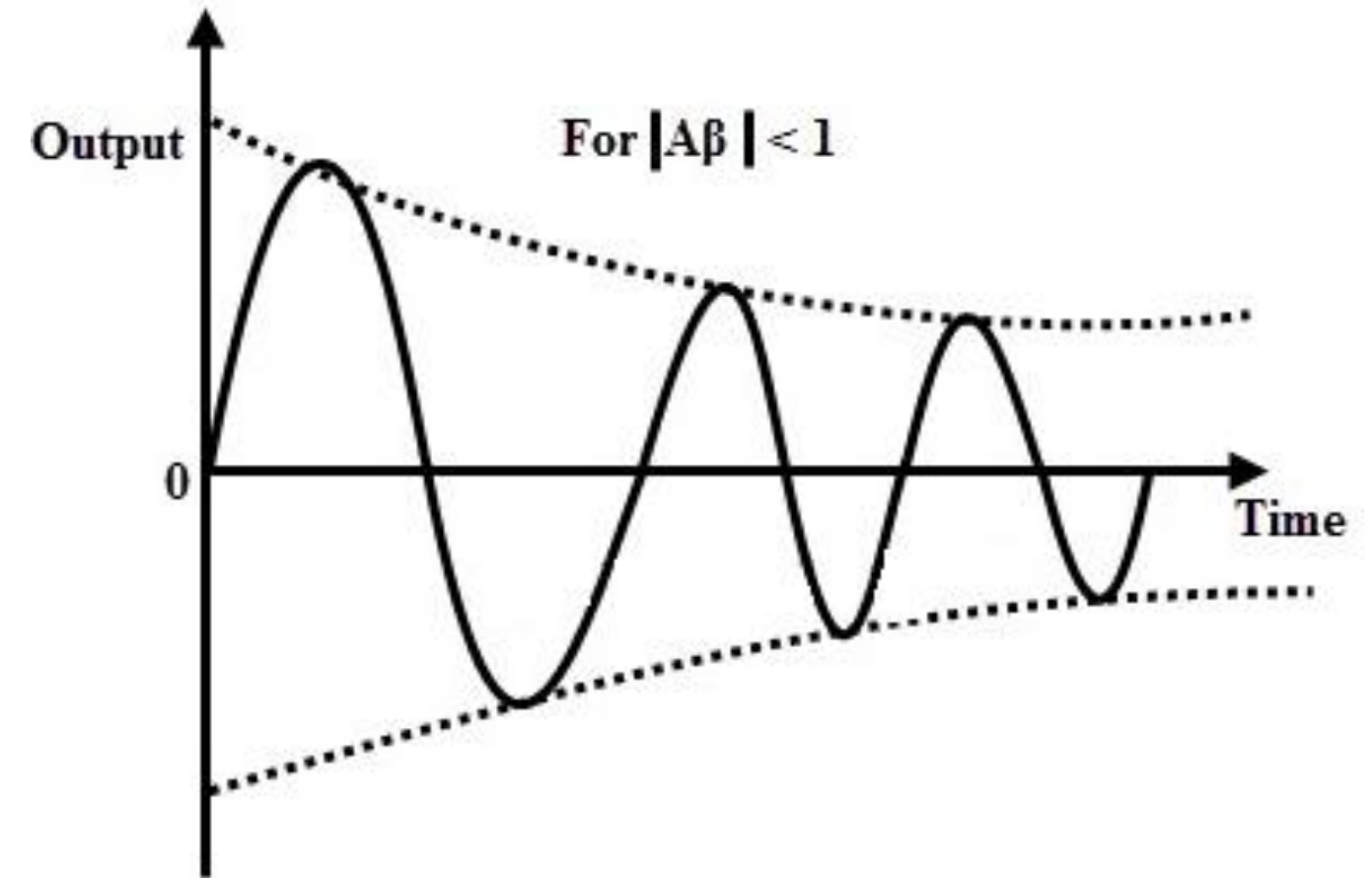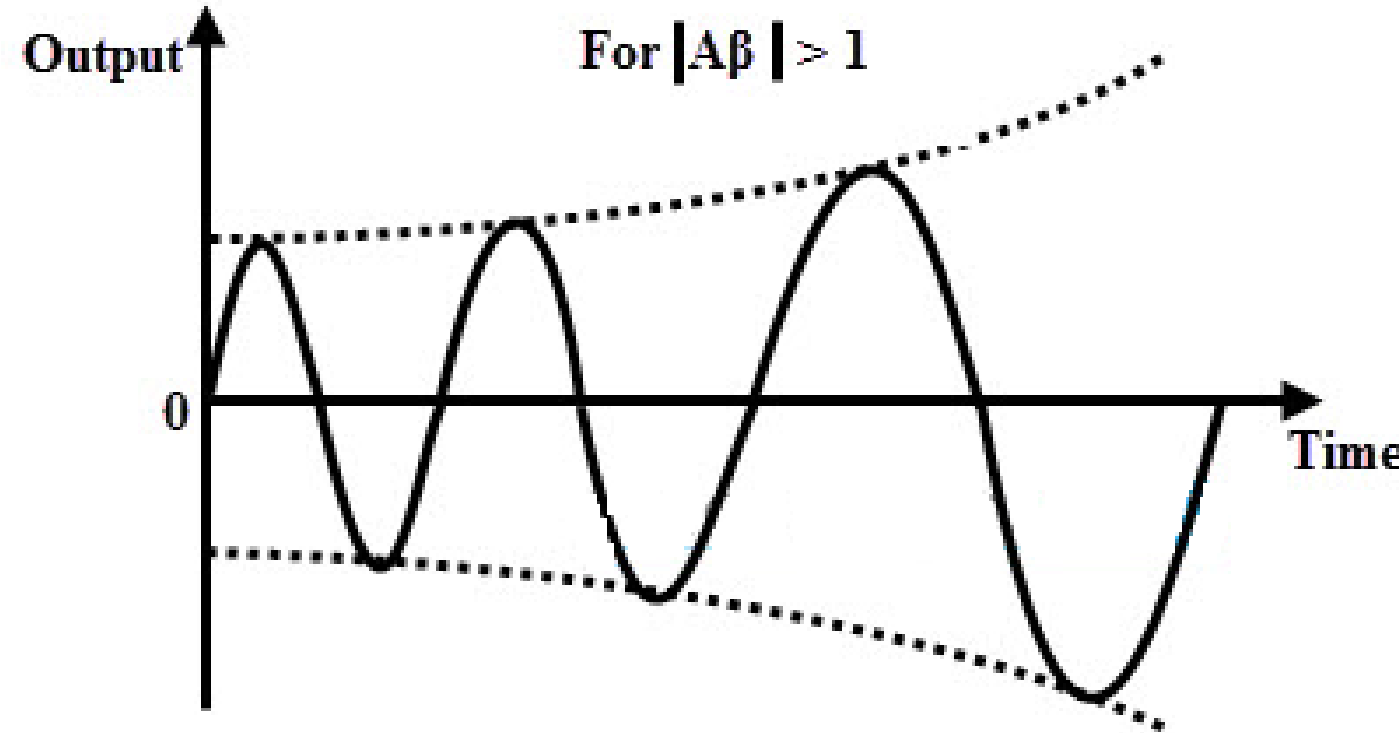




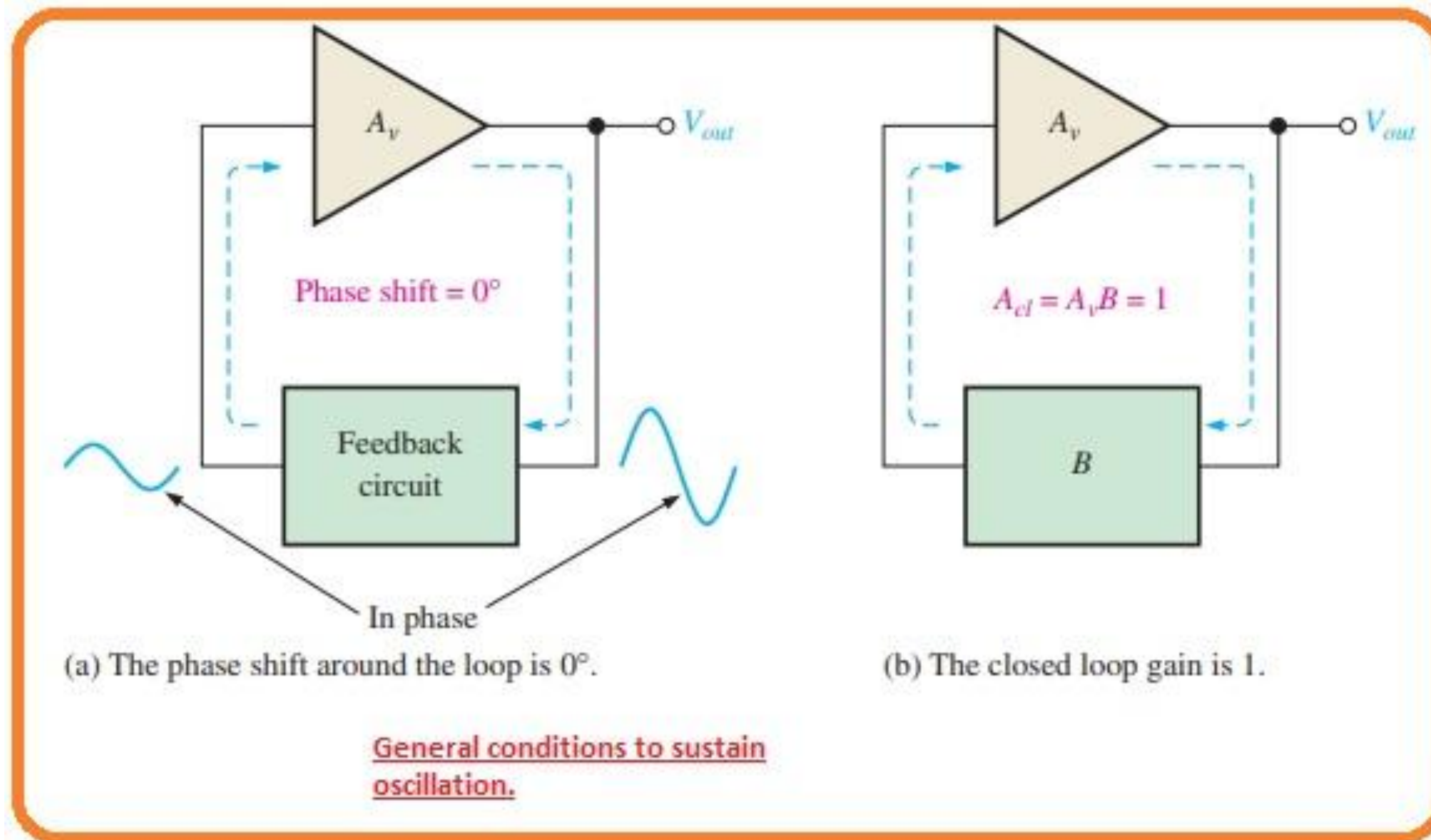
# Conditions for Oscillations- Barkhausen Criterion





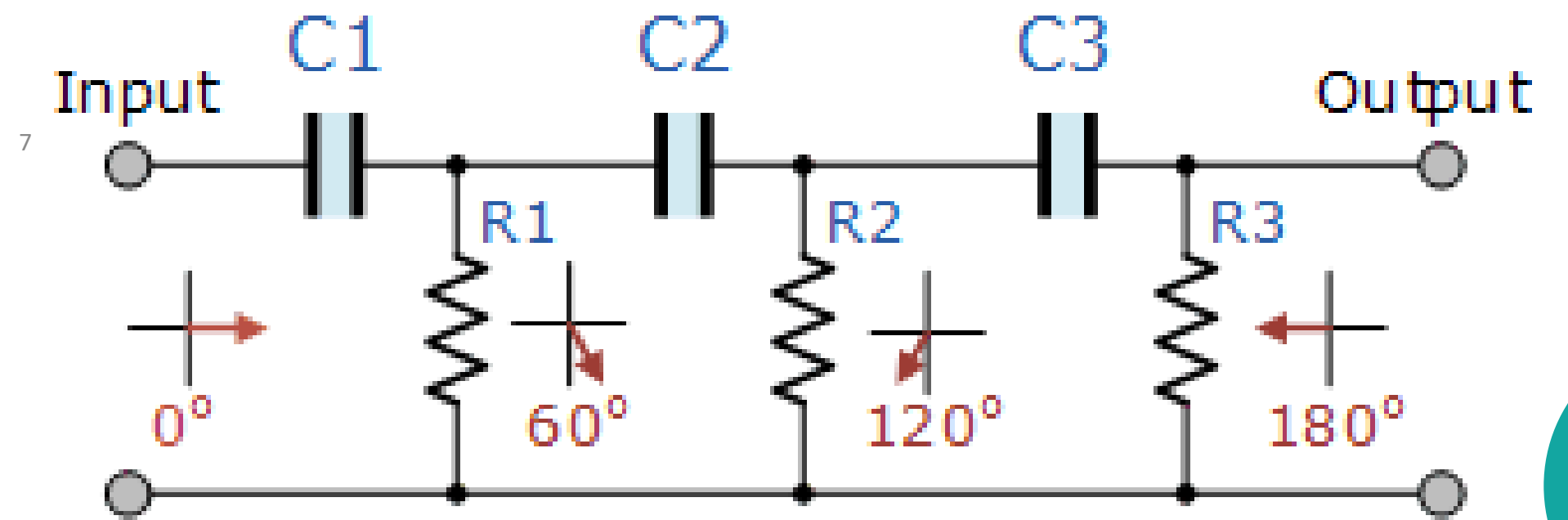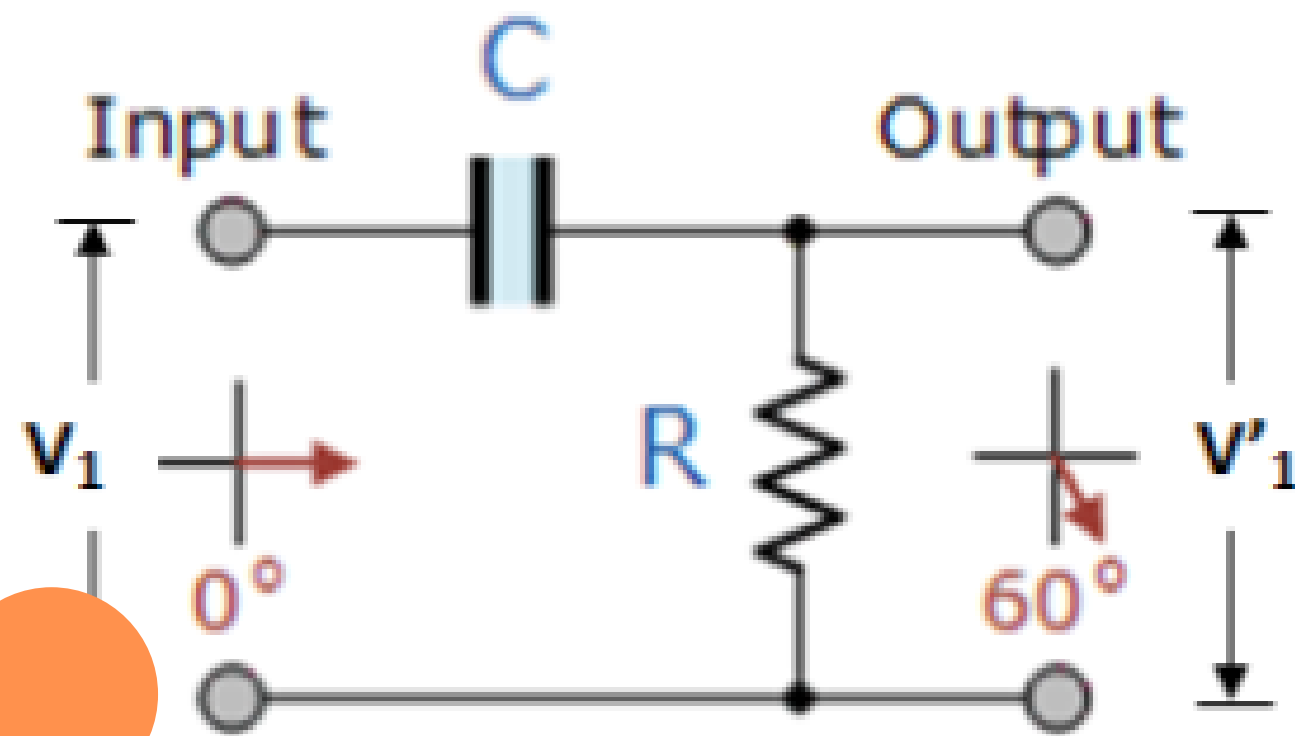
## RC Phase shift Oscillator

- In a phase shift oscillator, a phase shift of  $180^\circ$  is obtained with a phase shift circuit instead of inductive or capacitive coupling.
- A further phase shift of  $180^\circ$  is introduced due to the transistor properties. Thus energy supplied back to the tank circuit is of correct phase.





# RC Phase shift Oscillator

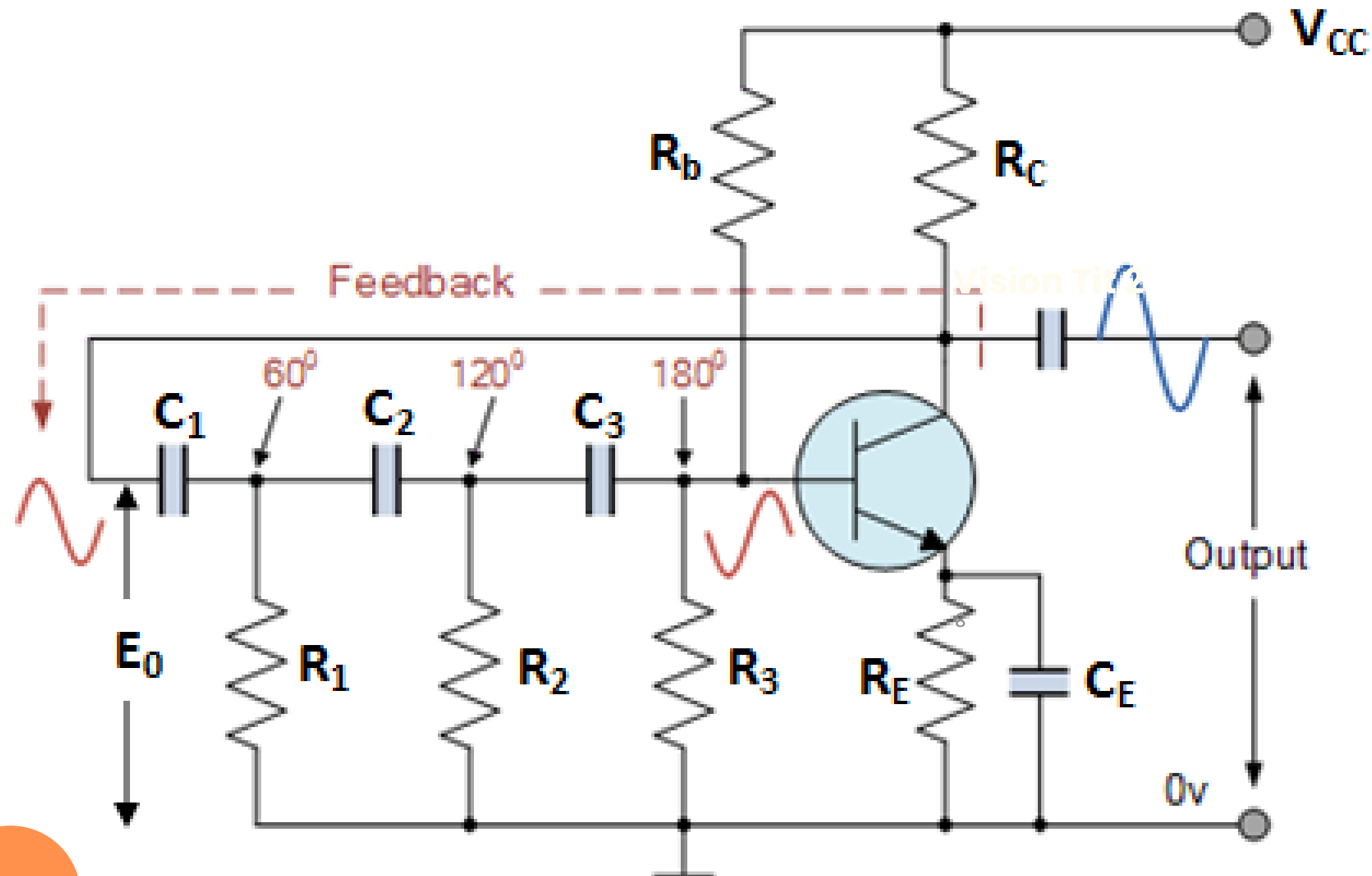

$$f_o = \frac{1}{2\pi RC\sqrt{6}}$$

$$R_1 = R_2 = R_3 = R$$

$$C_1 = C_2 = C_3 = C$$