



# **SNS COLLEGE OF TECHNOLOGY**

## **(AN AUTONOMOUS INSTITUTION)**

Approved by AICTE & Affiliated to Anna University  
Accredited by NBA & Accredited by NAAC with 'A+' Grade,  
Recognized by UGC saravanampatti (post), Coimbatore-641035.



## **Department of Biomedical Engineering**

**Course Name: 23BMB101-Electron Devices and Circuits**

**I Year : II Semester**

**Unit V – Feedback Amplifiers and Oscillators**

**Topic : Hartley Oscillator**



# INTRODUCTION




- The Hartley oscillator is an electronic oscillator circuit in which the oscillation frequency is determined by the tuned circuit consisting of capacitors and inductors, that is, an LC oscillator.
- Hartley oscillators are typically tuned to produce waves in the radiofrequency band (which is why they are also known as RF oscillators).
- The distinguishing feature of a Hartley oscillator is that the tuning circuit consists of a single capacitor in parallel with two inductors in series (or a single tapped inductor), and the feedback signal needed for oscillation is taken from the centre connection of the two inductors.

Vision Tit 2

Vision Title 3



## Construction

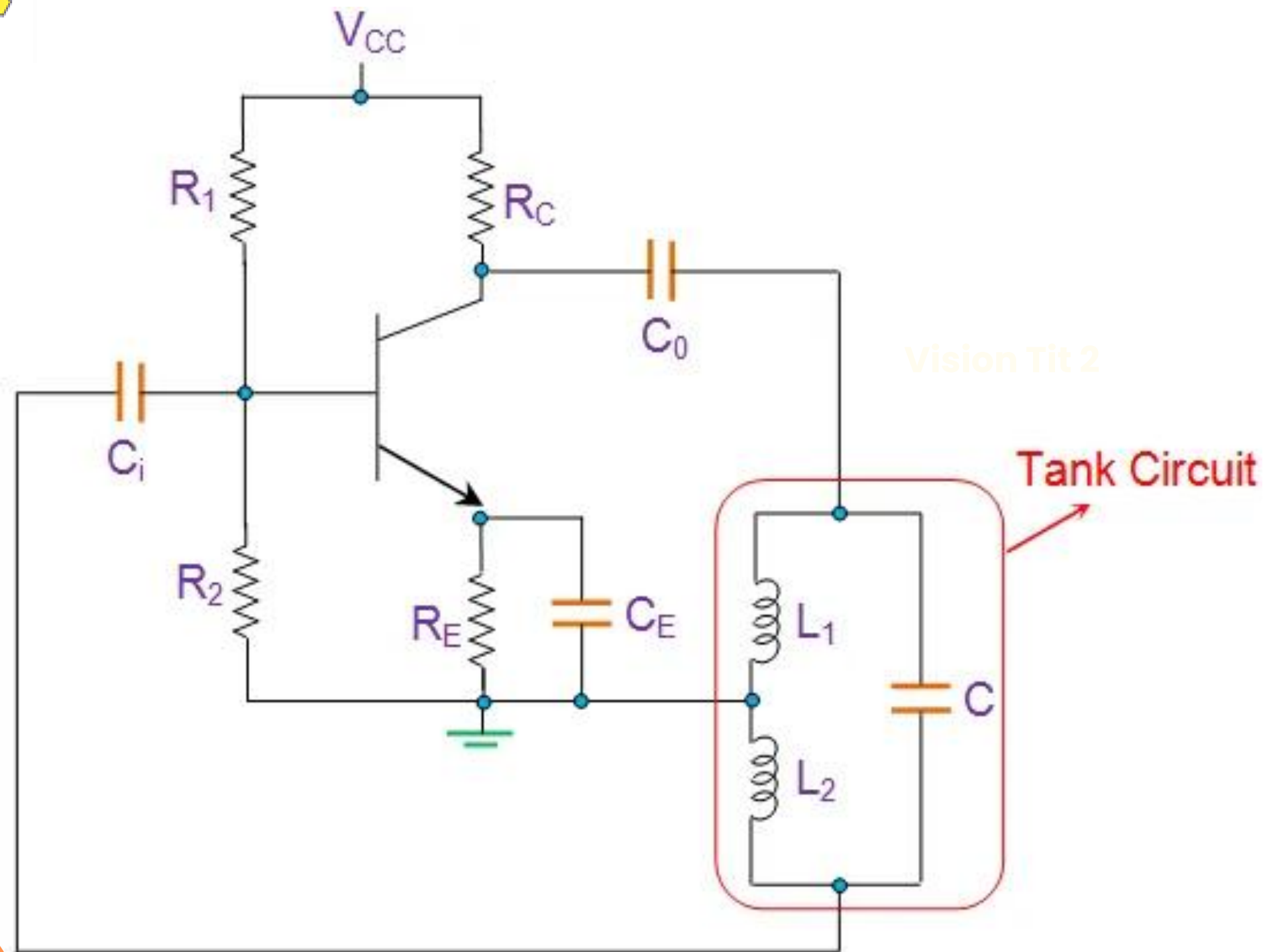

- Here the  $R_C$  is the collector resistor while the emitter resistor  $R_E$  forms the stabilizing network.
- Further the resistors  $R_1$  and  $R_2$  form the voltage divider bias network for the transistor in common-emitter CE configuration.



# Oscillator - Construction



- The capacitors  $C_i$  and  $C_o$  are the input and output decoupling capacitors while the emitter capacitor  $C_E$  is the bypass capacitor used to bypass the amplified AC signals.
- All these components are identical to those present in a common-emitter amplifier which is biased using a voltage divider network.
- On switching ON the power supply, the transistor starts to conduct, leading to an increase in the collector current,  $I_C$  which charges the capacitor  $C$ .
- On acquiring the maximum charge feasible,  $C$  starts to discharge via the inductors  $L_1$  and  $L_2$ . These charging and discharging cycles result in the damped oscillations in the tank circuit.



## Oscillators

- The oscillation current in the tank circuit produces an AC voltage across the inductors  $L_1$  and  $L_2$  which are out of phase by  $180^\circ$  as their point of contact are grounded.
- The output of the amplifier is applied across the inductor  $L_1$  while the feedback voltage drawn across  $L_2$  is applied to the base of the transistor.
- At this state, if one makes the gain of the circuit to be slightly greater than the feedback ratio given by

5

$$\beta = \frac{L_1}{L_2}; \text{ if the coils are wound on different cores}$$

$$\beta = \frac{L_1 + M}{L_2 + M}$$



# Hartley Oscillator

- The frequency of such an oscillator is given as

$$F = \frac{1}{2\pi\sqrt{L_{eff}C}}$$

*$L_{eff}$  is the effective series inductance which is expressed as  
 $L_{eff} = L_1 + L_2$ ; if the coils are wound on different cores  
 $L_{eff} = L_1 + L_2 + 2M$ ; if the coils are wound on the same core*