



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

19ECB302–VLSI DESIGN

III YEAR/ V SEMESTER

UNIT 2 –COMBINATIONAL LOGIC CIRCUITS

TOPIC 2 &3 –Pass transistor Logic, Transmission gates



OUTLINE



- A Brief History
- CMOS Gate Design
- Pass Transistors
- Transmission Gate logic
- Activity
- Assessment
- Summary



A Brief History



1958: First integrated circuit


- Flip-flop using two transistors
- Built by Jack Kilby at Texas Instruments

2003-Intel Pentium 4 mprocessor (55 million transistors)

512 Mbit DRAM (> 0.5 billion transistors) miniaturization of transistors Smaller is cheaper, faster, lower in power! Revolutionary effects on society



Annual Sales

 



Transistor Types



➤ **Bipolar transistors**


- npn or pnp silicon structure
- Small current into very thin base layer controls large currents between emitter and collector
- Base currents limit integration density

➤ **Metal Oxide Semiconductor Field Effect Transistors**

- nMOS and pMOS MOSFETS
- Voltage applied to insulated gate controls current between source and drain
- Low power allows very high integration



CMOS Gate Design-4 input NOR








 




Series and Parallel Connections



  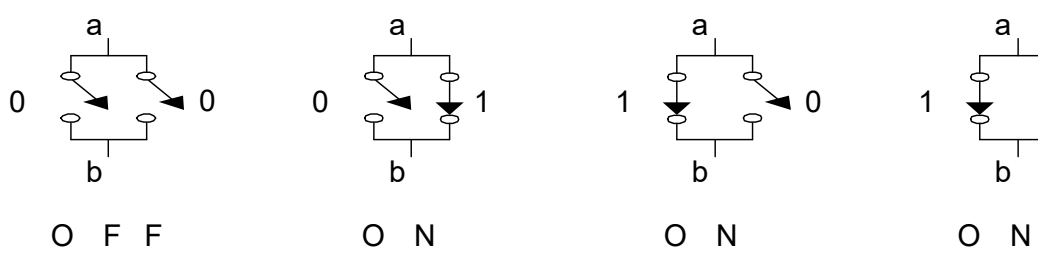     - nMOS: 1 = ON
- pMOS: 0 = ON
- *Series*: both must be ON
- *Parallel*: either can be ON





Conduction Complement



- Complementary CMOS gates always produce 0 or 1
- Ex: NAND gate- **.ns—n-MOS Series—pMOS parallel**
 - Series nMOS: $Y=0$ when both inputs are 1
 - Thus $Y=1$ when either input is 0
 - Requires parallel pMOS
- Rule of Conduction Complements
 - Pull-up network is complement of pull-down
 - Parallel \rightarrow series, series \rightarrow parallel




Compound Gates



- Compound gates can do any inverting function

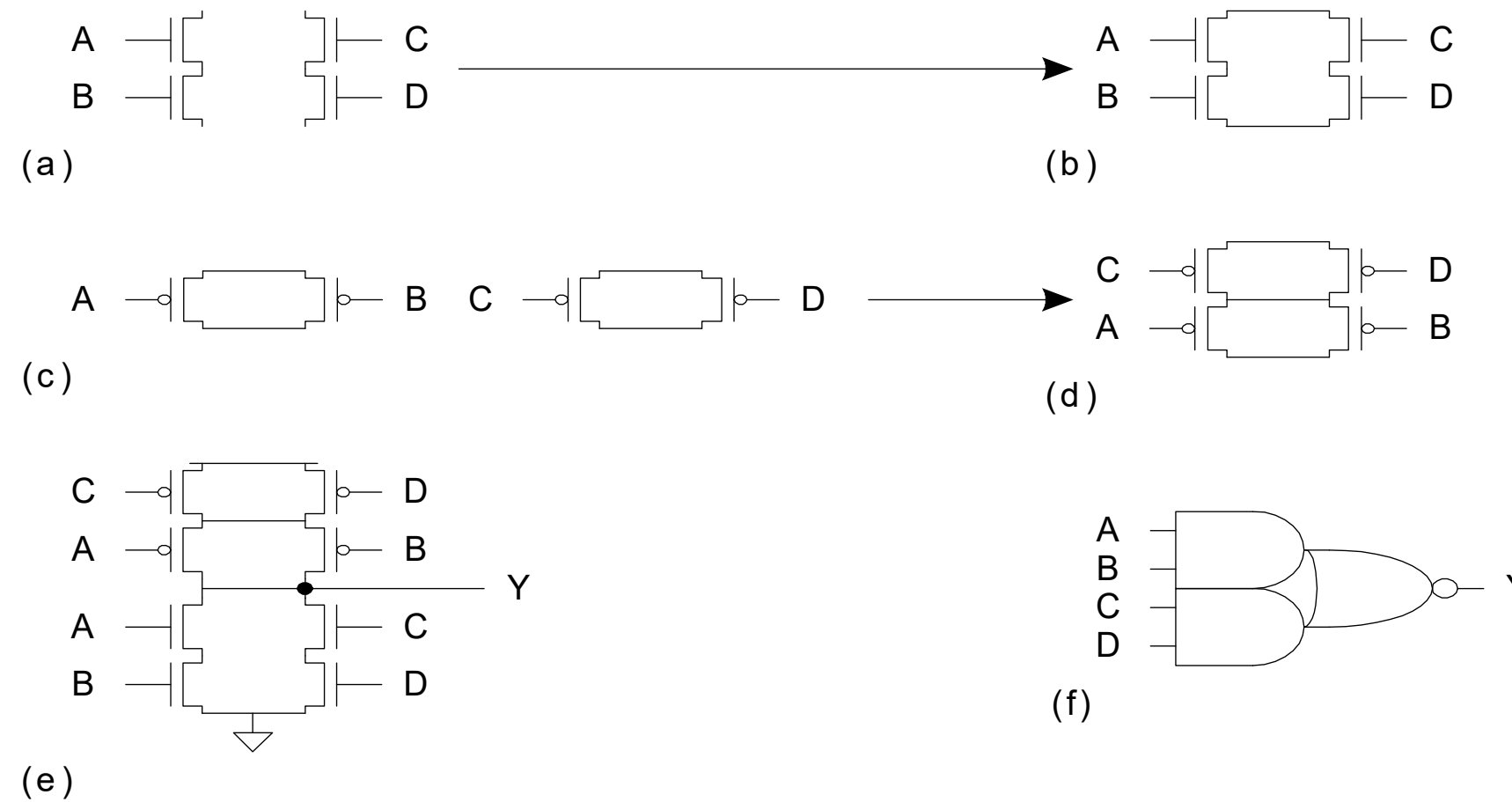- Ex: $Y = \overline{A B + C D}$ (AND-AND-OR-INVERT, AOI22)






Example: O3AI



$$Y = \overline{(A + B + C)} D$$

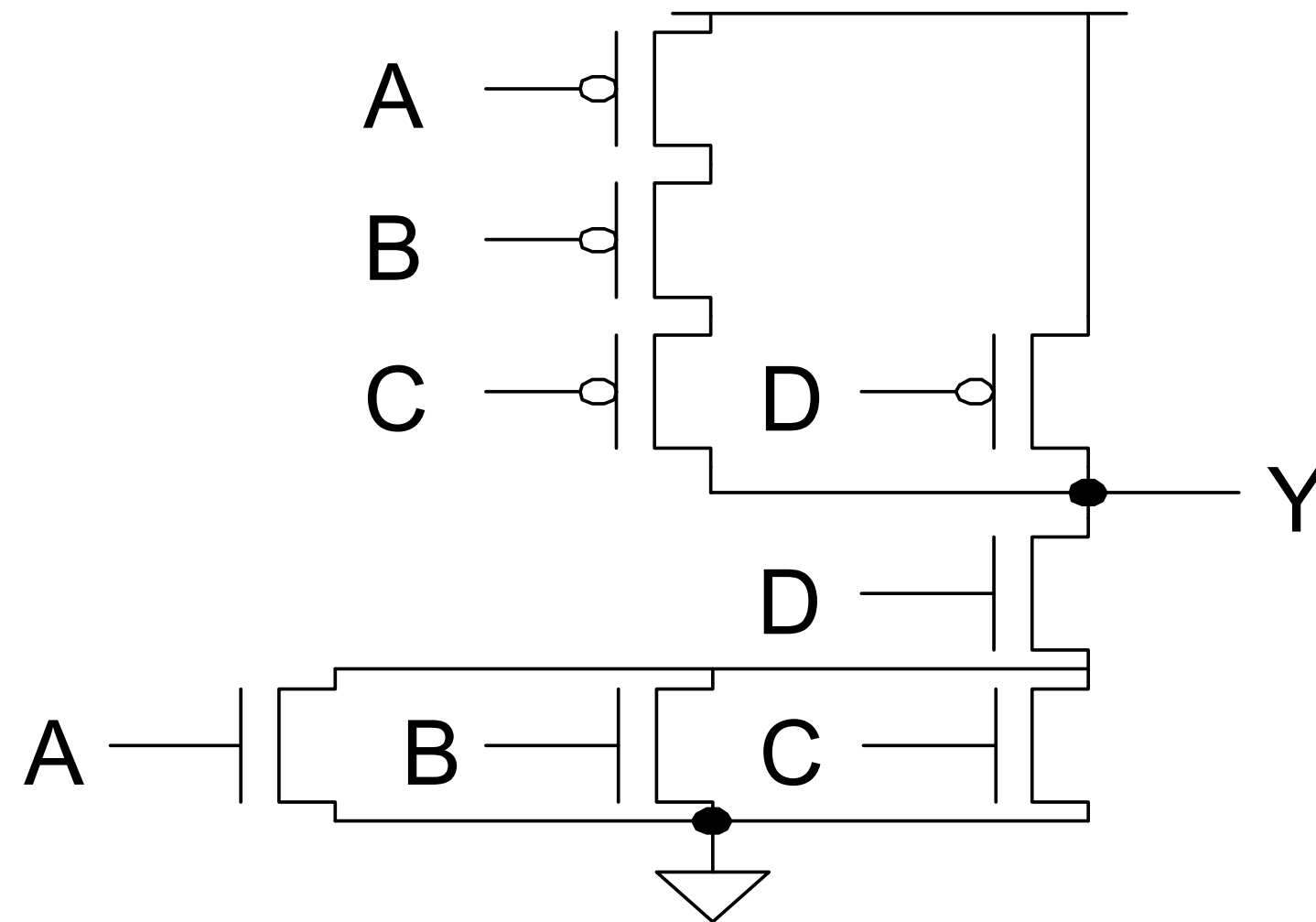EXAMPLES OF COMBINATIONAL
LOGIC/19ECB302-VLSI
DESIGN/J.Prabakaran/Assistant
Professor/ECE/SNSCT





Strength of Signal



How close it approximates ideal voltage source

V_{DD} and GND rails are strongest 1 and 0



- nMOS pass strong 0

But degraded or weak 1

- pMOS pass strong 1

But degraded or weak 0

Thus nMOS are best for pull-down network

  





EXAMPLES OF COMBINATIONAL
 LOGIC/19ECB302-VLSI
 DESIGN/J.Prabakaran/Assistant
 Professor/ECE/SNSCT








Transistors can be used as switches



Pass Transistors

    

     EXAMPLES OF COMBINATIONAL LOGIC/19ECB302-VLSI DESIGN/J.Prabakaran/Assistant Professor/ECE/SNSCT






Transmission Gates




- Pass transistors produce degraded outputs
- *Transmission gates* pass both 0 and 1 well

 
EXAMPLES OF COMBINATIONAL LOGIC/19ECB302-VLSI DESIGN/J.Prabakaran/Assistant Professor/ECE/SNSCT



$g = 0, gb = 1$

 


$g = 1, gb = 0$

 





Input

Output

$g = 1, gb = 0$

 

$g = 1, gb = 0$

    




Tristates



- Tristate buffer produces Z when not enabled

EN	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

 EXAMPLES OF COMBINATIONAL
LOGIC/19ECB302-VLSI
DESIGN/J.Prabakaran/Assistant
Professor/ECE/SNSCT






Non restoring Tristate



- Transmission gate acts as tristate buffer
 - Only two transistors
 - But non restoring
 - Noise on A is passed on to Y

 EXAMPLES OF COMBINATIONAL
LOGIC/19ECB302-VLSI
DESIGN/J.Prabakaran/Assistant
Professor/ECE/SNSCT






Multiplexers



- 2:1 multiplexer chooses between two inputs

S	D1	D0	Y
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1

 EXAMPLES OF COMBINATIONAL
LOGIC/19ECB302-VLSI
DESIGN/J.Prabakaran/Assistant
Professor/ECE/SNSCT






Gate-Level Mux Design




$$Y = SD_1 + \bar{S}D_0 \text{ (too many transistors)}$$

How many transistors are needed? 20

 

 EXAMPLES OF COMBINATIONAL LOGIC/19ECB302-VLSI DESIGN/J.Prabakaran/Assistant Professor/ECE/SNSCT






Transmission Gate Mux



- Nonrestoring mux uses two transmission gates
 - Only 4 transistors

 EXAMPLES OF COMBINATIONAL
LOGIC/19ECB302-VLSI
DESIGN/J.Prabakaran/Assistant
Professor/ECE/SNSCT





Assessment



How many transistors are needed to
make 2:1 Mux? ---

Draw 2:1 mux using TG

Draw 4:1 mux using TG

nMOS pass strong -----

EXAMPLES OF COMBINATIONAL
LOGIC/19ECB302-VLSI
DESIGN/J.Prabakaran/Assistant
Professor/ECE/SNSCT

But degraded or weak -----

pMOS pass strong -----

But degraded or weak -----

Thus nMOS are best for pull-down network



THANK YOU

EXAMPLES OF COMBINATIONAL
LOGIC/19ECB302-VLSI
DESIGN/J.Prabakaran/Assistant
Professor/ECE/SNSCT