

Application

Thus the $\frac{\lambda}{4}$ - wave line is used to transform any resistance to an impedance with a magnitude equal to R_0 of the line.

(or)

To obtain a magnitude match between a resistance of any value and a source of R_0 internal resistance.

The quarter wave line

The expression for input impedance of a dissipation less line is rearranged as

$$Z_s = R_0 \left[\frac{\frac{Z_R}{\tan(2\pi s/\lambda)} + jR_0}{\frac{R_0}{\tan(2\pi s/\lambda)} + jZ_R} \right]$$

Subs $s = \lambda/4$ for quarter wave line

$$Z_s = R_0 \left[\frac{\frac{Z_R}{\tan \frac{2\pi}{\lambda} \times \frac{\lambda}{4}} + jR_0}{\frac{R_0}{\tan \frac{2\pi}{\lambda} \times \frac{\lambda}{4}} + jZ_R} \right]$$

$$Z_s = R_0 \left[\frac{\frac{Z_R}{\tan \pi/2} + jR_0}{\frac{R_0}{\tan \pi/2} + jZ_R} \right]$$

$$Z_s = R_0 \left[\frac{jR_0}{jZ_R} \right]$$

$$Z_s = \frac{R_0^2}{Z_R}$$

$$(or) R_0 = \sqrt{Z_s Z_R}$$

($\because \tan \pi/2 = \infty$)

Quarter wave line - Applications

1) Used as a transformer to match a load of Z_R ohms to a source of Z_S ohms.

Such a match can be obtained if the characteristic impedance R_0' of the matching quarter wave section of the line is chosen so that,

$$R_0' = \sqrt{Z_S Z_R}$$

2) Used as an impedance inverter to transform a low impedance into a high impedance and vice versa.



3) Used to couple a transmission line to a resistive load such as antenna.

4) Used if the load is not pure resistance.

It should be connected between points corresponding to I_{max} (or) E_{min} at which places the transmission line has resistive impedances given by R_0/s (or) $S R_0$.

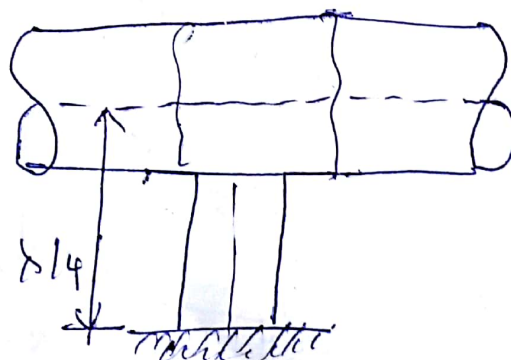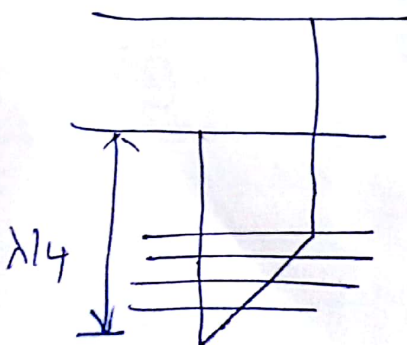5) Short circuited quarter wave line is used as an insulator to support an open-wire line or the center conductor of a coaxial line.

Such lines are referred to as copper insulators.



Quarter-wave lines as insulators