



**Dr. SNS RAJALAKSHMI COLLEGE OF ARTS & SCIENCE (Autonomous)**

**Coimbatore -641049**

Accredited by NAAC(Cycle-III) with 'A+' Grade  
(Recognized by UGC, Approved by AICTE, New Delhi and  
Affiliated to Bharathiar University, Coimbatore)

**DEPARTMENT OF GRAPHIC & CREATIVE DESIGN AND DATA ANALYTICS**

**COURSE NAME : COMPUTER SYSTEM ARCHITECTURE  
(23UCU402)**

**I YEAR /I SEMESTER**

**Unit II- Logic Gates  
Topic : K-MAP**



# Karnaugh Maps (K-Maps)

- A visual way to simplify logic expressions
- It gives the most simplified form of the expression

- Steps to solve expression using K-map-
- Select K-map according to the **number of variables**.
- Identify **minterms or maxterms** as given in problem.
- For SOP put **1's in blocks** of K-map respective to the minterms (0's elsewhere).
- For POS put **0's in blocks** of K-map respective to the maxterms(1's elsewhere).
- Make **rectangular groups** containing total terms in power of two like 2,4,8 ..(except 1) and try to cover as many elements as you can in one group.
- From the **groups made in step 5** find the product terms and sum them up for SOP form.

# Three-Variable K-Maps

$$f = \sum (0,4) = \bar{B} \bar{C}$$

		BC			
		00	01	11	10
A	0	1	0	0	0
A	1	1	0	0	0

$$f = \sum (4,5) = A \bar{B}$$

		BC			
		00	01	11	10
A	0	0	0	0	0
A	1	1	1	0	0

$$f = \sum (0,1,4,5) = \bar{B}$$

		BC			
		00	01	11	10
A	0	1	1	0	0
A	1	1	1	0	0

$$f = \sum (0,1,2,3) = \bar{A}$$

		BC			
		00	01	11	10
A	0	1	1	1	1
A	1	0	0	0	0

$$f = \sum (0,4) = \bar{A} C$$

		BC			
		00	01	11	10
A	0	0	1	1	0
A	1	0	0	0	0

$$f = \sum (4,6) = A \bar{C}$$

		BC			
		00	01	11	10
A	0	0	0	0	0
A	1	1	0	0	1

$$f = \sum (0,2) = \bar{A} \bar{C}$$

		BC			
		00	01	11	10
A	0	1	0	0	1
A	1	0	0	0	0

$$f = \sum (0,2,4,6) = \bar{C}$$

		BC			
		00	01	11	10
A	0	1	0	0	1
A	1	1	0	0	1

# Three-Variable K-Map Examples

		BC			
		00	01	11	10
A	0		1		
	1	1		1	1

		BC			
		00	01	11	10
A	0	1		1	1
	1	1			1

		BC			
		00	01	11	10
A	0			1	1
	1	1	1		

		BC			
		00	01	11	10
A	0			1	
	1	1		1	1

		BC			
		00	01	11	10
A	0		1	1	1
	1		1	1	

		BC			
		00	01	11	10
A	0				
	1				



# Four-Variable K-Maps

		CD			
	AB	00	01	11	10
00		1	0	0	0
01		0	0	0	0
11		0	0	0	0
10		1	0	0	0

$$f = \sum (0,8) = \bar{B} \cdot \bar{C} \cdot \bar{D}$$

		CD			
	AB	00	01	11	10
00		0	0	0	0
01		0	1	0	0
11		0	1	0	0
10		0	0	0	0

$$f = \sum (5,13) = B \cdot \bar{C} \cdot D$$

		CD			
	AB	00	01	11	10
00		0	0	0	0
01		0	0	0	0
11		0	1	1	0
10		0	0	0	0

$$f = \sum (13,15) = A \cdot B \cdot D$$

		CD			
	AB	00	01	11	10
00		0	0	0	0
01		1	0	0	1
11		0	0	0	0
10		0	0	0	0

$$f = \sum (4,6) = \bar{A} \cdot B \cdot \bar{D}$$

		CD			
	AB	00	01	11	10
00		0	0	1	1
01		0	0	1	1
11		0	0	0	0
10		0	0	0	0

$$f = \sum (2,3,6,7) = \bar{A} \cdot C$$

		CD			
	AB	00	01	11	10
00		0	0	0	0
01		1	0	0	1
11		1	0	0	1
10		0	0	0	0

$$f = \sum (4,6,12,14) = B \cdot \bar{D}$$

		CD			
	AB	00	01	11	10
00		0	0	1	1
01		0	0	0	0
11		0	0	0	0
10		0	0	1	1

$$f = \sum (2,3,10,11) = \bar{B} \cdot C$$

		CD			
	AB	00	01	11	10
00		1	0	0	1
01		0	0	0	0
11		0	0	0	0
10		1	0	0	1

$$f = \sum (0,2,8,10) = \bar{B} \cdot \bar{D}$$

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	1	1	1	1
	11	0	0	0	0
	10	0	0	0	0

$$f = \sum (4, 5, 6, 7) = \bar{A} \cdot B$$

		CD			
		00	01	11	10
AB	00	0	0	1	0
	01	0	0	1	0
	11	0	0	1	0
	10	0	0	1	0

$$f = \sum (3, 7, 11, 15) = C \cdot D$$

		CD			
		00	01	11	10
AB	00	1	0	1	0
	01	0	1	0	1
	11	1	0	1	0
	10	0	1	0	1

$$f = \sum (0, 3, 5, 6, 9, 10, 12, 15)$$

$$f = A \otimes B \otimes C \otimes D$$

		CD			
		00	01	11	10
AB	00	0	1	0	1
	01	1	0	1	0
	11	0	1	0	1
	10	1	0	1	0

$$f = \sum (1, 2, 4, 7, 8, 11, 13, 14)$$

$$f = A \oplus B \oplus C \oplus D$$

		CD			
		00	01	11	10
AB	00	0	1	1	0
	01	0	1	1	0
	11	0	1	1	0
	10	0	1	1	0

$$f = \sum (1, 3, 5, 7, 9, 11, 13, 15)$$

$$f = D$$

		CD			
		00	01	11	10
AB	00	1	0	0	1
	01	1	0	0	1
	11	1	0	0	1
	10	1	0	0	1

$$f = \sum (0, 2, 4, 6, 8, 10, 12, 14)$$

$$f = \bar{D}$$

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	0	0

$$f = \sum (4, 5, 6, 7, 12, 13, 14, 15)$$

$$f = B$$

		CD			
		00	01	11	10
AB	00	1	1	1	1
	01	0	0	0	0
	11	0	0	0	0
	10	1	1	1	1

$$f = \sum (0, 1, 2, 3, 8, 9, 10, 11)$$

$$f = \bar{B}$$

# Four-Variable K-Maps Examples

		CD			
		00	01	11	10
AB	00	1	1		1
	01	1	1		1
	11	1	1		1
	10	1	1		

		CD			
		00	01	11	10
AB	00	1	1		1
	01				1
	11				
	10	1	1		1

		CD			
		00	01	11	10
AB	00				
	01	1	1	1	
	11	1	1		1
	10	1			

		CD			
		00	01	11	10
AB	00		1	1	
	01	1	1	1	1
	11	1		1	1
	10			1	

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				





# Four-Variable K-Maps Examples

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				



# Four-Variable K-Maps Examples

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				




- Steps to design a combinational digital circuit:
  - From the problem statement derive the truth table
  - From the truth table derive the unsimplified logic expression
  - Simplify the logic expression
  - From the simplified expression draw the logic circuit
- Example: Design a 3-input (A,B,C) digital circuit that will give at its output (X) a logic 1 only if the binary number formed at the input has more ones than zeros.

	Inputs			Output
	A	B	C	
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

→  $X = \sum (3, 5, 6, 7)$

		BC			
		00	01	11	10
A	0	0	0	1	0
	1	0	1	1	1

$X = AC + AB + BC$

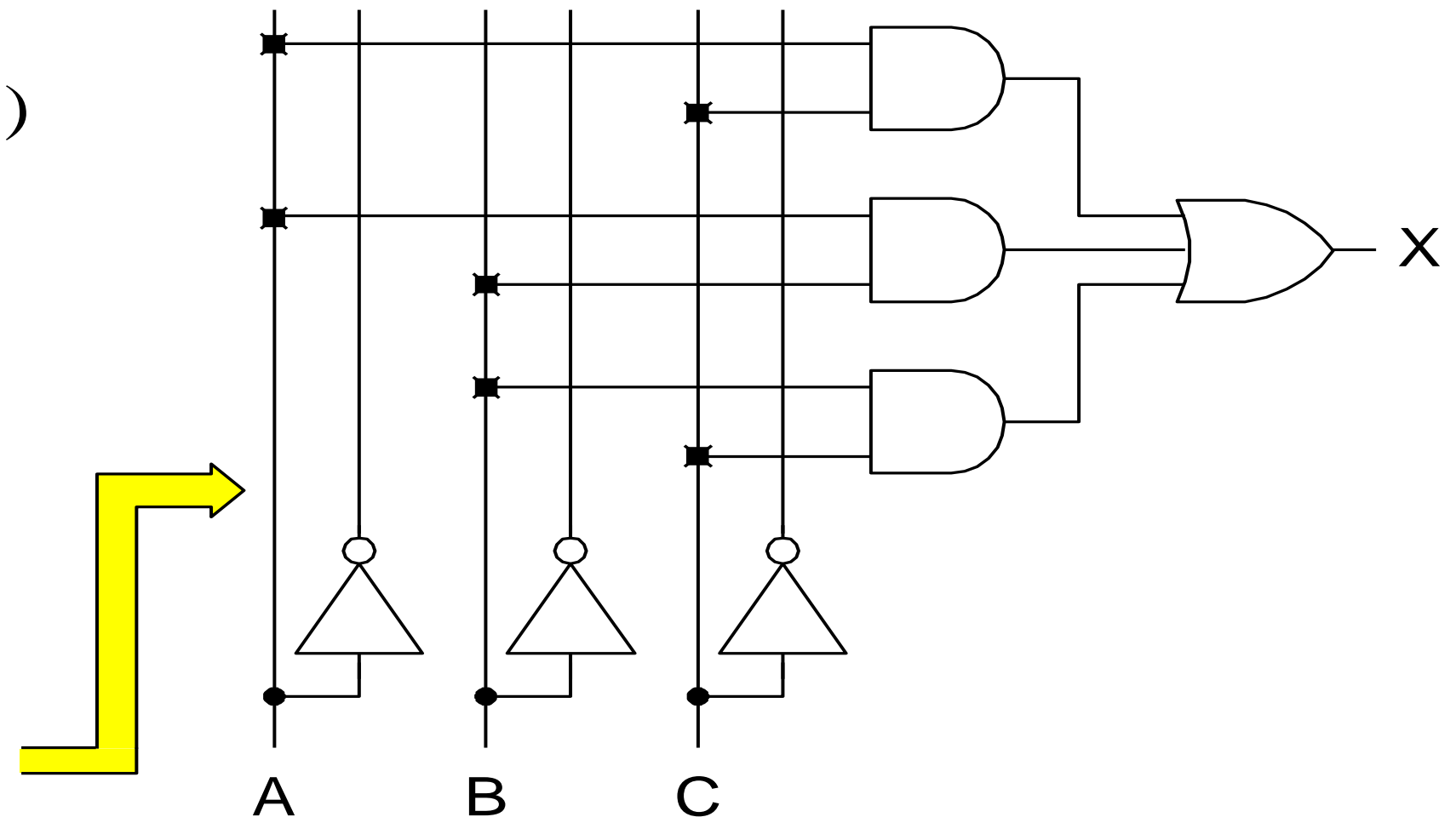

- Example: Design a 4-input (A,B,C,D) digital circuit that will give at its output (X) a logic 1 only if the binary number formed at the input is between 2 and 9 (including).

	Inputs				Output
	A	B	C	D	
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	0
15	1	1	1	1	0


→  $X = \sum (2,3,4,5,6,7,8,9)$

↓

AB \ CD	CD			
	00	01	11	10
00	0	0	1	1
01	1	1	1	1
11	0	0	0	0
10	1	1	0	0

↓
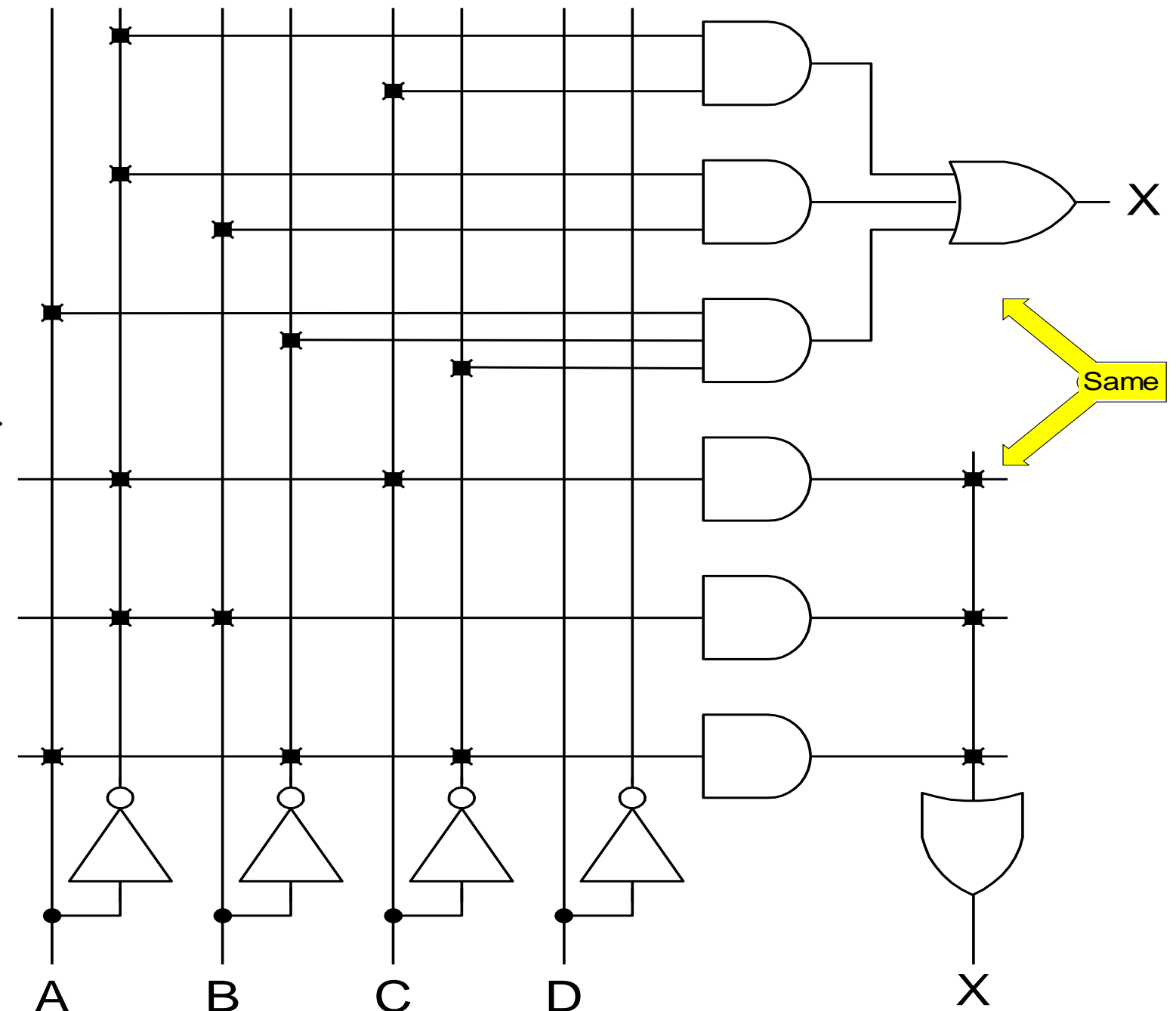
$$X = \bar{A}C + \bar{A}B + A\bar{B}\bar{C}$$



# Design of combinational digital circuits (Example)


- Example: Design a 4-input (A,B,C,D) digital circuit that will give at its output (X) a logic 1 only if there more ones than zeros in the binary number formed at the input.

	Inputs				Output	
	A	B	C	D		
0	0	0	0	0		
1	0	0	0	1		
2	0	0	1	0		
3	0	0	1	1		
4	0	1	0	0		
5	0	1	0	1		
6	0	1	1	0		
7	0	1	1	1		
8	1	0	0	0		
9	1	0	0	1		
10	1	0	1	0		
11	1	0	1	1		
12	1	1	0	0		
13	1	1	0	1		
14	1	1	1	0		
15	1	1	1	1		

X =

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

X =

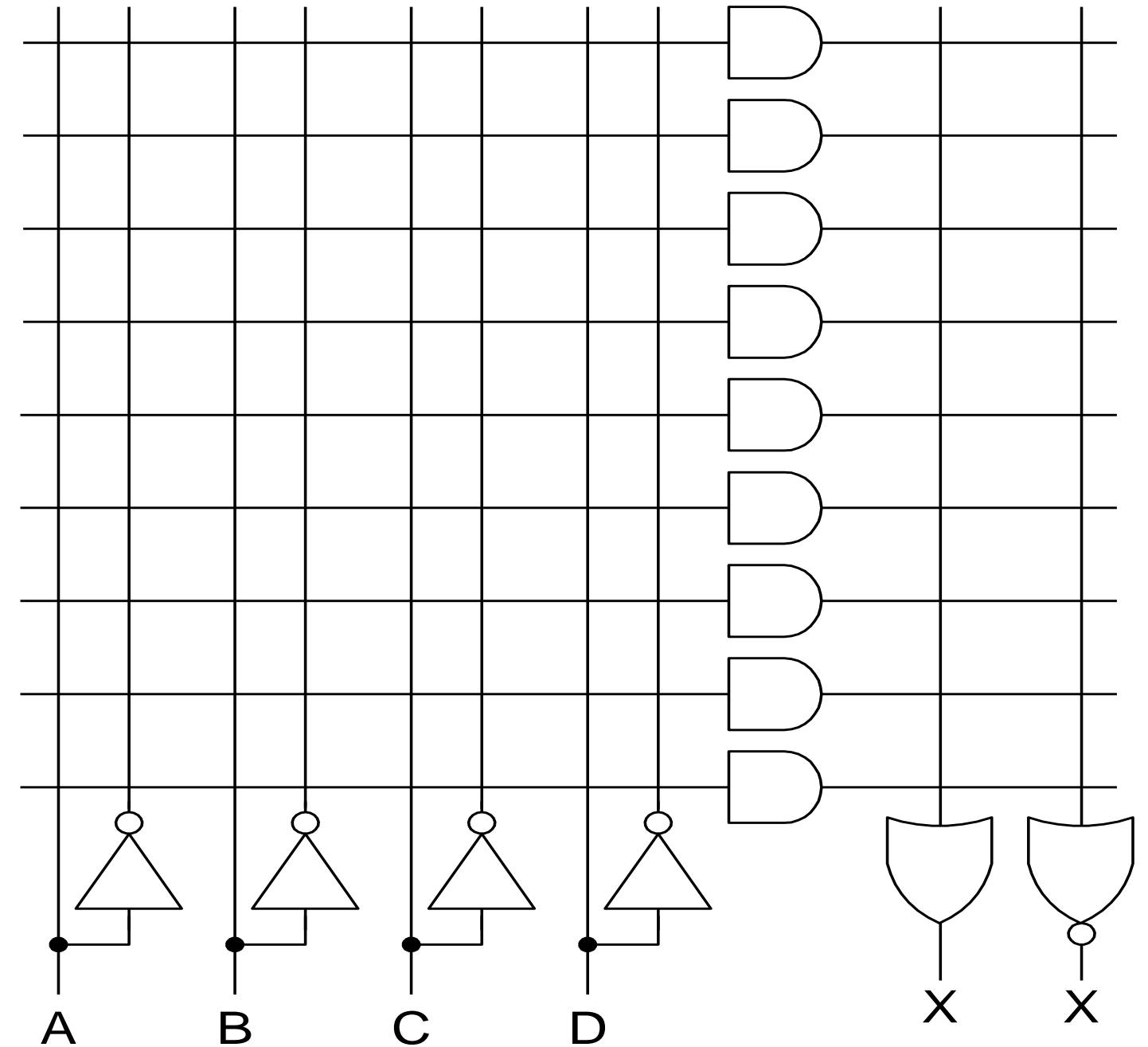

# References

- 1.M.Morris Mano, “Computer System Architecture” 3<sup>rd</sup> Edition, Prentice Hall of India ,2000, ISBN-10: 0131663631
2. V.K. Puri, –DIGITAL ELECTRONICS CIRCUITS AND SYSTEMS” McGraw Hill Education (1 July 2017). ISBN-10: 9780074633175 , ISBN-13: 978-0074633175
- 3.William Stallings, “Computer Organization and Architecture, Designing for Performance” PHI/ Pearson Education North Asia Ltd., 10th Edition 2016, ISBN 978-0-13-410161-3 — ISBN 0-13-410161-8.

## Thank You