

SNS COLLEGE OF TECHNOLOGY



(An Autonomous Institution)

Approved by AICTE, New Delhi, Affiliated to Anna University, Chennai

Accredited by NAAC-UGC with 'A++' Grade (Cycle III) &

Accredited by NBA (B.E - CSE, EEE, ECE, Mech & B.Tech.IT)

COIMBATORE-641 035, TAMIL NADU

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

Course Name: 23ECT203 LINEAR INTEGRATED CIRCUITS


II YEAR/VI SEMESTER

UNIT I –BASICS OF OPERATIONAL AMPLIFIERS

Topic : Ideal OP-AMP characteristics


Introduction to Ideal OP-AMP

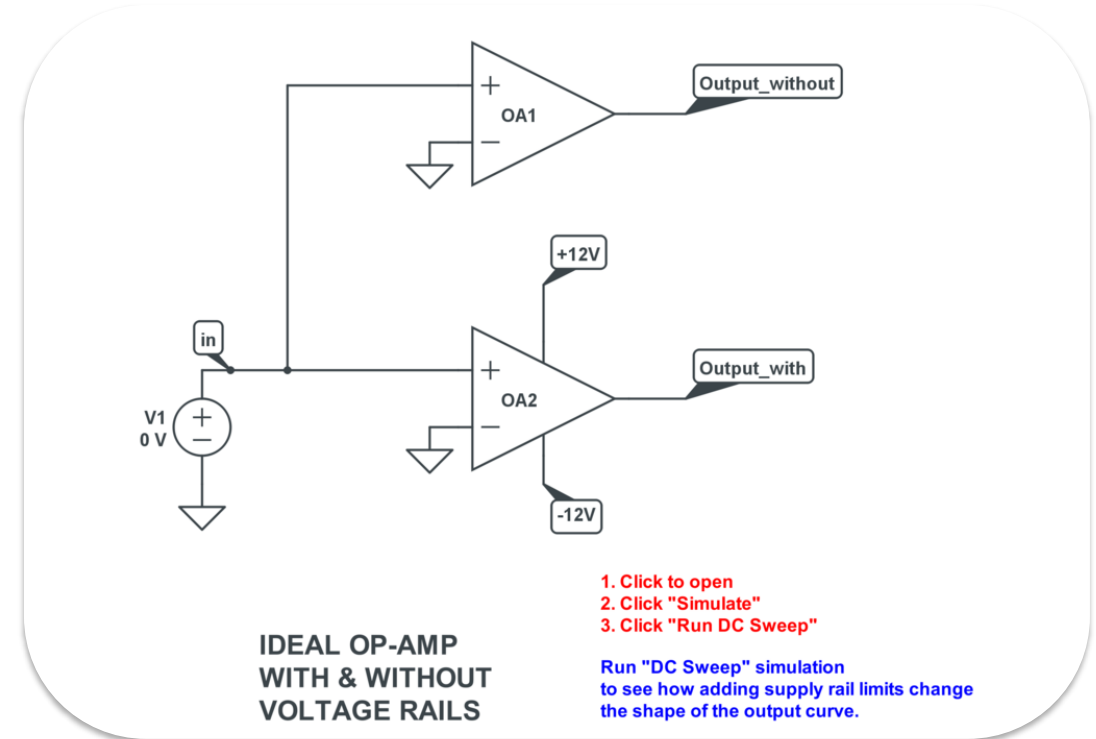- ✓ Infinite open-loop gain ($A = \infty$)
- ✓ Infinite input impedance ($Z_{in} = \infty$)
- ✓ Zero output impedance ($Z_{out} = 0$)
- ✓ Infinite bandwidth ($BW = \infty$)
- ✓ Zero offset voltage ($V_{io} = 0$)
- ✓ Zero input bias current ($I_b = 0$)
- ✓ Infinite CMRR (Common-mode rejection ratio)




Empathize

- ! **Real-world constraints:** Finite gain, bandwidth, and power supply limitations
- ! **Signal distortion:** Non-ideal characteristics cause output errors
- ! **Temperature effects:** Parameter drift affects circuit performance
- ! **Noise considerations:** Practical op-amps generate noise
- ! **Power consumption:** Ideal assumptions ignore energy requirements
- ! **Cost factors:** Higher performance increases component cost

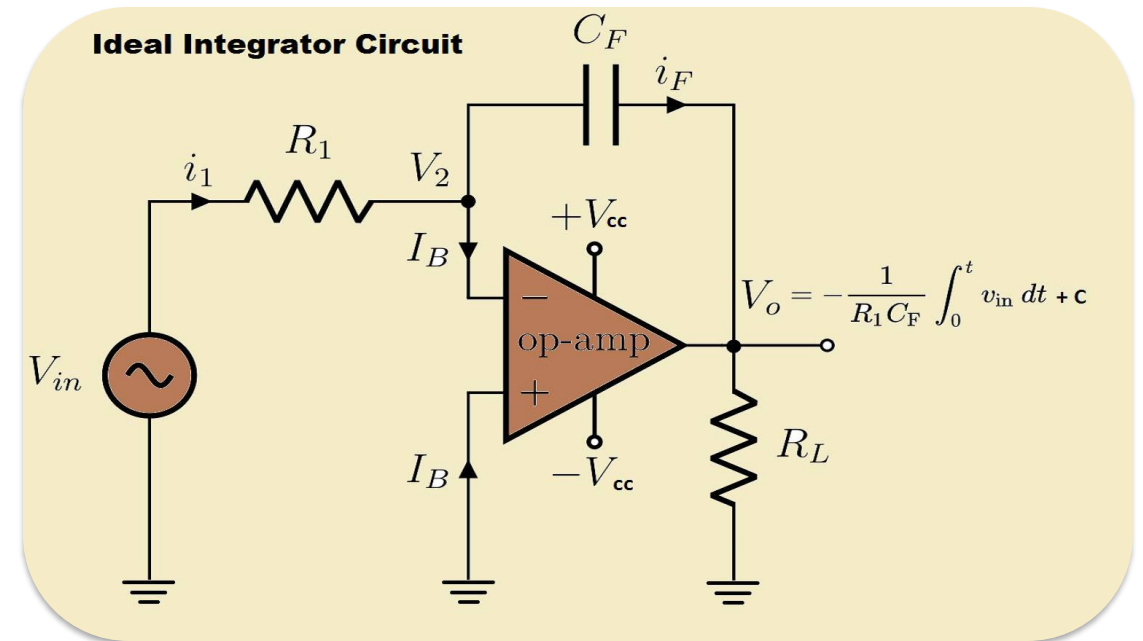





2 Define

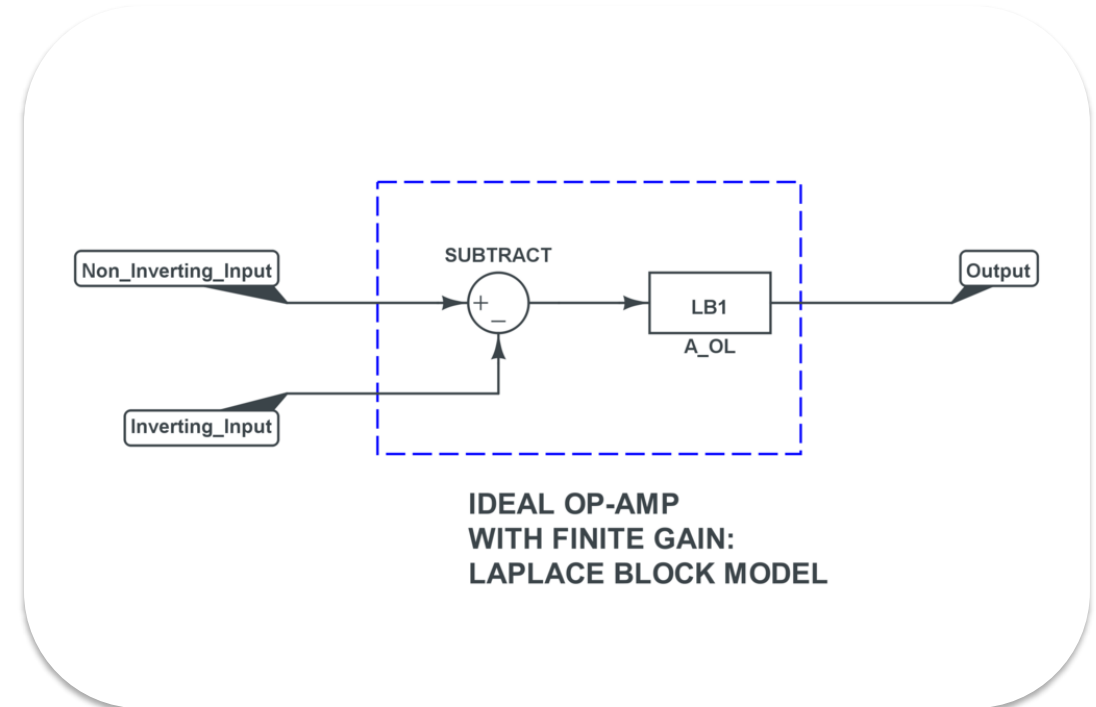- ⚙️ **Open-loop gain:** ∞ - Unlimited amplification capability
- ⚙️ **Input impedance:** ∞ - No current draw from input source
- ⚙️ **Output impedance:** 0Ω - Perfect voltage source
- ⚙️ **Bandwidth:** ∞ - Equal gain at all frequencies
- ⚙️ **Input offset voltage:** $0V$ - Zero output with zero input
- ⚙️ **Slew rate:** ∞ - Instantaneous response
- ⚙️ **CMRR:** ∞ - Perfect common-mode rejection




3 Ideate

- 💡 **Cascaded amplifiers:** Multiple stages to increase gain
- 💡 **Feedback techniques:** Negative feedback to improve stability
- 💡 **Buffer stages:** Input/output isolation for impedance matching
- 💡 **Frequency compensation:** Improving bandwidth response
- 💡 **Differential input:** Canceling common-mode signals
- 💡 **Precision trimming:** Reducing offset voltage and bias current
- 💡 **Hybrid configurations:** Combining multiple op-amp topologies

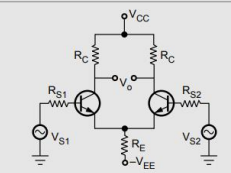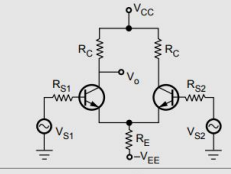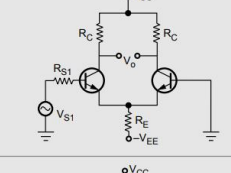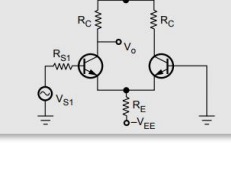Configuration	Circuit	A_d Voltage Gain	R_{in} Input Resistance	R_o Output Resistance
Dual Input Balanced Output		$\frac{h_{fe} R_C}{R_S + h_{ie}}$	$2(R_S + h_{ie})$	R_C
Dual Input Unbalanced Output		$\frac{h_{fe} R_C}{2(R_S + h_{ie})}$	$2(R_S + h_{ie})$	R_C
Single Input Balanced Output		$\frac{h_{fe} R_C}{R_S + h_{ie}}$	$2(R_S + h_{ie})$	R_C
Single Input Unbalanced Output		$\frac{h_{fe} R_C}{2(R_S + h_{ie})}$	$2(R_S + h_{ie})$	R_C


4 Prototype

- 🔧 **Breadboard implementation:** Quick circuit assembly and testing
- 🔧 **SPICE simulation:** Virtual testing before physical build
- 🔧 **Component selection:** Choosing parts with ideal-like characteristics
- 🔧 **Precision measurement:** Using test equipment to verify performance
- 🔧 **Iterative refinement:** Adjusting values to approach ideal behavior
- 🔧 **Temperature testing:** Evaluating performance across conditions
- 🔧 **Documentation:** Recording circuit behavior and deviations

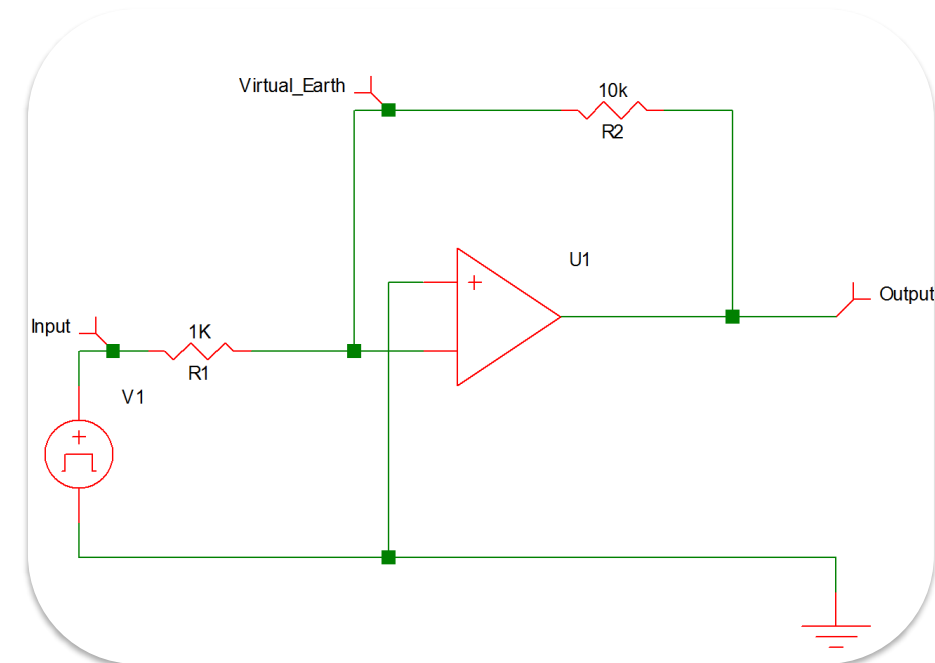

5 Test

- ▶ **Frequency response analysis:** Bode plot measurement
- ▶ **Slew rate testing:** Square wave response measurement
- ▶ **Input offset voltage:** Null circuit measurement
- ▶ **CMRR verification:** Common-mode vs. differential gain
- ▶ **Temperature drift:** Performance across temperature range
- ▶ **Noise analysis:** Output noise spectral density
- ▶ **Load regulation:** Output impedance measurement

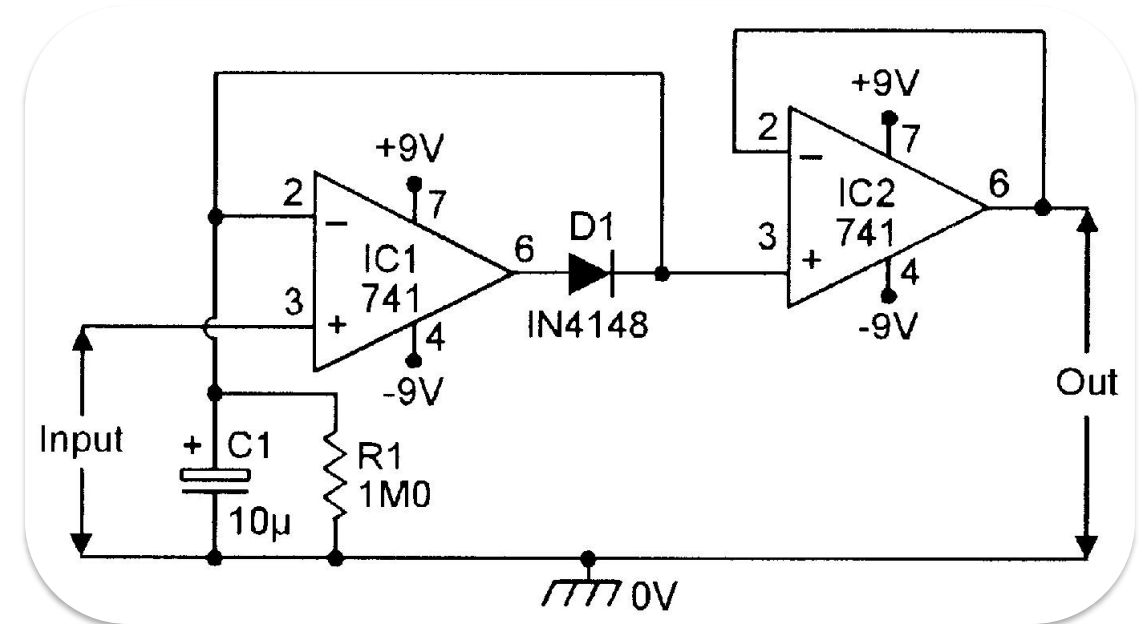

Key Ideal OP-AMP Parameters

↗ **Open-loop gain (A):** ∞ Unlimited amplification

➡ **Input impedance (Z_{in}):** ∞ No current draw


➡ **Output impedance (Z_{out}):** 0Ω Perfect voltage source

≡ **Bandwidth (BW):** ∞ Equal gain at all frequencies

⚡ **Input offset voltage (V_{io}):** $0V$ Zero output with zero input



✔ **Slew rate:** ∞ Instantaneous response

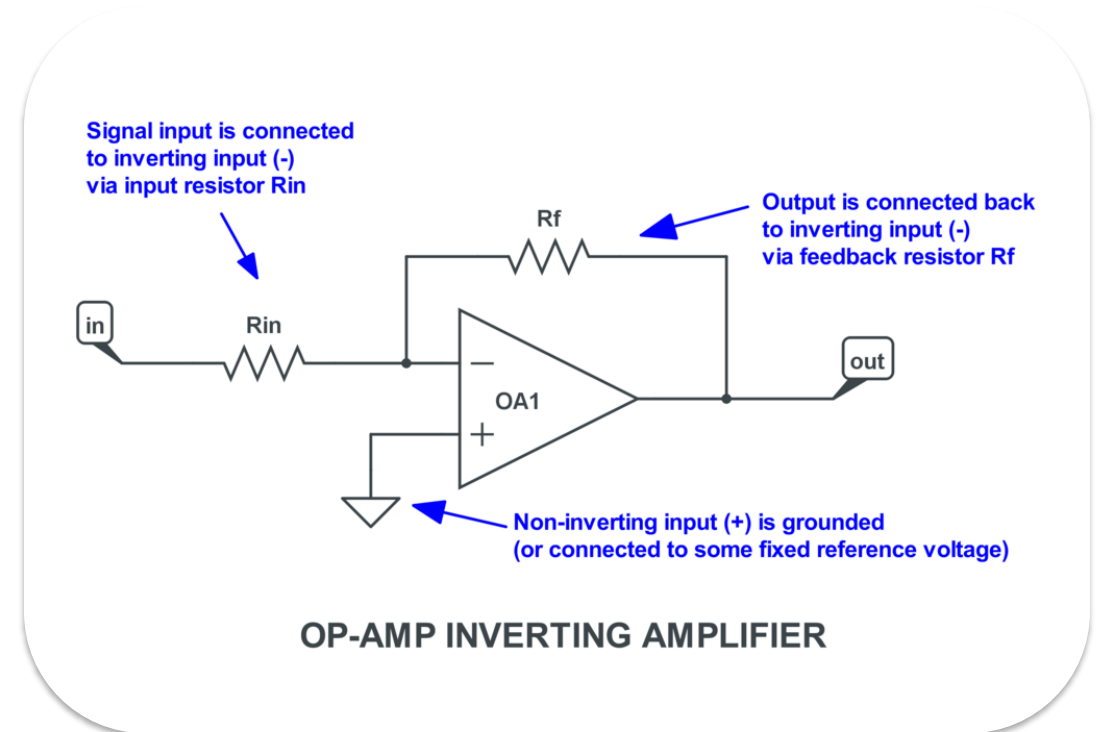↕ **CMRR:** ∞ Perfect common-mode rejection





Real-world Applications



Precision Amplifiers


-  **High-gain stages:** Exploiting near-infinite gain
-  **Instrumentation:** Accurate sensor signal conditioning

Active Filters

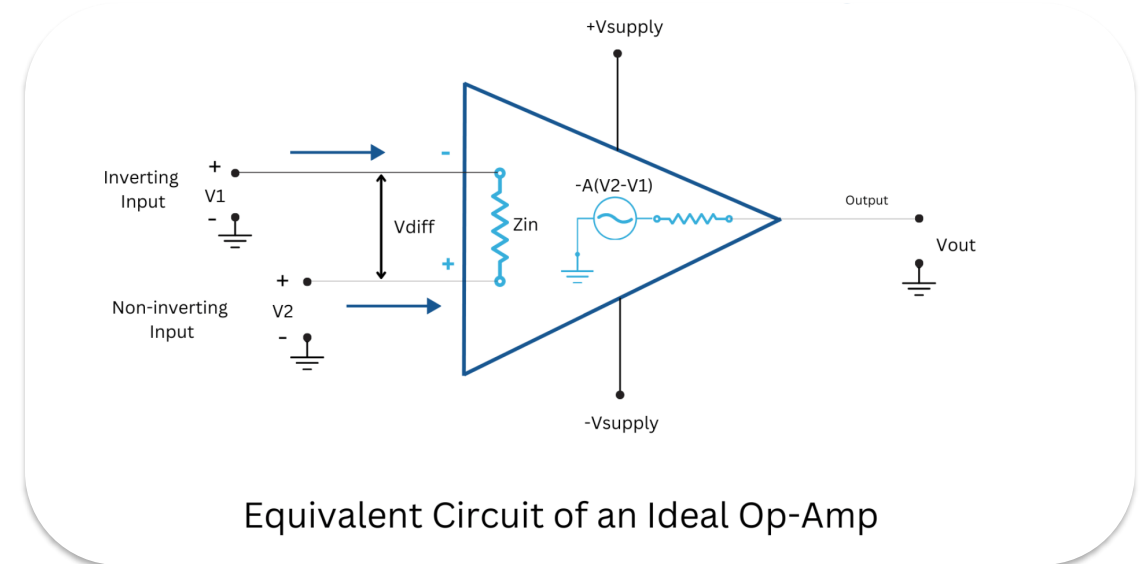-  **Frequency shaping:** Precise cutoff frequencies
-  **Q-factor control:** Adjustable filter characteristics





Signal Processing

-  **Buffering:** High input impedance, low output impedance
-  **Integrators/Differentiators:** Mathematical operations on signals



Activity

Activity Instructions

-  Form groups of 3-4 students
-  Discuss real-world limitations of ideal op-amp characteristics
-  Propose circuit solutions to compensate for non-ideal behavior
-  Prepare a 1-minute summary of your findings

Expected Outcome

- ✓ Identify key **practical limitations** in real op-amps
- ✓ Develop **compensation techniques** for non-ideal behavior
- ✓ Connect theory to **real-world applications**


Topic Focus

- ! **Finite gain** vs. infinite gain
- ! **Bandwidth limitations** and frequency response
- ! **Input/output impedance** effects on circuit performance

Group Discussion

5 min

Summary : MIND MAP

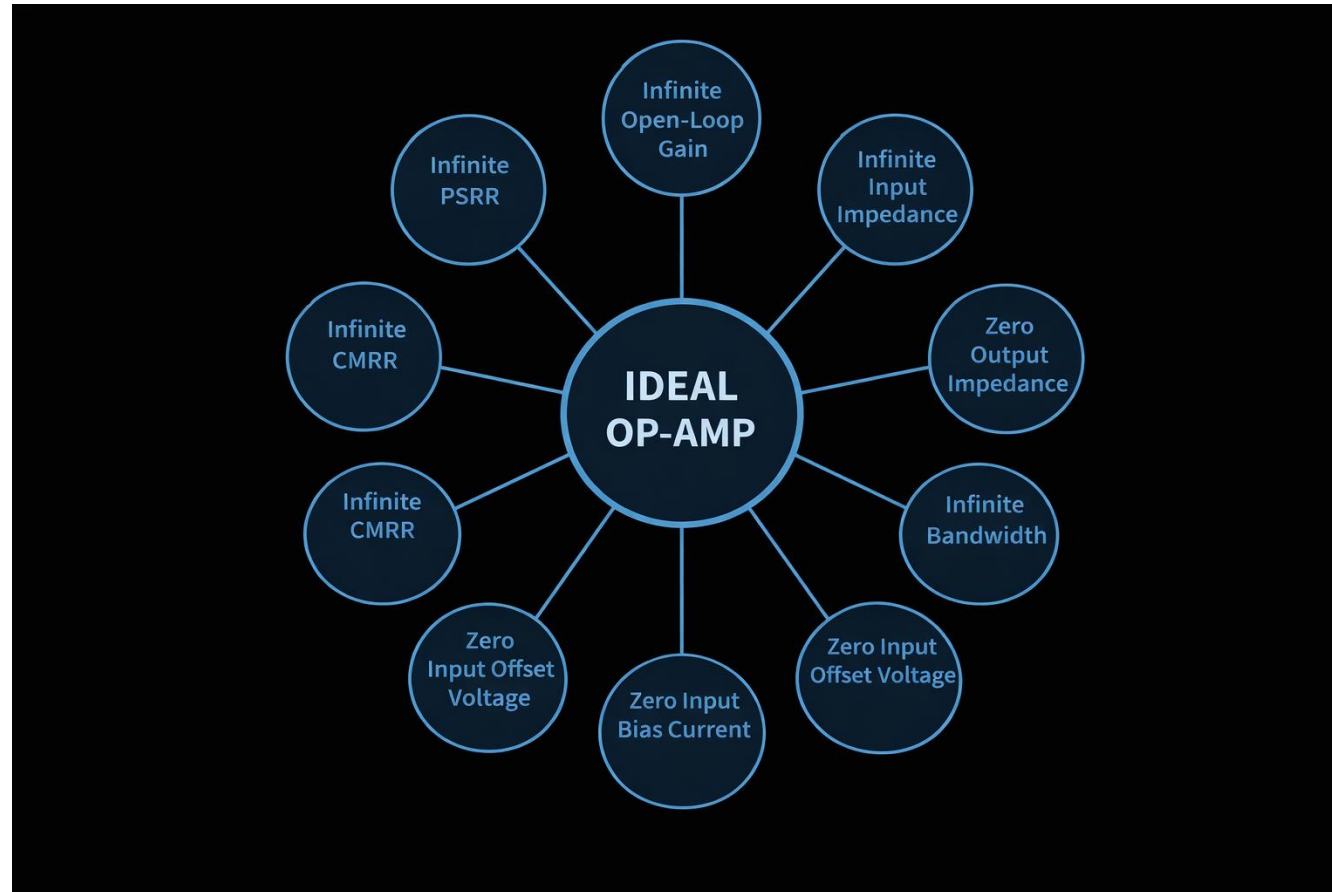



Conceptual Questions

- ② Explain why **infinite input impedance** is important in op-amp circuits
- ② Compare **ideal vs. real** op-amp bandwidth characteristics

Numerical Problems

- Σ Calculate output voltage of an ideal op-amp with $V_+ = 2.5V$, $V_- = 1.5V$, and gain = 10^5
- Σ Determine CMRR for an op-amp with differential gain = 10^5 and common-mode gain = 0.1

Application-Based Questions

- Δ Design a circuit to compensate for **finite input impedance** in a sensor interface
- Δ Explain how **slew rate limitations** affect high-frequency signal processing



Textbooks

- **Linear Integrated Circuits** - D. Roy Choudhry, Shail Jain, New Age International Pvt. Ltd., Fifth edition 2018
- **Design with Operational Amplifiers and Analog Integrated Circuits** - Sergio Franco, Tata Mc Graw-Hill, Fourth Edition 2014
- **OP-AMP and Linear ICs** - Ramakant A. Gayakwad, Prentice Hall/Pearson Education, 4th Edition 2001



Online Resources

- 🔗 **NPTEL:** Linear Integrated Circuits - https://onlinecourses.nptel.ac.in/noc24_ee73/preview
- 🔗 **Texas Instruments:** Operational Amplifier Basics - <https://www.ti.com/lit/an/sloa011a/sloa011a.pdf>
- 🔗 **Analog Devices:** Op Amp Applications Handbook - <https://www.analog.com/en/education/education-library/op-amp-applications-handbook.html>

THANK YOU