

SNS COLLEGE OF TECHNOLOGY



(An Autonomous Institution)

Approved by AICTE, New Delhi, Affiliated to Anna University, Chennai

Accredited by NAAC-UGC with 'A++' Grade (Cycle III) &

Accredited by NBA (B.E - CSE, EEE, ECE, Mech & B.Tech.IT)

COIMBATORE-641 035, TAMIL NADU

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING


Course Name: 23ECT203 LINEAR INTEGRATED CIRCUITS

II YEAR/VI SEMESTER

UNIT II –APPLICATIONS OF OPERATIONAL AMPLIFIERS

Topic : Differentiator and Integrator, Instrumentation amplifier

Stage 1: Empathize

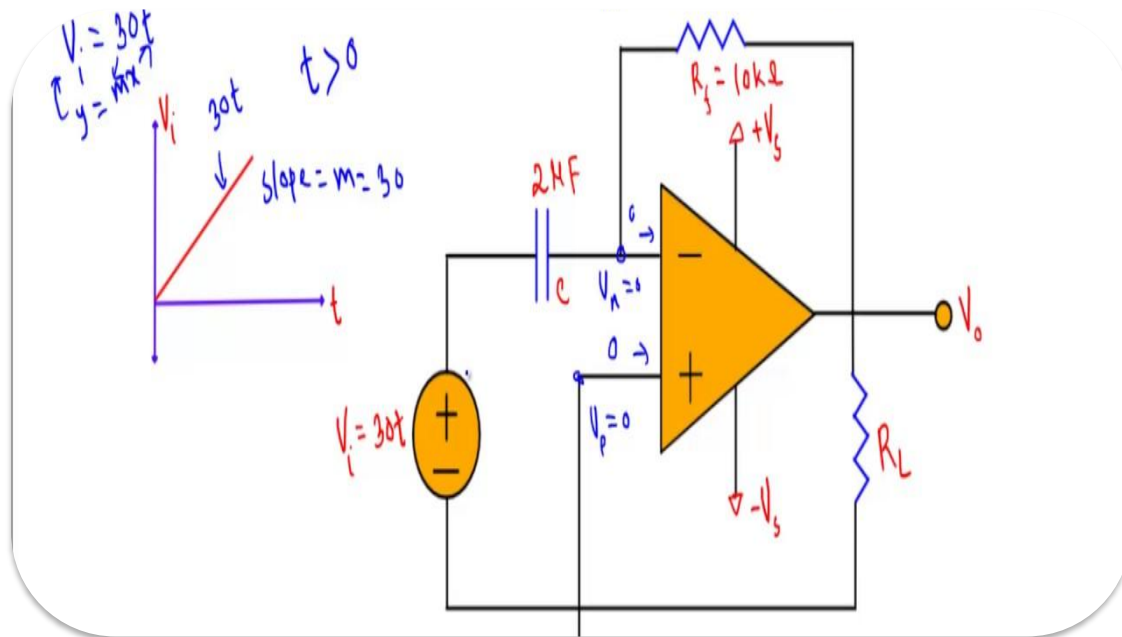

👤 Understand User Needs

Gain requirements, bandwidth specifications, noise tolerance

📊 Performance Requirements

Gain accuracy, frequency response, speed, precision


🚫 Identify Constraints

Power consumption, temperature range, size limitations, cost

⚙️ Practical Applications

Medical equipment, industrial controls, automotive systems

Stage 2: Define

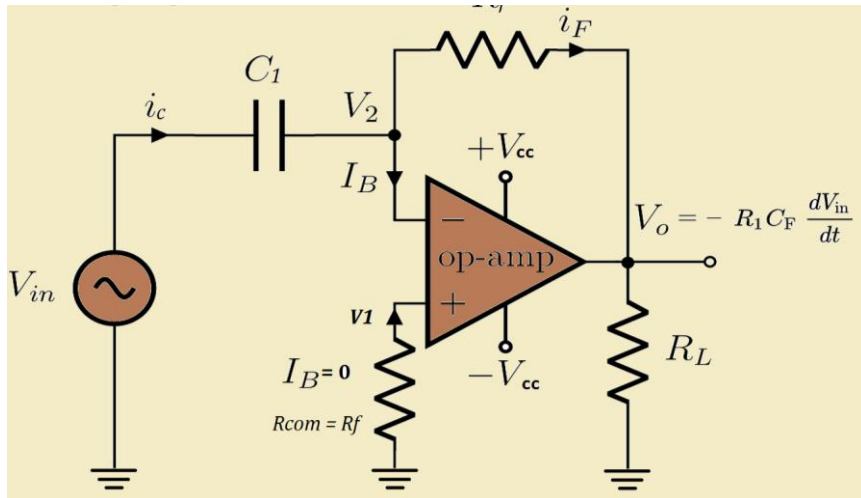

⚠ Problem Definition

- Circuit function
- Application needs
- Performance gaps

➡ Impedance Specs

- High input Z
- Low output Z
- Matching loads

📡 CMRR & Gain

- CMRR > 80dB
- Gain accuracy
- Bandwidth


✅ Success Criteria

- Metrics defined
- Test standards
- Tolerance limits

🚩 Design Goals Established

Optimize performance, minimize noise, ensure stability, meet power and thermal constraints

Stage 3: Ideate

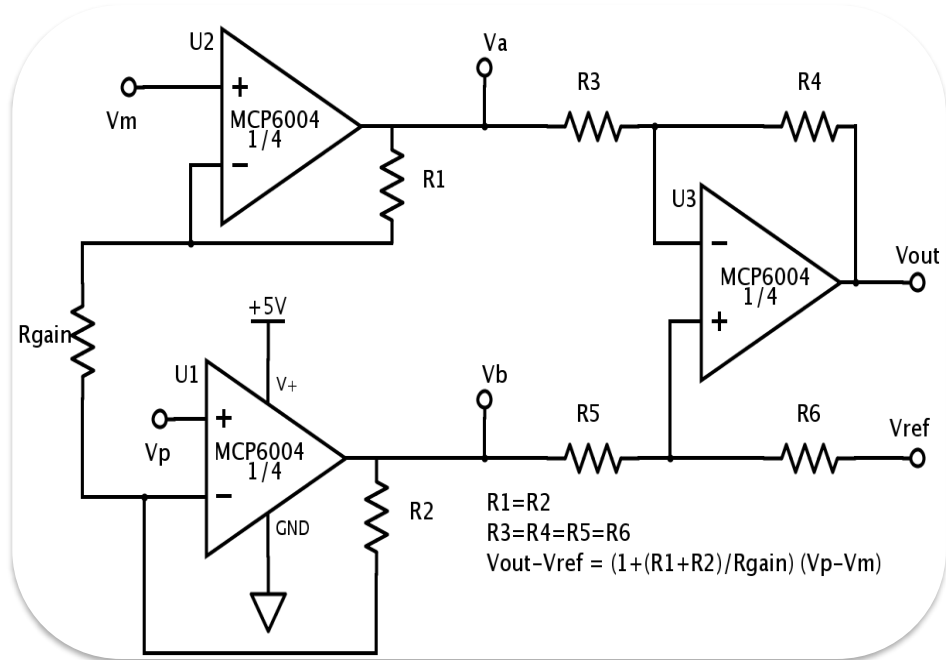

Circuit Configurations

- Differential pairs
- Feedback networks
- Multiple stages

Circuit Topologies

- Inverting configuration
- Non-inverting config
- Cascaded stages

Component Selection

- Precision op-amps
- Matched resistors
- Temperature-stable caps


Innovative Approaches

- Current-mode design
- Chopper stabilization
- Auto-zeroing techniques

Creative Solution Generation



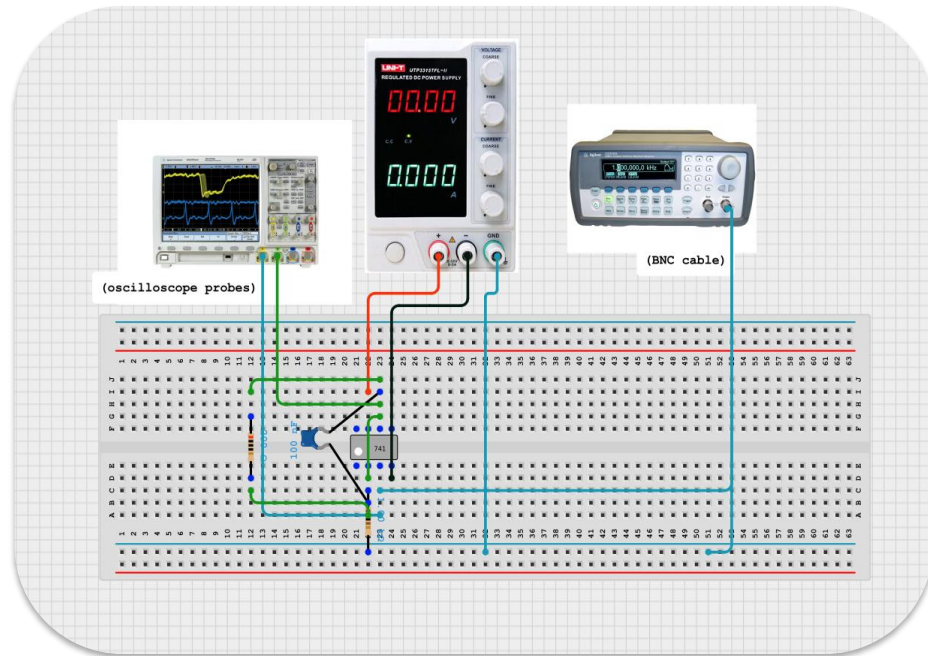Explore multiple circuit concepts, evaluate trade-offs, select optimal approach for specific



Simulation Tools

- SPICE analysis
- Multisim modeling
- Proteus design

Breadboarding

- Modular testing
- Stage-by-stage
- Real-time debugging

Testing Methods


- Frequency response
- Transient analysis
- Noise measurement

Iterative Refinement

- Component matching
- Precision selection
- Performance tuning

Rapid Prototyping Process

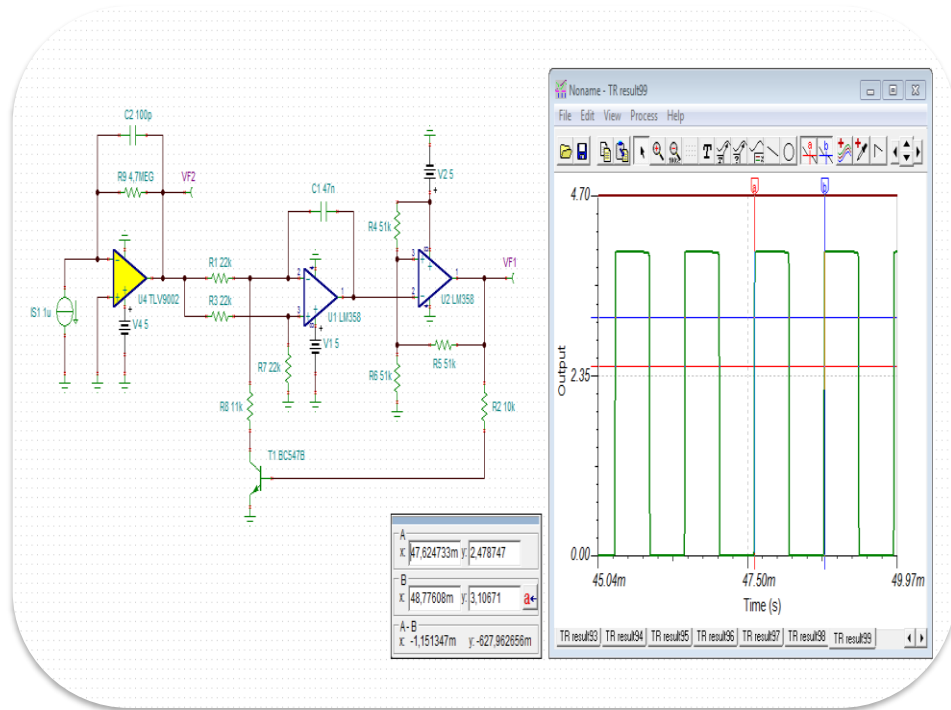Simulate → Breadboard → Test → Refine → Validate circuit performance before final implementation



Performance Testing

- Gain measurement
- Bandwidth analysis
- Noise evaluation
- Slew rate testing

Frequency Response


- Bode plot analysis
- Gain vs. frequency
- Phase margin check
- Stability testing

Noise Characterization

- Input noise density
- Output noise measurement
- Signal-to-noise ratio

CMRR & PSRR

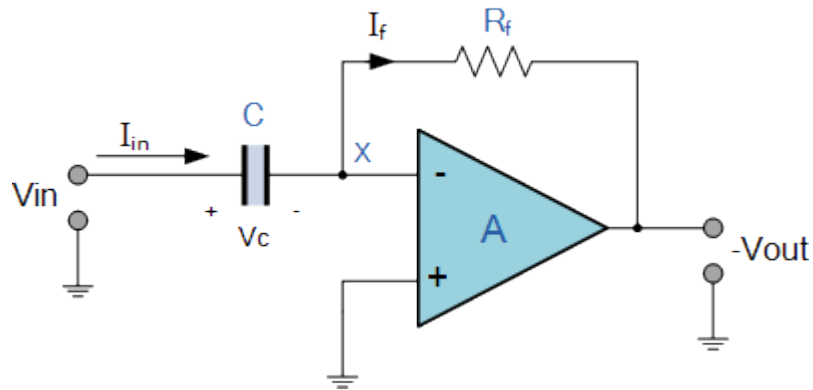- Common-mode rejection
- Power supply rejection
- Differential gain



Output Formula

$$V_{out} = -RC (dV_{in}/dt)$$



Configuration

- Capacitor in input
- Resistor in feedback
- Op-amp based



Characteristics

- Differentiates signal
- High pass filter
- Noise sensitive



Applications

- Slope detection
- Edge detection
- Pulse shaping



Exam Points


- Gain \propto frequency
- RC time constant
- Low-noise needed



Limitations

- High-frequency noise
- Stability issues
- Bandwidth limited

OP-Amp Integrator

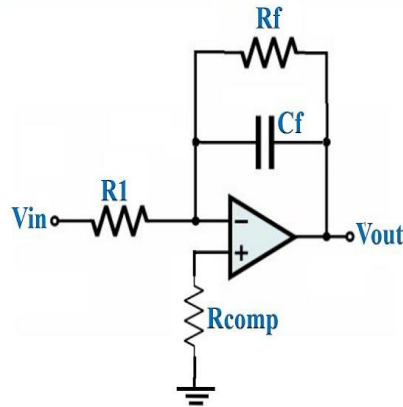

Σ Output Formula

$$V_{out} = -(1/RC) \int V_{in} dt$$

🔧 Configuration

- Resistor in input
- Capacitor in feedback
- Op-amp based

📈 Characteristics

- Integrates signal
- Low pass filter
- Accumulates input

🏠 Applications


- Analog computation
- Ramp generation
- Average value

🎓 Exam Points

- RC time constant
- Integration rate
- DC offset issue

📌 Note

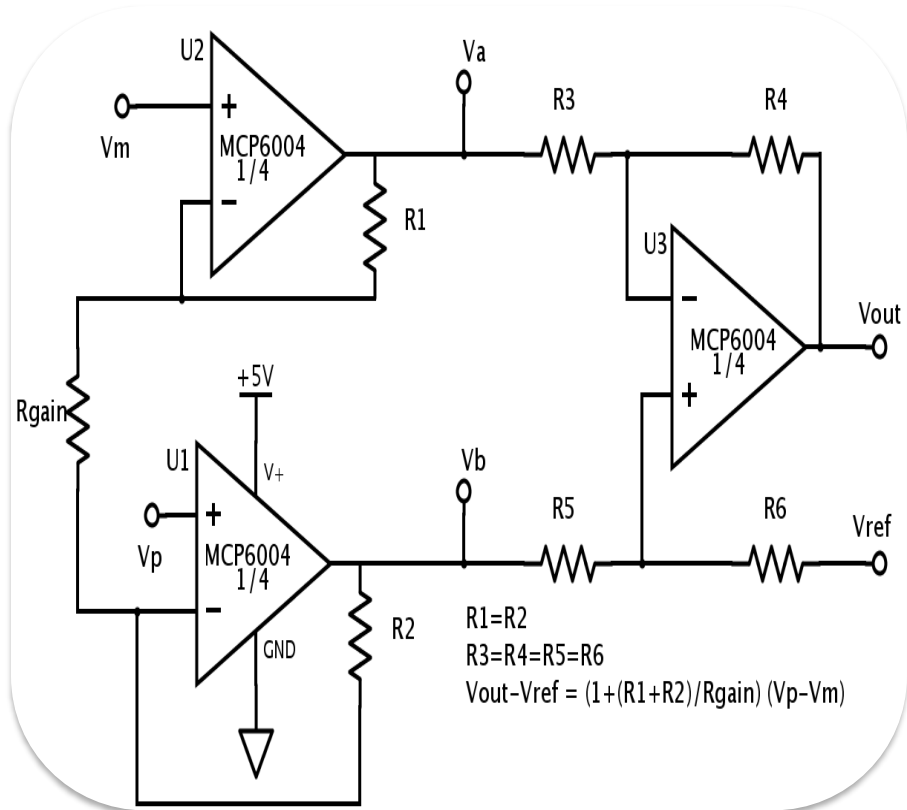- Prevents saturation
- Need reset circuit
- Frequency limit



Output Formula

$$V_{out} = (1 + 2R/R_g)(V_2 - V_1)$$



Configuration

- Three op-amp design
- Input buffers
- Differential output



Characteristics

- High input Z
- High CMRR
- Precision gain



Applications

- Sensor interfacing
- Bridge measurements
- Biomedical



Gain Control

- Single resistor R_g
- Adjustable gain
- Wide range



Exam Points

- Gain formula
- Differential input
- Buffer stage

Differentiator

Function

Differentiates input signal

Filter Type

High Pass Filter

Noise Immunity

Low - Sensitive

Applications

Edge detection, slope detection, pulse shaping

Integrator

Function

Integrates input signal over time

Filter Type

Low Pass Filter

Noise Immunity

High - Rejects

Applications

Analog computation, ramp generation, averaging

Instrumentation

Function

Differential amplification

Filter Type

Differential Filter

Noise Immunity

Very High (CMRR)

Applications

Sensor interfacing, biomedical, bridge measurements

When to Use Each Circuit

Differentiator: Edge detection, slope measurement, high-frequency signals

Integrator: Signal averaging, ramp generation, analog computation

Instrumentation: Precision measurements, sensor interfacing, differential signals

Design Thinking Stages

- Explain how Empathize applies to circuit design
- Define problem for amplifier circuits
- Ideate multiple circuit configurations
- Prototype simulation and testing methods
- Validate performance requirements

Differentiator Circuit

- Derive $V_{out} = -RC(dV_{in}/dt)$ formula
- Explain high-pass filter characteristics
- Discuss noise sensitivity issues
- Applications in edge detection

Integrator Circuit

- Derive $V_{out} = -(1/RC)\int V_{in} dt$ formula
- Explain low-pass filter characteristics
- Discuss signal accumulation effect
- Applications in analog computation

Instrumentation Amplifier

- Explain CMRR importance
- Derive gain formula $V_{out} = (1+2R/R_g)(V_2-V_1)$
- Discuss high input impedance advantage
- Applications in sensor interfacing

Activity: Design Thinking Applied to Amplifier Circuits

1

THINK

2 minutes



Individual Reflection

- Compare advantages and disadvantages of differentiator, integrator, and instrumentation amplifiers
- Consider noise immunity, frequency response, and application suitability
- Identify key differentiating factors for exam preparation

2

PAIR

2 minutes



Partner Discussion

- Which amplifier is best for sensor interfacing? Why?
- Compare differentiator vs integrator for pulse shaping
- Discuss trade-offs for high-noise environments

3

SHARE

1 minute



Group Presentation

- Present your group's amplifier selection decision
- Explain design thinking reasoning used
- Share key insights with the class

Mind Map - Design Thinking & Amplifier Circuits



Empathize

Understand user needs



Integrator

$$V_{out} = -(1/RC) \int V_{in} dt$$

Low pass filter




Define

Identify problems



Test

Validate solutions



Design Thinking & Amplifier Circuits



Differentiator

$$V_{out} = -RC(dV_{in}/dt)$$

High pass filter



Ideate

Generate solutions



Instrumentation

$$V_{out} = (1+2R/R_g)(V_2-V_1)$$

High CMRR



Prototype

Build models



Textbooks

1

D. Roy Choudhry & Shail Jain

"Linear Integrated Circuits"

2

Sergio Franco

"Design with Operational Amplifiers"

3

Ramakant A. Gayakwad

"OP-AMP and Linear ICs"

4

Robert F. Coughlin & Frederick F. Driscoll

"Operational Amplifiers and Linear Integrated Circuits"



Online Resources



Texas Instruments

Op-Amp Design Handbook



Analog Devices

Op-Amp Applications Handbook



Electronics Tutorials

Operational Amplifier Circuits



NPTEL

Linear Integrated Circuits Course



Thank You

