

SNS COLLEGE OF TECHNOLOGY



(An Autonomous Institution)

Approved by AICTE, New Delhi, Affiliated to Anna University, Chennai

Accredited by NAAC-UGC with 'A++' Grade (Cycle III) &

Accredited by NBA (B.E - CSE, EEE, ECE, Mech & B.Tech.IT)

COIMBATORE-641 035, TAMIL NADU

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

Course Name: 23ECT203 LINEAR INTEGRATED CIRCUITS


II YEAR/VI SEMESTER

UNIT I –BASICS OF OPERATIONAL AMPLIFIERS

Topic : Internal Circuit of IC 741


Introduction to IC 741

- The 741 is a classic operational amplifier IC introduced in 1968
- Widely used in analog circuits due to its stability and versatility
- Understanding internal circuit helps in troubleshooting and design optimization
- Consists of three main stages: input, intermediate, and output stage

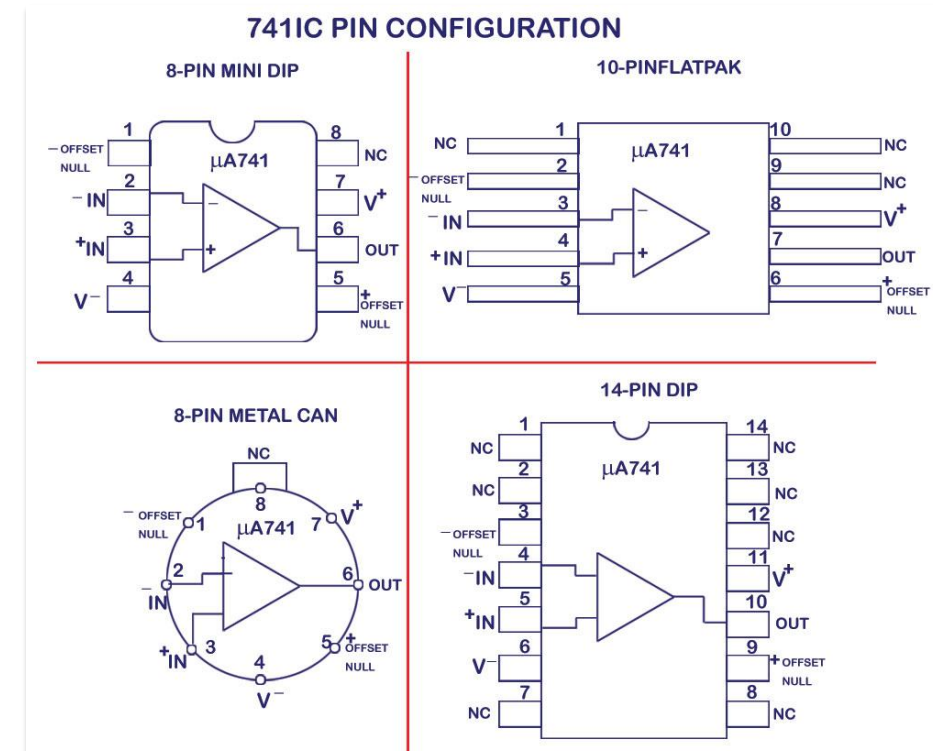


Stage 1: Empathize - Understanding IC 741 Challenges

- Complex internal circuit with 20 transistors makes analysis difficult
- Temperature variations affect circuit performance
- Understanding internal stages crucial for troubleshooting
- Students struggle with connecting theory to practical implementation

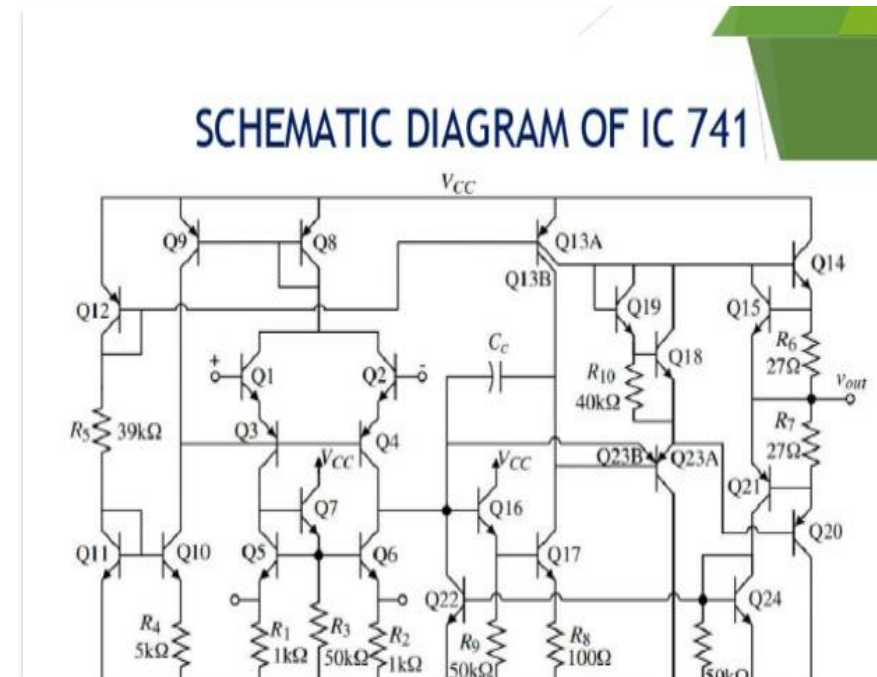


Stage 2: Define - IC 741 Circuit Requirements

- Input Stage: Differential amplifier with high input impedance
- Intermediate Stage: High voltage gain with frequency compensation
- Output Stage: Low output impedance with current limiting
- Bias Network: Provides stable reference voltages for all stages

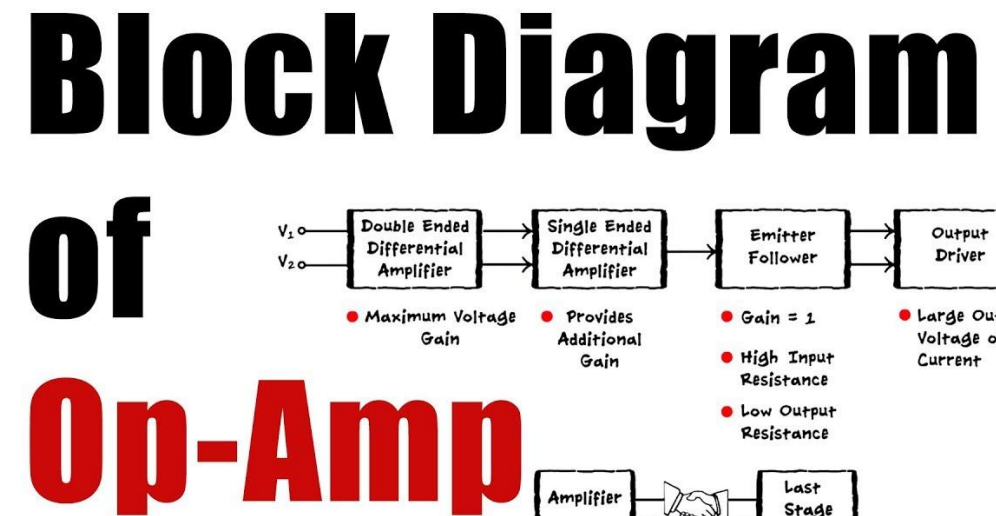


Stage 3: Ideate - IC 741 Circuit Solutions

- Simplify analysis by breaking circuit into functional blocks
- Use equivalent circuits to understand each stage's behavior
- Apply mathematical models for quantitative analysis
- Design experiments to verify theoretical predictions

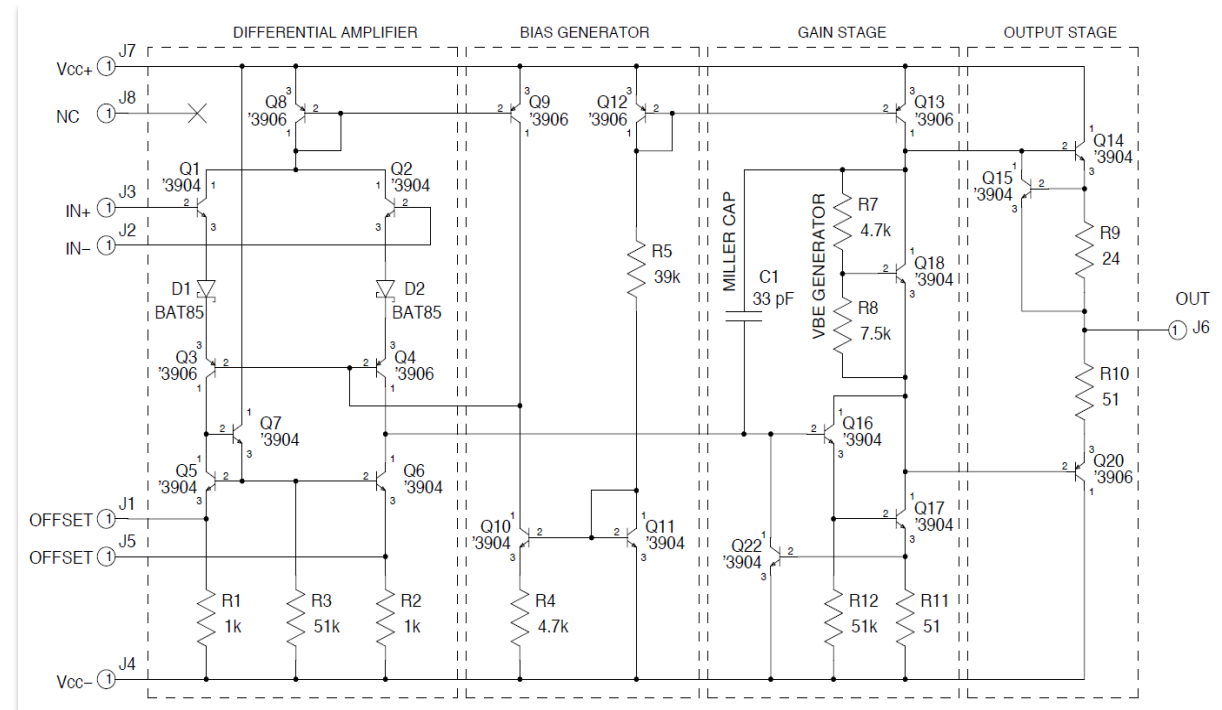


Stage 4: Prototype - Building IC 741 Circuits

- Create simplified models of each internal stage
- Build test circuits on breadboards to verify functionality
- Use simulation software to predict circuit behavior
- Document all connections and measurements for analysis

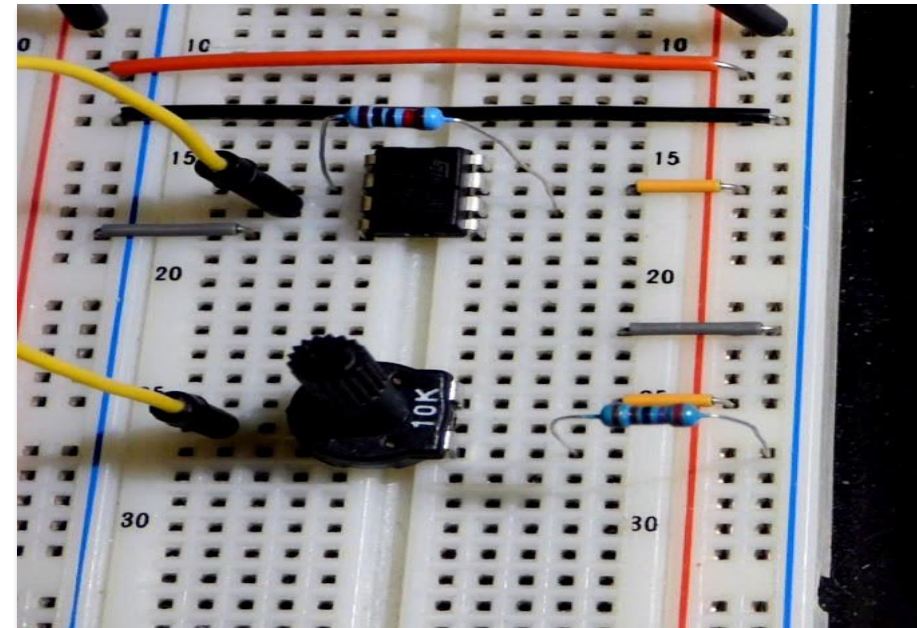


Stage 5: Test - Evaluating IC 741 Performance

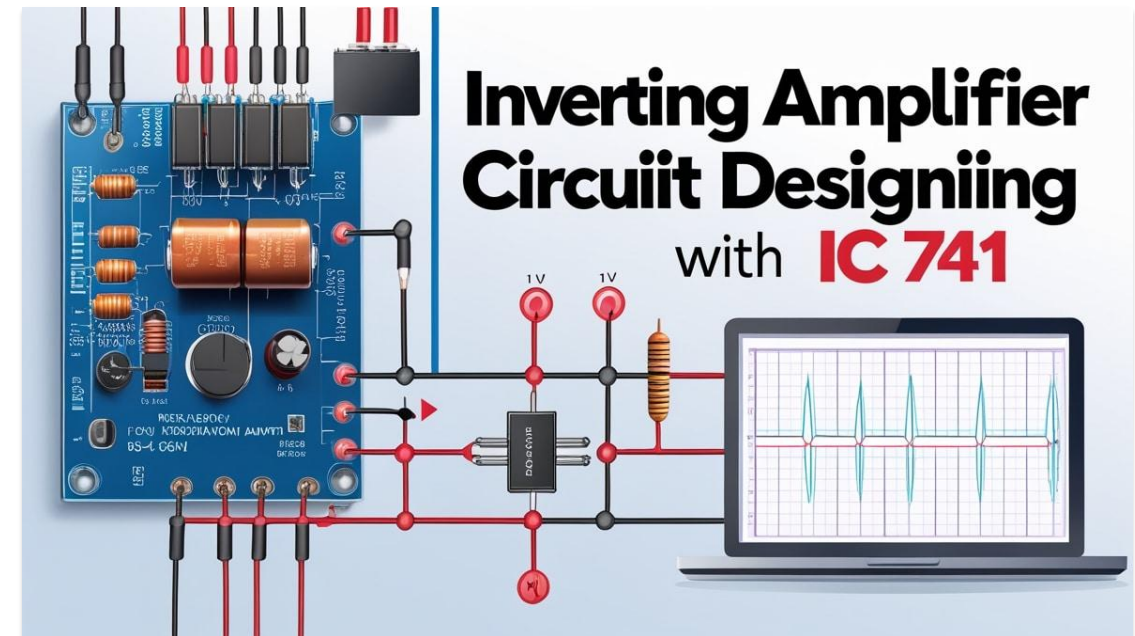- Measure input/output characteristics of each stage
- Compare measured values with theoretical predictions
- Test circuit behavior under different conditions
- Document performance limitations and improvement strategies




Input Stage of IC 741

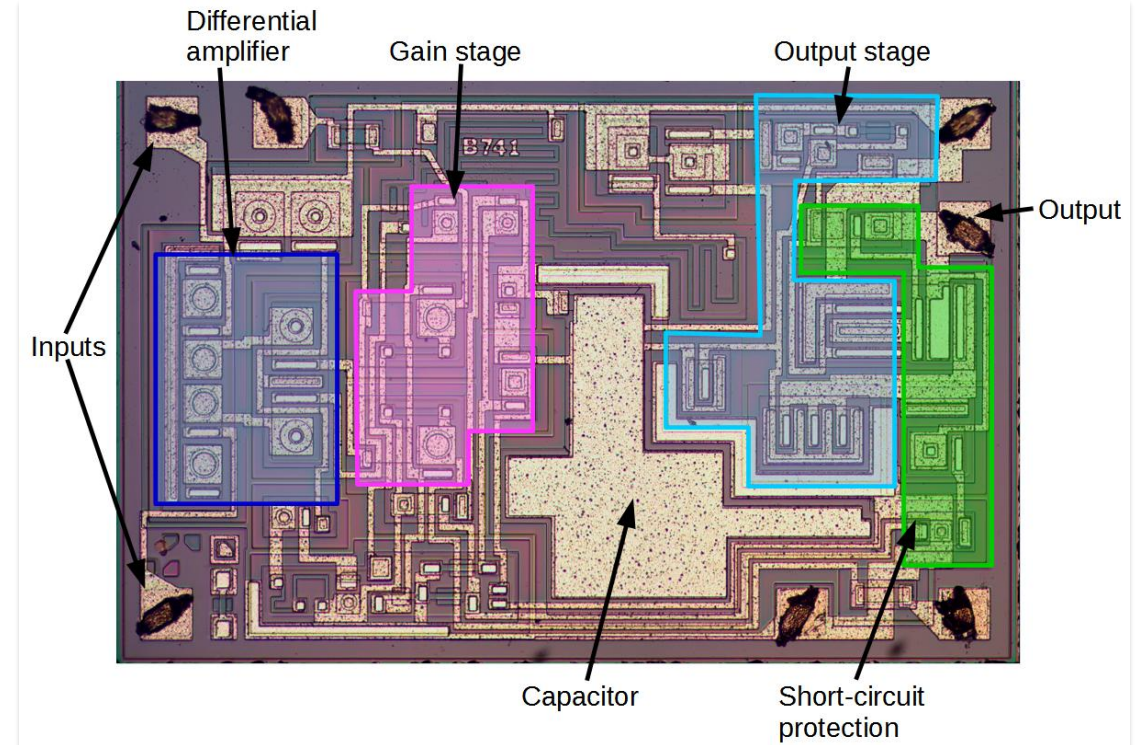- Differential amplifier configuration (Q1-Q4)
- Provides high input impedance and common-mode rejection
- Current mirror (Q5-Q6) improves linearity
- Input bias current compensation network (Q7-Q8)



Intermediate Stage of IC 741

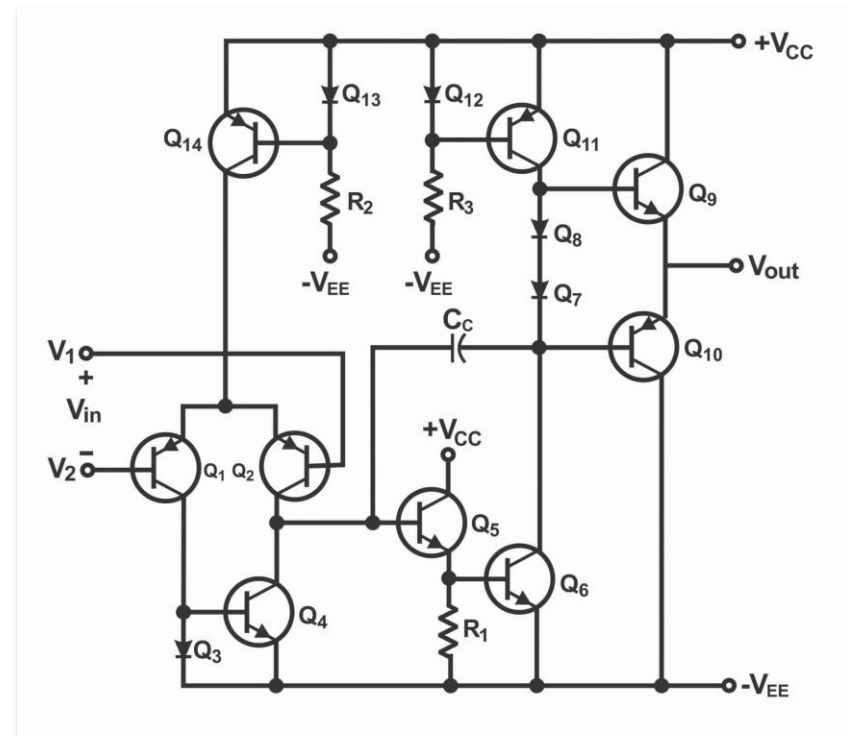- Darlington pair (Q16-Q17) provides high voltage gain
- Frequency compensation capacitor (C1) prevents oscillation
- Current source (Q13) provides stable biasing
- Buffer transistor (Q20) isolates input from output



Activity: THINK PAIR SHARE

THINK (2 minutes)


Analyze the given IC 741 circuit and identify its internal stages

PAIR (2 minutes)


Discuss your findings with a partner and compare notes

SHARE (1 minute)

Present your analysis to the class

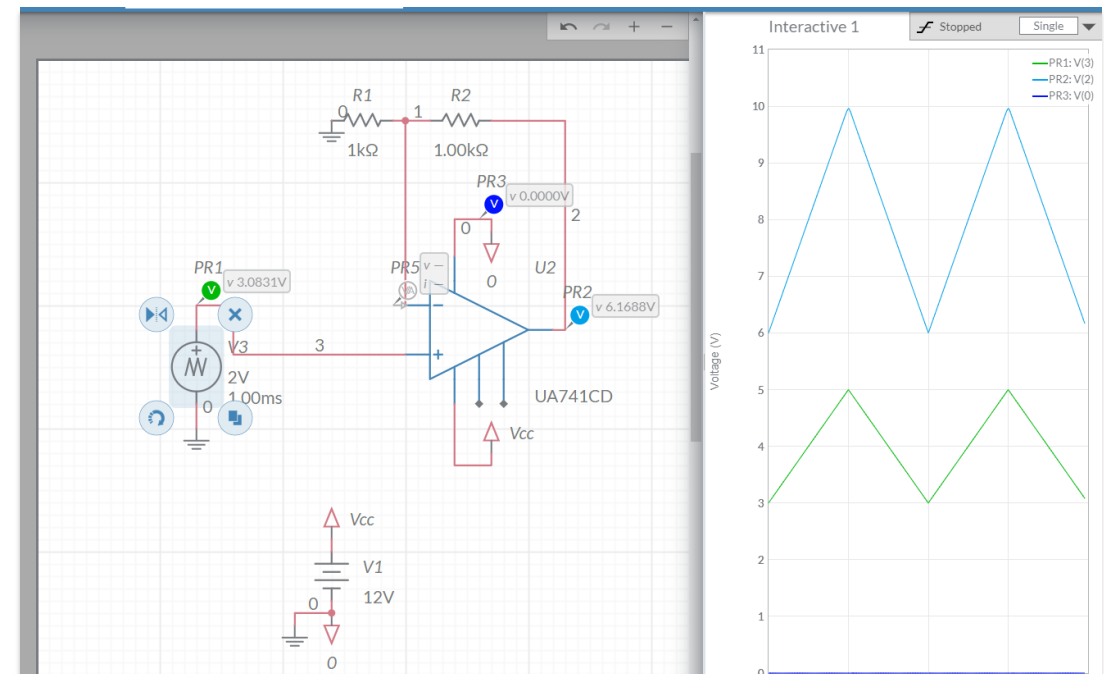

Mind Map: IC 741 Internal Circuits

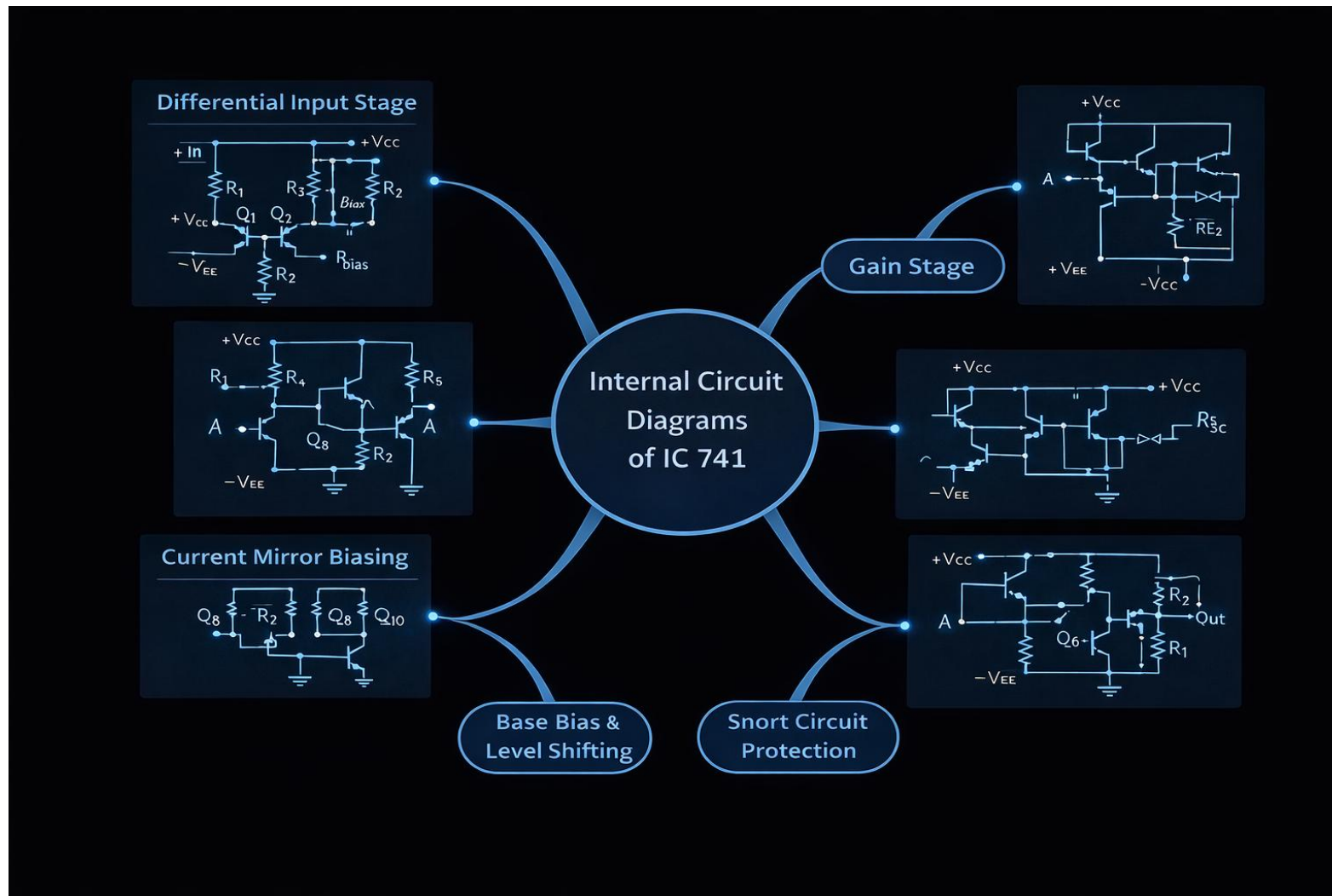

Assessment: IC 741 Internal Circuits

Short Answer

Explain the function of each internal stage

Problem Solving

Calculate voltage gain of the intermediate stage

Application

Design a simple circuit using IC 741

Critical Thinking

Compare ideal vs. real IC 741 characteristics

1). Op-Amp is abbreviated as _____.

Operational Amplifier

Operand amplitude

Operational amplitude

None of the above

2). Op-Amp is a _____ type of amplifier.

Current Voltage Power Resistance

3). Op-Amp is _____ coupled voltage type of amplifier.

AC DC ADC DAC

4). Op-Amp has _____ gain.

High Low Zero Medium

5). A device with direct current coupled, high gain electronic voltage type amplifier with one output and differential input is called _____.

Rectifier Amplifier Transformer Op-amp

6). Op-Amp has _____ inputs.

Single Similar Zero Differential


7). Op-Amp has _____ outputs.

Single Similar Multiple Differential

References

 **Linear Integrated Circuits** D. Roy Choudhry, Shail Jain New Age International Pvt. Ltd., Fifth edition 2018

 **Design with Operational Amplifiers and Analog Integrated Circuits** Sergio Franco Fourth Edition, Tata Mc Graw-Hill, 2014

 **OP-AMP and Linear ICs** Ramakant A. Gayakwad 4th Edition, Prentice Hall / Pearson Education, 2001

 **uA741 Datasheet** Texas Instruments Available online at ti.com

Thank You