

SNS COLLEGE OF TECHNOLOGY



(An Autonomous Institution)

Approved by AICTE, New Delhi, Affiliated to Anna University, Chennai

Accredited by NAAC-UGC with 'A++' Grade (Cycle III) &

Accredited by NBA (B.E - CSE, EEE, ECE, Mech & B.Tech.IT)

COIMBATORE-641 035, TAMIL NADU

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

Course Name: 23ECT203 LINEAR INTEGRATED CIRCUITS

II YEAR/VI SEMESTER

UNIT II –APPLICATIONS OF OPERATIONAL AMPLIFIERS


Topic :V/I & I/V converters, Voltage Follower, summer, subtractor

Operational amplifiers are fundamental building blocks in modern electronics, enabling precise signal processing and control in countless applications.

 **Design Thinking Methodology** Empathize Define Ideate Prototype Test


 **Op-Amp Applications** V/I Converters I/V Converters Voltage Followers Summing Amplifiers Differential Amplifiers

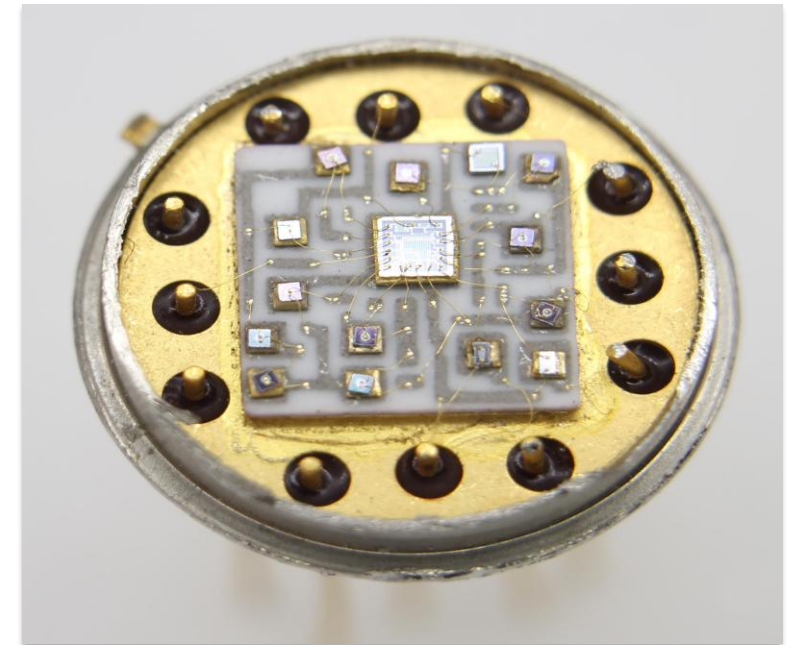 **Practical Implementation** Circuit Design Simulation Testing Applications




Modern operational amplifier integrated circuit

Stage 1: Empathize

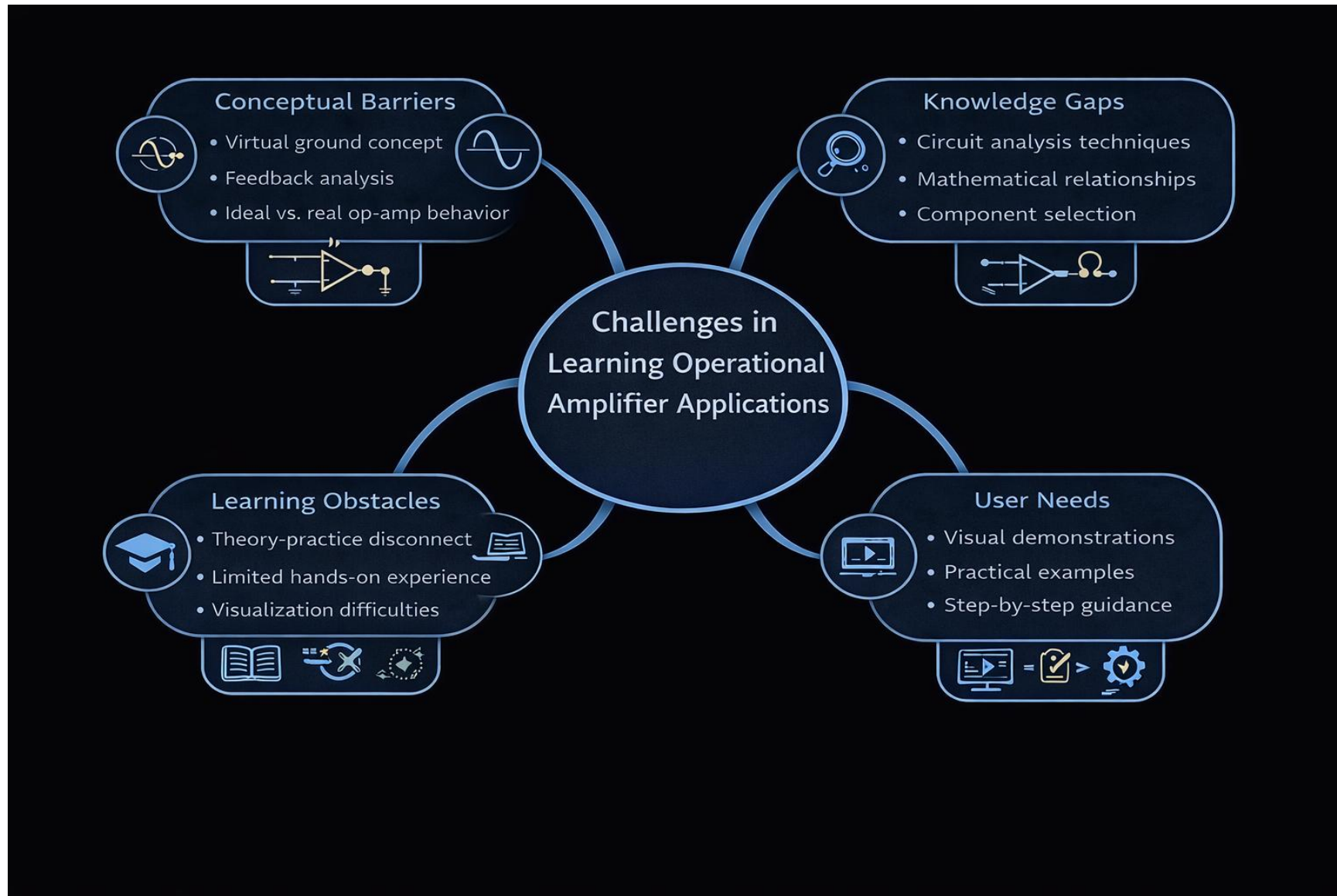



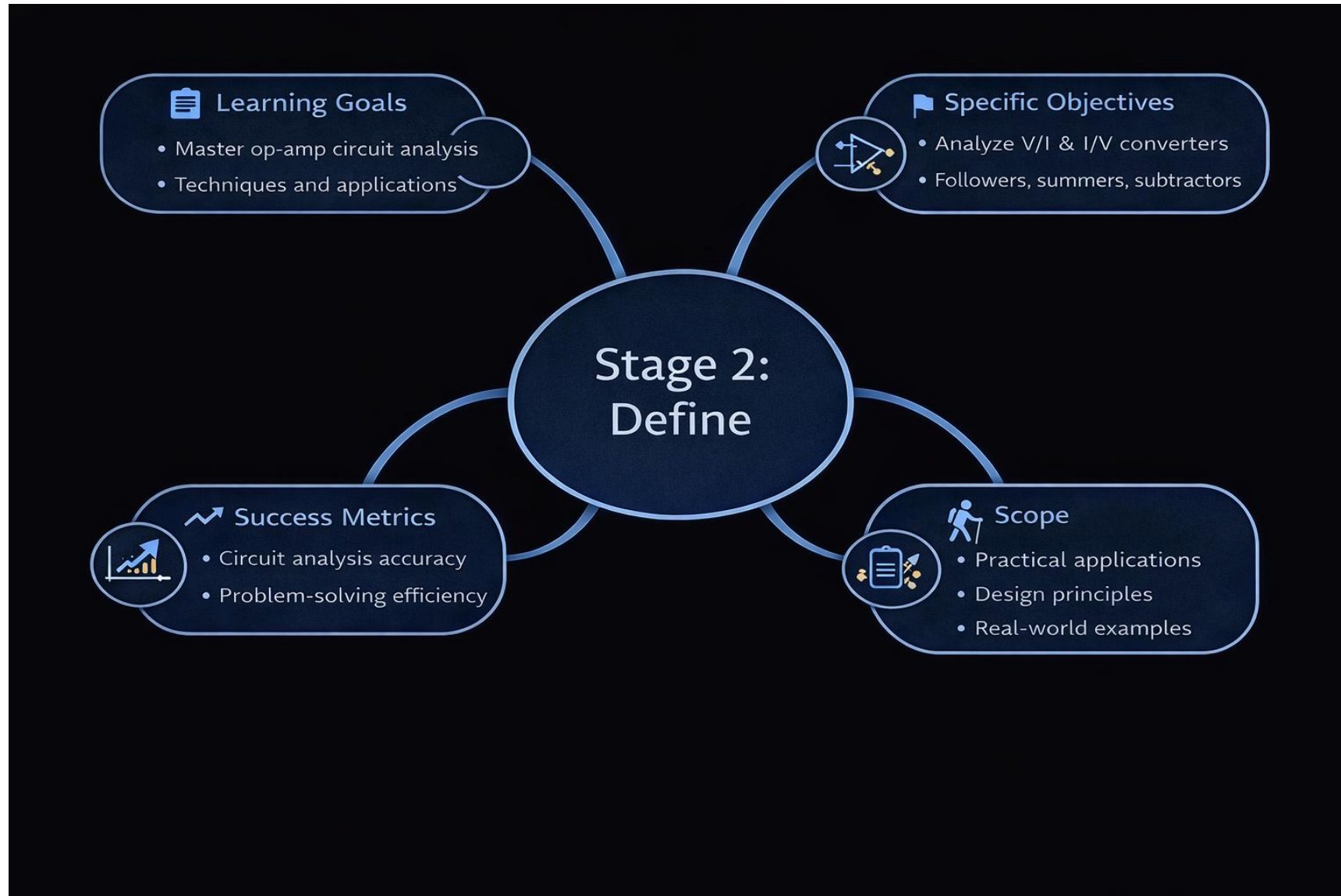


Stage 2: Define



Stage 3: Ideate

Brainstorming approaches to analyze and design operational amplifier circuits.

-  **Simulation Approaches** Virtual ground concept, nodal analysis, circuit simulation tools
-  **Analysis Techniques** Nodal analysis for V/I & I/V converters, superposition principle
-  **Problem-Solving Methods** Step-by-step circuit analysis, mathematical modeling
-  **Collaborative Design** Group brainstorming, peer review, knowledge sharing

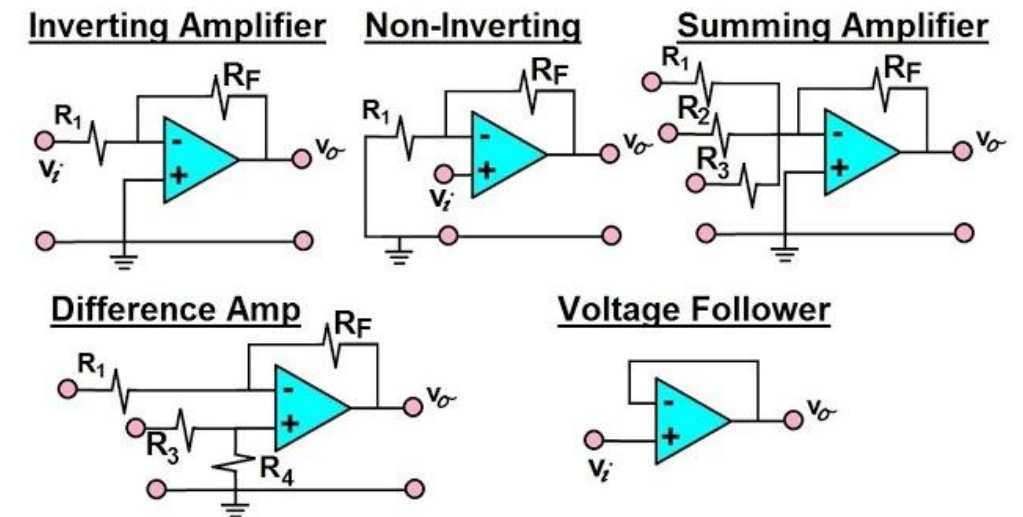

Stage 4: Prototype


Building and testing circuit prototypes for operational amplifier applications.

- 🔧 **Circuit Prototypes** V/I & I/V converters on breadboards with real components

- 📏 **Breadboard Implementations** Voltage followers with actual op-amp ICs and supporting components

- 🔄 **Simulation Models** Summer and subtractor circuits tested in simulation software


- 🔧 **Iterative Refinement** Component value adjustments for optimal performance

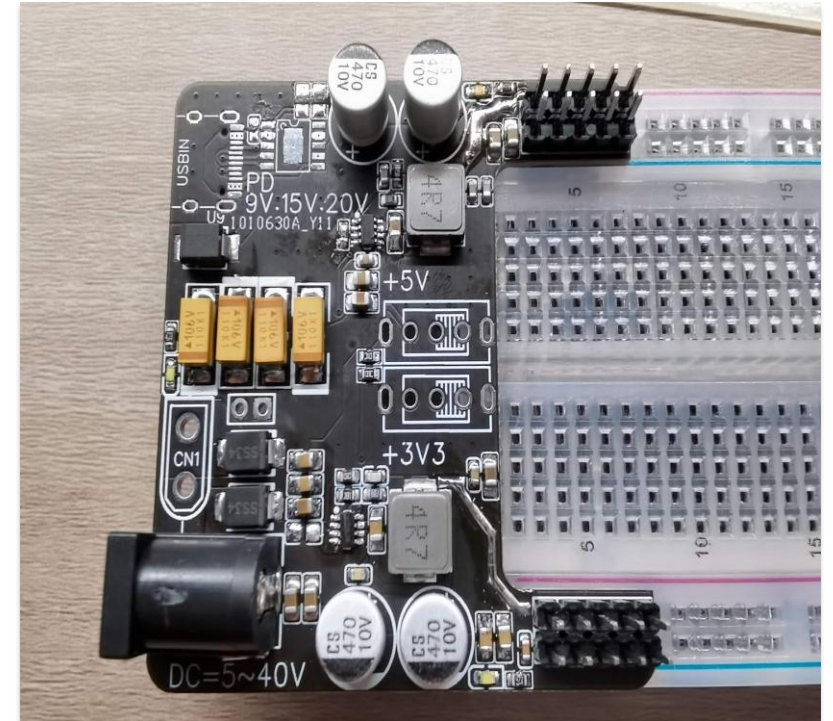

Stage 5: Test


Testing and evaluating operational amplifier circuits to validate design performance.

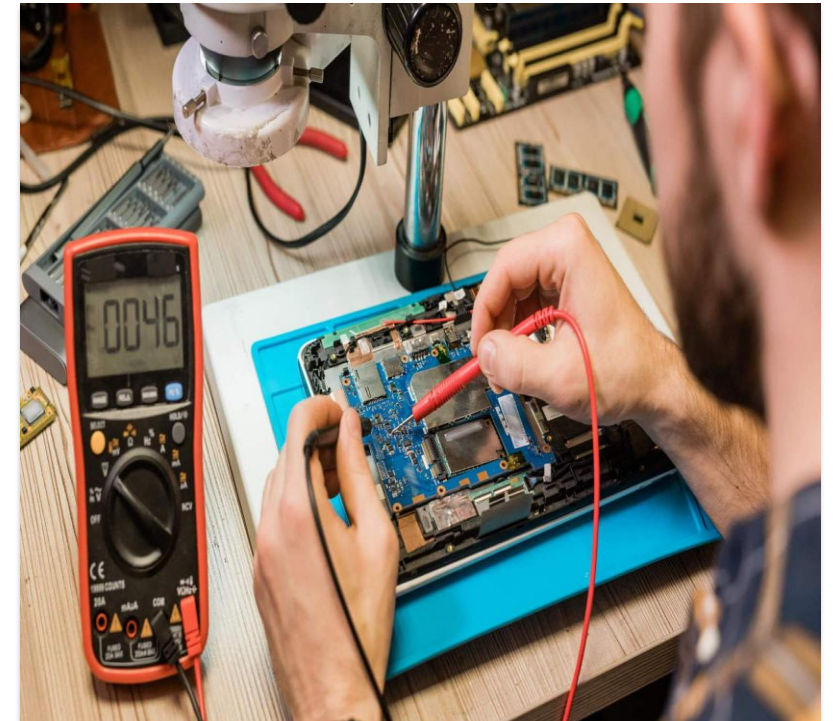- ▶ **Measurement Tools** Oscilloscopes and multimeters for signal analysis
- ✔ **Performance Analysis** Gain verification for V/I & I/V converters
- ⚙️ **Troubleshooting** Identifying issues in follower, summer, subtractor circuits
- 📊 **Feedback Collection** Comparing measured vs. theoretical values



Testing operational amplifier circuits with measurement equipment

Voltage-to-Current Converters

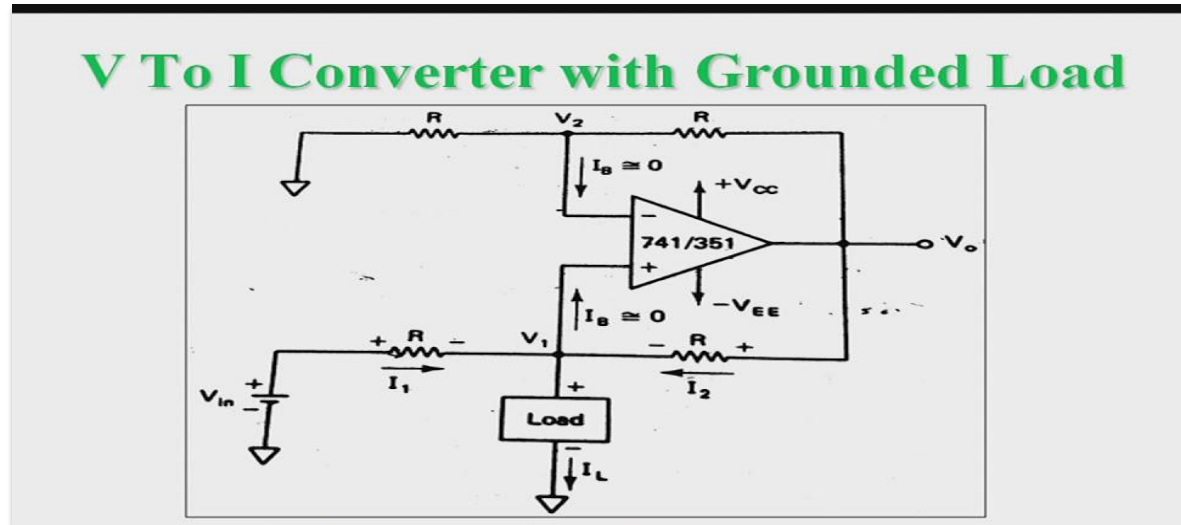

$$I_{out} = V_{in} / R$$



Conversion Function

Linear voltage-to-current transformation



Applications

LED drivers, current sources, sensor interfaces



Design Considerations

Load resistance, input voltage range, stability




Key Components

Op-amp, input resistor, grounded load

Voltage Follower

Voltage follower or Buffer amplifier

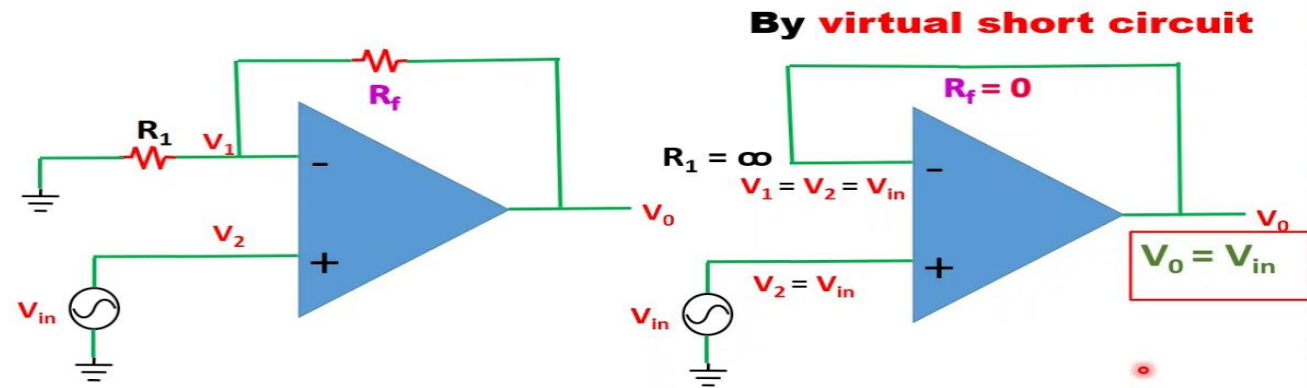

$$V_{out} = V_{in}$$



Unity Gain Buffer

Signal isolation without amplification



Applications

Impedance matching, signal buffering



Design Considerations


Slew rate, bandwidth, stability



Configuration

Output connected to inverting input

Summer (Summing Amplifier)

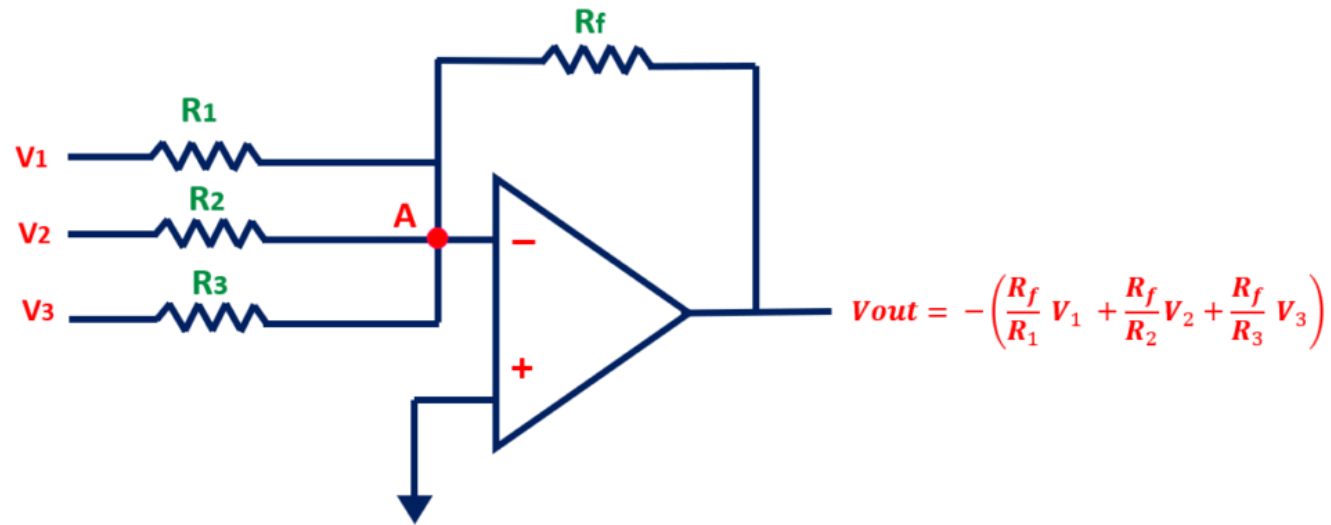

$$V_{out} = -R_f(V_1/R_1 + V_2/R_2 + V_3/R_3)$$

+ Addition Function

Multiple input voltage summation

💡 Applications

Audio mixing, digital-to-analog conversion

🛠️ Design Considerations


Input resistor values, saturation limits



Configuration

Multiple input resistors, feedback resistor, op-amp

Subtractor (Differential Amplifier)

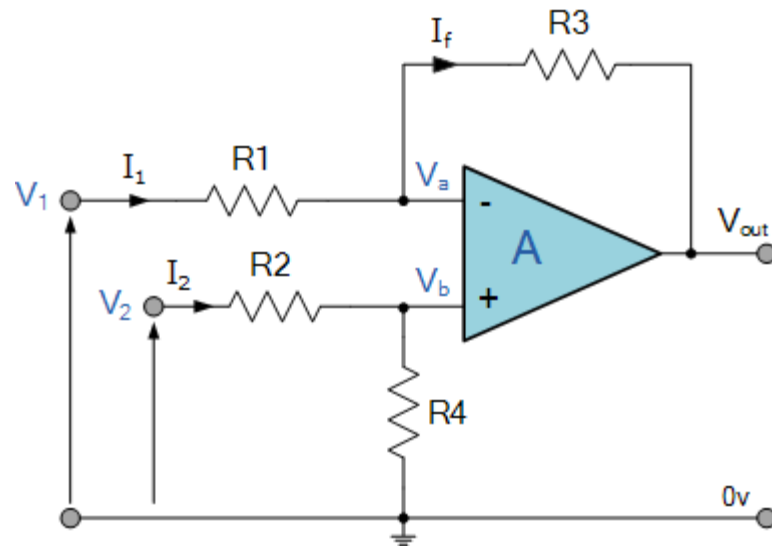

$$V_{out} = (R_f/R_1)(V_2 - V_1)$$

— Subtraction Function

Output proportional to input difference

💡 Applications

Signal difference measurement, noise rejection

🛠️ Design Considerations

Resistor matching, CMRR, bandwidth



Configuration

Two input paths with matched resistor ratios



Activity

Quick hands-on implementation of a voltage follower circuit to reinforce theoretical concepts.

Quick Circuit Build

Build a simple voltage follower with minimal components

Connect op-amp

Wire feedback

Apply power

Rapid Testing

Verify unity gain operation

1 Apply input

2 Measure output

3 Compare values

 5 Minutes

Minimal Materials


Breadboard

Op-amp IC

Power supply

Jumper wires

Concept Map

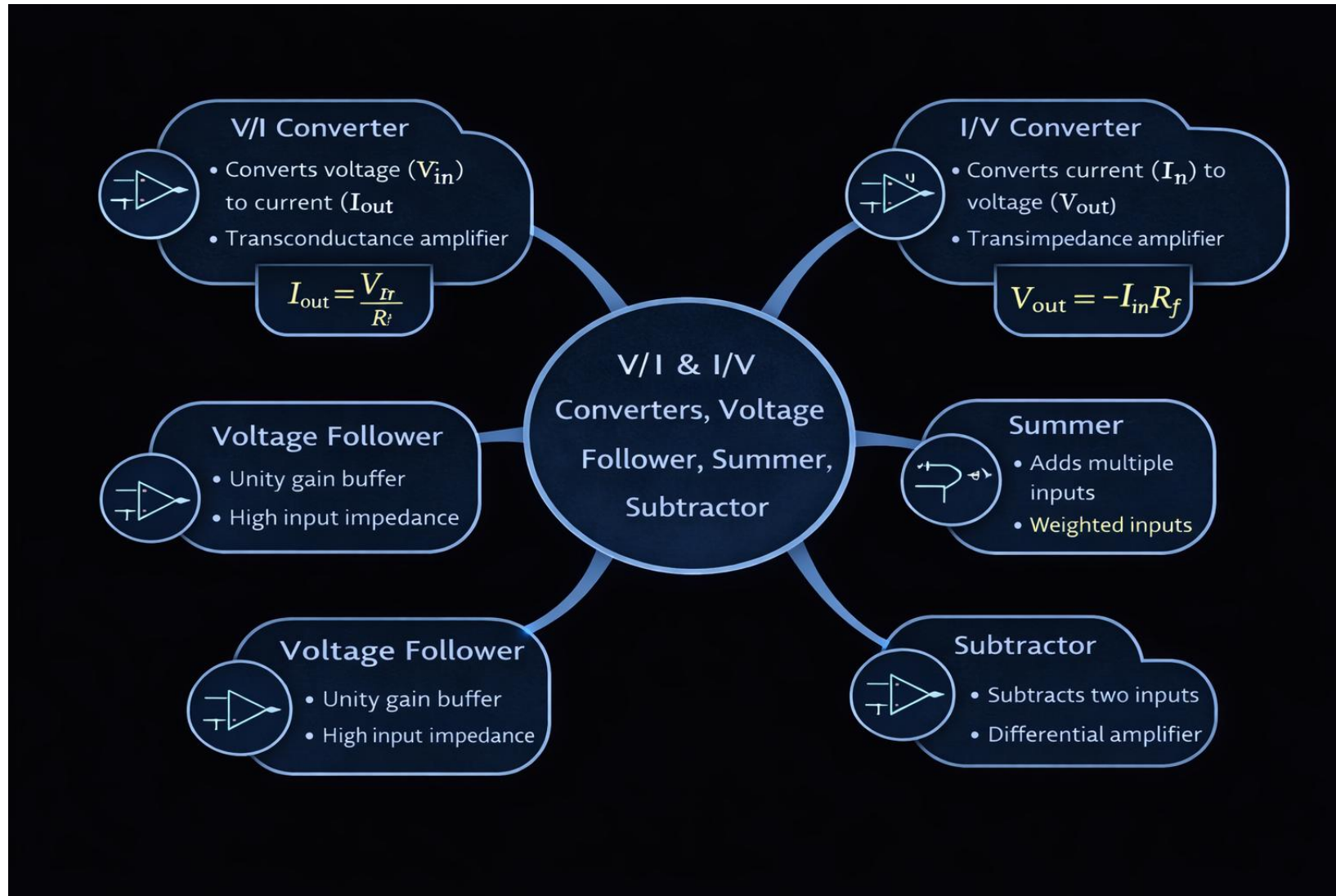

References

 **Jung, W.** Op Amp Applications Handbook Newnes, 2005

 **Carter, B. & Mancini, R.** Op Amps for Everyone 5th Ed., Newnes, 2018

 **Sedra, A.S. & Smith, K.C.** Microelectronic Circuits 8th Ed., Oxford University Press, 2020

 **Texas Instruments** Handbook of Operational Amplifier Applications Rev. B, 2022

Thank You