

SNS COLLEGE OF TECHNOLOGY



(An Autonomous Institution)

Approved by AICTE, New Delhi, Affiliated to Anna University, Chennai

Accredited by NAAC-UGC with 'A++' Grade (Cycle III) &

Accredited by NBA (B.E - CSE, EEE, ECE, Mech & B.Tech.IT)

COIMBATORE-641 035, TAMIL NADU


DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

Course Name: 23ECT203 LINEAR INTEGRATED CIRCUITS

II YEAR/VI SEMESTER

UNIT II –APPLICATIONS OF OPERATIONAL AMPLIFIERS

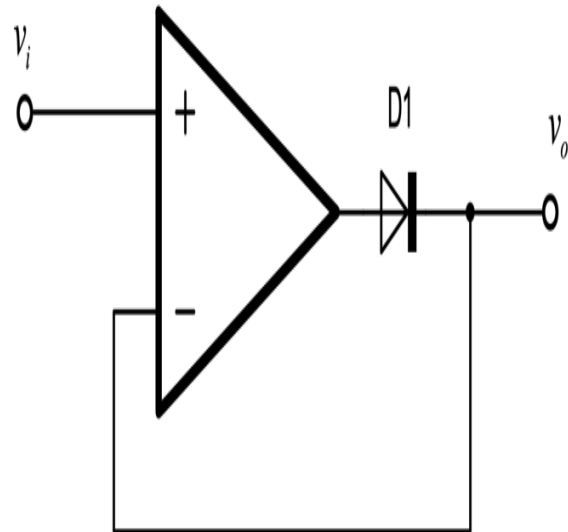Topic : Precision Rectifier and Peak Detector



What is Precision Rectifier?



Eliminates Diode Drop

Op-amp feedback removes V_f



High Accuracy

Precise absolute value output




Vs. Conventional

- Conventional: $V_{out} = V_{in} - V_f$
- Precision: $V_{out} = |V_{in}|$ (no V_f)
- Better for measurement systems



Basic Principle

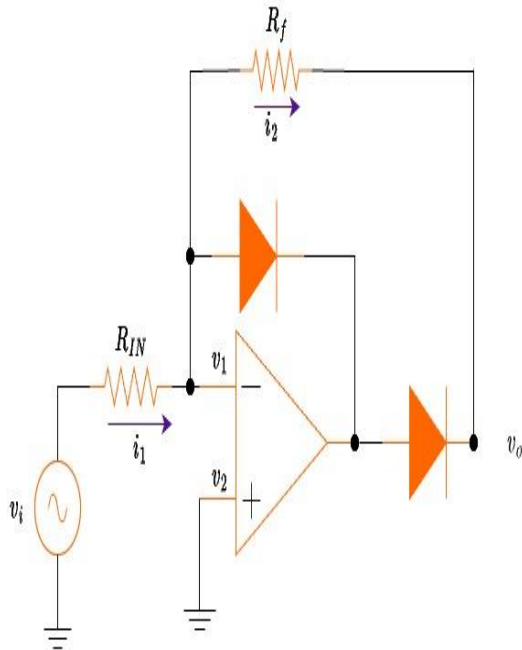Op-amp in feedback loop with diode creates ideal rectifier



Σ Output Formula

$$V_{out} = |V_{in}|$$

⊗ No Diode Drop

Op-amp eliminates V_f in feedback

High Accuracy

Output equals absolute input value

➡ Input

AC signal at inverting terminal

➔ Feedback

Diode rectifies output

➡ Output

DC = |AC| (rectified)

Key Characteristic: Output magnitude equals input magnitude, eliminates diode forward voltage drop through op-amp feedback loop

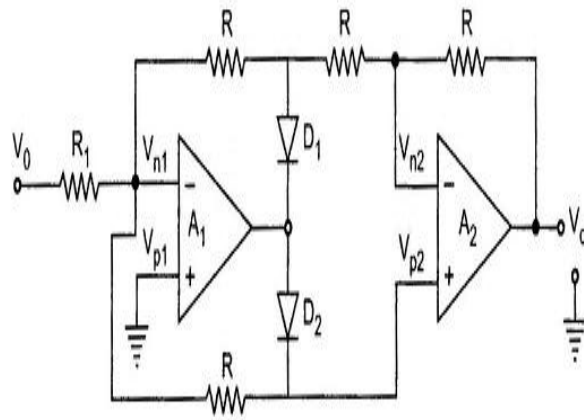


Fig. 2.63 Full wave rectifier

Full-Wave Rectification Both Half-Cycles

Two Op-Amps

Dual configuration for full-wave output

Bridge Config

Using precision diodes

High Efficiency

Better than half-wave (100% vs 50%)

Precision

Eliminates diode V_f completely

Positive Cycle

Rectified by first half


Negative Cycle

Rectified by second half

DC Output

Smooth rectified DC

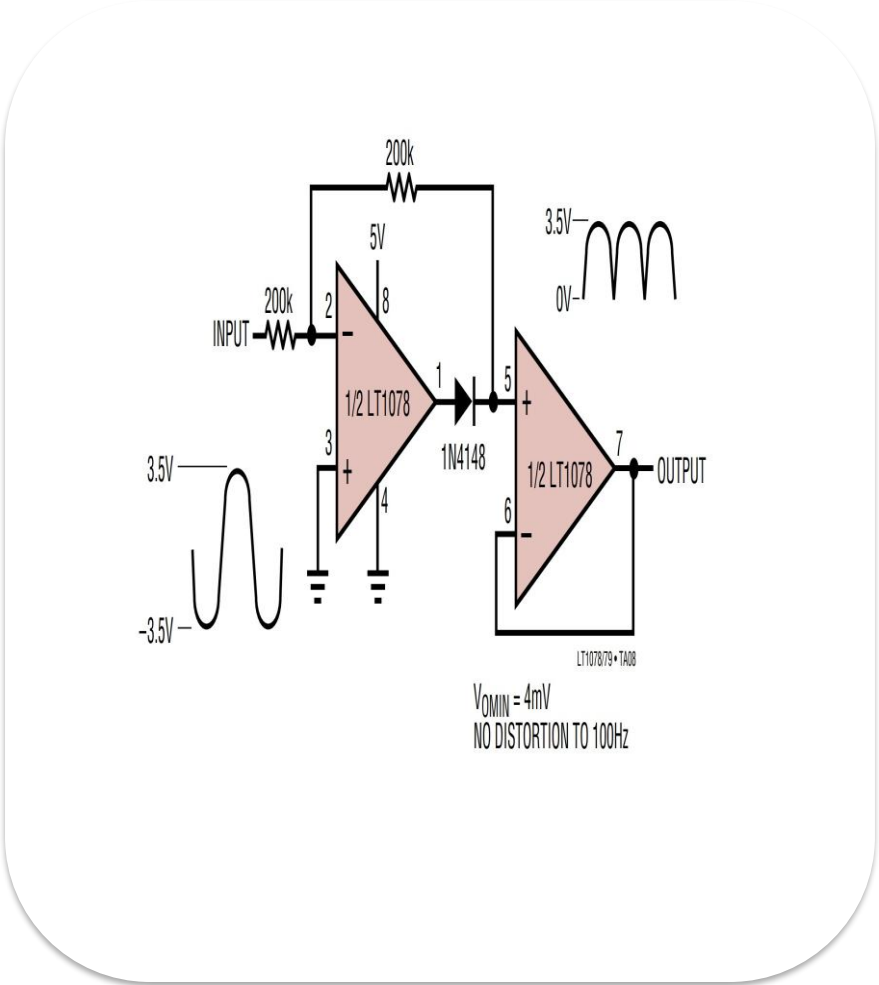Advantage: Double output frequency, smoother DC, higher efficiency compared to half-wave configuration



How It Works

Op-amp in feedback with diode eliminates V_f

Σ Output Formula
 $|V_{in}|$

Fast Response
Low propagation delay

High Accuracy
Eliminates diode drop


Low Distortion
Clean DC output

Input
AC signal applied

Output
 $|V_{in}|$ absolute value

Freq Response
Wide bandwidth

Applications of Precision Rectifier

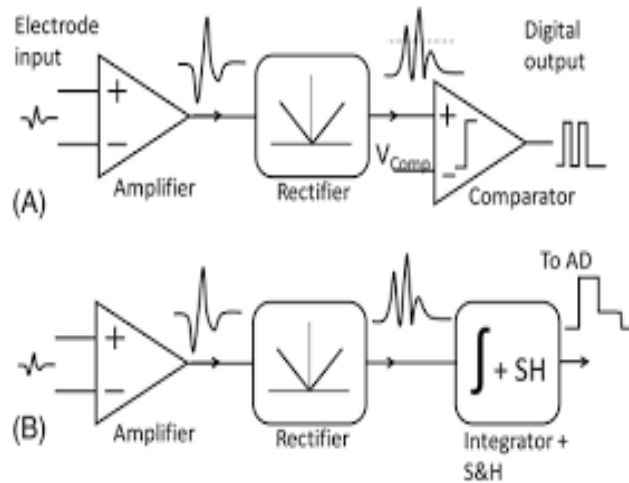

RMS Measurement

Calculate root mean square value

AC Voltmeter

Accurate AC without diode drop

Signal Processing

Absolute value detection

Mathematical

Absolute value computation

Analog Computing

Precision analog operations


Instrumentation

Measurement systems



Key Advantage: Precision rectifiers provide accurate $|V_{in}|$ output without diode voltage drop, essential for instrumentation and measurement systems

Introduction to Peak Detector

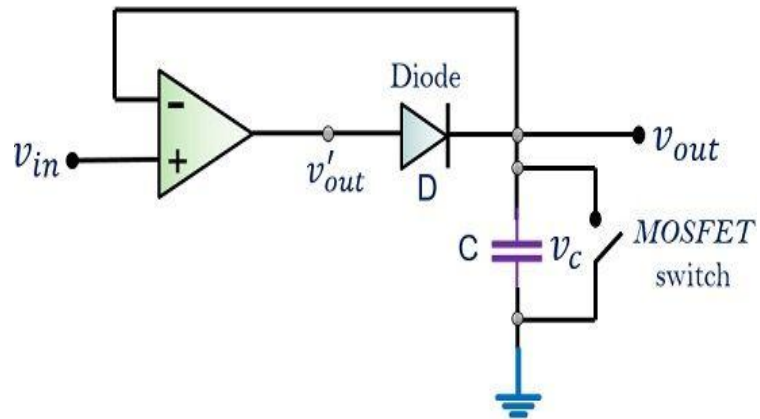

Peak detector circuit

Electronics Coach

? What is Peak Detector? Captures Maximum Voltage

📈 Peak Capture

Holds maximum value of input signal

📈 Envelope Detection

Follows amplitude variations


📦 Capacitor Holds

Stores peak voltage

✅ Diode Rectifies

Prevents discharge

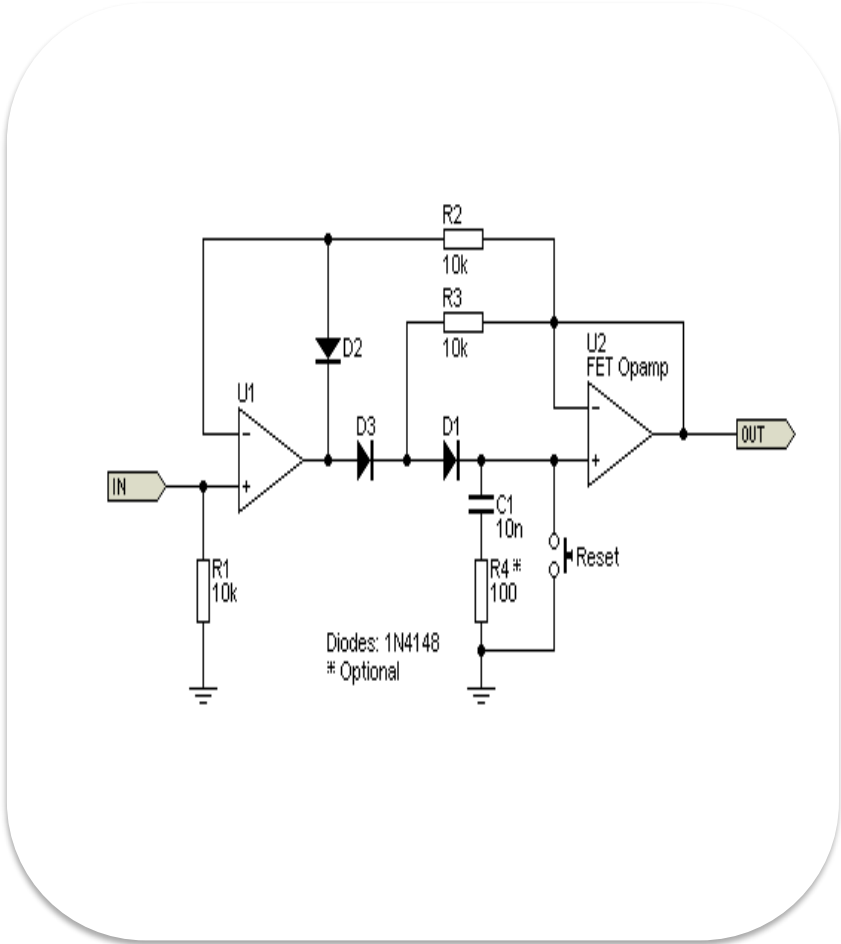Basic Principle: Input signal charges capacitor through diode to peak value; output follows input peaks; capacitor voltage represents peak value



Circuit Components

Op-Amp
Active element

→ **Diode**
Rectification


Capacitor
Holds peak voltage

Input Signal
Applied to non-inverting

Output Peak
Maximum input voltage

Reset Path
Resistor discharges C

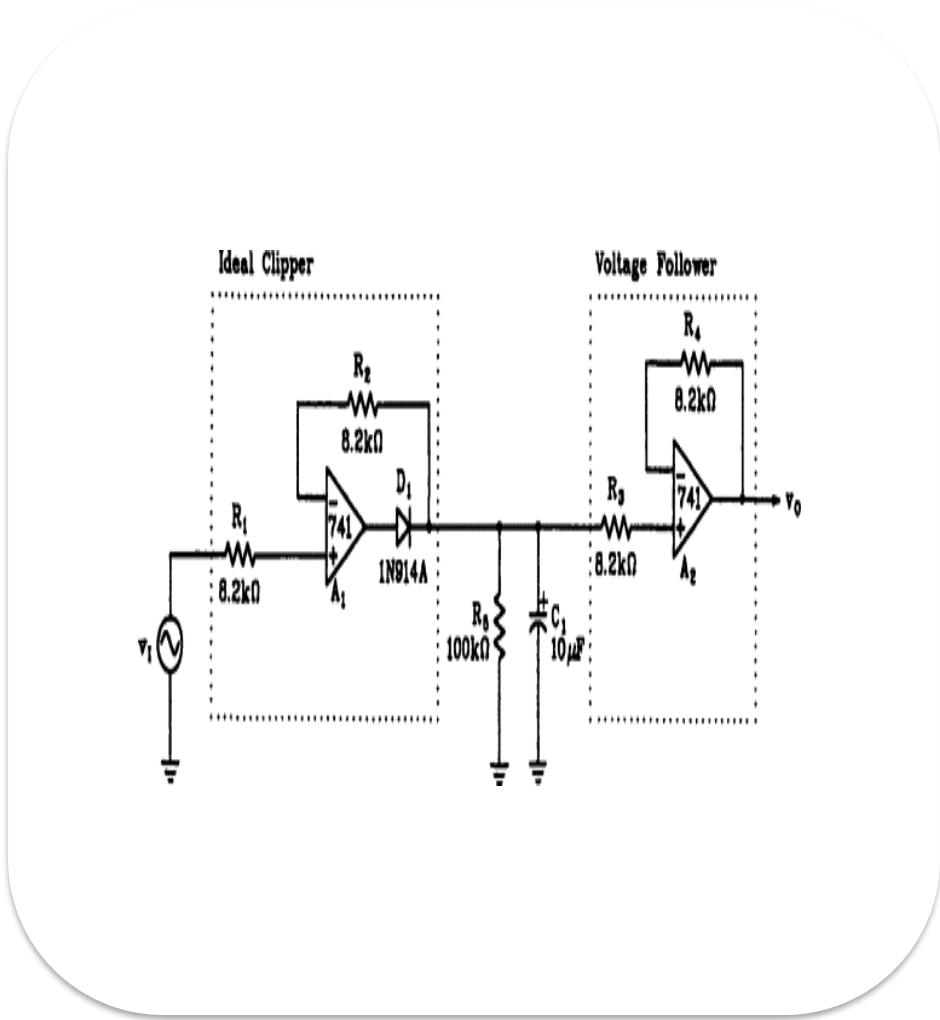Operation: Diode charges capacitor to peak when input rises; capacitor holds voltage when input falls



⚡ **Charging Phase**
Input rises → Capacitor charges to peak

↑ **Rise Phase**
Diode conducts, capacitor charges to peak voltage


↓ **Fall Phase**
Diode blocks, capacitor holds voltage

↻ **Holding**
Capacitor stores peak value

⌚ **Discharge**
RC time constant

↺ **Reset**
Follows new peak

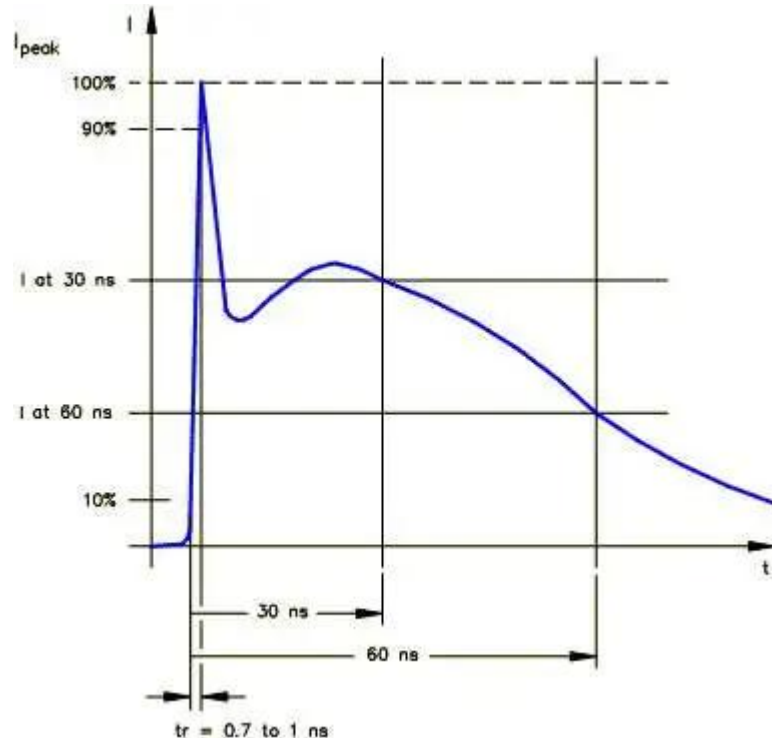Output follows input peaks - capacitor holds voltage between peaks, providing peak detection with memory effect



Key Parameters

🕒 Response Time

Depends on RC time constant

🔧 Accuracy

Capacitor value selection critical

📉 Droop Rate

Discharge through resistor

📈 Peak Capture

Maximum input voltage

✅ Advantages


- Simple circuit
- Accurate peak measurement

⚠️ Disadvantages

- Response time limited
- Droop affects measurement

Performance Note: RC time constant determines speed and accuracy trade-off; smaller C = faster response, larger C = slower droop

Applications of Peak Detector

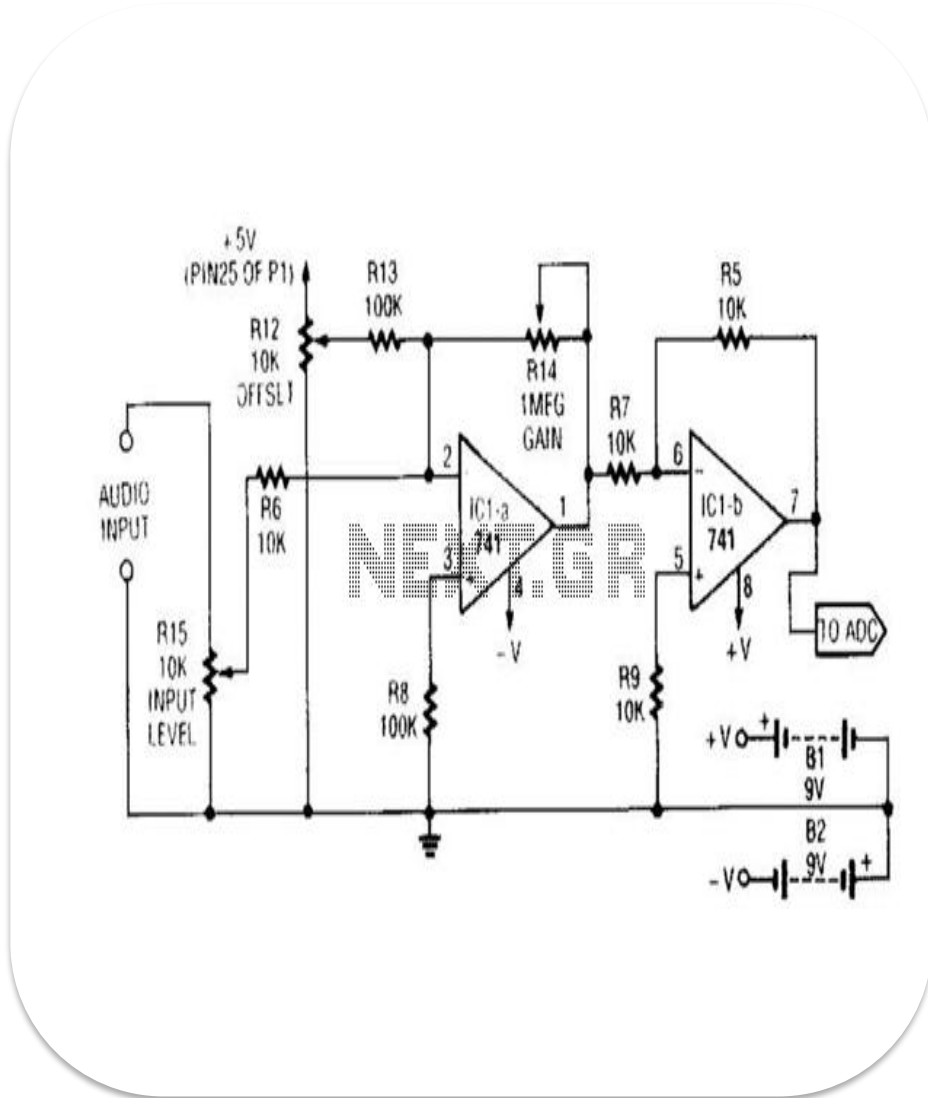

Real-World Applications

AM Demodulation

Envelope detection for amplitude modulation

Peak Measurement

Instrumentation and measurement systems

Audio Processing

Amplitude tracking and analysis

Signal Analysis

Pulse detection and waveform analysis


Sensor Readings

Peak value acquisition from sensors

Oscilloscope

Trigger and envelope detection

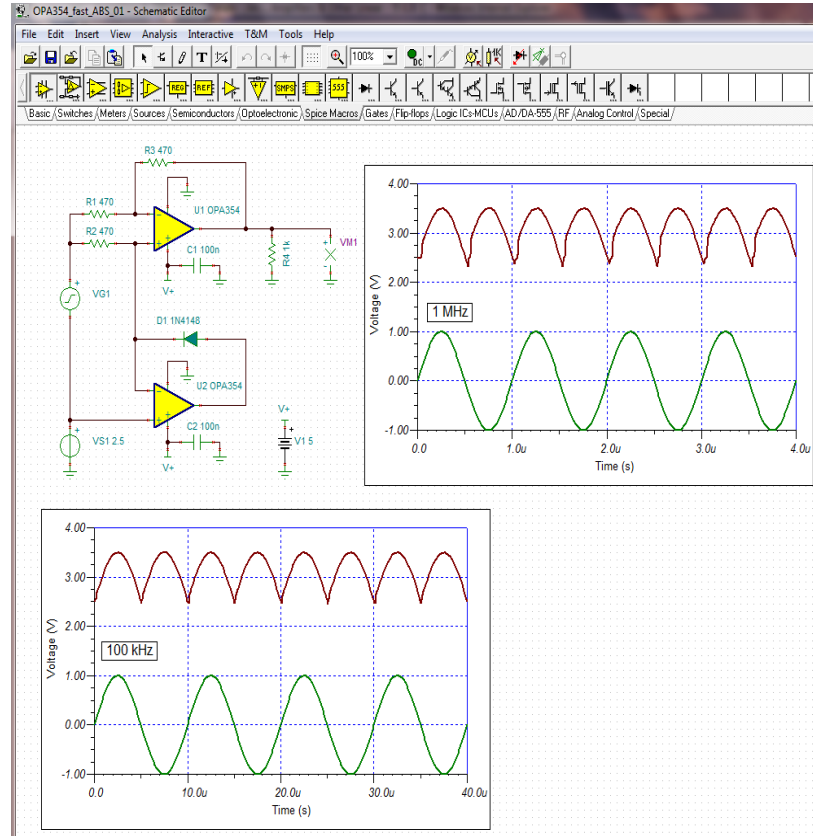Key Feature: Peak detectors capture and hold maximum voltage values for real-time amplitude monitoring and signal envelope extraction



← Precision Rectifier vs Peak Detector

⚙ Precision Rectifier

- Absolute value output $|V_{in}|$
- Instant response time
- No memory effect

📈 Peak Detector

- Holds peak value V_{max}
- Slower RC response
- Memory effect

📁 When to Use Precision Rectifier

- Need absolute value
- Fast response required
- Signal processing

📁 When to Use Peak Detector

- Peak measurement needed
- Envelope detection
- AM demodulation



Design Tip: For precision rectifier, use high-speed op-amp; For peak detector, select C based on RC time constant and signal frequency

Activity: THINK • PAIR • SHARE

1

THINK



Individual Reflection

- Compare precision rectifier and peak detector circuits
- Analyze output characteristics
- Consider design requirements

2

PAIR



Partner Discussion

- Discuss applications of each circuit
- Compare design considerations
- Evaluate performance trade-offs

3


SHARE



Group Presentation

- Present circuit selection rationale
- Explain best circuit for specific applications
- Justify design choices

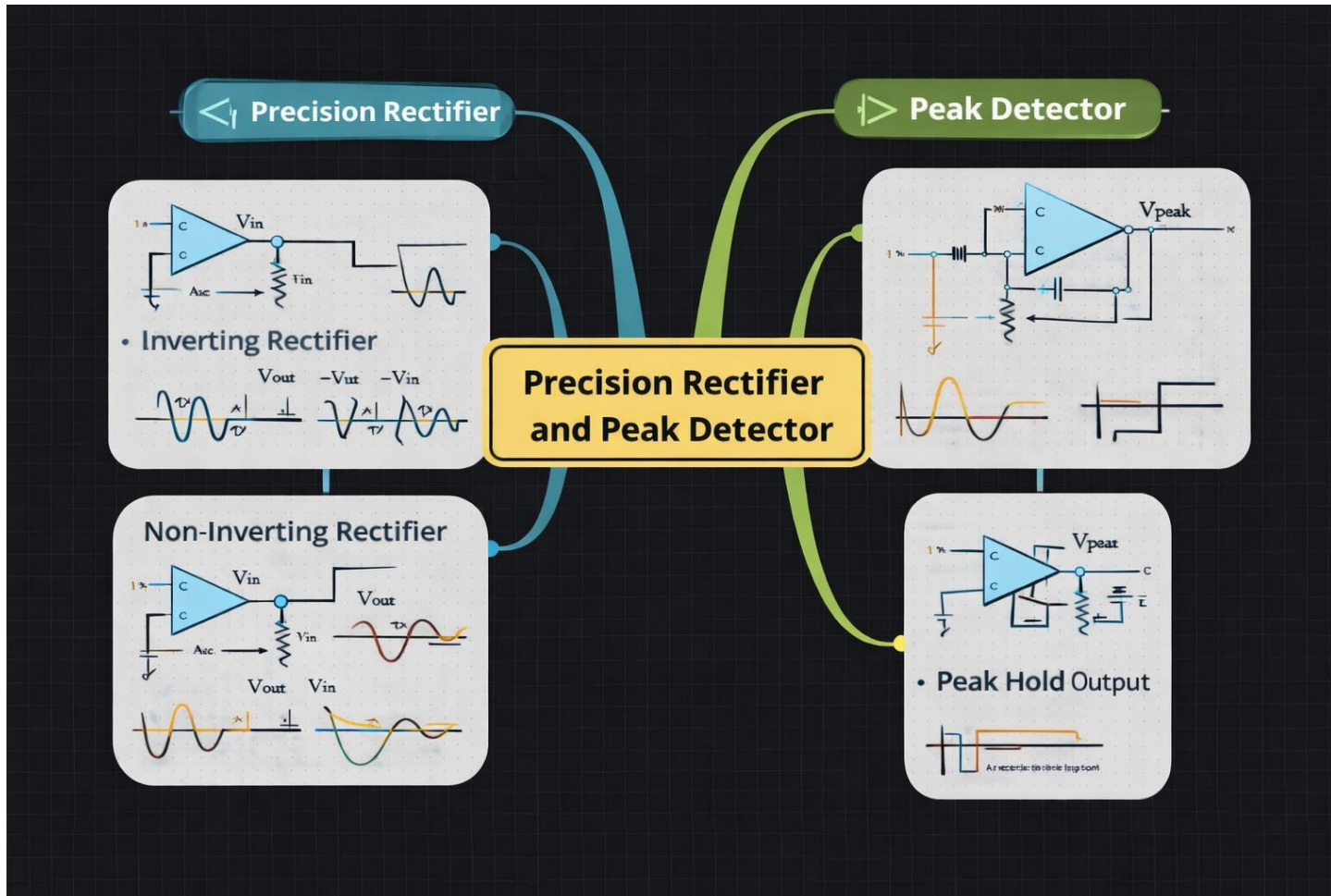Mind Map - Precision Rectifier and Peak Detector





Precision Rectifier

Q1: Derive Output Formula

$$V_{out} = |V_{in}|$$

Q2: Explain Diode Drop Elimination

Op-amp in feedback eliminates V_f

Q3: Compare Half-Wave vs Full-Wave

Half-wave: 50% efficiency

Full-wave: 100% efficiency



Peak Detector

Q4: Explain Working Principle

Diode charges capacitor to peak value

Q5: Derive Capacitor Charging Equation

$$V_c(t) = V_{peak}(1 - e^{-t/RC})$$

Q6: Calculate RC Time Constant

RC = R×C determines response time



Textbooks

1

Sergio Franco

"Design with Operational Amplifiers and Analog Integrated Circuits"

2

D. Roy Choudhry & Shail Jain

"Linear Integrated Circuits"

3

Ramakant A. Gayakwad

"OP-AMP and Linear ICs"



Online Resources



Texas Instruments

Precision Rectifier Applications -
Technical Literature



Analog Devices

Peak Detector Design Guide -
Application Notes



Electronics Tutorials

Rectifier and Detector Circuit
Design



NPTEL

Linear Integrated Circuits -
Video Lectures

Thank You

Understanding Precision Rectifiers and Peak Detectors is essential for measurement systems, signal processing, and instrumentation applications.



Precision Rectifiers

Provide absolute value output $|V_{in}|$ without diode voltage drop



Peak Detectors

Capture and hold peak voltage values using capacitors



Measurement Systems

Accurate measurement and signal analysis for instrumentation