

## DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

Course Code & Name : **23ECT203 & Linear Integrated Circuits**


Course Faculty : **Ms.V.Aishwarya AP/ECE**

### Puzzles / In Class Activities

Topics Covered: **Unit 2-APPLICATIONS OF OP AMP**

#### Puzzle 1

**Question:** What type of op-amp circuit is this?

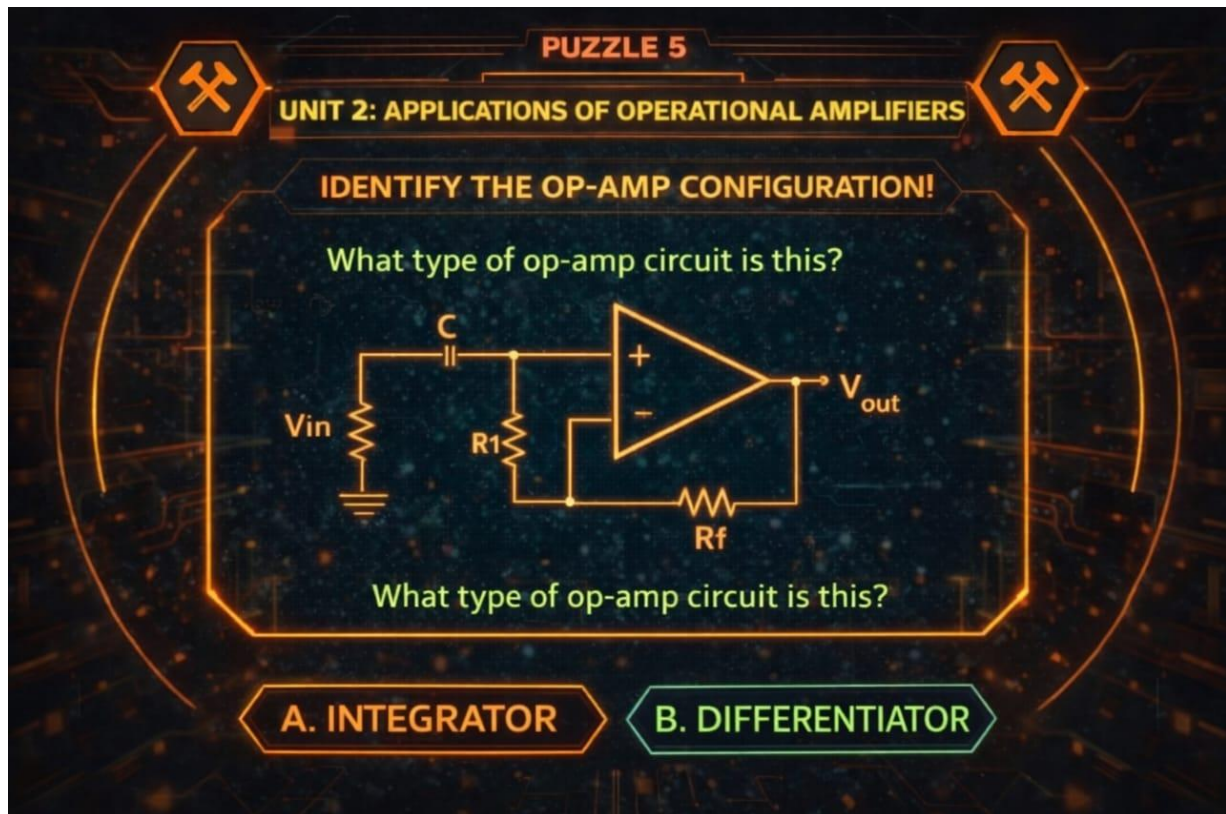

**PUZZLE 5**

**UNIT 2: APPLICATIONS OF OPERATIONAL AMPLIFIERS**

**IDENTIFY THE OP-AMP CONFIGURATION!**

What type of op-amp circuit is this?

What type of op-amp circuit is this?

**A. INTEGRATOR**      **B. DIFFERENTIATOR**

The diagram shows an operational amplifier with the non-inverting input (+) connected to ground. The inverting input (-) is connected to an input terminal labeled  $V_{in}$  through a resistor  $R_1$ . A feedback resistor  $R_f$  is connected between the output and the inverting input. A capacitor  $C$  is connected between the inverting input and ground.


Answer :

**PUZZLE 5**

**UNIT 2: APPLICATIONS OF OPERATIONAL AMPLIFIERS**

**CORRECT!**

This is an **INTEGRATOR** circuit.

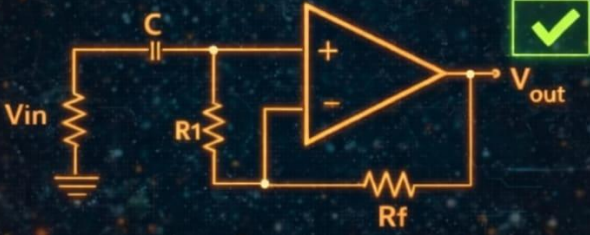

What type of op-amp circuit is this?

**INTEGRATOR**

**Puzzle 2**

**Question : Is the following circuit Inverting or Non Inverting**

**PUZZLE 4**

**UNIT 2: CONFIGURATIONS OF OPERATIONAL AMPLIFIERS**

**IDENTIFY THE OP-AMP CONFIGURATION!**

Is the following circuit **INVERTING** or **NON-INVERTING**?

**INVERTING**      **NON-INVERTING**

Answer:

